RADIO a TELEVISION NEWS

JUNE 1954 25 CENTS



Similar Same and the course

IN THIS ISSUE

RADIO ASTRONOMY

"BATRA-LINEAR"

OPERATION OF SYS TUBES

MEMOTE CONTROLS FOR

UNDAMENTALS OF COLOR TV

3-DANOS, 1-VERTICAL

COILS BY REMOTE CONTROL

THE CROSLEY "SUPER.Y"

ELIMINATION OF R. F. INTERFERENCE IN AUDIO SYSTEMS

A PHOTOTRANSISTOMZED PHOTOELECTRIC COMMTER

SOMIC LIQUID LEVEL INDICATOR ()

See Page 46)





You're in the chips!

Customer confidence in you and your way of doing business is the greatest single business asset you can have. The RAYTHEON Bonded ELECTRONIC TECHNICIAN program, now in its 10th year, has helped and continues to help many thousands of Radio and Television service dealers break down the barrier of public mistrust. And in so doing increases the volume and profit of these Raytheon Bonded Technicians.



Ask your Raytheon Tube Distributor if you can qualify for this priceless sales asset. If you can, the program costs you not one cent, it's Raytheon's investment in your future.

RAYTHEON MANUFACTURING COMPANY

Mauton, Mars. Chicago, Ill., Atlanta, Go., Los Appeles, Cal.

Malls, Chitogo, Illy Affordo, Goy Lot Angeles, Cali

Good Pay-Security-Promotions for You



RADIO-TELEVISION 3000 Radio broadcasting stations operating day and BROADCASTING night provide interesting jobs with good pay to tens of thousands of operators and technicians. 200 Television stations on the air , hundreds more under construction and still more authorized, creating job demand and bright future for men who qualify.



RADIO-TELEVISION 115 million home and auto Radios plus 25 million Tele-SERVICING vision homes (with total growing rapidly)
mean increasing opportunities for qualified servicemen. Many NRI students make \$10, \$15 a week extra fixing sets in spare time while training. Many NRI graduates start their own full-time business or take good jobs with dealers

Let Me Show How You Can Qualify for RADIO-TELEVISION, ALLE

NATIONAL RADIO INSTITUTE. WASHINGTON, D. C.,

as trained more men for

TRAINING plus OPPORTUNITY is the PERFECT combination for ambitious men. Let me send you a sample lesson from my course to prove you can keep your job while TRAINING at home in your spare time, for better pay and a brighter future. I will also send my 64-page book to show you that Radio-Television is today's field of OPPORTUNITY for properly trained men.

Practice Broadcasting or Servicing

with Kits of Parts I Send You

Nothing takes the place of practical experience. That's why NRI training is based on LEARNING BY DOING. My training includes kits of parts which you use to build equipment and get practical experience on circuit scommon to both Radio and Television. Shown at the left is the low-power Broadcasting Transmitter you huild as part of my Communications Course. It gives you experience putting a station "on the air," learning procedures required of broadcast station operators. Shown below is the modern Radio you build as part of my Servicing Course. You use it to conduct tests, get experience locating and correcting set

and correcting set troubles. My book shows other special-ly designed equip-ment you build to

get practical expe-rience, to bring to life things you learn from my illustrated All equip

Television Growth Making More Good Pay Jobs, Prosperity

Radio is bigger than ever and Television is still growing fast. Government, Aviation, Police, Ship, Micro-wave Relay, Two-way Communications Systems for buses, taxis, trucks, railroads are other growing fields providing good job opportunities and bright futures for men properly trained in Radio-Television.

Start Soon to Make 110, 115 a Week Extra Fixing Sets

You can start to cash in fast. Many men I train fix neighbors' acts, make extra money, starting soon after they enroll. Multitester built with parts I send helps locate and correct set troubles. Read at left how you build actual equipment that gives you practical experience with circuits common to both Radio and Television.

Mail Coupon - Find Out About **Tested Way To Better Pay**

Act now to enjoy more good things of life. Take NRI training for as little as \$5 a month. Many NRI graduates (some with only a grammar school education) make more in two weeks than the total cost of my training. Mail coupon today for Actual Lesson and 64-page Book—BOTH FREE, J. E. SMITH, President, National Radio Institute, Dept. 4FE Washington 9, D. C. OLIP ACT VEAU. Institute, Dept. 4F. OUR 40TH YEAR.

I Trained These Men

Got Laid Off, Good Thing E. T. SLATE, Cors

JOHN BRITTO, Hyatta-ville, Maryland.

home. NRI started me off right."-BERNARD SIERS,



Mr. J. E. SMITH, President, Dept. 4FE National Radio Institute, Washington 9, D. C.

Mail me Sample Lesson and 64-page Book, FREE. (No salesman will call. Please write plainly.)

NAME

ZONE STATE CITY.

VETS WRITE IN DATE



ADDRESS

Editor and Asst. Publisher
OLIVER READ, D.Sc., WIETI
Managing Editor
WM. A. STOCKLIN, S. S.
Technical Editor
H. S. RENNE, M. S.
Service Editor
CHARLES TEPPER

Assistant Editors
P. B. HOEFER
M. C. MAGNA

Television Consultant
WALTER H. BUCHSBAUM

Short-Wave Editor KENNETH R. BOORD

Art Editor

A. A. GANS, W2TSP
J. A. GOLANEK

Advertising Manager
L. L. OSTEN

Midwest Adv. Manager JOHN A. RONAN, JR.

Western Adv. Munoger JOHN E. PAYNE



COVER PHOTO: Making adjustments on a "Sonic Liquid Level Indicator" at the Paterson, New Jersey, plant of Bogue Electric Manufacturing Co. For the operational details see page 46. (Ektachrome by John Reardon)

ZIFF-DAVIS PUBLISHING COMPANY

B. G. DAVIS

Vite-Presidents
H. J. MORGANROTH
M. H. FROELICH

Secretory-Treasurer O. E. CARNEY

Circulation Manager M. MICHAELSON

BRANCH OFFICES

CHICAGO [1] 64 E. Lete St., AN 3-5200

LOS ANGELES (14) Statler Center, 900 Wilshire Blvd., Mich. 9856

Jirst in radiotelevision-audio-electronics Average Paid Circulation over 230,000



Reg. U. S. Pat. Hadio News Trademark Reg. U. S. Pat. Office • Television News Trademark Reg. U. S. Pat. Office.

CONTENTS	JUNE, 1954
Radio Astronomy	
TVI Troubleshooting (Part 2)	
Remote Controls for Marine Radiot	telephonesElbert Robberson 4
Voltage Stabilization for Scope Cali	brators
"Ultra-Linear" Operation of 6V6 Tu	bes David Hafler 4
Sonic Liquid Level Indicator	
	Receiver Circuits (Part 4)
Bandswitch Your Loading Coils by I	Remote Control
A Phototransistorized Photoelectric	Counter
	Nathan O. Sokal & Richard G. Seed 5
***************************************	ng Voltage Standing-Wave Ratios J. F. Sterner 5
Elimination of R.F. Interference in A	Audio Systems (Part 1)
	Bert Whyte 5
3-Bands, I-Vertical	
Mac's Radio Service Shop	John T. Frye 6
Service Hints on Crosley TV Sets	
More Old Time Operators Report	
	8
New TV Grants Since Freeze Lift	9
New TV Stations on the Air	9
A Video-Magnetic Tape Recorder.	12
DEP	ARTMENTS
For the RecordThe Editor	What's New in Radio 9
Spot Radio News 16	New TV Products 11
Within the Industry 24	Technical Books 12
Short-WaveK. R. Boord 65	Manufacturers' Literature 13



COPYRIGHT 1954
(All Rights Reserved)
ZIFF-DAVIS PUBLISHING COMPANY
WILLIAM B. ZIFF (1898-1953) FOUNDER
Editorial and Executive Offices
366 Madison Ave., New York 17, N. Y.
VOLUME 51 • NUMBER 6



SUBSCRIPTION SERVICE: All communications concerning subscriptions should be addressed to Circulation Dept., 64 E.

Lake St., Chicago I, Ill. Subscribers should allow at least four weeks for change of address.

Lake M., Chicago I, III. Subscripers should show at least four weven rev change or shoureas.

CONTRIBUTIONS: Contributions are advised to retain a copy of their manuscripts and illustrations. Contributions should be maded to the New York Editorial Office and must be accompanied by return postage, Contributions will be handed with reactions and revisions are necessary to meet the requirements of this bublication. Payment covers all authors, contributor's, and contestant's rights, title, and interest in and to the material accepted and will be made at our current false upon acceptance. All photos and drawings will be considered as part of the material purchased.



SPLITTING HAIRS

TO SPEED CALLS


To triple the voice-carrying capacity of coaxial cable, Bell Laboratories engineers had to create new amplifying tubes with the grid placed only two-thirds of a hair's breadth from the cathode. Furthermore, the grid wires had to be held rigidly in position; one-quarter of a hair's shifting would cut amplification in half.

Working with their Bell System manufacturing partners at Western Electric, the engineers developed precise optical means for measuring critical spacing insulators. On a rigid molybdenum grid frame they wound tungsten wire three ten-thousandths of an inch thick. To prevent the slightest movement they stretched the wire under more tension for its size than suspension bridge cables, then bonded it to the frame by a new process.

The resulting tube increases coaxial's capacity from 600 to 1800 simultaneous voices — another example of how Bell Telephone Laboratories research helps keep your telephone system growing at the lowest possible cost.



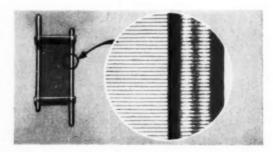This coaxial system electron tube amplifies more voices at the same time because of wider frequency band—made possible by bringing grid and cathode closer together.



Grid is shown above on left. Picture at right, enlarged 15 times, shows how wires are anchored by glass bond. They will not sag despite nearness of red-hot cathode.

BELL TELEPHONE LABORATORIES

IMPROVING TELEPHONE SERVICE FOR AMERICA PROVIDES CAREERS FOR CREATIVE MEN IN SCIENTIFIC AND TECHNICAL FIELDS





You'll say it's stupendous . . . the greatest and most valuable helper a TV Serviceman ever had!

An easy-wheeling, aluminum carrier that lets you move a heavy TV chassis (up to 27-inch tube) anywhere . . . with no lugging, no straining, no bumping. And no risk to tubes, floors, or polished surfaces. You save time, save money, save effort, and win renewed confidence from your customers.

Yours FREE!

This sensational work-saver now yours FREE with your purchases of Sylvania Tubes.

But don't delay! Offer expires August 31st. So, order your Sylvania Tubes and get your carrier reservation in NOW! Call your Sylvania Distributor for full details today!

SYLVANIA ELECTRIC PRODUCTS INC. 1740 BROADWAY NEW YORK 19, N. Y.

YIXAN Sylvania Electric University Tower Bldg. St. Catherine St.

LIGHTING · RADIO · ELECTRONICS · TELEVISION

June, 1954

(Canada) Ltd.



Brings advantage of distortion-free wider range found in E-V separate 3-way systems, in one compact speaker

E-V concentric Triaxial design gets the most from specialized driving media for each portion of the audio spectrum. Augmented bass response, full bodied mid-range and silky-smooth upper octaves to the highest audible frequencies provide excellent musical balance without masking effects or imposed distortions.

Model 12TRX. 12%e" diam. List, \$190 Audiophone Net, \$114 Model 15TRX. 15½" diam. List, \$225 Audiophone Net, \$135 Includes X36-1 crossover network and AT37 brilliance control

- Response 30-15,000 cps in Recommended Enclosures
- Exclusive E-V Concentric Mounting Insures Full Range, Complete Room Coverage
- Balanced Response Characteristic Provides Realism and Presence
- Adjustable Brilliance Control for Remote Mounting, Allows Matching to Room Acoustics
- Edgewise Wound Voice Coil Design Affords 18% More Efficiency
- Full 1/2 Section M-Derived Crossover
 Network Minimizes Distortion Products





AT HOME WITH COLOR TELEVISION

It was with feelings of mixed emotion that your editor undertook the responsibility to "guinea pig" a color television receiver at his home during the past several weeks. We knew, for example, that no souped-up laboratory model would provide the necessary data we were seeking. For the purpose a receiver would need to be taken right off a production line in order to serve as a fair basis for our tests.

But production models for immediate delivery to the public were not generally available back in March. The only exception was the announcement by Westinghouse that color television sets were now in production and were available for sale and delivery to the public. We decided to request the loan of a receiver from stock for test purposes at the consumer level. Our request was immediately granted and Model 840CK15 arrived promptly at our home in Greenwich, Conn. in its sealed carton via truck.

This location is 35 airline miles from the television antennas atop the Empire State Building in New York City. Our antenna is a 2-bay conical, vintage of 1951. It feeds a 2-channel coupler. One channel feeds a 24-inch monochrome receiver. The remaining channel was connected to the color set after curiosity prompted the decision to personally uncrate the set and connect it before the manufacturer's technician could arrive to handle the installation, the same as would be done for a customer (apologies to Westinghouse). Somewhat hurriedly we read the tuning instructions and turned on the set. Controls and tuning procedures were found to be about the same as on standard monochrome receivers. All seven channels were in good alignment and monochrome reception was highly acceptable. For comparison, the 24inch black-and-white receiver was placed near the new color set. As expected, there was an immediate reaction due to the small color screen compared to the large screen to which we had become accustomed. However, experience later showed that one can become acclimated in a hurry providing he draws his chair closer.

No colorcasts were available during the first three days of viewing. We became quite accustomed to the slight sepia tone as viewed on the color screen from black-and-white telecasts and this actually becomes pleasing to the eye. The technician from Westinghouse had arrived and checked all con-

trols, utilizing the color test patterns from WNBT. Three days later found us tuning in our first color television at home. It was "The New Review," CBS, and from the standpoint of subject matter was a poor example of color possibilities. Skin tones were yellowish and lip makeup was excessive. A slight adjustment of the flesh control partly corrected the jaundiced appearance of the actors. We experimented with the convergence control for the first time and, possibly due to aging of components, was found to be slightly out of register.

Our impatience for more color programming mounted as the days slipped by. We realized that we would have the loan of the receiver for but a limited time and that all too few colorcasts were scheduled. It seemed that we could enjoy about one hour per week of mediocre subjects, including the Scholz-Andrews fight. This editor doubts if any prospect for a color set could be sold from this example. Our enthusiasm for color reached a climax on March 28 when NBC set up their color cameras at New York's Botanical Gardens. This production was excellent from both color and production standpoints. It is a real thrill to enjoy the sparkle and life produced by various plants and flowers when seen in their true colors. A three-dimensional effect and an added depth to the picture results from color television. Small objects which are not even noticed on monochrome are readily identifiable. It has been noted that picture quality (at least at this writing) of color signals on the monochrome set were not as compatible as one would expect. For example, reception of color on a color set is found to be in good focus while the same signals received on the monochrome set always appear fuzzy and contrast excessive.

A total of approximately 125 hours use has now been chalked up on the color set. It is interesting to note that no corrections have been required on any secondary control since the first week of use. It is only necessary to adjust the fine tuning and the color control occasionally when receiving colorcasts. Contrary to many opinions, a color receiver is far simpler to tune than several monochrome sets used in the past.

Now that we have good quality color television receivers, the need remains for more and better telecasts in color. Yes—color TV is here and it's terrific!

big values new releases



send for ALLIED'S Latest Free Supplement



"Golden Knight"

24-Watt High Fidelity Amplifier

A standout choice for limited-budget home music systems. Features ±0.75 db, 20 to 40,000 cpa response; harmonic distortion less than 1% at rated output; I. M. less than 0.5% at normal listening level; low hum (80 db below rated output); switch for proper loading of G. E. Pickering or Audak cartridges; 3-position record equalizer; bass and treble controls; inputs for magnetic phono, mike, tuner and auxiliary. Finished in satin-gold. 8 x 14 x 9" deep. With connectors, shaft extenders and separate panel for cabinet mounting. For 110-130 v., 50-60 cy. A.C. Shpg. wt., 30 lbs. Guaranteed for one full year.



"Golden Knight" Hi-Fi Music Systems

Phone System: A super value, true hi-fi phone system, with prepared cables and color-coded plugs for easy custom installation. Includes: "Golden Knight" Amplifier; Electro-Voice SP-12B 12" Radax Speaker; famous Garrad RC-80 3-speed record changer, and G. E. RPX-050 triple-pluy cartridge with dual-tip sapphire stylus. Shpg. wt., 60 lbs.

94 5X 127. Net, only FM-AM Phone System: As above, but includes new Knight 727 FM-AM Tuner. Shpg. wt.,

94 5X 128. Net, only \$214.50



Knight VT Volt-Ohm-Milliammeter Kit

Terrific Value! Response to 2.5 mc. Bridge-type circuit; 1% resistors. Input res.: DC. 20 megs; AC. 1.5 megs. 43% meter. Ranges: AC p-to-p volts. 0-8-28-84-280-840-280-60-200; AC rms & DC volts, 0-3-16-30-100-300-1000; DC ma. 0-30-10-30-10-300-1000; res. 0-100-104-1004 (homs & 0-1-10-1000 megs; cap., 005-5, 05-5, 5-50, 5-500, 50-5000 mfd. With tubes, leads, case, instructions. For 110-120 v. DC or 60 cy. AC. Shpg. wt., 6½ lbs.

83 F 120. Net, only . . 83 N 121. Hi-V Probe; extends DC range to 30 KV . . \$6.95 83 N 122. Hi-Frequency Probe for AC range to 200 mc \$5.95



Wall "Trig-R-Heat" Soldering Gun

New transformerless quick-heat gun-very lightweight; per-New transformerless quick-heat gun—very lightweight; per-fect balance. Squeeze the trigger—you're ready to solder in 3 seconds. Long, narrow 6½" barrel. Features thermostatic-action "brain"—automatically regulates gun wattage from 150 to 400 watts to meet needs of the job. Built-in light; iron-clad ½" tip. U.L. Approved. For 110-120 v., AC or DC. Shpg. wt., 2 lbs.

46 N 850. Net, only\$7.85



JFD Super-Jet VHF Fringe Antenna

Model 2135. New, 2-bay all-channel VHF stacked array for fringe areas. Dual reflectors provide flat response on low channels. Conicaltype driven elements for broad band-width. High band sections consist of 2 driven elements and 2 directors each—spaced and phased for peak performance. With half-wave stacking bars. Entirely pre-assembled for easy installation. I square aluminum boom. Less mast and 300 ohm line. Shpg. wt., 18 lbs.

98 CX 465. Net... JET 213. As above, but single-bay array. Shpg. wt., 81/2 lbs. 98 CX 464. Net\$11.00

Knight Crystal Mike Value. A real buy in a moisture-aealed crystal mike for recording or Amateur use. Response, 60-7500 cycles. Output level, -50 db. High impedance. Insulated inner elements for safe AC-DC use. With 5-ft. shielded cable. Shpg. wt., 1 lb. 99 \$ 599. Net, only.....



ALLIED RADIO





New Knight Combination Tape Recorder and 8-Watt P. A. System

Amazing value in a versatile Hi-Fi recorder and powerful P.A. System. Records Amazing value in a versatile Hi-Fi recorder and powerful P.A. System. Records simultaneously during P.A. use. Outstanding features: quality push-pull 8-watt amplifier; 2 built-in oval speakers for play-back and P.A.; jacks for external speakers thelow); push-button control of recording and playback functions; 2 inputs for recording from mike, radio, phono, TV, etc., recording time scale. Exceptional response: 7.5° speed, ± 3 db from 65-10,000 cps; 3.75° speed, ± 3 db from 75-7500 cps. Recording time (1200 ft. reel): 7.5° speed, ½ hour continuously, one hour overall; 3.75° speed, one hour continuously, two hours overall. Maroon and gray luggage-type case, 9½ x 17¹, x 14¹, s² With crystal mike, 600 ft. reel of tape and take-up reel. 110-120 v., 60 cycle AC. 32 lbs. 94 RX 635. Net, only 96 RX 635. Net. only

Accessory Speakers: Two 12" speakers in 2-section case. With 25 ft. cables and plugs. 20 x 9 x 16". Shpg. wt., 21 lbs. 96 RX 637. Net. 342.00 Remote Control: For starting and stopping recorder. 18 ft. cable and plug. 2 x 3 x 3". 3 lbs. 96 R 636. Net. 56.64

Special Value Knight Recording Tape

Top quality !4" tape at very low cost. Plastic base smoothly coated with red oxide. Features low noise level and uniform output. Type "A".
98 R 898. 600 feet. Net each, \$1.37. 5 or more, each \$1.29 & R 899. 1200 feet. Net each, \$2.10.5 or more, each \$1.89



Servicemen's Corry-All Case Quantities

Limited




U-C Lite 'Big Beam' Hand Lamp

A "powerhouse" of brilliant portable light. Features 4" lamphead with parabolic reflector, double-atrength lens and long-life bulb; focuses for wide or narrow beam. Separate switches for flashing beacon and headlight. Beacon flashes 112 times por min. Head bracket adjustable 95° in vertical plane. Lamp, beacon arm and handle chrome-plated; battery case in red enamel. Uses one 6-v. hattery (not supplied). Shpg. wt., 3½ lbs. 78 J 350. Net, only 36.63 53 J 2028. Hurgeas F4H Battery. Net 67c

New Rider Books on Color TV



ALLIED RADIO CORP., Dept. 1-F-4 100 N. Western Ave., Chicago 80, III.	Supplement
Send FREE ALLIED Supplement No. 139.	
Enter order for	
	enclosed.
Name	
Address	
CityZoneSta	ite

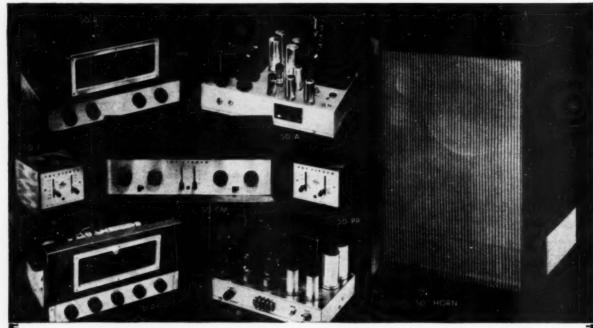

The Best Costs Less When You Buy

THE FISHER

Custom Audio Components

■ If you are buying 'for keeps' buy the best *first!* Buy FISHER, *quality* leader for seventeen years. Engineered for the professional, functionally designed for home use. "Of the very best!"—High Fidelity.

FM-AM TUNER, Model 70-RT

Features extreme sensitivity, low distortion and low hum. Armstrong system, adjustable FM-AFC and AM selectivity. Preamplifier-equalizer, 2 inputs, 2 cathode follower outputs. Six controls. Self-powered. \$184.50

FM-AM TUNER, Model 50-R

Same features as 70-RT above, but designed for use with external preamplifier-equalizer such as 50-C. Hum level better than 100 db below 2 volts output. Fully shielded and shock-mounted. Self-powered. \$164.50

MASTER AUDIO CONTROL, Series 50-C

16 choices of record equalization, plus separate bass and treble tone controls, loudness balance control. Five inputs and input level controls, two cathode follower outputs. Chassis only, \$89.50 · With cabinet, \$97.50

25-WATT AMPLIFIER, Model 70-A

50-watts peak! More clean watts per dollar. Less than ½% distortion at 25 watts (0.05% at 10 watts.) Response ±0.1 db, 20-20,000 cycles; 1 db, 10 to 50,000 cycles. Hum and noise virtually non-measurable! \$99.50

50-WATT AMPLIFIER, Model 50-A

100-watts peak! World's finest all-triode amplifier. Uniform within 1 db, 5 to 100,000 cycles. Hum and noise 96 db below full output. IM distortion below 2% at 50 watts. Highest quality components thruout. \$159.50

SPEAKER ENCLOSURE, Series 50

NEW! Regardless of the speaker or enclosure you are now using, the "50" Horn will revolutionize its performance. For use with 12" or 15" speaker systems. 50-HM(Mahogany) \$129.50 · 50-HB(Blonde) \$134.50

PREAMPLIFIER-EQUALIZER, Model 50-PR

Professional phono equalization facilities at low cost!
Independent switches for LF turn-over and HF roll-off.
Output lead up to 50 feet. Can accommodate any low-level, magnetic pickup. Self-powered.

\$22.95

HI-LO FILTER SYSTEM, Model 50-F

Does what ordinary tone controls cannot do, for it suppresses all types of noise with an absolute minimum loss of tonal range. High impedance input; cathode follower output. Use with any equipment. \$29.95

Prices slightly higher west of the Rockies

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORPORATION · 39 EAST 47th STREET · NEW YORK, N. Y.

ADVANCE! Raise your earning power-learn RADIO-TELEVISION-ELECTRONICS by SHOP-METHOD MASTER ALL PHASES!

HOME TR

GOOD JOBS AWAIT THE TRAINED RADIO-TV TECHNICIAN

There is a place for you in the great Radio-Television-Electronics industry when you are trained as National Schools will train you at home!

Trained technicians are in growing demand at good pay -in manufacturing, broadcasting, television, communica-tions, radar, research laboratories, home Radio-TV service, and other branches of the field. National Schools Master Shop-Method Home Training, with newly added lessons and equipment, trains you in your spare time, right in your own home, for these fascinating opportunities. OUR METHOD IS PROVED BY THE SUCCESS OF NATIONAL SCHOOLS TRAINED MEN, ALL OVER THE WORLD, SINCE 1905.

EARN WHILE YOU LEARN

Many National students pay for all or part of their training with spare time earnings. We'll show you how you can do the same! Early in your training, you receive "Sparetime Work" Lessons which will enable you to earn extra money servicing neighbors' and friends' Radio and Television receivers, appliances, etc.



LEARN BY DOING

ADIO TELEVISION

You receive and keep all the modern equipment shown above, including tubes and valuable, professional quality Multitester. No extra charges.

tunity in Radio-Television-Electronics, and an actual

Sample Lesson. No costno obligation. Use the coupon now-we'll answer by return airmail.

APPROVED FOR VETERANS AND NON-VETERANS Check coupon below

FREE! RADIO-TV BOOK

AND SAMPLE LESSON!

illustrated Book of Oppor-

Send today for National Schools' new,

T. R. F. Receiver

Both Resident and Home Study Courses Offered!

ATIONAL SCHOOLS LOS ANGELES 37, CALIFORNIA . ESTABLISHED 1905 IN CANADA: 811 W. HASTINGS STREET, VANCOUVER, B.C.

Radio Manufacturing, Sales, Service • Telecasting Television Manufacturing, Sales, Service Laboratories: Installation, Maintenance of Electronic Equipment **Electrolysis, Call Systems** Garages: Auto Radio Sales, Service

National Schools Training is All-Embracing

National Schools prepares you for your choice of many job opportunities. Thousands of home, portable, and auto

radios are being sold daily-more than ever before. Tele-

vision is sweeping the country, too. Co-axial cables are

now bringing Television to more cities, towns, and farms every day! National Schools' complete training program

qualifies you in all fields. Read this partial list of opportu-

Sound Systems and Telephone Companies, Engineering Firms Theatre Sound Systems, Police Radio And scores of other good jobs in many rela

TELEVISION TRAINING

nities for trained technicians:

Business of Your Own • Broadcasting

Signal Generator

You get a complete series of up-to-theminute lessons covering all phases of repairing, servicing and construction. The same lesson texts used by resident students in our modern and complete Television broadcast studios, laboratories and classrooms!



Audio Oscillator

ACTS FASTEST! MAIL TO OFFICE HEAREST Y (mail in envelope or paste on postal card)

NATIONAL SCHOOLS, Dept. RH-64 323 West Polk Street 4000 S. Figueroa Street Los Angeles 37, Calif. Chicago 7, III. Send FREE Radio-TV Electronics book and FREE sample

lesson. No obligation, n	o salesman will call.	
NAME	BIRTHDAY	19
ADDRESS		
CITY	ZONE STATE	

Check if interested ONLY in Resident Training at Los Angeles. VETERANS: Give Date of Discharge



no other rotor offers SO MUCH

a complete line

TR-2 the heavy duty rotor with compass control dial cabinet.

TR-4 the heavy duty rotor with meter dial cabinet.

TR-11 all purpose rotor with meter dial cabi-

TR-12 all purpose rotor for large TV antenna arrays with meter dial cabinet.

widely promoted on TV widely promoted to consumers on TV. ALL CDR ROTORS are PRE-SOLD for you through an extensive campaign to millions every week explaining the advantages of the CDR.

completely metchandised

completely merchandised. the easiest to sell in addition to the TV spot coverage. there are newspaper mats, window streamers, envelope enclosures ... and an animated point of sale display ... all the tools you need to sell the BEST SELLING ROTOR!

CORNELL-DUBILIER SOUTH PLAINFIELD, N. J.





THE RADIART CORPORATION CLEVELAND 13, OHIO

WILLIAM SCHOOLEY, owner SCHOOLEY TELEVISION SALES & SERVICE 3019 W. 111th Street Chicago, Illinois

"Here's proof the CQS Plan can really help your business"



"CBS-Hytron is running advertisements like these in LIFE. Maybe you've seen them and noticed they really do a selling job for us service-dealers. Well, I'm one service-dealer who is cashing in on a plan that's tailor-made for me."



"So, I'm using the CQS Tags on every job. Many of my customers now ask for them. They like the Tag's lay-it-on-the-line certification. Since December, I've ordered three lots of Tags . . . 500, 1000 and 2000."



"I like my customers to know I'm the dependable CQS service-dealer they read about in the big magazines like LIFE and the POST. So I make sure they do . . . by using the CQS Clocks, Signs, Decals, etc., available to any service-dealer."



"Take my word for it. Here's a plan that's so simple . . . so sound that any servicedealer is missing a real bet, if he doesn't tie in . . . and cash in. The boost that CQS has given my business proves it."



"Look at the 'sell' of these new CQS Streamers! Get aboard this CQS plan. It can do just as fine a job for you as it is doing for me. Take a tip. Find out today the facts about CQS. Prove to yourself that CQS can build up your business, too."

GET YOUR Certified QUALITY SERVICE TAGS...imprinted with your name and address. Use them on every job. Get your big, new CQS CBS-Star Kit. It contains:

- A. Six smashing, colorful CBS-Star stream ers. Each features a different CBS-TV star: Benny . . . Burns and Allen . . . Gleason . . . Godfrey . . . Murrow . . . and Marie Wilson. Each streamer is a different size and shape. Each one sells the Star Performance of your Certified Quality Service.
- B. New colorful inside/outside CQS decal.
- C. Business Builders Catalog showing the many hard-hitting sales aids available
- CBS-STAR KIT IS FREE with your order for CQS Tags . . . Kit alone, 25%.

special offer. Or use coupon:



CBS-HYTRON Main Office: Danvers, Mass.

A Division of Columbia Broadcasting System, Inc.


A member of the CBS family: CBS Radio - CBS Television Columbia Records, Inc. • CBS Laboratories • CBS-Columbia • and CBS-Hytron A CBS-Star Kit only @ 25¢ (for handling and mailing) I enclose \$..... to cover Tags and/or Kit. (Please send cash, check, m.o. . . . no C.O.D.'s.) HERE IS MY 3-LINE IMPRINT FOR TAGS (please print name and address) State

@ \$2.25, 250; \$3.50, 500; \$6.00, 1000

CBS-HYTRON, Danvers, Mass.

Please rush me:

June, 1954

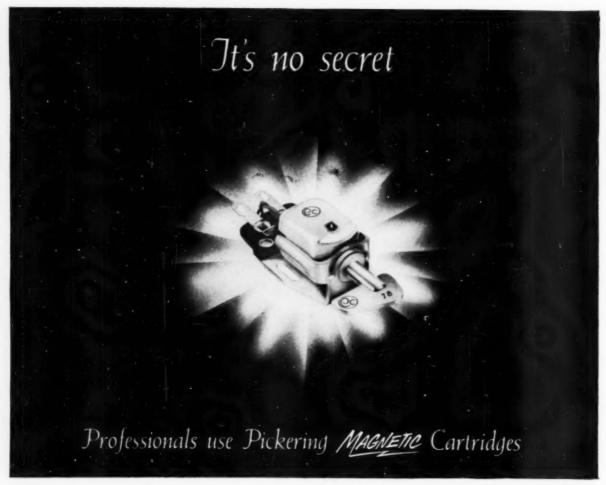

You're in the best of company if you use a Pickering Magnetic Cartridge. You have this in common with:

- 1. Leading record companies who use Pickering Cartridges for quality control.
- 2. Leading FM/AM good music stations and network studios.
- 3. Leading manufacturers of professional equipment for radio stations, recording studios, wired music systems and automatic phonographs, who install Pickering Cartridges for the maximum performance of their equipment.

Why Pickering Magnetic Pickups are the Choice of Recording and Broadcast Engineers!

"All modern disc recordings are made with Moderne cutters. Within the geometrical and mechanical limitations of recording and reproducing equipment, a Pickering Pickup will re-generate an exact replica of Moderne cutter response to the original program of music, speech or sound. This is a fundamentally inherent characteristic of the Pickering Pickup, supported by basic electromagnetic theory and countless

precise laboratory measurements. This is why Pickering Manuel Pickups provide the most nearly perfect coupling possible, between reproducing equipment and original program. This is why they sound cleaner...less distorted.

"Through the medium of the disc material, the reproducing system is effectively driven by the cutter electrical response itself."



PICKERING and company incorporated . Oceanside, L. I., New York

PICKERING PROFESSIONAL AUDIO COMPONENTS

"For those who can hear the difference"

... Demonstrated and sold by Leading Radio Parts Distributors everywhere. For the one nearest you and for detailed literature write Dopt. C-S.



Add Technical Training To Your Practical Experience-

GET YOUR FCC LICENSE IN A HURRY I

Then use our Amazingly Effective JOB-FINDING SERVICE

●TELLS HOW -

Here Is Your GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind un'il you suc-cessfully whatin your Commercial license, pre-vided you first sit for this examination within 50 days after completing

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL YOU GET

YOUR FCC LICENSE

If you have had any practical experience-Amateur, Army, Navy, radio repair, or experimenting.

• TELLS HOW-

Employers make JOB OFFERS Like These to Our Graduates Every Month

Letter from nationally known manufacturer of high quality AM and FM transmitters. "We are very much in need at the present time of radio-electronics technicians and would appreciate any helpful suggestions that you may be able to offer." Salary up to \$412 per month to start.

Letter from nationally known airplane manufacturer. "We training or experience in radar maintenance to perform operational check-out of radar and other electronics systems . . . starting salary . . . amounting to \$329.33 per month."

These are just a few samples of the job offers that come to our office periodically. Some in filled each of these jobs . . . it might have been you!

MERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY With **OUR Coaching AT HOME in Spare Time.**

Name and Address		9999	Lesson
221014 Wilshire St., Bakersfield, California	.2nd	Phone	10
Clifford E. Vegt	Est	Phone	30
Box 1016, Dania, Florida Francia X. Feerch		Phone	38
38 Beucler Pl., Bergenfield, New Jersey 8/8qt, Ben H. Davis	. Sat	Phone	36
317 North Roosevelt, Lebauon, Illinois Albert Schooll	.2nd	Phone	23
110 West 11th St., Escondido, California			1

Carl E. Smith, E.E., Consulting Engineer, President

CLEVELAND INSTITUTE OF RADIO ELECTRONICS Desk RN-65, 4900 Euclid Bldg., Cleveland 3, Ohio

TELLS HOW-

ENGINEERING OUR INCLUDED IN COACHING TRAINING & COACHING

Money-Making

FCC Commercial

Radio Operator LICENSE

Information

Our Amazingly Effective JOB-FINDING SERVICE **Helps CIRE Students Get Better Jobs**

Here are a few recent examples of Job-Finding results:

Thanks to your course I obtained my 2nd phone license, and am now employed by ervice at Great Lakes Naval Training Station as an Engineering Specialist, "Kenneth R. Leiser, Fair thaks, Mid. Del., Mellenry, Ill. and am now employed by Civil

GETS STATE POLICE JOB

"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police." Edwin P. Healy, 264 E. 3rd St., London, Ky

GETS BROADCAST JOB "I wish to thank your Job-Finding Service for the help in securing for me the position of transmitter operator here at WCAE, in Fittsburgh."

Walter Koschik, 1442 Ridge Ave., N. Braddock, Pa.

GETS AIRLINES JOB
"Due to your Job-Finding Service, I have been getting many
offers from all over the country, and I have taken a job with
Capital Airlines in Chicago, as a Badio Mechanic."
Harry Clare, 4537 S. Drexel Bird., Chicago, Ill.

Your FCC Ticket is recognized in all radio fields as proof of your technical ability

Get All 3 FREE

MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS Desk RN-65-4900 Euclid Bldg., Cleveland 3, Ohio (Address to Desk No. to avoid delay)

I want to know how I can get my FCC ticket in a minimum of time. Rend me your FREE booklet. "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC type exam and the valuable hooklet. "Money-Making FCC License Information." Be sure to tell me about your Television Exploracing Courts.

_	Paris	CHIN	re r	Bill	ç	()	ur	16																		
NAME					6 5			6.5		ě.	 		 			8	 x 7	. 16				×		* 1		
ADDRESS .								* ×	* *	6.	 .,	. ,	 	 			 		 	×		*	× ×		. *	,
CITY																			Ti	ξ.	*		. *			

Quality Features TUNG-SOL PICTURE TUBES



Gun made of best grade non-magnetic steel.

Glass bead type assembly is stronger both mechanically and electrically—gives greater protection against electrical leakage.

Rolled edges in gun minimize corona.

Custom built stem with greater spacing

Custom built stem with greater spacing between leads assures minimum leakage.

Low resistance of outside conductive coating minimizes radiation of horizontal oscillator sweep frequency.

Deuble cathode tab provides double protection against cathode circuit failure.

Selected screen composition resists burning (X pattern).

Rigid control of internal conductive coating provides utmost service reliability.

Designed for use with single or double field ion trap designs.

One-piece construction of parts assures better alignment.

Maximum dispersion of screen coating assures uniform screen distribution.

Tung-Sol makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle.

TUNG-SOL



You Can Build A Reputation On Tung-Sol Quality



* Presenting latest information on the Radio Industry.

By RADIO & TELEVISION NEWS' WASHINGTON EDITOR

THE ULTRA-HIGHS, shuttled to the grazing grounds for quite a spell while color held sway, have roared out of the quiet hinterland into Washington, to the halls of Congress, the inner sanctum of the Commission, and scores of offices of consultants and lawvers. The raging shift has been brewing since the beginning of the year when the FCC began receiving u.h.f. permits back; it has brought about a full-scale Congressional hearing on . . . "the status and development of the u.h.f. channels in the U.S.." under the chairmanship of Senator Charles E. Potter. heading a special subcommittee on communications on the Senate Interstate and Foreign Commerce Committee. Others named to the new group were Senators Andrew F. Schoeppel, Dwight Griswold, John O. Pastore, and Lester C. Hunt.

The hearing news was applauded by ultra-high operators and the recentlyformed u.h.f. association. Senators were also quite keen about the investigation, feeling that now it would be possible to probe thoroughly all of the ways that might be used to develop the upstairs channels, so that they could become solidly united with the lowband system. One of the key problems under survey is the affiliation of networks with the newcomers, particularly in mixed markets. Other points being considered are power, availability of less low-band channels than highband, differences between systems as to cost and operation, multiple-station acquisition, and the use of v.h.f. profits to build up the ultra-highs.

Reviewing the role that they'll play in the hearings, counsel for the u.h.f. association said: "Since the first of the year, a number of u.h.f. stations have been forced to suspend operations because of economic and regulatory problems beyond their control. Until the FCC and the television manufacturers, as well as the networks, approach the problem of u.h.f. in a more realistic and intelligent fashion, the great expectations of the industry cannot be fully realized. We hope to cooperate with the subcommittee by making available facts and witnesses."

To boost interest in the high bands, several plans have been offered. The Commission has proposed that the present rule be modified to allow one owner to operate seven stations, in-

stead of five, with two of the stations using the high bands. Senator Edwin Johnson, former chairman of the main committee, differed with the Commissioners, declaring that use of the higher bands should be made more attractive to multiple-station operators. He proposed, in a bill, that no one should operate more than five low-band stations; but they could control four v.h.f. and two u.h.f. stations, or three v.h.f. and four u.h.f. stations, or two v.h.f. outlets and six high-band units, or a single low-band and eight ultra-high outlets, or no low-band and ten stations on the higher channels The measure also provides that anyone with a veryhigh permit, issued before the enactment of the bill, who yields the permit within five years of its enactment, would be entitled to a couple of ultrahigh permits, with one of them serving substantially the same area as the abandened v.h.f. permit.

The problem of power, also a critical factor, prompted the Commission to propose that the minimum power for the high-channels be raised from one to five kilowatts to assure the best possible technical service. The lower powers, now in effect, were authorized because no high-powered gear was available when the ruling was placed on the books. Stations already authorized for low power would not be disturbed, but all new applicants would be obliged to use high power immediately, unless they could show that such high-power equipment was not available. Operators have complained that it was not possible to get high-kilowatt transmitters; now the manufacturers say that such transmitters will be available. Some of the broadcast makers have promised that before the year is out, 1000-kilowatt units will be available

The affiliation problem has provoked many, and one broadcaster saw to it that the Senators knew the score. In a sizzling letter to a group of the legislators, including Senators Johnson and Potter, Farris E. Rahall, owner of several TV stations, said that some of the stations were operating a monopoly, refusing neighboring stations a tie-in with networks, because they felt that their stations offered sufficient coverage. He cited the case of a station in Philadelphia which insisted that a network use their facilities

RADIO & TELEVISION NEWS



IT SAYS IT WANTS BETTER PROGRAMS AND SPRAGUE CAPACITORS.

Don't Be Vague... Insist on SPRAGUE



Accept no substitutes.

There is a Sprague
Distributer in every
sales area in the

sprague TVL's fill the top performance bill in the toughest TV circuits. High temperatures, surge voltages, ripple currents won't faze them. Like all Sprague capacitors, Twist-Lok 'Lytics are your first line of defense against expensive call-backs.

Insist on Sprague TEL-OHMIKE®

This capacitor-resistor analyzer is the handiest instrument you can buy! Moderately priced for radio and TV repair shops, the Model TO-4 Tel-Ohmike offers top quality and accuracy for every service need. Priced so you can afford it at \$73.50



Insist on Sprague

The smallest TV 'lytics made—and the only small ones for 85°C (185°F) up to 450 volts d-c. Guaranteed for low leakage and long shelf life, they withstand high temperatures, high surge voltages. From crowded TV chassis to jam-packed portables, Sprague Atoms fit 'em all.

SPRAGUE

Get your copy of Sprague's latest radio and TV service catalog C-610. Write Sprague Products Company*, 51 Marshall St., North Adams, Mass.

*Distributors' Division of Sprague Electric Company

WORLD'S LARGEST
CAPACITOR MANUFACTURER

United States, Write

for the name of your

nearest source of sup-

ply today.

* Trademark



only, and there was no need to provide service to any other station in the vicinity. The complaining telecaster pointed out that engineering studies revealed that actually the network station had inadequate coverage in the questioned area, some sixty miles away. Declared Rahall: "If Congress or the FCC is going to permit power stations . . . to dictate to the networks, we can expect approximately 35 TV stations to claim coverage of the U.S. population, which I think establishes monopolistic operations."

Urging support for Senator Johnson's view that networks and power stations should be denied their requests for additional stations, Rahall added that in his opinion the Commission committed an error in permitting power increases to the low-band stations. He felt that such boosts could be compared to the establishment of a number of 50-kilowatt AM broadcast stations.

DIRECTIONAL ANTENNAS were offered as an answer to some of the high-band problems, some believing that such an antenna could be used as a means of gaining more coverage.

When questioned why such antennas were not authorized in the rulings is sued on freeze-lift day, a member of the Commission said that an industry-government *ad hoc* committee had studied the proposal and felt that offset carrier frequency operation would help more in reducing co-channel spacing and minimize interference, too.

The fix that u.h.f. stations are in now, appears to have changed this at-Even Commissioner George titude. Sterling declared publicly that broadcasters who use the high bands would find help in the beam antenna. At an IRE meeting recently, he said that the rules actually define . . . "a directional antenna as one that is designed or altered for the purpose of obtaining a non-circular radiation pattern. Directional antennas may not be used for reducing minimum mileage separation requirements, but may be employed for improving service."

Detailing the design characteristics of a directional antenna, the Commissioner said that such an antenna . . "designed for changing the position of the major radiation lobe from the horizontal plane to any other vertical plane is considered a directional antenna for the purposes of licensed power and power limitations. Thus, an antenna designed for beam-tilting would not be considered an omnidirectional antenna in respect to these matters, even though the horizontal radiation pattern is not directional. As a result, such stations would be licensed for the power in the horizontal plane, and would be limited to the maximum powers authorized in the rules in any vertical plane."

The Commission was aware, Sterling added, that . . . "beam tilting may result in a licensed effective radiated power which is less than the maximum radiation. This condition would occur

A Brief Survey of COLOR TV

... how its
complex character
means job opportunity
for you



-by E. H. RIETZKE,

President, Capitol Radio Engineering Institute

A GOOD MANY YEARS AGO, when he was a young fellow, my Dad was one of the country's fastest typesetters. He could go anywhere and get a highly paid job with any newspaper in the country. Then came the linotype machine! Before he knew it, my Dad's job was obsolete. He had to start all over in another line of work.

How will you get along in the age of Color TV that has already arrived? Will you have to start all over? Or will you be prepared? The choice is a matter of black-and-white-or color. As you may know, color tv involves handling an understandably much more complicated signal than for black-andwhite; the components must be in perfect balance; the margin for error is practically zero. Technical personnel need new skills in working to closer tolerances. Microwave relays and coaxial cables require added equipment and special adjustments. Before a station can originate color it needs a great deal of additional equipment, much more expensive and vastly more complicated than that for black-and-white. Slide and film equipment also require additional components and maintenance. Color camera chains are much more complex, requiring more highly skilled adjustments and care. Reports of network experiments indicate that live telecasting in color increases technical man-hours required by 30 to 50%. Lighting personnel need more skill in handling new-and delicate-problems. That's a very quick run-down from the transmitter end. Every step is a technical opportunity.

What about color receivers? They'll be bigger-with roughly twice as many receiver tubes as black-and-white. There is at least one more tuning knob the chroma control for color saturation. Maintenance is complicated, to say the least, with three highly critical video channels to trouble-shoot instead of one. Service contracts for color receivers will cost considerably more than for black-and-white, according to one highly qualified source-which should give you an idea of servicing complexity-and earnings possibilities. much for transmission and reception. Manufacture of color equipment is another field for trained technicians.

Most well-informed sources agree that color television will be spread all over the U.S. by 1956 at the latest. The years between now and then are crucial. If you are interested in an honest-togoodness career in this booming part of the booming electronics industry, here's how you can step ahead of competition, move up to a better job, earn more money, and be sure of a well-paid job: Study radio-television-electronics via CREI. You don't have to be a college graduate. You do have to be willing to invest some of your spare time-at home. You can do it while holding down a full-time job. Thousands have.

Since 1927 CREI has provided men

with the technical knowledge that leads to more job security—and more money. CREI starts with fundamentals and takes you along at your own speed, not held back by a class, not pushed to keep up with others who have more experience. You master the fundamentals, then get into more advanced phases of electronics engineering principles and practice. Finally you may elect training at career level in high specialized applications of radio or television engineering, or aeronautical radio.


The coupon below, properly filled out, will bring you-without cost-a factpacked booklet, "Your Future in the New World of Electronics," which includes outlines of courses offered, a resume of career opportunities, full details about the school, our Placement Bureau (with more requests for trained men currently on file than we can fill), and the names of some of the organizations using CREI training (like All American Cables & Radio, Inc., Canadian Broadcasting Corp., Columbia Broadcasting System, RCA Victor Division, United Air Lines, to name a few). I urge you-for your own goodto send for this free booklet immedi-

NOTE: CREI also offers Resident School instruction, day or evening, in Washington, D. C. New classes start once a month. If you are a veteran discharged after June 27, 1959, let the new GI Bill help you obtain resident (or home study) instruction. Check the coupon for more data.

CAPITOL	RADIO	ENGINEE	RING	INS	TITUTI	E
An Acer	edited Tech	nical Institute	Founde	ed in	1927	

3224 16th Street, N.W.	Dept.	116-A	Washington	10, D. C.
Send booklet "Your Future in the New World of Elec- tronics" and course outline.	CHECK FIELD OF GREATEST INTEREST	☐ Practica ☐ Broadca FM, TV ☐ Practica	d Advanced A.1 I Radio Engineer st Radio Engine) I Television Engi tical Radio Engi	ing ering (AM, incering
Name	**********			Check : Residence

City Zone ... State

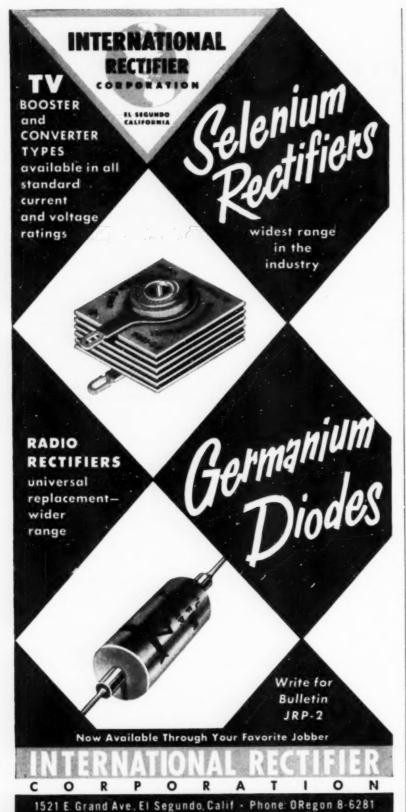

CHICAGO: 205 W. Wacker Drive · Phone: Franklin 2-3889 NEW-YORK: 501 Madison Avenue · Phone: Plaza 5-8665 where the power radiated toward the more distant portions of the service area is reduced by beam tilting for the purpose of increasing the signal strength at relatively close locations."

The Commissioner noted that his colleagues were willing to listen to proposals for changes. "To the extent the Commission might relax its directionalizing rules to aid u.h.f. stations in obtaining better coverage because of their power limitations," Sterling continued, "consideration must be given to the number of people that would gain service, as compared to those who would lose service or have it degraded as well as the remote possibility of co-channel interference."

TOWER SHARING, which has had a phenomenal success in New York City, will soon become a factor in Dallas, where two stations, operating on channels 4 and 8, will become neighbors on a common antenna, 1521 feet above the flatlands of Texas.


The stations, WFAA-TV and KRLD-TV, told the Commission that the antenna site is actually 828 feet above mean sea level, but the effective antenna height above average terrain for each antenna would be 1685 feet. KRLD-TV said that they plan to use a six-bay antenna and operate on 100 kilowatts, while WFAA-TV reported that they would use a 12-bay job and an output of 316 kilowatts. The antenna structure was described as a triangular-guyed tower, with fifteen sets of double-guy wires for support, and the longest guy leads extending to over 1000 feet from the base. The installation will cost over one-million dollars, and will include transmitter buildings for each station, which will house all of the necessary radiating gear.

The structure, a candelabra-type affair, will be located about sixteen and a half miles southwest of Dallas, and will, it was said, provide each station coverage of 80 to 85 miles for class B service.

A UNIQUE VIDEO-RECORDING system, capable of recording up to 80 percent of televised information, has been designed and constructed by scientists at the Naval Research Laboratory in Washington.

The development, prompted by the increasing number of applications of TV to military operations, features the use of a film-recording system, with a free-running shutterless camera in conjunction with an electronic shutter, to provide a versatile system adaptable to a wide variety of TV line and frame rates. The electronic shutter, which replaces the more familiar mechanical shutter on the camera, blanks and unblanks the recording picture tube. Used in a 525-line system with a camera having a pull-down time of 72° or less, up to 80 per-cent of televised information can be recorded, using a 24-frame-per-second re-cording rate. No provisions have been

(Continued on page 96)

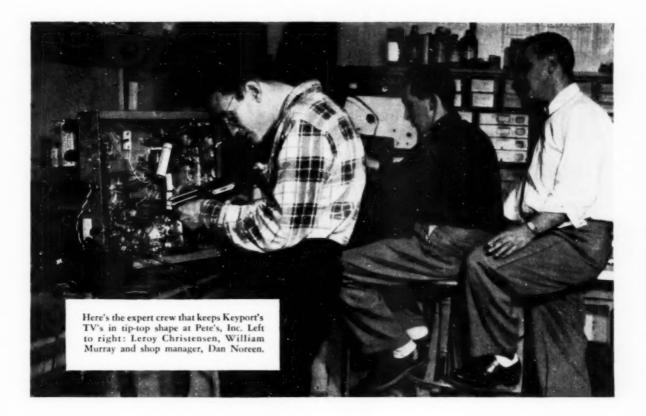


G-E Field Clinics cut repair time, step up number of calls,"

Says M. Kuarloyg, Pete's, Inc., Keyport, N. J.

"Can't keep our men away from those G-E Field Clinics," writes M. Kuarloyg, head man at Pete's, Irc., Keyport, N. J. "Their meetings give us a keen edge over competitors' service methods—we've cut down repair time and stepped up the number of calls. Customer satisfaction increases, too, because when we fix sets they stay fixed."

G-E Field Clinics show the quickest ways to diagnose and correct TV troubles...how to increase efficiency of service operations. Call your G-E Distributor for date and location of clinic nearest you.

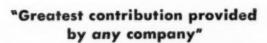General Electric Co., Radio & Television Department, Electronics Park, Syracuse, N.Y.



"Without reservation, I feel G-E's Field Clinics are the greatest help any company has given the TV service business."

You can put your confidence in_

GENERAL E ELECTRIC

NEW INVENTION OUTMODES L PRESENT ANTENNAS!

53 CLAIMS GRANTED IN 5 U.S. PATENTS ON NEW REVOLUTIONARY ANTENNA INVENTION!



ELECTRONIC ORIENTATION SWITCH

The 9-position selector switch electronically antenna in a stationary for the individual installation. position. POLYMICALENE

Low Loss External Air Dielectric

Matched Impedance

Eliminates End Sealing

Eliminates Condensation

Up to 50% less loss

Than Tubular When Wet **Easily Spiraled**

No Breaking or Shorting Patents Pending - T M. Re



THIS IS ALL YOU NEED!

The price includes the complete antenna rotates the and the 9-position electronic orientation switch. The Air Dielectric Polymicalene Transmission Line is purchased as required

> 76 your Distributor or Dealer can't supply you... Contact us for the name of one who can

- **★ GUARANTEED TO POSITIVELY OUTPERFORM** ALL OTHER ANTENNAS (with or without rotor motors) on ALL UHF, and ALL VHF stations 2 thru 83 from ALL directions.
- ★ GUARANTEED to positively give you the CLEAREST, SHARPEST, most PERFECT GHOST-FREE pictures possible in both COLOR and black-white.



UP TO 10 TIMES MORE POWER-FUL THAN ALL PRESENT CONVENTIONAL ANTENNAS!

New, revolutionary antenna, while being up to 10 times more powerful than conventional antennas, is still able to receive all television and FM stations from all directions without a rotor motor of any kind. The electronic orientation switch used with a new type transmission line developed specifically for this extra powerful antenna now makes it possible to clearly receive stations heretofore considered out of range. It is now possible to put up just one antenna, use just one transmission line, pay for just one installation and receive the finest possible reception from the stations in and coming to your area regardless of their direction.

NOW!! SOLVE YOUR ANTENNA PROBLEM

47-39 49th STREET, WOODSIDE 77, N. Y.

4 CONDUCTOR TRANSMISSION LINE

EXETER 2-1336

ONCE AND FOR ALL.





INDUSTRY

FRANK SWINEHART has joined the engineering department of the Turner



Company, Cedar Rapids manufacturer of microphones for amateur, broadcasting, and p.a. applications.

He is a graduate of Tri-State College and will be engaged in engineering and

research work for the company.

He was formerly associated with
Radiart Corporation, the Astatic Corporation, and Brush Development Company. He will now make his headquar-

ters in Cedar Rapids.

JAMES M. SKINNER, JR. has been named vice-president of Philco's television division . . . Standard Coil Products Co., Inc. has appointed HAROLD F. **BEALE** to the post of assistant to the president . . . NAT WELCH is the new vice-president in charge of sales for ORRadio Industries, Inc., manufacturers of Irish sound recording tape . . . SIDNEY A. STANDING has rejoined Raytheon as manager of its cathode-ray tube division. He will make his headquarters at the firm's new Quincy, Mass. plant . . . LOUIS W. SELSOR has been promoted to the post of distributor sales manager for Jensen Manufacturing Company of Chicago . . ABRAHAM HYMAN has been named head of the recently expanded TV antenna development section of Brach Manufacturing Corp. . . . Telectro Industries Corp. has appointed NATHAN GROSSNER to the post of chief engineer and sales engineer of its transformer division . . . E. DUDLEY BELL is the new general manager of Solar Manufacturing Corp. . . . Westinghouse's tube division has named FRANKLIN P. HINMAN acting manager of manufacturing for the division, and HARRY F. PULLEY acting manager of the division's Elmira. N.Y. plant . . . SEVERIN JONASSEM. industrial designer, has recently accepted a position with Philco in the TV product development department. For the past nine years he has operated his own studios in New York . The appointment of GEORGE J. DES-POSITO to the executive staff of Pyramid Electric Company has been announced by the company. He will be administrative assistant to the executive vice-president . . . EDWARD JAHNS has been appointed vice-president in charge of production at the Recordio plants of Wilcox-Gay Corporation . . . GEORGE S. BOND is the new advertising manager of P. R. Mallory & Co., Inc. He has been with the firm since 1937 . . . Radio Craftsmen, Inc. has promoted EDWARD S. MILLER to the

post of vice-president and JOHN NAR-RACE to the chief engineer's position . ALLEN S. NELSON has been appointed manager of distributor sales for International Rectifier Corp. of El Segundo, California . . . GORDON LE MAY is the new assistant sales manager for RMS of New York . . . The equipment sales division of Raytheon has named JOHN F. MORTEN marketing services manager . . . SAVA JA-COBSON is the new head of product engineering for Pacific Mercury Television Mfg. Corp. of Van Nuys, California . . . RAUL H. FRYE has been named vice-president in charge of engineering for National Company, Inc. He was formerly with Raytheon . Capitol Radio Engineering Institute has appointed EDWARD H. GUILFORD to the post of assistant to the president. He has been associated with the educational branch of radio-electronics field during his entire business career D.C. attorney, has been elected executive vice-president of Micamold Radio Corporation.

GRAEME W. STEWART has been appointed advertising and sales promo-



tion manager of Stewart-Warner Electric, the radio, television, and electronic products division of Stewart-Warner Corporation.

Mr. Stewart, who has been regional

sales manager in Indiana, Kentucky, Ohio, and West Virginia for the past year, will be responsible for the expanded national advertising in both consumer and trade magazines and will develop and provide sales helps and plans in the promotion field at the dealer level.

Prior to joining the firm, Mr. Stewart was in business in Denver and Cumberland, Maryland.

PRECISION POTENTIOMETERS CORPO-RATION has been organized as a subsidiary of MASTER MOBILE MOUNTS, INC. The new firm, at 1243 West Pico Blvd., Los Angeles, will manufacture precision pots and precision windings . STAN WHITE INC. has been established at 725 S. LaSalle Street in Chicago to manufacture and sell highfidelity components. The new firm is a division of EDDIE BRACKEN ENTER-PRISES . . . Herman Kaye has formed a new organization known as THE CALTECH ELECTRONICS CORP. The firm is located in a new, modern structure at 8930 Lindblade Ave., Culver City, California, where a line of hi-fi RADIO & TELEVISION NEWS

PHILCO announces

announces 3 new super-performance

TV antennas

The finest TV antennas in their class...designed by the world famous Philco Laboratories after thorough research into receiver requirements in all types of locations...designed to give complete customer satisfaction...to meet competition on any level!

PHILCO SUPER CONICAL UHF-VHF ALL-CHANNEL ANTENNA

Full 45" dowelled aluminum antenna elements and full 53" dowelled aluminum reflector assure strong signal pickup on VHF channels 2 through 13 . . . top quality performance on UHF channels 14 to 83. Single or stacked array Super Conicals produce new balanced performance... super picture quality plus high gain. All-aluminum construction in the Super Conical... it's easy to erect: Part No. 45-3096.

PHILCO SUPER YAGI VHF ANTENNAS

Quick-rig model with ten elements gives top fringe-performance on VHF channels 2 through 13. Excellent front to back ratio (6 to 1). This Super Yagi eliminates ghosts in strong signal areas...selects signals from adjacent weak area channels or cochannel stations. 10 db to 12 db gain depending on channel. Strong, all-aluminum: Patt No. 45-3112. (Single channel 2 thru 13 and broadband 2 thru 6; 7 thru 13; 4, 9, 6).

PHILCO PARAFLECTOR ALL-CHANNEL UHF ANTENNA

Light weight pre-assembled all-channel UHF antenna. Outstanding performance in far-fringe areas. High gain . . . 8 to 10 db. Exceeds gain of corner reflector of like dimensions. Impedance matched to 300 ohm line. Completely assembled, allaluminum construction...can be mounted on existing masts for immediate use... all-channel paraflector weighs only 1½ lbs: Part No. 45-3071.

See them today at your Philco Distributor



PHILCO CORPORATION

ACCESSORY DIVISION

"A" and Allegheny Ave., Philadelphia 34, Pa.



For complete information write to desk 15-F

UNIVERSITY LOUDSPEAKERS INC. 80 SOUTH KENSICO AVENUE WHITE PLAINS, N.Y.

gear and audio equipment will be manufactured . . . TRIO MANUFACTURING CO. of Griggsville, Ill. has announced the purchase of FALCON ELECTRONICS COMPANY, Quincy, Ill. The Quincy operation will be moved to Griggsville and be housed in the new TRIO plant . . STRONGHOLD PACIFIC CORPORATION has changed its name to OLYMPIC SCREW & RIVET CORPORATION. No management changes are contemplated . . ELECTRALAB, INC. has been acquired as a subsidiary by FARRINGTON MANUFACTURING CO.

E. W. GLASENAPP is the new general manager of Victoreen Instrument Company's resistor de-

partment.

9

Prior to joining the company, Mr. Glasenapp was associated with the Service Equipment Company and was instrumental in organizing Wilkor

Products, Inc. With the latter firm he held the position of comptroller and di-

rector of purchases.

In addition to supervising resistor research and development work for *Victoreen*, he will also organize an expanded national sales and service program and create a new staff of district sales managers and factory representatives.

VIRGIL GRAHAM has been placed in charge of the engineering department of the Radio-Electronics-Television Manufacturers Association. He succeeds Ralph R. Batcher who has resigned after nearly four years of service.

Mr. Graham will retain the title of associate director of the department, which he formerly held in an honorary capacity and will continue to perform the duties of that office as well as those of chief engineer.

Closely associated with RETMA's engineering activities since 1929, Mr. Graham comes to the Association on a full-time basis from *Sylvania Electric Products Inc.*, where he has been director of technical relations since 1946.

SELBY J. SINCLAIR has been elected president of Emerson Radio of Canada,

画

Ltd., a new organization which has been established to manufacture and merchandise the complete line of Emerson products in that country.

The new firm, with headquarters

at Mount Royal, Quebec is currently in production.

Norton J. Anderson is general manager of the Canadian firm while Rupert K. Grant is the sales manager.

SYLVANIA ELECTRIC PRODUCTS INC. has begun manufacturing operations (Continued on page 111)

MORE DEALERS ARE INSTALLING

CHANNEL MASTER'S


CHAMPION

THAN ANY OTHER ANTENNA IN
TELEVISION HISTORY!


All-channel reception: VHF & UHF


model no

HORIZONTAL POLAR PATTERNS

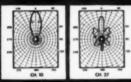

Gain

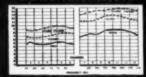

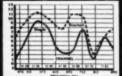

ONLY THE CHAMPION enjoys this overwhelming acceptance: over 300,000 already sold!

ONLY THE CHAMPION is powered by the unique "Tri-Pole," the triple-powered dipole system that provides fabulous VHF-UHF fringe area performance. 100% aluminum; rugged, exclusive alloy. Installs in a flash!

ONLY THE CHAMPION gives you this four-star promotion program:

- * FREE newspaper ads
- * FREE TV film commercials
- * FREE colorful display material
- * FREE consumer literature

See your Channel Master distributor for full details.

The antenna America knows best!

Introduced to millions through the editorial pages of their favorite magazines and newspapers, and on TV.

DON'T BE MISLED BY "LOOK-ALIKES" . . . THERE'S ONLY ONE REAL CHAMPION!

Model no. 325: Single bay: Model no. 325-4, Four bay: Model no. 325-6, Super Champ



CHANNEL MASTER CORP.

the World's Largest Manufacturer of Television Antennas

Copyright 1954 Channel Master Corp



Home Study Courses in TELEVISION SERVICING offered by RCA INSTITUTES



Study Television Servicing—from the very source of the latest, up-to-the-minute TV and Color TV developments. Train under the direction of men who are experts in this field. Take advantage of this opportunity to place yourself on the road to success in television. RCA Institutes, Inc. (A Service of Radio Corporation of America), thoroughly trains you in the "why" as well as the "how" of servicing television receivers.

FIRST HOME STUDY COURSE

IN COLOR TV SERVICING

Now you can train yourself to take advantage of the big future in Color TV. RCA Institutes Home Study Course covers all phases of Color TV Servicing. It is a practical down-to-earth course in basic color theory as well as how-todo-it servicing techniques.

This color television course was planned and developed through the combined efforts of instructors of RCA Institutes, engineers of RCA Laboratories, and training specialists of RCA Service Company. You get the benefit of years of RCA research and development in color television.

Because of its highly specialized nature, this course is offered only to those already experienced in radio-television servicing. Color TV Servicing will open the door to the big opportunity you've always hoped for. Find out how easy it is to cash in on color TV. Mail coupon today.

Color

Television

SEND FOR FREE BOOKLET

Mail esupen in envelope or poste on postal card. Check sourse you are interested in. We will send you a booklet that gives you complete information. No salesman will call.



RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION & AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

HOME STUDY COURSE IN BLACK-AND-WHITE TV SERVICING

Thousands of men in the radio-electronics industry have successfully trained themselves as qualified specialists for a good job or a business of their own—servicing television receivers. You can do this too.

This RCA Institutes TV Servicing course gives you up-tothe-minute training and information on the very latest developments in black-and-white television.

As you study at home, in your spare time, you progress rapidly. Hundreds of pictures and diagrams, easy-to-understand lessons help you to quickly become a qualified TV serviceman.

There are ample opportunities in TV, for radio servicemen who have expert training. Mail coupon today. Start on the road to success in TV Servicing.



RCA INSTITUTES, INC. Home Study Dept. 654 350 West Fourth Street, New York 14, N. Y. Without obligation on my part, please send me copy of booklet on:

☐ Home Study Course in Television Seguicing.
☐ Home Study Course in Color TV Seguicing.

Name____(please print)
Address_____

City____State____

"Not in 55,973 years

have I had an imp that operated so efficiently in such high temperatures," says L. (Lucifer) Satan, Hades strong man. "What's more, the improved Jet Imps are tough and won't scar under heat."




Jet Imps are designed to operate at 100°
Centigrade (212° F.—boiling point) 15° higher operating temperature than most molded capacitors available today. This means that Jet Imps not only withstand emergency conditions but also under normal operating temperatures, such as the high temperatures under a TV chassis, Jet Imps have a real safety margin for long trouble-free service.

The rugged low loss thermosetting plastic case of the Jet Imps enables them to pass the RETMA Humidity test. Jet Imps are small too, built to the sizes which conform to the requisite design factors for the finest capacitors.

See your Pyramid jobber for the new Imp.



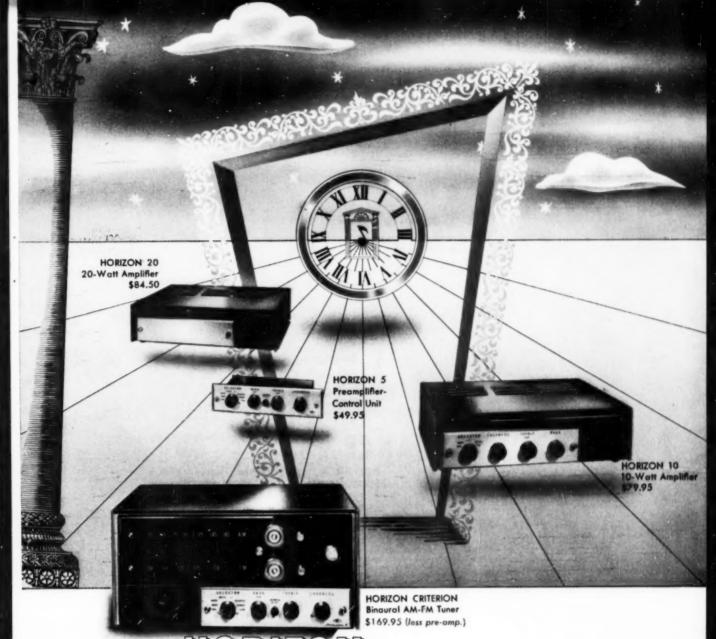PYRAMID ELECTRIC COMPANY, 1445 Hudson Blvd., North Bergen, New Jersey



line in high fided

Now - National - world's most respected maker of professional radio receiving equipment - brings you a new concept in high fidelity - the new HORIZON line! This new integrated system with advanced manufacturing techniques based on the latest research available, is so unique in circuitry, so far ahead in performance and styling it obsoletes present equipment on the market!

See it — hear it — this month!

For complete specifications, write Dept. RN-654, National Co., Inc.

tuned to tomorrow National





hardware prevents corrosion losses

Single Bay ... only \$9.95 List. Also

available in Dual and 4 Bay Stacks.

niez eorporation

permanently. Pre-assembled . . .

guaranteed 3 years!

3602 Crenshaw Boulevard, Los Angeles 36, California Branch: 315 West Walton, Chicago, Illinois

Overseas Distributor: Ad Auriema, Inc., 89 Broad St., New York 4, N.Y. Canadian Factory Distributor: Atlas Radio Corp., Ltd., 560 King St. West, Toronto 2-8.

moisture . . . not affected by extreme

Single Bay . . . \$10.95 List. Also

available in 2 and 4 Bay Stacks.

heat, cold or wind.

NOW... 2 SENSATIONAL **EICO SCOPE VALUES!**

NEW AMAZING FEATURE PACKED 7" PUSH-PULL OSCILLOSCOPE

Only EIGO Has All These Feeture

- HOR. PRIS. BESP.: Set ± 0 on 10 cpc 200 hc, -4 ob of 500 hs HOR. SENGE: 3 valts rms/inch SWEEP RANGE: 15 cps-100 hc 54TEP PRIS. COMPENSATES ATTEMBATES designates freq. (Starting presentation processes)
- enstortion, everlanding. CATMORE POLLOWER Inputs 4s

- Deth amplifier?
 PREM-PULL outputs in both amplifiers
 RETURN TRACE RAMMING
 INT. VOLTAGE CALIFORNION & CENTERIN
 1.53. full screen without distortion.
 DRECT COMMENCIAL COLUMNIC PROPERTY.
- IT PAMEL: Intensity mod. input;



EL 470K WIRED \$129.50

EICO EXCLUSIVE! 5" PUSH-PULL SCOPE, 425K, Amazing feature-packed economy-priced

Wired, \$79.95. KIT, \$44.95. PUSH-PULL V &

e AC & BC volts: 0-5, 10, 100, 500, 1000 V (30 KV with HVP-1 probe). e 5 ohm to 1000 megs. e BC Input Z 26 largs. e 4½ meter movement in can't-burn-out circuit. e 1% mult. resis-tors.

HIGH VOLTAGE PROBE \$6.05 • Extends range of VTVMs extends range of VT voitmeters to 30 KV.



SOK SWEEP GEN. KIT \$34.95.

Continuous coverage of all TV & Fm freqs. from 500 &c to 228 mc.
Swasp width variable 0.30 mc.
Crystal marker oscillator, variable amolitude.



WIRED \$49.95.



o DC Input 2 86 o 1% mult, resists

950A-K R-C BRIDGE & R-C-L COMP. KIT \$18.05. WIRED \$29.05.



· Measures & tests all resistors; .5 ohm to 500

megohms.

• Every type condenser, 10 mmf to 5000 mfd.

• 0-500 DC voltage source for capacitor leakage testing.

625K TUBE TESTER KIT \$34.95. WIRED \$49.95.

CATHODE RAY TUBE CHECKER 130K, WIRED \$24.95 KIY \$17.95



• Illum, gear-driven
"Speed Rollchart."
• New lever-action
switches for individual testing of avery ● Tests all conventional & TV tubes.

read & open

PIX TUBE ADAPTER for Tube Testers \$4.50. Checks TV picture tubes

Se, wave output at power-line freq, with full-scale readings of .1, 10 or 100 V, peak-to-peak o Accuracy ± 5% of full-case on each range.

SV & 12V BATTERY ELIMINATOR KIT 1050K HIT 529.95, WIRED \$38.95,

- DC output: 0-8 V or 0-16 V.
 Continuous current rating:
- Continuous current rating:
 A at 6 V, 6 A at 12 V.
 Intermittent current rating:
 A at 6 V, 12 A at 12 V.
 Secarate Voltmeter & Am-



NOW! ONLY IEICO- KITS

& WIRED INSTRUMENTS Gives You LIFETIME SERVICE &

'at less than our cost of handling (See EICO Guarantee Card enclosed with each Kit & Instrument).

CALIBRATION GUARANTEE

BAR GENERATOR 352K, WIRED \$19.95 KIT, \$14.95

TV picture V&H linear ithout hard-to-find stati snamitted tast pattern.

Produces 16 V or 12 H irs. Operates on TV chan-is 3, 4, or 5.



SESK MULTIMETER KIT \$24.95 WIRED \$29.95.

585K MULTIMETER KIT \$29.98 WIRED \$34.93.

20,000 Ω/V; 31 ranges.
 DC/AC/Output volts: 0-2.5, 10, 50, 250, 1000,

5000. • DC Current: 0-100 us; 10,

100, 500 ma; 10 A. • Ohms: 0-2K, 200K, 20

EICO SCOOPS!

232 K PEAK-to-PEAK VTVM with DUAL-PURPOSE AC/DC Uni-Probe



B

(Pat. Pand.)

KIT \$29.95 WIRED \$49.95

Measures directly p-p voltage of complex and sine waves: 0.4, 14, 42, 420, 1400, 4200 V p-p. DC/RMS sine voltage range: 0-1.5, 5, 15, 50, 150, 500, 1500 v. Ohms: 0-1000 megs. 7 nonskip ranges on every function. Calibration without removing from cabinet. Zero center. Freq. Resp. 30 cps-3mc. 1% precision ceramic multipliers. Exceptional stability and accuracy. Compact, portable 81/2x5x5", smart, rugged.

NEW! UNI-PROBE! Terrific time-saver! Only 1 prot for all functions-a half-turn of probe-tip selects DC OF AC-OHMS!

249 K PEAK-to-PEAK VTVM with 735" METER KIT \$39.95 WIRED \$58.95

B44 K FLYBACK TRANSFORMER AND YOKE TESTER Kit \$23.95 Wired \$34.95

Tests all flybacks and yokes, in or out of TV set -in just seconds! Detects even 1 shorted turn!

Exclusive separate calibration for air-and ironcore flybacks assures utmost accuracy. Large 41/4" meter, 3 colored scales. Compact, portable smart, rugged. (81/2x5x5").

1171K RES. DECADE BOX KIT \$19.95 WIRED \$24.95 BECADE CONDENSER BOX KIT \$180K KIT \$14.05 WIRED \$19.05 RTMA RESISTANCE SUBSTITUTION BOX 1100K WIRED \$8.05 KIT \$5.50



315K DELUXE SIG. GEN. KIT \$39.95. WIRED \$59.95.



Covers range of 75 kc to 150 mc.
 7 calibrated scales: accuracy better than 1%.

Bandspread vernler tuning.

tuning.

• 4-step RF shielded output multiplier: co stant output Z.



e Complete sine wave coverage, 20-200,000 cps in 4 direct-reading

536K MULTIMETER KIT \$12.90. WIRED \$14.90. S26K MULTIMETER KIT \$12.90. WIRED \$16.90.



• 1000 Q/V; 31 ranges • DC/AC volts: Zere te 1, 5, 10, 50, 100, 500, 5000. • DC/AC Current: 0-1, 10 ma; 0.1, 1 A.

ma; 0.1, 1 A. Ohms: 0-500, 100 K,

148K SIG. TRACER KIT \$19.00.



CRT to all

320K SIG. GEN. KIT \$19.95. WIRED \$29.95. 322K BIG. GEN. KIT \$23.05. WIRED \$34.96.



Fundamentals 150 kc to 34 mc, harmonics to 102 mc.
 5-step band switching.
 Colpits audio oscil-

Colpitts audio oscillator generates 400 cps pure sine wave voltage.
 Permits pure RF, modulated RF, or pure


Write NOW for FREE latest Catalog R-6

Ask your jobber for FREE EICO business building decals.

Seperate Assembly & Operating Manuals supplied with each EICO KIT!

SAVE OVER 50%! See the famous EICO line TODAY, at your local jobber

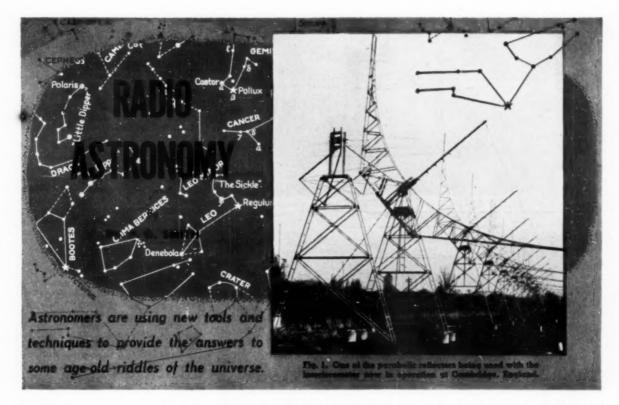ELECTRONIC INSTRUMENT CO., Inc., 84 Withers Street, Brooklyn 11, N. Y.



N 1942 radar operators in England began to report a new kind of jamming observed on their meter-wavelength receivers. Weak radar echoes became lost in the "grass" on the (radar) screen, as if swamped by "noise" from a powerful transmitter. In the Army Operational Group, a scientist named J. S. Hey-later to be known as one of the pioneers of the new science of radio astronomy-examined the reports. He established that the source of the "jamming" was no enemy station, but the sun, and he noticed that at that time an exceptionally large sunspot was crossing the sun's face.

Radio amateurs can detect this radiation from the sun during periods of sunspot activity, and even television screens are affected by it, but few people know that the sun and some other celestial objects are radiating short radio waves continuously.

The first observations of this steady radiation were made in 1932 by an American radio engineer, Jansky, who was investigating the level of noise picked up by a sensitive receiver on a frequency of 20 mc. He found that a directional antenna gave a greater noise signal when pointing at the constellation of Sagittarius, in the brightest part of the Milky Way, than in directions away from this high concentration of stars. Ten years later, a radio amateur, Reber, built a parabolic reflector antenna 30 feet in diameter, in his own yard, and used this to make a map of received signal strength on frequencies up to 500 mc. over a large part of the sky.

Then came one of the most startling

discoveries, again first hinted at by J. S. Hey. Workers in Australia and England found that the radio waves picked up by Jansky and Reber came, not only from the Milky Way but also from some quite definite points in the sky, as though individual stars were transmitting to us. But there were no bright stars at these points, and it was not until 1952 that these "radio stars" were identified with visible objects in the sky; even then the objects were so faint and inconspicuous that it needed the 200-inch Hale telescope at Mt. Palomar to find them. Many astronomers have become interested in this new science as an extension of astroncmical techniques, and radio-astronomy is now being put to use in many parts of the world extending our knowledge of the solar corona, interstellar gas, nebulae, and even of our own ionosphere. In this article we shall be concerned less with the results than with the methods, since the problems of technique are of great interest and are not well known.

The two main problems facing the radio-astronomer wishing to study radio waves from some object or region in the sky are simply stated. First, the power available in his antenna is usually not greater than about 10-16 watt. Second, the beam width of his antenna is usually vastly greater than the angular size of the object, and the radiation picked up may well have come from many other objects in this region. Both these difficulties, of signal strength and resolving power, clearly call for large antenna systems and the radio astronomers are, in fact, build-

ing large antennas for this work. In Manchester, England, there is now under construction a very remarkable parabolic reflector antenna. This will be 250 feet in diameter, and it will be so mounted that it can be directed towards any part of the sky. The reflector will be made of wire mesh, and the accuracy of its surface will be such that it can be used on wavelengths as short as a half meter or less. But many observations can be made with much smaller antennas by using the principle of the radio interferometer.

If two similar antennas spaced several wavelengths apart and both directed towards the sun, are connected to the same receiver, as in Fig. 6A, it is possible to distinguish the radiation received from the sun against a background of radio waves from the stars behind it, although this background may be several times more intense than the solar radiation. The records of total power received from such a radio interferometer as the sun moves slowly across the sky would be like those in Fig. 3, showing some actual records on various wavelengths. In each the sinusoidal variation of signal is due to the sun passing in and out of the interference zones of the spaced antennas, whereas the steady signal, most evident on the longer wavelengths, is from the extended source of the Milky Way background. An improved method of recording recently used makes a record of only the sinusoidally varying signal, giving the intensity of the solar radiation without any confusion from the background radiation. The method of achieving

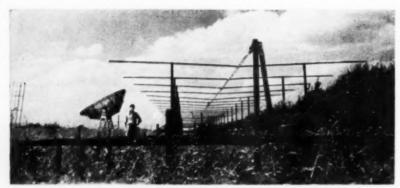


Fig. 2. Array of full-wave dipoles at 3.7 meters. This array is one-half of an interferometer for detecting radio stars. See text for full details.



The 600-inch "radio telescope" installation at the Nava! Research Laboratory which is being used to study radio "signals" from the sun, moon, and stars. Scientists use this research tool to extend man's knowledge of the universe and to assist in forecasting the conditions for radio communications work.

this, known as phase-switching, will be described after we have examined more closely the problem of detecting these exceedingly small signals.

The character of the signals received from the sun and the stars is exactly the same as that of "receiver noise. If we connect the input of a receiver first to an antenna and then to a dummy load, the difference in signal may be demonstrated as a change in


the output of a detector circuit, but this change may be only a few per-cent of the output, most of which is due to the receiver noise. It is necessary to record this difference without including receiver noise, and this is achieved in the schematic of Fig. 6B. The use of a phase-sensitive detector enables a long time constant to be used in the output circuit, and the smoothed output records the difference between the two levels of noise. An improvement is again made in Fig. 6C, where the antenna noise is continuously compared with the noise generated in a controllable local source, in practice, a noise diode. The output from the local source is automatically adjusted to equality with the antenna noise, and a record of the current in the diode gives a direct record of antenna noise unaffected by the characteristics of the receiver. The records in Fig. 3 were made in this way.

These methods of detecting small noise signals have been widely used in the measurement of the total noise power received at an antenna. But in radio astronomy it is often necessary to select only that part of the noise which is coming from a small source in the sky, perhaps a radio star or a sunspot, and to disregard a large proportion coming from a diffuse background of other sources. A new method of de-

tection is then used.

In the schematic of Fig. 6D a pair of antennas is connected in a radio interferometer with a device for reversing the phase of the signal from one antenna periodically. The lobes of the interferometer radiation pattern then shift by a half lobe width, due to the phase shift, and the signal from a source smaller than the lobes of this pattern will change periodically by an amount depending on its position in the pattern. Again a phase-sensitive detector is used to measure this periodic change in output. In Fig. 4 we see the recorded output of such a phaseswitching receiver connected to a large interferometer operating at a wavelength of 3.7 meters, shown in Fig. 2. The output is centered on zero, and the groups of oscillations each record the passage of a radio star through the antenna receptivity pattern as the earth rotates. This method of recording radio stars has been used in the accurate location of some of the most intense radio stars. A record from the intense radio star in Cassiopeia using part of the same interferometer is shown in Fig. 5.

The interferometer in Fig. 2 is locat-

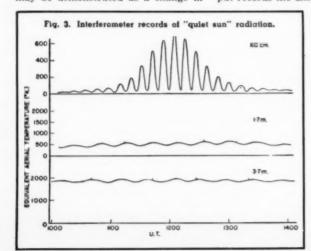

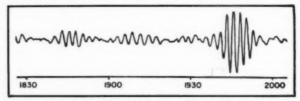


Fig. 4. Part of interferometer recording showing the presence of several of the minor "radio stars.

Fig. 5. Section of record with high sensitivity showing intense source in Cassiopeia. See text for details.



ed along an east-west line so that each radio star is detected as it crosses the meridian, a line from the zenith to the south point. The time of this crossing, found from the record, gives the position of the star in the sky. The timing may often be carried out to an accuracy of about 0.1 second, but unfortunately the actual position of the star cannot be determined quite as accurately as this. For one thing, the position of the interferometer axis must be known, and with the antennas of Fig. 2 this cannot be defined to better than about 2 minutes of arc. The interferometer in Fig. 7 was specially built for such work, and the line joining the bearings of the two parabolic reflectors was determined to 10 seconds of arc. These reflectors are two of the antennas of the "Wurzburg" radar set much used by the Germans during the war. They are 27 feet in diameter, and the two are mounted 900 feet apart, 200 wavelengths at 1.4 meters, the wavelength used in the most accurate direction finding experiment yet made. With this interferometer, a radio star in the constellation of Cassiopeia was located within an area only 10 seconds by 30 seconds of arc. The position was given to astronomers at Mt. Palomar, who found with the 200-inch telescope a new type of nebula exactly in the right place.

This new branch of science is certainly providing new tools for the astronomer in his survey of the heavens, but it may also prove to be a useful approach to some studies of the ionosphere. When Hey first detected radiation from a radio star, he distinguished it from the background because the signal was fluctuating in a peculiar way. This effect we now know to be very similar to the scintillation, or "twinkling," of ordinary stars. It is caused by refraction in irregularities in the earth's ionosphere, through which the radio waves pass, and by studying the fluctuations in signal it has been found that the irregularities are in the upper part of the F-region. inaccessible to pulse-sounding methods. It appears that the top of the F-region occasionally becomes corrugated, to an extent of about one per-cent of its total depth, the wavelength of the corrugations being about 5 km. The whole structure is drifting across the earth at a speed of several hundred milesper-hour, and the effect on the ground is similar to the moving pattern of sunlight on the bottom of a swimming pool when waves disturb the surface. The cause of this ionospheric disturbance is still unknown.

Another useful way of investigating the ionosphere has been suggested. As the radio waves from a radio star pass through the ionosphere they may be refracted in such a way as to make the star appear in the wrong position. The amount of this displacement may be measured, and depends primarily on the total number of electrons in a vertical column right through the ionosphere. Pulse-sounding methods are not suitable for this measurement, and

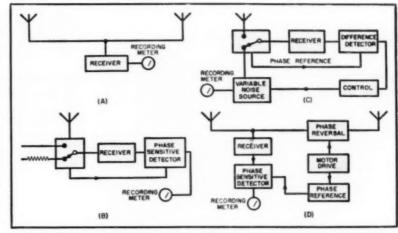


Fig. 6. (A) How two similar antennas, spaced several wavelengths apart, are used to detect radiation from the sun. (B) Use of a phase-sensitive detector to eliminate receiver noise. (C) Improved version of the circuit shown in (B) in which the antenna noise is continuously compared with the noise generated from a controllable local source, a noise diode. (D) A pair of antennas connected in a radio interferometer with a device for reversing phase of the signal from one antenna periodically.

it is likely that understanding of the ionosphere, still full of mysteries, will be helped by these new experiments.

The most exciting discoveries of radio astronomy have been in the search for sources of radio waves in our galaxy and in extragalactic nebulae, and this search is being pursued with great vigor in several places. The new Manchester antenna will be used in this work. Recently some details were published on a new antenna1 at the Ohio State University designed to carry on the search. There is, however, a large interferometer antenna now in operation at Cambridge, England, which may well be called the largest radio-telescope in the world. Its parabolic reflectors cover an area close to 50,000 square feet. Results from a survey of radio sources in the Northern sky should be available in a few months' time. No description of this instrument has yet been published, and a picture of one of the reflectors in Fig. 1 is the only one available as yet. It is hoped that this instrument will provide some further clues to the solutions of the great problems "What are radio stars?"; "How many are there in our galaxy?"; "Do other galaxies have radio stars like ours?"—questions we may hope to have answered in only a few years from now.

REFERENCE

 Kraus, J. D. & Ksiazek, E.; "New Techniques in Radio Astronomy," Electronics, September 1953

Fig. 7. Parabolic reflectors used in an interferometer for accurate direction finding.

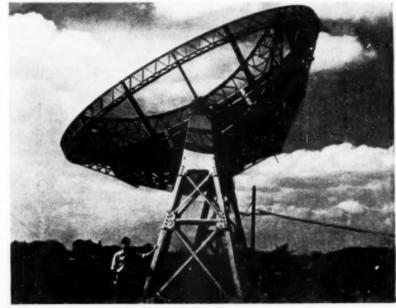


Fig. 1. Appearance of a 1.5 mc. FM beat on the face of a CRT. This pattern is not stationary but changes with the variations in sound carrier modulation.





CARL J. QUIRK

Allen B. Du Mont Laboratories

Author, "A Handbook of Television Interference"

Part 2. Tells how TV interference gets into the set, how it may originate in the set, and how to calculate the frequency of the TVI pattern on the picture tube.

N LAST month's article the five most common types of interference normally encountered in TV receivers were identified. As listed, these are: unmodulated, frequency modulated, video modulated, burst modulated, and mixed modulated. The next step is to determine how these interference signals get into the circuits of the TV set—and where they come from.

Most service technicians are aware that a superheterodyne receiver, whether radio or TV, has numerous responses. These responses can be considered as "slots" or "gates" in the frequency spectrum associated with a desired channel or frequency. It is through these "gates" that the undesired signals will enter to cause trouble.

Video Gate—The video passband of a TV receiver is normally between 0 and 4 mc. Any strong signal whose frequency lies within these limits may be picked up after the video detector. Standard radio broadcast stations are the main source of such trouble.

I.F. Gate-This is the i.f. passband of the receiver which, for all practical purposes, is about 3.5 mc. to 4.0 mc. wide. The opening provided by this "gate" is determined by a design specification of the receiver known as i.f. rejection. There are some cases, however, when two very strong signals will enter the receiver and beat together in the r.f. stage or mixer to produce an i.f. signal. Such a condition is not affected by the i.f. rejection of the receiver. Another source of interference in the i.f. range is the harmonics of the receiver's oscillator, particularly the second harmonic. This beats with the video or sound carriers of other channels to produce an i.f. signal in the set.

3. Lower Adjacent Channel—This is the 6 mc. immediately below the de-

sired channel in frequency. The opening provided by this gate is determined by the adjacent channel sound rejection. Interference that enters this way is usually due to another TV station operating in this channel.

4. Desired Channel-This is the frequency range of the station to which the set is tuned. Those interference signals which enter through this gate are generally the most difficult to eliminate since there is no filter that can differentiate between a desired signal and an undesired signal having the same frequency. Such interferences normally require elimination at the source or possibly the use of extremely directional antennas. One of the most common sources of this "onchannel" interference is the local oscillator of a neighboring receiver. Another source is the set itself, where harmonics of the video i.f. or sound i.f. fall into the channel to produce annoying interferences. This may also result from co-channel interference, the result of another station operating on the same channel.

5. Upper Adjacent Channel—This is the 6 mc. above the desired channel. Most commonly, the interference entering this gate is caused by the video carrier of a TV station occupying this upper channel. This interference exhibits itself as a back-and-forth motion from which it derives its name of "windshield-wiper" effect.

6. Image Band—Most TV receivers operate the oscillator on the high side of the incoming signal. The image band is located above the oscillator by an amount equal to the i.f. The opening provided by this "gate" is dependent upon the image rejection of the receiver.

Internal Sources of TVI

Any TV receiver is a potential generator of interference to itself. The number of possible sources of interference in any set depends upon its circuitry. For example, an intercarrier set will not include all of the interference sources of a split-channel set. First, let us consider those sources of interference which are common to both intercarrier and splitchannel receivers.

1. Video Detector. Harmonics of the video carrier i.f. which are produced in the video detector stage are either radiated back into the tuner, or find their way back through the set wiring to beat with the video carrier. As a rule, this presents a problem only when the harmonic falls directly into the channel being viewed. For example, the 3rd harmonic of a 25.75 mc. video i.f. is 77.25 mc., which is the video carrier of channel 5. The 4th harmonic of a 45.75 mc. video i.f. is 183 mc., which can beat with the video carrier of channel 8 to produce a 1.75 mc. interference.

A relatively common interference seen in many TV sets is the very fine herringbone pattern commonly referred to as "grain." Technically, it is a 4.5 mc. FM beat. The pattern (it must be watched closely) varies with the sound modulation of the desired channel.

This interference originates at the video detector as a result of the heterodyning of the sound i.f. and the video i.f. carriers. Theoretically, if the sound i.f. amplitude at the video detector were very low, the beat would not exist. Its presence is usually more prevalent in intercarrier sets than in split-channel receivers because in the former, the sound carrier runs higher in amplitude at the video detector.

Most TV sets use a 4.5 mc. trap in the video amplifier circuit to attenuate this undesired signal. Fig. 2 shows a 4.5 mc. trap in a Du Mont RA-306 chassis.

Sound in picture is another effect originating in these circuits when the sound carrier is too strong. This condition can, in many intercarrier sets, be tuned out by the customer who will still get usable pictures and sound.

However, this is not true for a splitchannel set, where the sound would be lost with a small amount of detuning. Fig. 3 illustrates a normal overall response curve which shows the position of the sound carrier. An intercarrier set should have an average sound attenuation of 30 db with respect to the video carrier. In terms of voltage, the ratio of the video carrier amplitude to the sound carrier amplitude is about 13 to 1. If, however, the ratio of video to sound is only 3 to 1 (approximately 10 db) or less, the sound will be quite evident in the picture. In such a set, it will be necessary to detune and raise the video carrier to provide adequate attenuation, with the resultant loss of fine picture detail.

2. Horizontal Output Circuit. Barkhausen oscillation occurring in this circuit will produce a "burst-type" interference, characterized by one or two vertical dark lines on the left side of the CRT. In addition, the 15,750cycle sweep voltage generated in these circuits may interfere with both the sound and video signals to produce

"buzz" and horizontal bars.

Intercarrier receivers have some additional sources of interference which do not apply to split-channel sets. Due to the relatively high level of the 4.5-mc. signal in the video detector of intercarrier sets, a beat is produced with the harmonics of the video i.f. carrier. Because of the 4.5mc. signal, the interference will vary in accordance with the sound modulation of the program being viewed. For example, the 2nd harmonic of a 25.75 mc. video i.f. plus 4.5 mc. results in a frequency of 56 mc. which, in turn, beats against the video carrier of channel 2 (55.25 mc.) to give an interference of 0.75 mc. The 2nd harmonic of 45.75 mc. (video i.f. of 41 mc. i.f. sets) plus 4.5 mc. may beat with the video carrier of channel 6 (83.25 mc.) with a resultant interference of 3.75 mc. Other interference relationships can be determined in a similar way for high harmonics. Fig. 1 shows the pattern caused by a 1.5 mc. beat of the type described here.

It is, of course, also possible for the various harmonics of the sound i.f. (21.25 or 41.25 mc.) to interfere with the video carrier of a received channel. The interference would be recognizable as FM whose pattern would vary with the sound modulation of the

desired channel.

Another possible source of FM interference, particularly in splitchannel receivers, is the sound discriminator and, in some cases, the sound limiter. If the level is high enough, harmonics of the sound i.f. are generated and find their way back into the front end to produce "inchannel" interference.

Calculating the Frequency

Throughout the discussion thus far, the interference has been referred to as a beat or heterodyne pattern on the CRT screen. To an experienced ob-

server, a mere look at the pattern will be sufficient to permit him to determine the beat frequency with sufficient accuracy. A completely inexperienced observer may not know quite how to

One might ask, "What difference does it make what the frequency of the beat is?" Actually, it makes no difference, if the source is obvious. On the other hand, as so often happens, there are a number of possible sources. One method of determining which is the one causing the trouble is to determine the beat frequency. For example, suppose a TV set has an interference pattern on channel 12, and it is suspected that a harmonic of the video i.f. originating at the video detector is the source of the interference. Let us assume that the set uses a 25.75 mc. video i.f.

Now, the 8th harmonic of 25.75 mc. appears at 206 mc. and can beat with the video carrier of channel 12 located at 205.25 mc. to produce a 0.75-mc. signal. If, however, we had no idea what a beat of 0.75 mc. looked like, we could only guess that this was what was appearing on the screen and, in many cases, we would find that prescribed cures for this type interference had no effect. Obviously, the reason they had no effect was because the interference was caused

by some other source.

The most usual type of unmodulated interference pattern consists of dark vertical or diagonal lines as shown in Fig. 4. Now, if we were to take one scanning line and concern ourselves with each segment of this line that was dark due to this interference, we would find that the dark segment was caused by the positive half cycle of the interference signal. This assumes that the signal is applied to the cathode of the CRT which is the most common practice at this time. Obviously, the negative half cycle of this signal occurred during the light portion immediately following the blacked-out segment. Since the length of the horizontal scanning line represents a specific length of time, it follows that the greater the number of these dark segments that occur during one line the greater the frequency of the beat at the CRT cathode.

Since the horizontal scanning frequency is 15,750 cps, the time con-

Fig. 4. Beat pattern caused by unmodulated r.f. signal above 15.750 cps. These lines can also appear vertically.



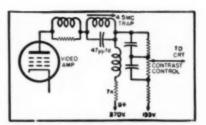


Fig. 2. A 4.5 mc. trap is commonly used between the video amplifier and CRT to eliminate this signal from the picture.

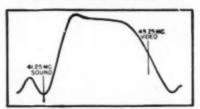


Fig. 3. Typical over-all response curv for an intercarrier set. Note that the sound carrier is at a trapped frequency.

sumed by one complete scanning line including trace and retrace is 1/15,750 seconds or 63.5 microseconds. However, since about 10 microseconds of each scanning line time is lost in blanking and retrace, the visible length of the scanning line represents approximately 54 microseconds. Therefore, to find the frequency of the beat on the CRT, merely divide the distance between two dark lines by the visible length of a scanning line, multiply this by 54, and divide the result into 1. This gives the beat in megacycles. This particular method is quite cumbersome, but probably the most accurate. There is, however, a much simpler way.

Assume that there is a pattern of 10 ertical or diagonal dark interference lines on the screen of the CRT. This means that each scanning line is modulated 10 times. Each scanning line, however, represents one cycle of a 15,-750 cps signal. Therefore, the frequency of the beat must be 10 times 15,750, or 157,500 cps. Although not as accurate as the method previously mentioned, this is much simpler and as accurate as necessary for most cases. Merely count the number of lines, either vertical or diagonal, and multiply this number by 15,750 for the fre-(Continued on page 77)

5. Horizontal bar interference. Interference signals below 15.750 cps at the CRT cause this type of pattern.





Simple and economical to build, these units are source of income for marine radio technicians.

THE main disadvantage of the marine radio service business is its periodic slumps. You may have a fleet of a hundred or a thousand boats normally in port—but, come the Fourth of July, and they're gone for a week. You don't have to sit twiddling your thumbs waiting for them to come back, if you fill in with building some of the radiotelephone remote-control units described in this article.

On most boats, the main equipment will have been installed in a cabin below, where it is protected and is close to battery and ground connections. The result is that when the boat is under way and the skipper is at the helm above, as shown in Fig. 1, he is as mute as a mackerel. A regulation handset cord will stretch only four feet, so if he wants to talk on the phone he must stop boating. The obvious solution to his problem (and he will be happy to hear of it) is a remote-control unit at the helm.


Unfortunately, the engineering of many of the smaller manufacturers has not advanced to the point of providing remote control, and the manufacturers who do make remote units design them to be used only with their own gear. Consequently, many boatmen go without or do with makeshift adaptations.

Here is a unit which can be used

with any marine radiotelephone on the market employing relays and an electronic push-to-talk circuit. It can be connected to any properly adapted set, and will provide all of the features essential for communication. Construction is simple—extensive facilities are not necessary.

The basic requirements of such a unit are to provide loudspeaker reception of whatever traffic is on the air.

Fig. 2. Schematic diagram and parts list for remote control unit to be used ir conjunction with marine radiotelephone. The socket is for handset shown in Fig. 3.

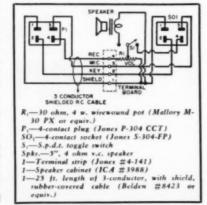

a volume control, a means for transferring the audio from the speaker to the handset earpiece, a microphone circuit, and a control circuit. In addition to the control unit a telephone handset with a push-to-talk switch is needed, but a simple arrangement can be made to use the handset for the radiotelephone at both the main and the remote positions.

The circuit shown in Fig. 2 fulfills all of these requirements. It will be noted from the parts list that components are standard items, available at any parts house. The cost of materials should come to about \$12 per unit.

Operation is most easily illustrated with a radiotelephone having the handset circuit of Fig. 3. In this transceiver, handset connections are brought to a 4-contact socket on the panel, and the handset has a mating plug. The ground is a common return, not only for receiver audio, but also the relay-keying circuit and microphone. Voltage for the microphone is provided by the voltage drop across a heavily bypassed portion of the modulator cathode bias resistor, while voltage to actuate the antenna and power-switching relay is obtained from the low-voltage d.c. input.

Since these circuits are all of very low impedance, no crosstalk or noise pickup results, and the ground wire and the other three wires are twisted together in the handset cord. It is perfectly feasible to extend the handset circuits a considerable distance without noticeable loss or objectionable distortion.

Connection between the radiotele-

phone and the remote control is made by means of 3-conductor and shield, rubber-covered cable, with the shield acting as the common return. In the make-up of this cable the transceiver end is soldered into the plug, but the remote end connects into a terminal strip. The reason for not soldering this end right into the circuit is that in most installations the cable must run through numerous bulkheads or lockers. It is much easier and neater to bore round 5/16" holes to snake the bare cable end through than to gnaw out square holes to pass the plug.

Mounting and construction details for the remote control box are shown in Figs. 4 and 5. Fig. 6 shows most of the parts needed.

Some work is required on the radiotelephone if it does not have the panel socket and handset plug mentioned previously. All this will amount to is connecting a short cable and socket to the set's handset strip, and a plug to the handset cord. Handset or remote connections are then made by plugging into this cable socket.

Some radiotelephones will be found to have handset audio supplied by condenser coupling from the plate of the receiver power-amplifier tube. In this case remove the condenser and rewire to the circuit of Fig. 3, a matter of changing a couple of connec-tions. In sets with "floating" input, one side of the battery-input circuit is used for the handset common. On these, disconnect the ground return of the voice coil and the ouput transformer, and connect these returns instead to the common handset circuit. Note that nothing in the remote unit should be grounded or connected to the cabinet.

Operation of the unit is simple. At the main position the desired frequency is selected with the receiver on "loudspeaker." Gain is set for a healthy signal level, then the speakerhandset switch is thrown to "handset." The handset is removed, the remote cable plugged in its place, and the tandset taken to the remote station and plugged into the control. At this point, reception may be had in either the speaker or the earpiece by throwing the switch on the control unit. and with audio set to a comfortable ievel by the volume control. Since most marine-phone modulators work "wide open," with maximum possible gain at all times, no control of microphone level is provided. The transmitter filaments must, of course, be on if instant transmission is desired.

A profitable offshoot from this is the wiring of boats for remote speakers connected to the broadcast radio. It is astonishing to learn the number of people who buy yachts to get away from the annoyance of telephones and radios—and then spend most of their time aboard the boat telephoning and listening to the radio!

Keep track of parts cost and manufacturing labor. A 100% markup is about standard and will cover over-

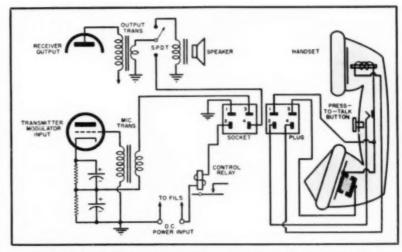


Fig. 3. Typical handset circuit of a marine radiotelephone. The remote unit plugs into the socket shown for the handset and the handset plugs into the remote unit.

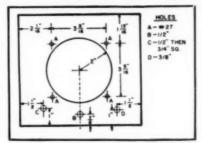


Fig. 4. Front of remote speaker unit showing details for mounting components.

SPEAKER

SOCKET

VOL

CONT

SWITCH


TERMINAL

BOARD

Fig. 5. Rear view of front panel of remote speaker showing position and wiring layout for the various components.

head and give a fair profit. Be as efficient as possible, then do not feel at all bashfull if the price comes to more than peanuts—these units customarily sell for from \$40 to \$50, plus installation.

Fig. 6. Components for a marine radiotelephone remote control are standard.

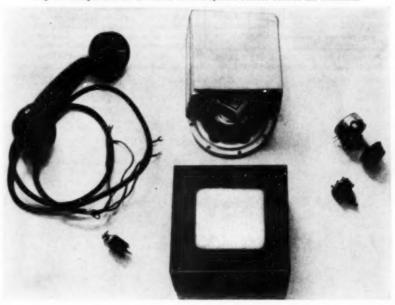



VOLTAGE STABILIZATION FOR

SCOPE CALIBRATORS

By RONALD L. IVES

Fig. 1. Over-all view of the "modified"
Heath Model VC-1 voltage calibrator.

A simple circuit change insures stable operation of this test unit in areas where voltage fluctuations are common.

MANY owners of small oscilloscope voltage calibrators, either of the kit type or "home grown," find that these instrument adjuncts are

SIGNAL SI

robbed of much of their usefulness by line voltage fluctuations. This trouble, already severe in many areas, is increasing because loads are growing faster than distribution systems. Fortunately, relatively minor and inexpensive changes in most oscilloscope voltage calibrators will make them dependable to within less than one per-cent at any setting.

The conventional oscilloscope calibrator consists of a source of sine waves, usually the power line; a biased diode, to clip the sine waves into semi-square waves; and a power

Fig. 2. Original Heathkit voltage calibrator circuit with additions shown in heavy lines. In addition to new input and output terminals, new feet, handle, and shaft lock on the variable 50,000 ohm resistor, circuitwise the changes consist of the addition of a line plug and fuse, a pilot light, resistor R₁, and regulator tube. V₁.

supply, to bias the diode. One of the more popular circuits is shown in Fig. 2. This is essentially the circuit used in the *Heathkit* Model VC-1 calibrator. (Heavy lines show the alterations made.) In the original circuit, the clipping level is constant only when the d.c. supply voltage is constant, and this voltage depends upon the line voltage.

The d.c. supply voltage, and hence clipping level, can be stabilized in a voltage calibrator of this type by the addition of a voltage regulator tube, a modification costing only a couple of dollars and requiring perhaps an hour of labor. The resultant instrument quite closely resembles, in circuit and performance, the *Du Mont* voltage calibrator, an instrument most of us would like to own if we could afford it.

Operation of an unregulated voltage calibrator is quite simple. Sine waves, derived from the power supply through a resistor and an isolating condenser, are impressed across two halves of a dual diode. The cathode of the first diode is biased positive with respect to ground so that it will not conduct until the positive voltage

(Continued on page 85)





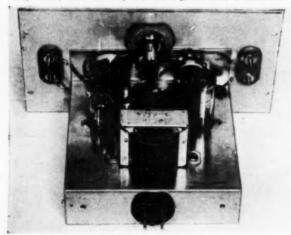


Fig. 4. Bottom view shows parts added to original circuit.

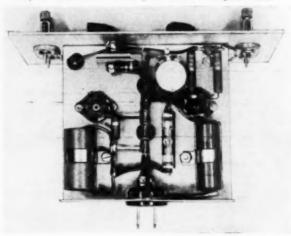

"ULTRA-LINEAR" OPERATION OF 6V6 TUBES

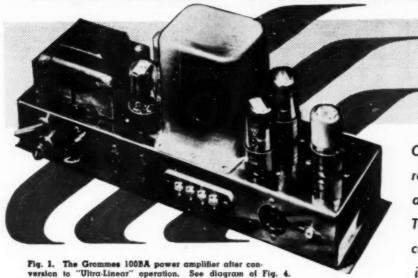

One of the best designs in recent years covering an audio amplifier using 6V6 tubes. The author, in this case, has converted a Grommes unit to illustrate his design idea.

Acro Products Company

L VER since the introduction of "Ultra-Linear" circuitry, there has been a steadily growing interest in amplifiers utilizing this type of output stage coupling. The basic arrangement has become popular in ardent audiophile circles and has also found commercial and industrial applications where extremely low distortion is required.

Essentially, the "Ultra-Linear" circuit is illustrated in Fig. 2. The screens of beam power output tubes are connected to taps on the primary of the output transformer; or if it is desired to operate the screens at a different a.c. potential than the plates, to a tertiary winding on the output transformer. Either arrangement requires a transformer with the correct ratio of screen load to plate load if optimum results are to be obtained, and a mismatch will lead to inefficiency and/or increased distortion.

The "Ultra-Linear" arrangement has been mistakenly referred to as a feedback circuit. This is not correct since negative feedback would produce a reduction in gain which does not occur with the "Ultra-Linear" circuit. It would be just as incorrect to refer to a triode as a tetrode with feedback as it is to analyze the "Ultra-Linear" circuit as a feedback circuit. Instead it must be considered as a new and different type of tube structure which is neither triode nor tetrode.

The circuit provides some of the advantages of both triodes and tetrodes, and it overcomes some of the disadvantages of each of these types. For example, it is more efficient and provides more power output than triodes. Its capabilities in this respect parallel the capabilities of tetrodes. However, it has low internal impedance, almost as low as triodes and about one-tenth that of tetrodes; this provides good

loudspeaker damping. Lastly, and most important of all, it has a more linear input-output relationship at most power levels than either triodes or tetrodes which means that its distortion is lower than other methods of operation. This alone justifies the use of the circuit in those cases where low distortion is the guiding criterion.

"Ultra-Linear" circuit achieved popularity in deluxe amplifier arrangements such as conversion of the Williamson circuit.2 It has been widely used with tubes of the KT66, 807, and 5881 type for circuits in the 20 to 30 watt power bracket-for circuits of truly outstanding characteristics suitable for the most critical usage. Naturally, 20 or 30 watts is a lot of power for living room use-just as 200 horsepower is a lot of power for a deluxe automobile. However, there are definite advantages to high powered amplifiers which are operated at a fraction of their potential output just as there are definite advantages to high powered cars which are run at a fraction of their capabilities.

Nevertheless, not all of us want, or can afford, 200 horsepower cars; and not all of us feel the need for, or wish to spend the money for, amplifiers of 20 or more watts power rating. Many audiophiles and music lovers are very happy with amplifiers in the 10 to 15 watt power bracket. The popularity of this range is demonstrated by the sales success of thousands of Williamsontype amplifiers as well as tens of thousands of lower cost amplifiers using 6V6 tubes providing 10 to 15 watts of power output. Undoubtedly, the greatest number of amplifiers in home use utilize the type 6V6 tube in one of several popular circuit arrangements, all of which have essentially similar performance characteristics.

The possibilities of using the "Ultra-

Linear" arrangement with 6V6 tubes in medium-powered amplifiers has been investigated carefully. It has been found that the tube is well suited for this mode of operation since its dynamic input-output characteristic can be linearized by proper selection of a tapping point for screen connection.

The characteristics of the 6V6 are not at all similar to the 6L6 family, and the connection arrangement which is optimum for 6V6's is quite different from that which can be used with the large tube types. As a tetrode, the 6V6 permits 10 to 15 watts of output depending on plate supply voltage and bias. These ratings are based on the point where clipping of a sine wave becomes visible—which happens when the grids start to go positive, and the driving source cannot furnish power to the tubes.

If the same tubes are triode connected (by strapping the screen to the plate), power output, using the same criteria, is reduced to 2½ to 3½ watts. When the "Ultra-Linear" connection is used, the power output depends on the position of the screen taps. If a 50% tap is used, power is reduced to about one-half of the tetrode capability. If a greater than 50% tap is used, power is reduced toward the triode limitations. At a tapping point of about 24%, power output is within 90% of the tetrode condition, and distortion at all levels up to maximum is minimized. This point, therefore, has been selected as the optimum operating point for "Ultra-Linear" use.

It would be possible to take an even lower tapping point and obtain slightly more power output than the tetrode connection, but the distortion at low levels and the internal impedance both begin to increase as the tap is brought closer to the zero per-cent point which

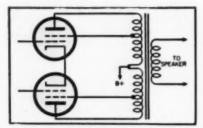


Fig. 2. Basic "Ultra-Linear" arrangement.

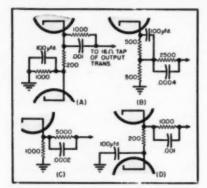



Fig. 3. Various feedback arrangements from voice coil of the output to the cathode of an early stage. See text for discussion.

is coincident with conventional tetrode connection.

Thus the "Ultra-Linear" operating point has been set at a compromise level in which the factors of maximum power output, distortion at various levels, and internal impedance have all been weighed against each other. It must also be mentioned that listening tests at various tapping points with no feedback around the amplifier validate this selection of the tapping point. This was done without feedback on the assumption that the best amplifier without feedback would also be the best after the application of feedback. In these listening tests, the triodes fell behind because they could not handle the power (after all, 3 watts is insufficient for musical peaks), the tetrodes were somewhat screechy and boomy (too much internal impedance for satisfactory speaker damping), and the 24% point sounded natural and smooth even without connection of the amplifier feedback loop.

Use of the "Ultra-Linear" circuit involves utilization of an output transformer with the correctly placed taps. A special transformer, the Acrosound TO-310, has been designed specifically for this application; and its parameters were selected so that it would not limit the ultimate capabilities inherent in the circuit. For example, its bandwidth has been set at ± 1 db from 10 cps to 100 kc. so as to provide the low phase shift and good transient performance desired in the most critical applications. Similarly, its distortion characteristics complement those of the "Ultra-Linear" circuit and permit low distortion at both high and low levels from 20 cps to over 20 kc.

Fig. 4. The Grommes 100BA power amplifier converted to "Ultra-Linear" operation.

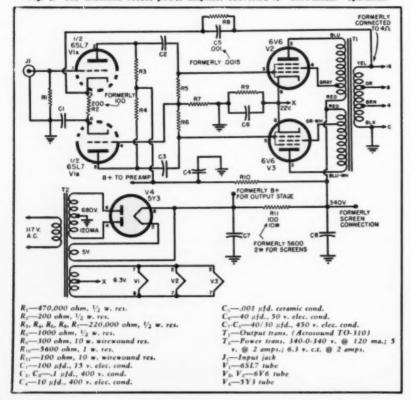

Circuit Considerations

There are many 6V6 circuits which have become popular, but by far the most commonly used is that in which a twin triode phase inverter is used to drive a pair of 6V6's; and feedback is carried from the output winding of the output transformer to the cathode of one of the triode sections. This basic configuration is simple, practical, economical, and adequate. The a.c. grid-to-grid voltage requirements of the 6V6 output stage are not stringent, and the phase inverter supplies ample drive without the need for an intermediate push-pull stage such as is used in the Williamson-type circuit. Since there are only two stages, the problems of utilizing feedback are simplified (as there is less phase shift in the circuit), and the designer can use less elaborate circuitry and components while preserving a satisfactory margin of stability.

Generally the phase inverter tube is a high mu triode such as the 6SL7 or 12AX7 in order to obtain as much gain as possible within the two stages. Actually, except for gain considerations, the specific type of inverter is of comparatively little consequence—circuit performance is determined almost completely by the mode of operation of the output tubes with respect to bias, supply voltage, and impedance match; the quality of the output transformer; and the proportion of feedback. The voltage amplifier stage contributes relatively little, as compared to the contribution of the output stage, to the over-all quality of the amplifier.

Conversion of these circuits to "Ultra-Linear" operation can be done by substituting an output transformer which has properly placed taps for connection to the 6V6 screens. Generally, this substitution will make an immediate decrease in distortion.

If the original amplifier used a screen dropping resistance, this is removed for "Ultra-Linear" operation; and the screens are connected to the tapping points on the primary of the output transformer. It is important to observe polarity and to connect the screen to the same primary side of the transformer as that from which the plate is energized. Otherwise an oscillitory condition will be provoked. Similarly, polarity must be observed between upper and lower output tubes, or the feedback from the secondary side of the transformer may be in the incorrect phase and cause regeneration.

When the screen resistor of the original circuit has been removed, the screen bypass condenser must also be disconnected. This can be readily put to good use by paralleling it across one of the filter condensers of the power supply for extra filtering and lowered power supply impedance.

The only other changes which need be made involve the feedback resistor and feedback compensating condenser which shunts this resistor (or in some circuits bypasses it to ground). The ratio of series resistor to shunt resistor in the feedback path determines both the total gain in the circuit and the proportion of feedback. For example, with a 6SL7 phase inverter and feedback from the 16-ohm tap of the Acrosound TO-310 transformer, the power amplifier will have 17 db of feedback and require a maximum input signal of 3 volts to drive it to full output when the ratio of feedback to cathode resistance is 5 to 1. If the ratio is changed to 7.5 to 1, the amplifier will be driven with a 2 volt input, but the feedback is cut down by 3 to 4 decibels. Similarly, a 12AX7 has about 50% more gain than a 6SL7. If this tube is used with a 7.5 to 1 ratio of resistance, the amplifier can be driven to full output with 2 volts of signal while still maintaining 17 db of feedback. In the original construction, it is recommended that the 12AX7 be used so as to obtain this increased sensitivity. However, in converting an existing amplifier, the constructor can leave the 6SL7 tube in the circuit and can adjust for the required sensitivity by varying the feedback resistor. If necessary, he can sacrifice a portion of the feedback in order to maintain sufficient gain for the preamplifier stages which are being used.

In many commercial amplifiers, the power amplifier section must be sufficiently sensitive to be driven by 1 volt of input because of the relatively low gain of the earlier stages. If this is the case, it is necessary to diminish the feedback (by increasing the feedback resistor). However, the most modern preamp designs are intended to supply about a two volt input such as is found on Williamson-type amplifiers. Any of these preamps will handle the converted 6V6 amplifier and still permit 14 or more db of feedback. This is sufficient feedback to reduce distortion, hum, noise, and internal impedance to low values suitable for top quality applications. Thus the more common frontend arrangements will serve with the "Ultra-Linear" 6V6 amplifier while preserving an adequate proportion of feedback. When the 12AX7 is used, the designer has an additional 3 or 4 db of latitude in his choice of gain versus proportion of feedback.

In some amplifiers which are of the public-address type rather than the high-fidelity type, inadequate feedback is used which is limited to 6 db or less. Conversion of these amplifiers with the increased feedback which results from a 5 to 1 resistor proportion will produce insufficient gain. In those cases, there must be either a sacrifice of feedback or the addition of more gain in the early stages. However, in these amplifiers the original quality is generally so poor that the substitution of the "Ultra-Linear" output arrangement will make a decided improvement in performance even if only 6 db of feedback is used. The relative improvement in a low grade amplifier is even greater than is achieved by converting a fairly good amplifier which has a high proportion of feedback.

When feedback in excess of 12 db



Fig. 5. Bottom view of converted Grommes amplifier showing new output transformer

is used, there is some possibility that the amplifier response will peak in the ultrasonic region even though the response without feedback is flat over a very wide range. This peaking can be eliminated with a consequent improvement in transient response, by adding a network to change the phase of the feedback voltage in the peaking region. One simple arrangement is to add a small condenser across the feedback resistor. A suitable condenser value in the type of circuit under discussion is one which makes the product of the feedback resistor in ohms and the condenser in microfarads equal to unity. Several typical circuits using a 5 to 1 resistor proportion are illustrated in Fig. 3. In these arrangements, the feedback connection is brought to the cathode or pair of cathodes of the phase inverter stage. All of the arrangements have the same proportion of feedback and the identical phase correction.

Circuit Conversion

These conversion considerations are exemplified in the conversion of the Grommes 100BA amplifier, Fig. 1, the circuit of which is shown converted in Fig. 4. This amplifier is typical of many which come both with and without preamps in the \$40 to \$60 price bracket. Both former values and converted ones are indicated on the schematic. There are only three electronic parts changes in addition to the new output transformer.

Physically, it takes only two additional holes for mounting the output transformer—the remaining holes line up without alteration. The transformer fits rather snugly but inasmuch as it contributes no heating, its proximity to other parts causes no difficulty.

Any power supply which is satisfactory for the original circuit is also suitable for the "Ultra-Linear" conversion since the "Ultra-Linear" circuit is less critical as to supply regulation than the tetrode circuit. In the Grommes 100BA no filter choke is used, and the converted circuit works just as well without one although a single 100 ohm resistor was added in converting in order to reduce the hum voltage.

The converted amplifier has extraordinary specifications for its size and price. In fact its spees read amazingly like those of a conventional triode Williamson amplifier. Frequency response is flat \pm .5 db from 20 cps to over 100 kc. at a 1 watt level. (By increasing the size of the cathode condenser of the 6SL7 the low end response can be made flat to below 5 cps.) At 10 watts, response is flat \pm 1 db from 20 cps to over 60 kc., and clean waveform is preserved from 20 cps to 30 kc. even at this high a level.

The transient response as evaluated by square waves is shown in Fig. 6. There is a minimum of transient distortion and phase shift at these two extremes of the audio band.

Intermodulation distortion is extremely low. It runs about .1% at 1 watt, rises to .4% at 8 watts, and to .5% at 10 watts. It is still below 1% at 11 watts. These tests were made with 40 and 7000 cps mixed 4 to 1 and are based on equivalent sine-wave output. This is the conventional method of rating which is used for practically all commercial amplifier equipment.

The quality of a low cost 6V6 amplifier is normally not up to the top high-fidelity standards which have been set by the Williamson-type amplifiers produced in recent years. However, it is now possible, by using the "Ultra-Linear" circuit arrangement and a top quality output transformer, to convert these run-of-the-mill amplifiers into ones whose quality is comparable with the best obtainable in the


(Continued on page 117)

Fig. 6. Square-wave performance (A) at 20 cps and (B) at 20 kc. See text for details.





SONIC LIQUID LEVEL INDICATOR

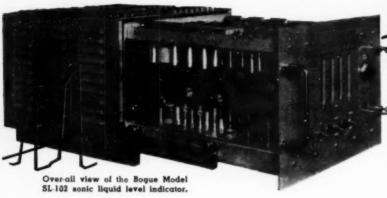

A safe, explosion-proof instrument for measuring liquid levels in tanks without floats or other moving parts.

TO MEET a long standing need for accurate gauges, free from floats and similar moving parts, The Bogue electric Manufacturing Co., has developed the SL-102 sonic liquid level indicator, shown being tested on this month's cover. Synchros, potentiometers, and other rotating data transmitters have been eliminated in the sonic system. The system does not use direct current within the tanks, and the liquid is not a conductor of electric current. The equipment is, therefore, safe and explosion-proof.

Sonic liquid level indicators are being used to gauge petroleum storage tanks and similar containers filled with corrosive and radioactive liquids.

The indicators may be arranged to deliver digital level data to commercially available tape printers for inventory purposes. The recorders may be operated up to several thousand feet from the indicators without the use of special equipment. When desirable, level information can be transmitted over greater distances using wire-radio transmission networks.

The SL-102 sonic system is completely automatic, and is capable of compensating for variations in sound velocity due to temperature and gravity changes within the liquid being measured, without any external equipment. It is also possible to read an interface level of two immiscible liquids in the same tank.

The system consists of an indicator and two transducers in each storage tank being gauged. The transducers, with proper protection, are installed at the bottom of the tank and are the only transmitting and receiving devices to come in contact with the liquid. Any number of tanks containing differing liquids may be read by one


SL-102 indicator with the aid of a switching relay, R-102. The accuracy of this instrument is ±.01 foot.

The system consists of two sonic gauges, one measuring the surface level and the other the spacing between a series of acoustic reflectors placed along the sound path of a second transducer.

A pulse transmitted from the level measuring transducer is propagated to the surface of the liquid where it is reflected back to the transducer. The elapsed time interval is used to gate a timing oscillator, the frequency of which is directly proportional to the velocity of propagation of the pulse.

The period of each cycle of the timing oscillator is chosen to equal the time required for a sound pulse to travel .01 foot up and back through a particular liquid, so that the total number of cycles in the interval between transmission and return of an

Fig. 1. How the indicator system operates to gauge liquids in various storage tanks.

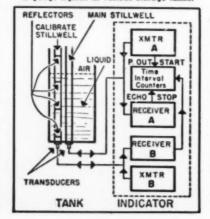

CLAYTON R. KIELICH

Systems Engineer
Boque Electric Manufacturing Co.

echo equals the actual level in hundredths of a foot. This information is translated to a liquid level reading on the decade counter of the indicator.

The transmitted pulse train at 400 kilocycles is transmitted at a rate of 20 times-per-second. Each pulse is 40 microseconds in duration. The calibrating pulse is identical to the indicating pulse. The reflectors, located at known distances in the stillwell of the calibrating system, provide pulses to adjust the timing frequency to exactly correspond to the velocity of propagation in the particular liquid. The number of reflectors used will depend on the depth of the tank.

Transmitter A and receiver A, along with the time interval counters, are designated the "main" system and, in conjunction with the associated transducer, gauge the surface level. Fig. 1.

The second system, or the "calibrate" section, consists of transmitter B, which directs the sound pulse along the path fitted with accurately located reflectors, and receiver B which amplifies the received echoes. The amplified reflector echoes are applied to the time interval counters where they calibrate the main system.

To support the acoustic reflectors in the calibrate section and to contain the sound energies within a small part of the tank, two stillwell pipe assemblies are installed in the tank. These stillwell pipes are acoustically treated internally with a material that is impervious to corrosive and non-corrosive liquids.

The transducers used with the system are made up of ammonium dihydrogen phosphate (adp) crystals. The crystals are encapsulated in a stainless steel container, measuring 5 inches in diameter. The crystals are protected by an acoustically transparent window of teflon that is impervious to corrosive liquids.

The indicator is housed in a table mounting cabinet, 15½ inches high, 1911/16 inches wide, and 21 inches deep. The weight of the indicator is approximately 116 pounds. The unit is mounted on slide rails making it readily accessible for inspection and maintenance. The system operates from 117 volts, 60 cycles, single-phase power and consumes 270 watts.

-30-



BY MILTON S. KIVER Television Communications Institute

Part 4. Tuner, video i.f., video amplifier, and sound circuits of typical color TV sets described in detail.

N LAST month's article we examined in some detail the block diagram of a color television receiver designed to operate with a tri-gun color picture tube. Now we are ready to consider the actual circuits which each of the blocks represented.

R.F. Tuner. The introduction of color in no way alters or modifies the r.f. section of the television receiver. Thus, the r.f. amplifier should still possess high gain and low noise; the oscillator still provides a signal which, when mixed with the incoming signal, will produce the desired difference or video i.f. frequencies. For the reception of v.h.f. signals, either a turret tuner or a continuous arrangement is employed. For u.h.f. reception, continuous tuning is the most common method although there is also available an 82-channel turret tuner.

A typical v.h.f. turret tuner circuit is shown in Fig. 1. Cascode amplifiers are common in the r.f. stage, although some manufacturers favor single highfrequency miniature pentodes. The oscillator tube is invariably a triode, usually half of the mixer tube. The latter may be another triode (i.e., 1/2 of a 6J6) or pentode (1/2 of a 6U8). This arrangement requires only two tubes for the entire tuner section.

In the tuner shown in Fig. 1, the cascode r.f. amplifier uses a 6BZ7 duotriode. One section of a 6J6 serves as the mixer while the other section functions as the oscillator. Balanced 300ohm and unbalanced 75-ohm (coaxial line) input impedances are provided by a center-tapped primary winding, L:014. All signals must pass through a high-pass filter designed to attenuate all signals below channel 2.

The secondary winding, $L_{101,8}$, is tuned by the input capacity (of the first triode unit) in series with alignment trimmer C_{100} . Loading of L_{1010} by R_{101} provides the required bandpass, particularly on the lower v.h.f. channels. The a.g.c. bias is applied to the first triode of V101 through decoupling resis-

Direct coupling is used between the first triode plate and the second triode cathode. This is normal in cascode circuits. With cathode feed to the second triode, C_{100} is used to place the grid at r.f. ground potential. Since the two triode sections of V_{101} are in series across a common plate supply, the cathode of the second triode is positive with respect to chassis ground. A di-

Editor's Note: Part 1 of this series, which appeared in the March, 1955 issue, explained color mixing and its application in color TV. Part 2, appearing in the April issue, described the NTSC color signal. The block diagram of a typical color TV receiver was described in the May issue. This and forthcoming articles will describe and analyse the various circuits used in present color TV sets. In view of the many requests received, Radio & Television News will publish this series in reprint form. The first three parts are in a single usuit (50 cents), the balance will be reprinted in individual parts at 20 cents each. For quantities of 50 or more, write for quotations. Address your inquiries to Radio & Television News Reprint Editor, 366 Madison Ave., N. Y. 17, N. Y.

vider across the "B+," consisting of R_{103} and R_{113} , places the grid of the second triode at a sufficiently positive potential (with respect to its cathode) for proper operating bias.

The signal at the plate of the second triode of V_{int} is inductively coupled into the grid circuit of the mixer. At the same time, a voltage from the oscillator is similarly brought into the mixer circuit. The mixer combines both signals to produce the desired i.f.

and then transfers this signal to the following i.f. stages.

The oscillator is of the ultraudion variety with a front panel fine-tuning control.

Video I.F. Section. The video i.f. system follows the r.f. tuner. This will consist, usually, of four and sometimes five separate stages. See Fig. 2. In the conventional black-and-white television receiver, three i.f. stages was the number most frequently used, although four stages were found in some sets. The increased number of i.f. stages in a color receiver stems, in part, from the wider bandpass required (4.2 mc.) and from the greater precautions that must be taken to insure that the response curve will possess the right form

The desired response curve for the video i.f. section is shown in Fig. 3. Of particular interest is the care with which the low frequency end of the curve must be shaped so that it provides the proper amplification for the color subcarrier and its sidebands. Note that the curve is flat down to approximately 41.65 mc. and then the "rolloff" is quite steep. The steep decline is needed to prevent the sound carrier from receiving too much amplification, producing a 920-kc. beat note at the video second detector which would appear on the screen as an interference pattern. Furthermore, too much sound voltage at the detector will produce a fine-grained 4.5-mc. pattern on the screen and/or sound bars. The latter effect, of course, can occur in all television receivers, whether they be of the black-and-white or color variety. The 920-kc. interference, however, arises only when a color signal is being re-

Video i.f. systems in color receivers

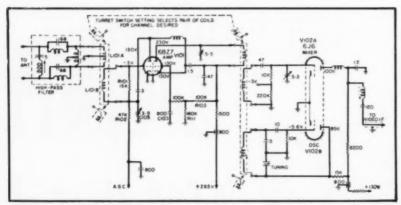


Fig. 1. Typical r.f. tuner used with color TV receiver. This is a turret-type unit for v.h.f. only, however combination v.h.f.-u.h.f. models are also used.

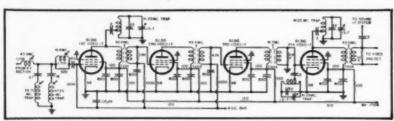


Fig. 2. The video i.f. circuits of one color TV receiver. Four stages are used here to assure a wider and more uniform bandpass than for black-and-white sets.

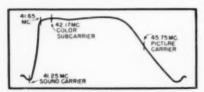


Fig. 3. Video i.f. response curve of a color TV receiver. Note the steep slope of the curve between 41.25 and 41.65 mc.

follow the same practice as for black-and-white receivers in so far as interstage coupling is concerned. Most common types of coupling are bifilar coils and/or single wound coils. For example, the circuit of Fig. 2 uses bifilar coils predominantly $(T_{\min}, T_{\min}, T_{$

The interstage coils are stagger-tuned, ranging from a low frequency of 41.4 mc. to a high frequency of 45.5 mc. Also present are five shunt traps, three tuned to the sound i.f. signal of 41.25 mc., one to the video carrier frequency (39.75 mc.) of the adjacent higher channel, and one to the sound carrier frequency (47.25 mc.) of the adjacent lower channel.

A number of sets resort to complex coupling circuits in one or more i.f. stages in order to obtain the desired attenuation at certain trap frequencies, such as the adjacent-channel video carrier, adjacent-channel sound carrier, and the sound carrier of the channel being received.

In one RCA color receiver, a bridged-T circuit is inserted between the tuner and the first video i.f. amplifier. See Fig. 4. The network contains a trap tuned to the accompanying sound carrier, 41.25 mc. In order to reduce interference from this source (i.e., cross modulation), the sound carrier is attenuated as soon as possible in the i.f. amplifier. (The signal is not removed completely, however, since enough must be available for the sound system. The latter ties into the video system at a subsequent point.)

A more elaborate bridged-T network, combined with an *m*-derived bandpass circuit, is employed between the first and second i.f. stages. This contains two rejection traps, one tuned to 39.75 mc. (video carrier of adjacent higher channel), the other tuned to 47.25 mc. (sound carrier of adjacent lower channel). A second such complex coupling network is found between the final i.f. stage and the video second detector. This, too, contains two traps, one for the accompanying sound carrier at 41.25 mc. and one for 47.25 mc.

It will be noted from Fig. 4 that the sound take-off occurs in the plate circuit of the final video i.f. amplifier. This does not necessarily denote a split-sound type of receiver, as mentioned earlier, but stems from a desire on the part of the set designer to avoid any interaction between the color subcarrier and the sound carrier that could produce (by mixing) a 920 kc. beat note. The sound carrier is permitted to travel with the video signal up to the plate of the final video i.f. amplifier and then it is diverted to a germanium crystal where it mixes with the video carrier to produce a 4.5 mc. signal. In the meantime, the monochrome and color subcarrier signals proceed to the video second detector for their demodulation. By this arrangement, the sound signal can be strongly attenuated in the video detector thereby minimizing the development of a 920 kc. beat signal.

Automatic gain control is applied to the first two or three video i.f. stages in the same manner, and for the same reason, that it is applied in monochrome receivers. The r.f. amplifier also receives all or a portion of the same a.g.c. voltage.

Sound Channel. As indicated previously, the sound signal is diverted from the video path in the plate circuit of the final video i.f. amplifier. This signal and a portion of the video carrier are then mixed in a germanium diode to produce the desired 4.5 mc. intercarrier sound signal. See Fig. 5. This is followed by several 4.5-mc. i.f. amplifiers and then the signal is applied to a ratio detector. Here the audio intelligence is recovered from the FM signal. Further amplification by audio voltage and power amplifiers raise the signal to the proper level for operating a loudspeaker. Just how extensive this portion of the audio system is will be governed by the price range of the receiver. If a highfidelity system is desired, then the audio stages can be elaborated, perhaps by the addition of push-pull output, phase inversion, feedback net-


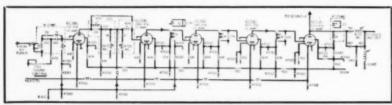


Fig. 4. Five stage video i.f. system employed by RCA in its color TV sets.

Fig. 5. Sound i.f. and audio circuits of a typical color television receiver.

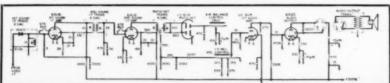

works, etc. The system shown in Fig. 5 is commonly found in most TV receivers where economy and good sound is desired.

Luminance Channel. The video signal is demodulated in the video detector (Fig. 7), providing an output 0 to 4 mc. monochrome signal plus the I and Q color sidebands. (The color subcarrier, it will be remembered, was deleted at the transmitter.) The detector itself may be either a germanium diode (1N60 or its equivalent) or one section of a vacuum tube. There appears to be a definite swing toward the germanium crystal but vacuum tubes are still widely used.

Beyond the detector, both the monochrome and color sideband signals are applied to at least one stage of amplification before they are separated In the circuit of Fig. 8, the output from the video second detector is applied first to the triode section of a 6U8, then to the pentode section. Both signals remain together only in the triode because at the grid of the pentode, a portion of the signal is fed to the bandpass amplifier, which is the input stage to the chrominance section of the receiver. Hence, separation of the monochrome and color signals might be said to occur at the output

of the triode video amplifier. The second video amplifier in Fig. 8 deals solely with the monochrome portion of the total color signal. This fact is further accentuated by the 3.58 mc. series trap which is present in the plate circuit of this stage. The trap attenuates any 3.58 mc. color subcarrier voltage which may be present here in order to prevent it from reaching the picture-tube screen and producing a visible interference pattern. The presence of the 3.58 mc. trap limits the response of the luminance or monochrome channel to a somewhat lower value, usually 3.0 or 3.2 mc. Since most present monochrome receivers operate within this bandwidth, both in their i.f. and video amplifier systems, any loss of detail will be no more apparent on color sets than on black-and-white sets.

At this point the reader may wonder why a special 3.58 mc. trap is required when, in fact, no 3.58 mc. color subcarrier is being sent with the signal The answer rests in the fact that while it is true that at no time is there any voltage at precisely the 3.58 mc. frequency, the phase excursions of the color signal cause the carrier to move back and forth from frequencies above 3.58 mc. to frequencies below 3.58 mc.

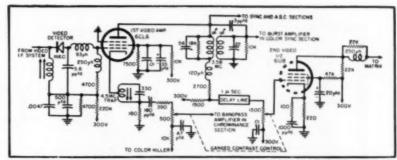


Fig. 6. Video amplifier circuit using two pentodes and a 3.58 mc, trap in the first video plate circuit for recovering the 3.58 mc, burst signal for color synchronizing.

Furthermore, most of the color energy is concentrated in the sidebands around the 3.58 mc. frequency and if we remove the bulk of this energy with a trap, we minimize any tendency of the color signal to produce interference patterns on the screen.

Another fact to note is this: The frequency of the color subcarrier (and hence, the frequency of its sidebands as well) was purposely chosen so that all this energy would fall midway between the clusters of energy of the monochrome signal. Any color signal reaching the screen of a monochrome receiver will tend to at least partially cancel itself out on successive frames so that its visibility is reduced. The same action occurs in a color set when the color signal reaches the screen via the luminance channel. Hence, the combination of the 3.58 mc. trap with the frequency interlace principle act to reduce the visibility of any interference pattern from this source to a considerable degree.

Returning to the circuit of Fig. 8, the luminance signal is finally applied to the matrix section where it combines with suitable I and Q signals to provide the original red, green, and blue voltages.

Two additional representative video amplifier systems are shown in Figs 6 and 9. The circuit in Fig. 6 is taken from an RCA schematic and employs a 1N60 crystal diode as the video second detector. The output of this stage is fed to a 6CL6 video amplifier. Here both chroma and monochrome signals are amplified. The monochrome signal is then transferred to a second video amplifier and from this stage to the matrix network. The chroma signal is taken from the cathode circuit of the 1st video amplifier and transferred to the bandpass amplifier which stands at

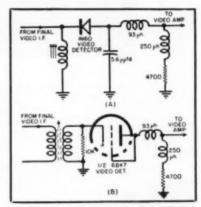


Fig. 7. Two types of video second detectors found in color TV sets. (A) Germanium diode; (B) triode vacuum tube with grid and plate connected to form a diode.

the head of the chrominance section.

There are a number of things to note about Fig. 6. A 3.58 mc. resonant cir-

cuit in the plate circuit of the 1st video amplifier transfers the 3.58 mc. signal to a burst amplifier for use in the color sync section of the receiver. The same arrangement also attenuates the amount of 3.58 mc. voltage reaching the second video amplifier. The response of this latter amplifier extends to approximately 3.2 mc., enabling it to impose additional attenuation on the color subcarrier.

Connection to the sync and a.g.c. circuits is made at the plate of the 1st video amplifier. Also, a 1.0 microsecond delay line is inserted in the path of the luminance signal between the 1st and 2nd video amplifiers. The delay

line is terminated in a 1500-ohm potentiometer which serves as a contrast (Continued on page 128)

Fig. 8. Video amplifier circuit using a triode-peniode tube.


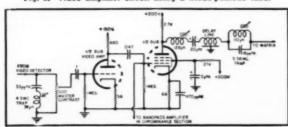


Fig. 9. Cathode follower video amplifier circuit for color TV.

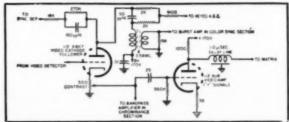

- BANDSWITCH YOUR LOADING COILS BY REMOTE CONTROL

By LEON A. WORTMAN, W2LJU

Add a luxury touch to your mobile rig. This inexpensive control unit can be built and installed in a few hours.

That's what they say and that's how I feel when I put W2LJU/mobile on the air. The installation uses a bandswitching transmit-

ter, bandswitching converter, and pushto-talk operation.

"So what? So lots of guys have bandswitching rigs and converters and push-to-talk."

"So this," I say, "I also have bandswitching loading coils on the whip at the rear of the car and remote control for them at the dashboard! I never have to get out from behind the wheel when changing bands. And, what's more, I can change bands and retune in a matter of seconds . . . while the car is in motion!"

"Man, what luxury!"

It all came about because I am basically a very lazy fellow, I think. Anything I can devise which adds to convenience or minimizes the expenditure of effort, that's for me. I used to have to drive 45 miles each morning to get to my office in the country from my apartment in New York City. And, of course, I had to make a repeat trip each night in the return direction. Not knowing exactly what time I would get home to the city each night worked a bit of a hardship on the wife. When I would work into the city on my way home on 10-meters, one of the gang would telephone the wife to tell her I was on my way and would arrive in so much time. Some of the fellows even provided a phone patch and the wife was posted about my trip home by direct QSO from the apartment where she was waiting supper to the car speeding along the highway, via ham radio.

All well and good, but the fly in this delicious ointment was my penchant for passing the driving time by working the mobile on 75-meters for QSO's with the gang in the country, 20-meter mobile for DX at the half way mark of the drive which took me along the Hudson River with its wonderful conditions for working out, and 10-meter mobile for civilian defense, short skip, and city contacts. When you're highballing along the road and making good time, it's pretty annoying to have to stop the car to change bands. How nice it would be to just push a button instead of having to get up from behind the wheel with the tool kit in hand (maybe it's raining or snowing to add to the misery), unscrew the loading coil, screw in the next one, put the tools away, get back behind the wheel, tune up the rig, start the car, and continue along the way. This can become pretty exasperating, especially should the band drop out right after you've gone through this major operation. It could mean stopping and getting out and going through the whole horrible routine all over again.

After suffering that procedure for quite some unpleasant time and reacting to each necessary band change like most people do to changing a flat tire, I designed and built the unit shown in the accompanying photos and diagrams. It makes bandswitching from the driver's seat completely practicable. The device costs only about \$12, exclusive of the loading coils which all multi-band mobiles have anyway. It can be constructed

1-4" x 6" pc. (top)
1-31/2" x 10" pc. (back)
1-31/2" x 10" pc. (front)
2-6" x 10" pc. (idex)

All pieces cut from polystyrene or lucite stock,

The bandswitching mechanism shown mounted on the

whip antenna and the dashboard control box with the indicator lights. The en-

tire system is extremely compact and easy to build.

Details of coil cover. Drill a 34" dia. hole in top piece, centered 134" from forward edge. 2" from side edges. Cut 2" corner wedges in side pieces as shown to avoid scraping against car body as the whip assembly swings while car is in metion. Parts are joined with liquid cement.

and put in operation in an afternoon's time.

There are available from some of the radio parts houses and surplus outlets 6-volt, impulse-operated, ratchet-type rotary switches. These have shafts and long side bolts which fit standard ceramic switch wafers. Because we have never seen two mobiles exactly alike, each representing the likes and economies of the individual owner-operator, the type numbers of the parts used in W2LJU/mobile are unimportant here. The technique used in achieving the end result is the important thing and sufficient data is given here to guide you in your own construction of a similar unit.

We obtained four ceramic wafers to fit the 6-volt switch. They are of the 3-pole, 3-position, non-shorting type. The 3-pole, 3-position wafers were chosen because of their physical construction which enables continuous rotary action, resulting in the cycle of band selection repeating itself automatically at every fourth impulse. Three of the switch wafers are connected in parallel and used for the r.f. section, contacting the loading coils. The fourth wafer is used for the remote indicator section at the dashboard of the car. The remote indicator is an aluminum box (steel will do as well) 4"x4"x2". Located at the upper edge of the box, for convenience, is the bandswitching control for the loading coils. It is a spring return, push-to-make, single-circuit switch. This switch remotely actuates the 6volt ratchet unit at the whip. A group of three pilot lights is mounted at the edge of the 4"x4"x2" control box which is most easily seen by the operator seated behind the wheel. These indicate which of the three bands the whip is loaded for. This technique of identification makes it quite impossible to have the wrong loading coil "in" for any band when the pilot lights indicate which is the correct one.

The setup, as we said earlier, at W2LJU/mobile was for 75, 20, and 10. No coil is necessary for 10, of course. Loading coils are required for the other two bands. Therefore, as seen in the photographs, the two loading coils are screwed together, the lower frequency, or 75-meter coil, at the top side. As shown in the schematic diagram, the 75- and 20-meter coils are in series when operating on 75. For 20-meter operation, the 75-meter coil is shorted out. For 10-meters, both coils are shorted out. The photos and diagram show the wiring technique used. The whole thing is simplicity itself and non-critical in setting up.

For weather protection, a housing was fabricated of 14" thick sheets of clear plastic. Lighter weight and opaque plastics will probably do just as well and are less expensive. The housing is slipped over the coils and switching mechanism after they have been screwed into the whip mounting in the usual way. The housing is held securely in place by the pressure of the whip screwed down into the top coil. If your loading coils are of the high "Q" type, it may be necessary to trim them a turn or two to restore resonance to that portion of the band in which you intend to do your operating. Adjustments can be made to the coils by unscrewing the whip, lifting the plastic housing, and screwing the whip back onto the coils. The housing has no electrical effects on the coils and can be replaced on the coils when the final adjustments have been made.


This specific setup has been in operation for over a year now in all sorts of weather from high summer heat to winter freezes, and spring rains. Except for taking the pictures for this story, the housing has not once been removed not even for maintenance. It

F1—10 amp. Juse
S1—S.—S.-p. push-to-make, spring-return switch
S.—S.-p. push-to-make, spring-return switch
S.—S.-p. push-to-make switch wafer (to fit RL, mechanism, see text)
RL1—6 volt, d.e. rotary solenoid mechanism (see text)
PL., PL2, PL2—Pilot lamps, 6-8 volt operation
SO,—6-prong Jemale connector
J.—6-prong male connector


Schematic and parts list covering the remote control for mobile loading coils.

has never failed to give us loyal and efficient service. Measurements with a diode type field strength meter show no measureable difference in power radiation between the conventional one-coil-at-a-time method and this remote control bandswitching arrangement. This device has been an identification for W2LJU/mobile and has aroused considerable interest among hams who have seen it. And every one says, "Man, what luxury!"

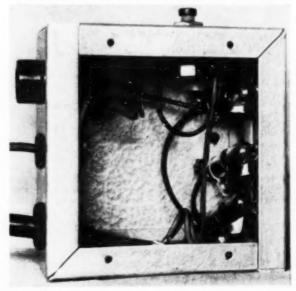The dashboard remote indicator housed in a $4'' \times 4'' \times 2''$ aluminum box. The panel lights show for which band whip is loaded.



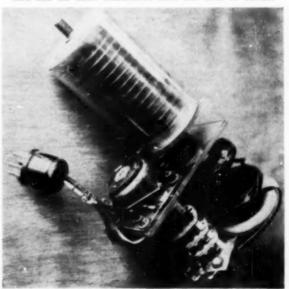Close-up view of the switching mechanism. Surplus parts are used and the entire construction costs less than 12 dollars.



June, 1954

A PHOTOTRANSISTORIZED

PHOTOELECTRIC COUNTER

By
NATHAN O. SOKAL
and
RICHARD G. SEED

Construction details on a simple "on-off" unit to count interruptions in steady beam of light.

NE of the most fascinating members of the new transistor family is the phototransistor, a photosensitive device of amazing sensitivity with built-in transistor amplification. These units have recently become commercially available, and offer extremely interesting and varied possibilities to the electronic experimenter.

The authors will describe one of the gadgets they have made with this unit; the reader's ingenuity can easily extend these basic ideas to a host of similar projects. The device to be described is a portable phototransistorized photoelectric counter.*

The counter, shown in Figs. 1 and 2, is contained in the proverbial "black box." Fig. 2 is the circuit diagram.

The phototransistor is most easily understood by considering first the photodiode. The photodiode is a germanium crystal which behaves like an ordinary crystal diode, except that the back current depends on the amount of light falling on the sensitive region. The characteristic curves for a typical germanium photodiode are shown in Fig. 4. Note that the voltage and current are in the "back" direction—the direction of high resistance of the rectifier. In the phototransistor, the current of the photodiode is multiplied by transistor action inside the crystal. Fig. 5 illustrates a typical characteristic curve for a phototransistor, showing the increased current sensitiv-

 Patent Pending. The commercial version of this device will be manufactured by Photocontrols Company, 20 Ware St., Cambridge 38, Mass.



Fig. 6 illustrates the optical system. The light source is a small incandescent lamp which has a mirror or a lens to collimate the light into a narrow beam—an ordinary narrow-beam flashlight will do. The collecting lens gathers light from the beam and focuses the light onto the sensitive area of the

phototransistor, which is placed at the focal point of the lens.

The sensitive area of the phototransistor is only about 0.05 inch by 0.1 inch. Any off-axis displacement of the image greater than this amount puts the light spot off the sensitive area. Displacement of the light source also displaces the image. Thus the light source must be kept within a certain distance of the optical axis, or it will be ignored. This means that the phototransistor, in a properly-designed optical system, can give very good rejection of strong spurious light while accepting relatively weak light from the intended source. For example, the unit can easily be operated outdoors in bright sunlight by an ordinary flashlight twenty-five feet away.

To get a quantitative idea of this

Fig. 2. Schematic of photoelectric counter.

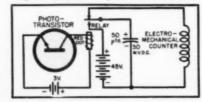


Fig. 1. External and internal views of the photoelectric counter. An X-25 phototransistor is the heart of the device.

COLLECTING

point, refer to Fig. 7. If θ is measured in radians (one radian equals 57.3 degrees) and F_L is the focal length of the lens, then the image displacement, d, is approximately $\theta \times F_t$. Since d cannot exceed about ± 0.05 inch, and if F_t is about 2.8 inches, then θ is about \pm 0.04 radian, or about 2 degrees total. Thus the device sees only in a rectangular cone about 2 degrees tall and 1 degree wide. The sensitive cone can be widened, if desired, by defocusing the lens. In practice, imperfections of the lens do a certain amount of unavoidable defocusing, so that the angular discrimination of the device would probably be not quite as good as calculated, unless a good-quality lens were used

Circuit Operation

Referring to the circuit diagram of Fig. 2, the operation of the unit can be traced as follows: A steady beam of light shines on the phototransistor, causing enough current flow to keep the relay closed. When the beam is broken by the object to be counted, the current decreases, and the relay opens, discharging the charged condenser through the counter, advancing the counter one count. When the light beam is restored, the relay closes again and the condenser is again connected to the battery, thus recharging the condenser to be ready for the next count.

This method of counting by charge transfer via the condenser usually uses less battery power than the more conventional method of connecting the counter directly to the battery. This is because the beam interruption in most practical cases is much longer than the time required for the counter to operate. With the counter connected directly to the battery, current keeps flowing even after the counter has operated, for as long as the beam remains

interrupted. This drain on the battery after the counter has done its job represents wasted power. The condenser, however, delivers a measured amount of energy on every count, just enough to do the job, irrespective of how long the beam is interrupted.

If greater sensitivity is desired, a transistor amplifier can be added, as shown in Fig. 3. A CK722 transistor will extend the operating distance by about three times; a CK721 or 2N34 by about five or six times. Adjust the "dark-current balance" control until the relay contacts open with no light

on the phototransistor.

If desired, a photodiode can be substituted for the phototransistor in the circuit of Fig. 3; the performance will then be about the same as that of a phototransistor without the extra transistor amplifier. Because of the variability in transistor characteristics, some CK722's may not work well in the circuit of Fig. 3; all CK721's and 2N34's should be satisfactory.

The phototransistor used in this device was an X-25, n-p-n grown-junction type, manufactured by Transistor Products, Inc., Boston 35, Mass. The transistor amplifier shown in Fig. 3 used a CK721, p-n-p diffused-junction type, made by Raytheon Manufacturing Co., Newton, Mass.

The collecting lens was a fifty-cent condensing lens 2 inches in diameter and 2.75 inches in focal length, available on the surplus market.

The relay was a 630 ohm, 5 milliwatt, Advance sensitive relay which happened to be available. A less expensive choice might be one of the sensitive relays now on the surplus market, having a resistance of several thousand ohms, and a sensitivity of about 20 milliwatts. The experimenter can make the relay more sensitive, if desired, by carefully decreasing the spring tension and the contact gap.

The only limitations on the choice of battery voltage and the relay are that the "light" current should close the relay, the "dark" current should let it open, and the voltage and dissipation on the phototransistor should not exceed 25 volts and 40 milliwatts respectively. If the reader wishes to calculate the proper values, he merely lays off a load line on the characteristic curve of Fig. 5, similar to the one illustrated there. One point of the line lies on the voltage axis at the battery voltage, E, and another point lies on the current axis at a current of E/R. where R is the relay coil resistance. The load line is a straight line connecting these two points, and the circuit operates at point A in the dark, and some point similar to B in the light, the exact point depending on how much light is available. The example shown in Fig. 5 is for a six-volt battery and a 1000 ohm relay.

The authors found that two flashlight cells in series were sufficient to power their unit.

The counter used was a 110 volt a.c. unit operated at 45 volts d.c. from a 50 µfd. condenser. A lower-voltage

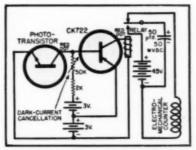


Fig. 3. Circuit of counter with transistor amplifier and dark-current cancellation.

counter would have the advantage that it could use the same battery that powers the transistor and relay. The proper value of capacitance is found by experiment. Use the value that turns over all counter wheels simultaneously, e.g., going from 9999 to 0000.

Performance

Reliable operation can be obtained at distances of 25 feet with a flashlight as the light source. The device shows excellent rejection of ambient light, due to its high angular discrimination, and can be operated easily in bright sunlight. With a transistor amplifier, distances well over a hundred feet can be obtained from a flashlight source. The reader is encouraged to test the distance achievable with an automobile headlight but he is cautioned to be very careful when aiming the unit at large distances and keep in mind the tremendous directional sensitivity of the unit

This photoelectric counter is easy to build and can be an interesting weekend project. It can also serve as an excellent introduction to the fastgrowing field of transistors and photosensitive semi-conductor devices.

The authors wish to thank Vladimir Kenn of the *Photocontrols Company* for his help in developing the device.

REFERENCES

1. Shive, J. N.: "Properties of the M-1740 P.N Junction Photocell," Proceedings of the IRE, November 1952.

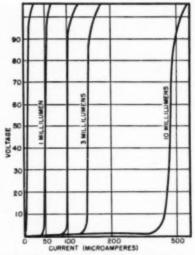


Fig. 4. Characteristics of a typical germanium photodiode. Compare with Fig. 5.

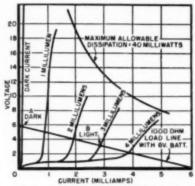


Fig. 5. Performance characteristics of a typical germanium phototransistor. See text.

 Shive, J. N.: "A New Germanium Photoresistance Cell," Physical Review, April 1949.

3. Morton, J. A.: "Present Status of Transistor Development" Proceedings of the IRE, November 1952.

4. Seed, R. G. & Holt, R. B.: "Photodiodes and Phototransistors," Electronic Design, September and November 1955.


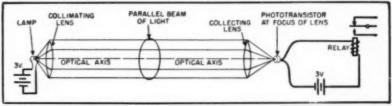


Fig. 6. Optical system for collimating and collecting the light.

Fig. 7. Optical system with an off-axis light source and image.

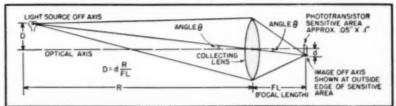

Comparison Methods for DETERMINING VOLTAGE



Fig. 1. Bench setup showing arrangement of transmission line for v.h.f. work.


A simple method for matching a load to a transmission line or for determining if a load is correctly matched.

COMBINATION of high-quality television test equipment such as a sweep generator, a high-gain oscilloscope, and a demodulator probe or detector provides a quick and accurate means for matching impedances, determining voltage standing-wave ratios, and measuring line attenuation. The technique described in this article is based on the observation and measurement of voltage standing-wave ratios to determine impedance matches. A good match between a component or circuit under test and a transmission line results in a v.s.w.r. approaching one. If the v.s.w.r. is not close to one, the circuit or component may be replaced by pure resistive loads having various values until the v.s.w.r. obtained with the original setup is duplicated: the impedance of the component or circuit may then be determined by direct measurement of the substitute

The Comparison Method

The complete physical arrangement of a suitable combination of test equip-

Fig. 2. Pattern produced by shorted line.

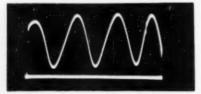

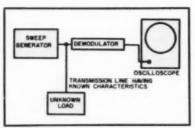


Fig. 3. Test equipment arrangement for determining impedance match by v.s.w.r.

ment is shown in Fig. 3. The output cable of the RCA WR-59C sweep generator is coupled to one end (input end) of the transmission line. sweep generator must have good linearity and a constant output voltage over its frequency range. The input of an RCA WG-291 demodulator probe or a simple detector is connected to the same end of the line. The output of the demodulator or detector is fed to the vertical input terminals of the RCA WO-56A oscilloscope. The scope used in this method must have good linearity and good sensitivity.

If the impedance of the load and the characteristic impedance of the line are equal, the voltage which appears across the demodulator or detector is independent of the frequency.¹ In other words, if there is a perfect match between the load and the line, the voltage does not change as the generator sweeps through its frequenJ. F. STERNER

RATIOS

Tube Dept.. Radio Corporation of America

When the load impedance differs from the characteristic impedance of the line, however, the voltage across the detector or demodulator varies with a change in frequency. The amplitude of this variation is a function of the reflected voltage.

If the line is shorted at the output end, highest impedance appears across the input end of the line at frequencies at which the length of the line is an odd number of quarter-wavelengths. At these frequencies, therefore, maximum voltage develops across the demodulator or detector. Lowest impedance and minimum voltage appear at frequencies at which the line is an even number of quarter-wavelengths. Fig. 2 shows a typical pattern which may be observed on the oscilloscope. The number of voltage peaks in the waveform is directly proportional to the frequency swing of the generator and the length of the

This shorted-line method may be used to measure reflected voltage over a wide range of frequencies, provided that the vertical-amplifier gain control of the oscilloscope is adjusted initially so that the peak-to-peak amplitude of the waveform is equal to ten divisions on the screen of the scope. If the cable is then terminated by a load, the vertical distance between the maximum and minimum peaks of the waveform represents the reflected voltage. For example, a waveform having an amplitude of one division represents a reflected voltage equal to ten per-cent of the incident voltage over the range of frequencies covered.

Attenuation in the line may also be measured, provided the sweep generator has blanking of the sweep oscillator so that a zero base line can be observed on the scope. If there are no losses in the line, the reflected wave equals the incident wave, and the voltage minimum is coincident with the

zero base line. The distance from the zero base line to the voltage minimum therefore provides a measure of the attenuation due to losses in the line. Care must be used in this method to prevent the existence of any large degree of reactance at the short itself. To make an effective short for 300-ohm line, it is convenient to strip back the line about one-half inch and twist the leads together. For coaxial lines, it is better to strip back the inner polyethylene insulation about one-quarter inch and short the outside braid directly to the inner conductor.

When measurements are made at v.h.f., the transmission line should be 75 to 100 feet long. 300-ohm line may be wound around a cardboard box, a packing carton, or any low-dielectric form. The spacing between the turns should be equal to or greater than the width of the line being used, as shown in Fig. 1. Coaxial cable may be placed in any convenient location without regard to spacing between turns.

For most applications in which the frequency is below 216 megacycles, the detector or demodulator used in the measurements may be an RCA WG-291 demodulator probe or a simple detector such as that shown in Fig. 5A. An alternate detector for balanced input is shown in Fig. 5B. Either of these detectors may be constructed on a phenolic board ½6-inch thick.

The entire test setup may be checked by the connection of a 14-watt or 1/2-watt carbon resistor, having the same value as the line impedance, directly across the termination or output end of the line. The line connection to the resistor leads must be made in the area directly adjacent to the body of the resistor. The pattern observed on the screen of the oscilloscope should be similar to that shown in Fig. 6. It may be necessary to try several resistors having the same nominal value as the line before a good match is obtained because of variations in the resistance values and in the characteristic impedance of the line due to manufacturers' tolerances. When a good match has been obtained, the characteristic impedance of the line may be determined by measurement of the resistor.

Use of Comparison Method

The application of this method to the determination of impedance matches can best be illustrated by an example. If it is desired to determine the match of a 300-ohm transmission line to a television tuner, the tuner is connected as the load in the arrangement shown in Fig. 3. In this case, because the effect of the match is limited to a bandwidth of 4.5 megacycles, a television calibrator such as the RCA WR-39C is used in conjunction with the sweep generator and the oscilloscope. The calibrator is loosely coupled to the input end of the line. See Fig. 7.

The sweep generator is set to the same frequency as the television tuner. Fig. 8 shows typical traces produced on the screen of the scope, represent-

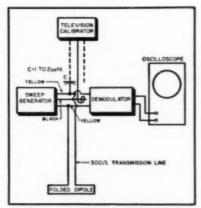


Fig. 4. Simplified block diagram shows the arrangement of test equipment for matching a transmission line to an antenna.

ing a good match and a mismatch, respectively. The efficiency of the match may be determined from the standing-wave ratio, as follows:

Efficiency = (v.s.w.r. - 1)/(v.s.w.r. + 1)where: $v.s.w.r. = E_2/E_1$

 $E_z = \text{peak of reflected wave}$ $E_z = \text{valley of reflected wave}$

A similar arrangement may be used to determine the transformation ratio of a matching transformer. The primary of the transformer is connected as the load, and resistors are substituted across the secondary until a v.s.w.r. of unity is obtained.

This arrangement is also useful in the matching of a transmission line to an antenna. In the case of a two-element array, for example, the sweep generator and demodulator are connected to the same end of the line as the receiver or transmitter, and the antenna is connected as the load. A good match is obtained by adjustment of the spacing between the two elements of the antenna to give a v.s.w.r. as close to unity as possible. See Fig. 4.

The technique described in this article is simple, and the instruments are readily available. Accuracy of the method is within ten per-cent of that obtained using a slotted-line technique. The engineer or technician willing to spend the few minutes necessary to set up the equipment will find this method extremely useful.

REFERENCE

 Bauer, John A.; "Special Applications of Ultra-High-Frequency Wide-Band Sweep Generators," RCA Review, Sept. 1947.30

Fig. 8. Tube loading effect across the antenna circuit of a TV tuner. (Top) The tuner presents a good match to the antenna over the passband as indicated by the two marks. This is the condition with the filaments turned on and "B+" applied to the circuit. (Bottom) Trace with the power removed from the tuner and the reactive components of the tuner circuit less tube grid loading causing a mismatch. This shows that the input transformer is properly designed for the type of tube used in this circuit, i.e., the grid circuit applies a resistive component across the anienna transformer so as to effect a good match from the 300-ohm input to the tube.

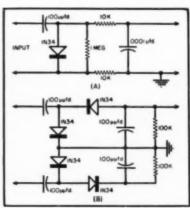


Fig. 5. (A) Detector circuit for use with test equipment shown in Fig. 1. (B) A detector circuit for a balanced input.



Fig. 6. Oscilloscope pattern produced by a 300-ohm line terminated by 330-ohm resistor.


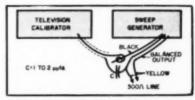


Fig. 7. How a television calibrator is coupled to the input end of transmission line.

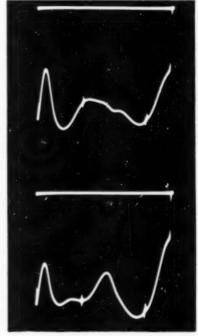

ELIMINATION OF R.F. INTERFERENCE IN AUDIO SYSTEMS

Ву

MAJOR EUGENE F. CORIELL, USAF

Armed Forces Radio Service, New York

Part 1. A survey of the interference problem, eliminating r.f. at the source, shielding, and grounding procedures.

ADIO-FREQUENCY interference with electronic equipment is a problem as old as radio. The various broadcast and communications services may interfere with each other and, in turn, may suffer interference from household appliances and industrial equipment. As a result, a large body of literature has accumulated on this general subject, augmented by comparatively recent work done to reduce interference in and to television receivers. In this latter connection, there is an excellent summary of corrective measures for TV in a recent Remington Rand publication.

The present article discusses r.f. interference with audio equipment. This is a phase of the general problem which has received little attention in the literature, at least in this country, and which is becoming increasingly important with the rapid growth of the audio field. The gear subject to r.f. interference includes broadcast audio facilities, tape and disc recorders, motion picture sound systems, high-fidelity home music layouts, public address equipment, intercoms, and other installations operating in the audio spectrum. Some of the remedies listed herein are peculiar to audio systems; others include standard shielding and grounding practices and other general interference suppression techniques.

It should be noted that a well-designed and carefully installed professional plant, such as a recording or broadcast audio facility, should experience little trouble with r.f. interference from transmitters, even in the presence of strong radio frequency fields. However, not all installations approach the ideal, and not many non-professional audio devices, such as home tape recorders and music systems, are designed with "built-in" automatic inter-

ference protection. It is hoped these articles will be useful for affected gear in both categories.

The r.f. interference may be heard in the earphones or speaker as the actual transmission of a broadcast or communications transmitter, or as various noises such as clicks, pops, whines, "hash," etc. The familiar radio elements—radiation (and/or conduction), detection, and amplification—are present when this occurs. The fact that the audio gear may have no front end or tuner as such is, alas, no bar to the excellent reception of unwanted r.f.

Radio frequency energy is generated not only by transmitters, but also by motor and generator brushes, household light switches, relay contactors, heating appliance thermostats, and sometimes by the innocent-appearing lamp bulb. The arcs and sparks of some of these devices are essentially oscillatory discharges which create wavetrains of many frequencies. Other possible sources of r.f. noise include the older type of diathermy machines, induction furnaces, and r.f. test equipment. Microphone cables, phonograph cartridge leads, d.c. power supply wiring, and a.c. power lines act as antennas which pick up r.f. from the sources mentioned and re-radiate or conduct it to associated audio equipment. The a.c. lines may also conduct r.f. directly from source equipment to audio facilities. The tendency of various kinds of conductors to collect radio frequency energy is shown by the fact that it is possible, under certain critical conditions, for the long wires carrying the firing current for blasting caps to collect enough r.f. to detonate the cap and set off the explosive charge.2 Getting back to audio, r.f. may also be picked up by inductive elements like amplifier input transformers. Somewhere in the system, rectification takes place in a non-linear element. The demodulated energy is then amplified along with the wanted signal. There are two main ways of eliminating or reducing this trouble. One is to prevent it at the source—in other words, the prevention of radiation and/or conduction. The other way is to get rid of the interference after it arrives at the audio gear.

Elimination at Source

The first step, of course, is to identify the source of the interference. This may take some doing unless the offending agency is a broadcast station or other generator whose signal is recognizable. For pin-pointing other sources of r.f., the characteristics of the offending sound may offer clues. A whining noise which occasionally changes pitch suggests a motor or generator with speed varying under changing loads. "Hash" may be due to fluorescent lights or to small a.c./d.c. appliances like shavers or fans. Clicks and pops at irregular intervals may be caused by light and power switches. Other characteristics such as time of day, frequency of the interfering voltage, and rate of repetition may further narrow down the possibilities. In smaller buildings where this is practicable, all lighting and power circuits, except the a.c. feed to the audio gear, can be turned off and restored one by one until the noise reappears. The familiar tracing technique of using a receiver with an electrostatically shielded loop antenna as an exploring coil sometimes brings results.3 So does a wavemeter and also an ingenious and easilybuilt neon bulb gadget called an "r.f. sniffer," 4 in the presence of fairly strong fields. Having located the origin of the trouble, it may be possible to reduce or eliminate the difficulty by one or more of the following measures, which are standard "suppression-at-the-source" techniques used for r.f. protection of various types of electronic

1. Supply a.c. power to the offending equipment through r.f. filters, or use bypass or feedthrough condensers. This prevents radio frequency energy from being carried away from the source equipment by the power lines which

may conduct it or re-radiate it to audio systems. Fig. 1 shows a filter of this type.

 Induction heating furnaces and some r.f. test gear may require shielded rooms to prevent excessive radiation, even when properly operated and individually well shielded.

3. Keep the negative brush lead on d.c. motors as short as possible.5

4. Check with utility company on the possibility of insulators on nearby high-tension lines causing interference. Even if the insulator is not cracked, any roughness on its surface may cause breakdown of the air over that area and cause corona discharge. Low-voltage circuits from the same or adjacent poles may pick up the radiated disturbance and conduct or re-radiate it to audio gear in the building served.⁵

5. Check for "stuttering" thermostats or defective contacts in heating appliances, and chattering power relays that fail to close their contacts

firmly.

6. Switches for lighting and power circuits can cause interference by their arcs. This is especially true of heavily inductive circuits. These may be suppressed by RC or LC filters.⁶

7. Connect condensers from motor and generator brushes to ground or frame, keeping condenser leads as short as possible to reduce radiation. Note that condensers so used may constitute a shock hazard on ungrounded devices. Safety considerations generally limit the size of the condenser to $1~\mu$ fd., and the degree of suppression obtainable by this means is therefore limited accordingly. The local electric code authority can be of help on this point.

8. Incandescent bulbs of the roughservice type, old style tungsten lamps with "W" filaments, and even miniature panel pilot lights may generate

very annoying disturbances.

9. Neon bulbs used in oscillator circuits may cause r.f. interference.

10. Fluorescent lamps are a familiar source of trouble and can sometimes be suppressed by a small plug-in type filter inserted in the wall socket supplying the lamp. A typical unit of this type is the Cornell-Dubilier "Quietone" IF-6. In aggravated cases, chokes, condensers, or filters like the Mallory Z8A may be installed in the internal circuits of the lamp. It may also be helpful to move the ballast reactor closer to the lamp to shorten the internal wiring and thereby reduce radiation.6 It should be noted that fluorescent lamp interference is often unpredictable. Not all lamps of an identical type will give trouble, and a particular unit may interfere at some times and not at others. It has been the writer's experience that fluorescent lights should not be used in broadcast and recording studios, although there are numerous installations in which they are used successfully.

 Neon signs are potential causes of trouble if their high-voltage leads have poor connections and/or are not well shielded. All metal portions of the sign, the transformer housing, and the wiring shields should be bonded together and grounded.⁶

12. Mercury rectifier tubes can be silenced by condensers between the positive terminal and ground, and by r.f. chokes in the positive lead.

13. When the number of interfering sources and the number of affected audio installations warrants the cost, the use of the *Aerovox* type ANL37 interference analyzer may simplify selection of the proper type of filter for a.c. power lines.

14. In case of interference from the stepping relays of private automatic telephone exchanges, the telephone company should be asked to install

filters.

15. For detailed data on locating and suppressing r.f. interference sources, the reader is referred to G. L. Stephens' excellent volume⁶ from which some of the prevention-at-the-source material in this article was obtained.

Suppression at Audio Gear

While it is certainly desirable to eliminate interference at the source, there are numerous occasions when this is difficult or impossible, as for example, in the case of a broadcast transmitter. Remedies must therefore be applied to the affected audio equipment. These include treatment of audio and power lines, modification of circuits, substitution of special components, and most important of all, careful analysis of the shielding and grounding of the entire audio system. In this connection, it bears repeating that r.f. interference from transmitters should be no problem in a professional audio facility if it is carefully designed and installed in accordance with the best broadcast and/or recording standards. The following data includes design and installation precautions of good engineering practice as well as what might be called "bruteforce" remedies. The distinction between the two approaches, and the applicability to non-professional equipment of the various measures described. should be obvious from the text.

Faced with an existing r.f. interference problem, the first thing to do is to find out what element in the system is acting as the antenna or the pickup


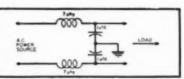


Fig. 1. Filter used to prevent high-frequency industrial equipment from feeding r.f. to a.c. supply line. May also be used in the a.c. leads of audio gear to keep out r.f. conducted along the power line. Inductance values refer to the Ohmite Z-20, 5 ampere power-line choke, in which two 7 µhy, windings are on a single ceramic core. Suppression range includes the b.c. band and extends upward to 15 or 20 mc. Whether condensers are to be on the line side or the load side of the chokes should be determined by trial. Circuit by Ohmite.

coil-the audio wiring, the power cables, or circuit components. An audio pair can be checked by determining whether the interference ceases when the pair is disconnected from its destination across which an equivalent load resistor has been shunted. Inductive elements acting as pickup coils-transformers, filters, and equalizers—can sometimes be located by circuit tracing with a crystal or diode probe feeding a high-gain amplifier. The r.f. pickup and rectification may occur in the same element, or each phenomenon may take place at a different point. In the latter case, the effective point of rectification will be farther along toward the system output. This point may be determined by applying the input of a test amplifier with a shielded audio probe successively to various circuit or chassis components and wiring joints, working back from the system output until the interference disappears. This procedure should be used with caution, to make sure the application of test leads to high impedance circuits does not of itself cause noise, hum, and other interference. Having determined the circuits and/or components involved, the measures described herein may be applied. These are grouped under the headings "Shielding and Grounding" (in this article), 'Lines and Cables." "Amplifiers and Power Supplies," "Prevention of Rectification," and "Miscellaneous Remedies" (in Part 2).

(Continued on page 90)

Fig. 2. (A) The r.f. voltage appears between ground and long "B—" leads and is coupled to preamplifier proper through stray capacities such as C. (B) Remedy is to ground low side of input transformer secondary to preamplifier chassis and remove ground from power supply to prevent ground loop. Circuit from the book "Elements of Sound Recording" by Frayne and Wolle, John Wiley & Sons.

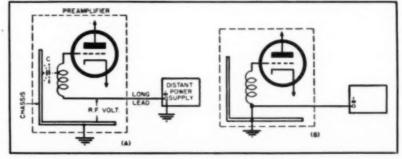



By BERT WHYTE

HE preface to this column has been used as a sounding board by me, for many purposes. Quite often I let off steam about this or that subject which I feel is not in the best interests of music and high fidelity sound. Sometimes I damn and othertimes, I praise. In all of this I hope I have been at least entertaining and informative, and perhaps, even helpful. You know, help is a funny thing. Some people can't get enough of it, others resent the whole idea, still others cast a cynical and jaundiced eye towards anyone who presumes to offer help. Well, as I've said before, some people like vanilla and some like chocolate. Since the basic premise of this column is to be helpful, I'll try to meet this obligation to the best of my ability.

Recently I enjoyed a conducted tour of the Pickering magnetic cartridge plant in Oceanside, Long Island. It was a most interesting experience to say the least. I was amazed at the amount of precision work that goes into the manufacture of a magnetic pickup. As is common in most electronic manufacturing plants, most of the delicate work is performed by women. The dexterity of some of these women was fascinating to watch as they wound minute coils, or positioned styli. My reason for mentioning this visit, is because of something I learned which may be helpful to those of you who happen to use Pickering cartridges. It seems that there has been a change in the output voltage in recent models of the 120 and 140 series pickups. A little over a year ago, it was found that the 70 millivolt output of the original model cartridge would cause some distortion when used with some of the newer models of front-ends and preamps. This is due to the fact that the phono channels on these units have a gain of over 48 db. To correct for this, the output of the 120 and 140 series cartridges was dropped to 50 millivolts. The output of the new 260 turnover unit is 30 millivolts and presents no problems. So, if you are the owner of a late model preamp and an "older" Pickering cartridge, try putting a resistance across the terminals and see if it sounds any different to you. It is certainly not a serious problem, and one which is easily solved. I shall try to find out the serial number which ended the use of the higher output coil in the pickups, and pass it on to you.

LE SACRE DU PRINTEMPS Minneapolis Symphony Orchestra conducted by Antal Dorati. Mercury "Olympian" MG50030, AES curve. Price \$5.95.

I'm going to make some pretty strong statements in this review, so I'd like a few things understood. (A) I do not own any stock in Mercury Records. (B) I am not married to the daughter of the chief recording engineer, nor am I a cousin of Antal Dorati. (C) I am under no compulsion or duress and the material contained herein is the product of my own free

Having thus unburdened myself, I can proceed with the business at hand. To wit: I think this is the greatest recording since the invention of the phonograph! Yes, you heard me right! Of all the countless thousands of recordings I have heard, this is positively the last word. Let us examine this marvel and see wherein lies its great-

It would be difficult to single out one particular element as the significant contribution to its superiority. Any "favorite" or "best" recording is, of course, a reflection of an individual's taste in repertoire, conductors, and performance, and the technical qualifications. It also goes without saying that "one man's meat is another man's poison." Even when a majority of so-called "experts" agree that such and such a recording is the "best," there will be legions of dissenters for one or another reasons. A person can be told about a certain Beethoven 5th, that has the finest performance and sound. But if that person doesn't like the Beethoven 5th, what cares he for the recording's other qualities? Or this person may love the Beethoven 5th, but can't stand this particular performance or sound. And so ad infinitum. The ideal of course, is a magical amalgam of all three pre-requisites. As far as I am concerned this recording comes closest to realizing this ideal. I freely admit I'm prejudiced in favor of the

work itself. I've been fascinated and thrilled with this controversial score ever since I heard it in Europe many years ago. What there is about the music that is so compelling is hard to put your finger on. Sure, it is programmatic. But its "primitiveness" stems more from the music itself than from the program ascribed to it. Indeed, with the advent of Disney's "Fantasia" we were shown an entirely new programmatic concept of the score. This is provocative music and it has its private meanings in everyone's private little world. In matters of performance, this version is almost totally different in concept than the other available recordings. Mr. Dorati has realized a particular ambition with this recording, having "pointed" towards conducting "Le Sacre" ever since he was signed for the Mercury "Olympian Series." To this end, he has programmed "Le Sacre" as part of the regular concert repertoire of the Minneapolis Symphony, for the past several years. All this careful planning and enthusiastic anticipation has resulted in a performance which is absolutely overwhelming in its impact. In a score which is notable in itself for the generation of excitement, this reading is a blood-tingling, nerve-shattering experience.

Throughout the work, Dorati emphasizes the rhythmic elements which is as it should be. From the Introduction to the "Dances of the Adolescents," and on through the "Game of Abduction" and "Spring Rounds," Dorati drives his men at an almost frenetic tempo. But for all this headlong pace and blazing intensity, the score remains completely articulate. There is no blur or fusion of important polytonalities or polyrhythms. The remainder of the reading from the "Pagan Night" to the final "Sacrificial Dance" is unbelievable. Dorati and his orchestra give an absolutely stunning display of virtuosity. The incredibly difficult polyrhythms of the "Sacrificial Dance" are negotiated without a single "flurp"! From a comparative viewpoint, Dorati's reading is most closely paralleled by that of Stravinsky himself. Strangely, the authenticity usually ascribed to composer-conducted readings, is not fully realized in the Stravinsky recording. Dorati has taken one further step in the direction of rhythm and balance which makes his reading altogether unique.

Now for the all important question of sound: Nothing in my entire experience with recorded music has ever impressed me so much. This is the cleanest, most distortion-free, most beautifully balanced sound in phonographic history! From every possible aspect, this recording wins hands down. Dynamic range? Unbelievably wide. Frequency response? Only the most advanced equipment will do it full justice. You will hear sounds in this recording, you probably thought were impossible to engrave on a disc. Stratospheric, piercing piccolos and flutes.

(Continued on page 121)

The opinions expressed in this column are those of the reviewer and do not necessarily reflect the views or opin-ions of the editors or the publisher of this magazine.



THE Crosley "Super-V" represents a completely new design in small, compact television receivers which compares in sensitivity and performance to the larger models. This article will discuss the changes, problems, and features of the "Super-V" chassis which are of interest and importance to the service technician.

A full complement of circuits are used in the "Super-V" receiver. Although only 15 tubes are used, six of them are double tubes and one is a multipurpose tube; thus, this chassis is equivalent circuit-wise to a receiver using 23 single tubes. The sensitivity of the "Super-V" is high, eliminating nuisance calls and performance problems inherent in any receiver designed with a limited sensitivity.

One of the most striking differences in the "Super-V" from the service standpoint is the mechanical changes brought about by the radically new vertical chassis design. The chassis slips over the neck of the picture tube, much like a deflection yoke or focus coil, as shown in Fig. 1. A large circular opening in the center of the chassis provides adequate clearance for the neck of the picture tube, and permits the chassis to be mounted in a position in front of the deflection yoke in a plane parallel to the face of the picture tube. The tube sockets and circuit components are mounted on the chassis in the area surrounding the circular opening. This arrangement permits a small, compact design without crowding the components or eliminating essential circuitry. The chassis and picture tube are independently mounted on the wood baseboard, which is also used as the bottom of the cabinet.

The tuning, volume-on-off, contrast,


"Super-V" 15-tube TV set with a vertical chassis.


horizontal hold, and vertical hold controls are located on the side of the cabinet. The brightness, vertical linearity, and vertical size controls are inside, on the chassis, as shown in Fig. 2.

The chassis layout in the "Super-V" is ideal from the tube-changing standpoint. All tubes are on the back side of the chassis and are readily accessible by removing the back of the cabinet. It is possible to see right down into the tube-socket pin holes. Note: Turn off the set before removing any of the tubes.

The cabinet is designed to fit over the chassis and tube assembly like a bonnet, as shown in Fig. 6. It is held

Fig. 2. Rear view of the "Super-V" chassis with the back of the cabinet and the high-voltage cage cover removed. Note accessibility of tubes and adjustments.

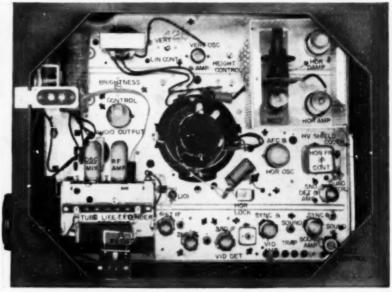

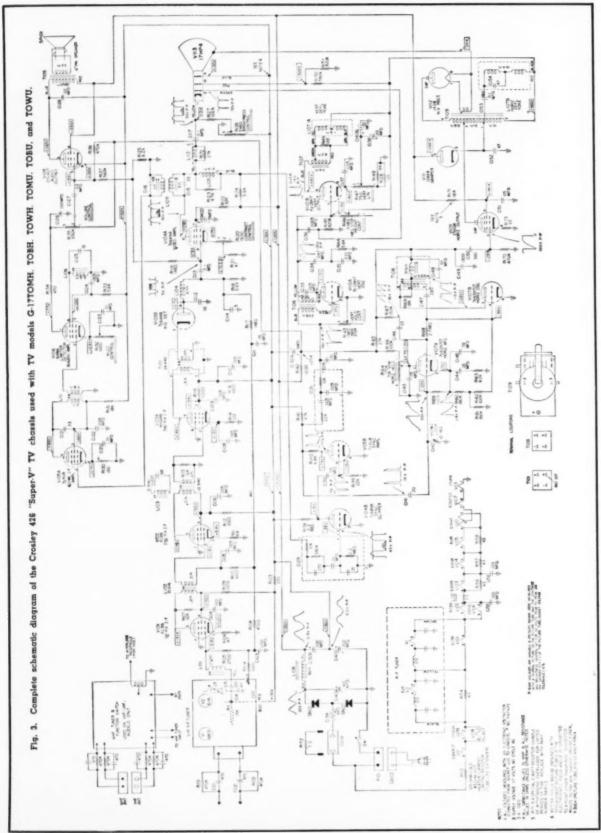

to the chassis mounting board with four 5/16" hex head machine bolts which extend up through the bottom, two on each side, and three wood screws. One of the wood screws is located in the bottom front, the other two are in the rear corner blocks. To remove the cabinet, take off the back and antenna terminal board, remove or disconnect the speaker, and take out the mounting screws. The lightweight cabinet is easy to handle and, once it is removed, most of the circuit components

and the circuitry are exposed to view'

"B+" and Heater Circuits

The block diagram of the "B+" and heater circuitry used in the "Super-V" chassis is shown in Fig. 4. A good general working knowledge of this block diagram is very important to any television service technician in tracking down symptoms and locating troubles in the "B+" and heater circuits. Starting with the a.c. power plug, note that one side of the a.c.

line passes through the interlock connector and through the "on-off" switch directly to the chassis, which is used for the common electrical ground. This makes the chassis "hot." Since, in most cases, one side of the power line is grounded, the chassis will be either at ground potential or 117-volts a.c. above ground, depending on which way the power plug is inserted into the a.c. outlet. To eliminate the shock hazard associated with this arrangement, take care when working on the chassis to

Table 1. Alignment procedure for the video i.t. and sound circuits of the Crosley 426 "Super-V" TV chassis.

			VIDEO I.	F. ALIGNMENT				
STEP	SIGNAL GENERATOR FREQUENCY CONNECT TO		OUTPUT NDICATOR	CONNECT TO	ADJUST	REMARKS		
1	24.4 mc.	Test point 2 on tuner through a .01-µfd. con- denser	V.T.V.M.	Junction of R110 and C111	T _{1et} for maximum	Limit generator out- put to give less than —2 volt reading Put —3 v. on a.g.c.		
2	22.9 mc.	Same as above	Same as above	ame as above Same as above L ₁₀₃ (rear slu maximum		Use first peak from Tinnerman-clip end of coil		
3	21.9 mc.	Same as above	Same as above	Same as above	L ₁₀₂ (front slug) for minimum	Use first null from coil form end. Ad- just input level to give at least .5-volt null		
4			Repeat steps	2 and 3	- X 1880-4			
5	25.5 mc.	Same as above	Same as above	Same as above	L ₁₀₂ for maximum			
6	25.1 mc.	Same as above	Same as above	Same as above	L:01 (front slug) for maximum	Use first peak from Tinnerman-clip en of coil		
7	27.9 mc.	Same as above	Same as above	Same as above	L ₁₀₁ (rear slug) for minimum	Use first null from coil form end. Dis regard this step i 27.9 mc. trap ha not been added		
8	25.1 mc.	Test point I on tuner	Same as above	Same as above	L ₂ (brass screw) for maximum	Connect a 100-ohn resistor in serie with a 1000-µµfd condenser across L		
9	25 mc. center frequency 10 mc. sweep Raised tube shield of V. (6J6) and chassis		Oscilloscope	High side of R ₁₂₀ contrast control and chassis	All i.f. slugs for curve below:	Set contrast contro at minimum		
		equired in the aliquetul as an over-all			I F C			
			SOUND A	IGNMENT				
10	4.5 mc. 400 cps amplitude modulated (30% or greater)		Oscilloscope	Pin 11 of CRT through de- tector probe	L ₁₀₉ (rear slug) for minimum	Set tuner to unuse channel		
11	Tune in local T	V station			L ₁₀₆ for maximum sound output	Set "buzz control" (R122) one-quarte turn from clockwis stop		
12					L ₁₁₁ and L ₁₀₉ (front slug) for maximum sound output	If signal in area in too strong to obtain peaks, remove an tenna temporarily		
13					"Buzz control," R123, for minimum noise & L104 for maximum sound	Signal must be weat to allow noise (has to come through		

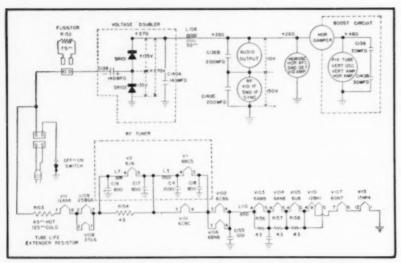


Fig. 4. Block diagram of the "B+" and heater circuits of the "Super-V" chassis.

keep clear of any externally grounded conductors such as antenna leads, water pipes, ground test leads, and other TV chassis.

The other side of the a.c. line passes through the interlock and branches out into two circuits. One goes through the "fusistor" to the half-wave voltage doubler rectifier circuit. The "fusistor" is used as both a fuse, which opens on a direct short or overload. and current-limiting resistor, which limits the maximum current which can flow through the input condenser, C_{100} , during the initial charging period, i.e., when the set is first turned on. This protects both the condensers and selenium rectifiers. The bottom rectifier, SR_{102} , conducts on the negative peak of the a.c. input and develops +135 volts across its terminals. (The amplitude of the rectified voltage is dependent on the "B+" load and is less than the input peak voltage, in this case, 1.41×117 volts or 165 volts.) On the positive peak, the top rectifier, SR_{ini} , conducts and develops an output of +135 volts. Since the two voltages are in series across the output condenser, C_{ini} , they add to produce a total of approximately 270 volts for the "B+" supply.

The output from the doubler circuit is passed through the filter, choke $L_{\scriptscriptstyle 100}$ and condensers $C_{\scriptscriptstyle 132R}$ and $C_{\scriptscriptstyle 140C}$, which eliminates most of the hum component. The +260-volt supply provides the basic power requirements for all the "B+" circuits in the receiver. Some tubes such as the sound detector, video amplifier, horizontal oscillator, and a.f.c. are operated directly off the +260-volt "B+". However, the tubes in the r.f., i.f., and sync circuits must be operated on a lower voltage and are, therefore, connected (in a parallel string) in series with the audio output tube across the +260volt "B+" circuit. In normal operation, the 25L6 output tube is self-biased to a point which places approximately +150 volts at its cathode. This is the "B+" voltage required by the other tubes. The a.c. coupling and interaction between the circuits is kept to a minimum by using the two 200-µfd. bypass filter condensers, C_{uus} and C_{luc} .

The horizontal and vertical amplifiers, requiring a higher voltage than the 260 volts available from the "B+" supply, obtain 480 volts from the "B+" boost circuit, as in most con-

ventional receivers.

The other lead from the a.c. line is connected through the "tube life extender" resistor R_{183} , to the high side of the heaters which are, in turn, connected in a combination series-parallel circuit, as shown in Fig. 4. The "tube life extender" resistor limits the amount of current flowing in the heater circuit when the set is turned on. The current-limiting resistor is needed because the resistance of the tube heaters is much less when cold than when The high resistance of the current-limiting resistor when it is cold is sufficient to limit the amount of heater current which can flow when the set is first turned on, thus effectively eliminating the high-current surges which would otherwise shorten the life of the tube heaters.


Tubes in the receiver should not be pulled out while the set is turned on. A glance at the heater circuit will show that some of the tube heaters are shunted by either a resistor or another tube. Therefore, should one of the parallel tubes such as V_{100} , V_1 , or V_{102} be pulled out while the set is on, the tube that is left is forced to carry the entire load, placing an excessive strain on its heater. Should Vz. V 1613, V_{101} , or V_{108} be removed while the set is turned on, it will result in an excessive amount of current being forced through the associated shunt resistor, which may cause it to change value or otherwise destroy its usefulness. (Note: In later production receivers, the three 43-ohm resistors have been replaced by one 126-ohm, 10-watt resistor.)

Tuners

The "Super-V" employs a Standard Coil turret tuner with a pentode r.f. amplifier. (See Fig. 5.) It can be field converted to receive u.h.f. by replacing unused v.h.f. strips with u.h.f. strips. This chassis is also available with a factory installed continuous-coverage u.h.f. tuner, shown in Fig. 7, which converts u.h.f. signals to channel 5 or 6. The u.h.f. tuner is also available with a complete set of instructions for field conversion, and is recommended for fringe-area reception or wherever full channel coverage is desired.

The u.h.f. tuner employs the same double-conversion system used in previous models. It is, however, a new design and employs several interesting features. New pin-type u.h.f. an-

Fig. 5. Schematic diagram of the v.h.f. turret tuner using a pentode r.f. amplifier. The test points indicated are used in the alignment procedure of Table 1.

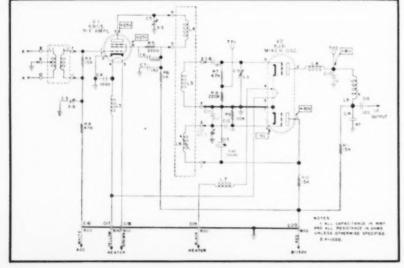

tenna connections are used because it was found that during the development and field testing of the u.h.f. tuner, conventional screw-type antenna terminals in a 300-ohm balanced line represented a considerable discontinuity which resulted in a poor voltage standing-wave ratio. The conventional screw terminals are satisfactory for v.h.f. reception.

The oscillator in the converter operates approximately 82.5 mc. below the u.h.f. channel frequency to which it is tuned, producing an 82.5-mc. i.f. signal. This is picked up on the "Super-V" by setting the v.h.f. tuner on either

channel 5 or 6.

The u.h.f. variable tuning unit is composed of three silver-plated, semicircular rings which act as one-quarter wave tuned lines; two for the r.f. preselector, one for the oscillator. The end inductors L_1 , L_2 , and L_8 (see Fig. 7), are formed by making a loop in the connecting lead on condensers C., C., and C_{18} , respectively. The converter is aligned on the high end of the band by adjusting the size and shape of these loops. The preselector is aligned on the low end by adjusting condensers C_4 and C_5 . The oscillator is aligned on the low end by varying C_{18} .

A 6T4 u.h.f. oscillator triode is used in a modified Colpitts grounded-plate circuit. The output of the oscillator is inductively coupled to the mixer circuit by means of the loop formed in the lead which passes through the hole in the oscillator shield and connects the oscillator grid, pin 6, to the .1 $\mu\mu$ fd. blocking condenser, C_{ii} . Moving this loop toward C_5 increases the oscillator-to-mixer coupling, and moving it

away decreases it.

There is, in some cases, an appreciable variation in the amount of crystal capacity between crystals of the same type. For this reason, it is usually best when replacing the 1N82 crystal to try three or more different ones. Particular care should be exercised to make sure the crystal contacts are clean and that they make good contact in the socket clips. For best results, the crystal current should not fall below 0.4 milliampere, or exceed 5 milliamperes at any point in the tuning range as measured at the test point (T.P.).

The i.f. signal developed in the crystal mixer circuit is amplified in the 6BK7A cascode amplifier before it is coupled through the function switch, SW_1 , to the v.h.f. tuner input. The double-tuned broadband i.f. input transformer (T_i) is aligned at the center frequency of 82.5 mc. The function switch (SW_1) is used both to switch the antenna connections and to control the "B+" to the u.h.f. converter.

To facilitate the construction and testing of u.h.f. units with available u.h.f. signal generator equipment, the u.h.f. tuner is designed with a 50-ohm single-ended input impedance. In order to match this input to a standard 300ohm antenna system, an impedancematching network called a balun is used (CA: in Fig. 7.) Shown in Fig. 9A, it consists of two pieces of 125-ohm



Fig. 6. Chassis removal is rapid and exposes all tubes and components for servicing.


transmission line, each cut to a quarter-wavelength near the center of the u.h.f. band. The two sections are connected in parallel at the 50-ohm (tuner) end and in series at the 300ohm (antenna) end, as shown in Fig.

Video I.F. and Amplifier

The three-tube video i.f. circuit is similar to the one used in other Croxley models. A broadband circuit employing low-side capacitive coupling is used between the mixer and the 1st i.f. amplifier. (See Fig. 3.) The series circuit formed by L_0 and C_{11} constitutes an effective filter which suppresses the oscillator energy present in the mixer plate circuit. This is an important factor in keeping oscillator radiation to a minimum so as to eliminate interference with other TV sets.

Service technicians in plagued with adjacent channel interference will be interested in learning that a 27.9 mc. adjacentchannel trap is available which can be easily installed and adjusted without removing the cabinet. This trap is a small coil and condenser assembly connected together to form a parallel-(Continued on page 108)

Fig. 7. Schematic diagram of the continuous-type u.h.f. tuner available with the "Super-V" chassis either factory installed or for field installation. The dial cord stringing guide in the lower right-hand corner should be followed exactly.

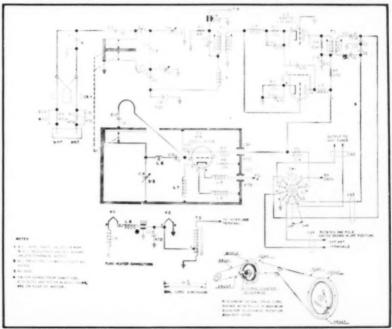


1954 TV RECEIVER SPECIFICATIONS

Continuation of the list of mechanical and electrical specifications on new TV sets for service technicians. See next issue for additional listings.

MFR.	CHARRIE	TUBES							VIDEO I.F.	H.V.4	U.H.F. PRO- VISION	POWER	SPECIAL FEA- TURES
	CHASSIS	TUNER	LF.	VIDEO2	AUDIO	SWEEP3	P.S.	CRT	FREQ. (MC.)	(KV.)	VISION	(WATTS)	TURES
HALLI. CRAFTERS	C1400D D1400D	6BZ7	6CB6 6CB6 6CB6	12BY7 6AU6	6AU6 6AU6 6AL6 6AV6 6AQ5	6AV5, 6AQ7	5U4G 5U4G 1B3	24CP4 or 27RP4A	45.75 45.75	18	11	275	5, 10, 1
MAN	301	6BQ7 or 6BZ7 6J6	6CB6 6CB6	1N60 or 1N64 6AH6	6AU6 6AU6 6AU6	12AU7, 6AL5 6SN7, 6BQ6	Sel. Rect. 6W4	21YP4 or 17HP4	41.25	15	11	155	
HOFFMAN	406	6BQ7 or 6BZ7 6J6	6CB6 6CB6 6CB6	6AL5* 12BY7 12AU7*	6AU6 6AU6 6AV6 6K6	12AU7, 6AL5* 12AU7*, 6BQ6	Sel. Rect. 6W4	21YP4	41.25	16	Strips	155	
	TV-180- 3W	6BZ7 12AZ7	6CB6 6CB6 6CB6	1N64 12BY7	6AU8 6T8 6K6GT	6U8, 6BE8 12BH7, 12B4 6AL5, 12AU7 6BQ6GT, 6AX4GT	1	17YP4 21ZP4A 21WP4 21XP4	36.6	14	All- Channel Tuner Optional	175	5, 10
	TV-190- 3W	6X8 6BZ7	6CB6 6CB6 6CB6	1N64 6AU6 6AQS	6AU6 6T8 6V6GT	6C86, 12AU7 12B4, 6AL5 6BQ6GT, 6AX4GT 12AU7	Sel. Rect. 1B3GT	17YP4 21ZP4A	45.75	14.5	All- Channel Tuner Optional	175	5, 10
	TV-190- 5W	6X8 6BZ7	6CB6 6CB6 6CB6	1N64 6AU6 6AQ8	6AU6 6T8 6L6GA	6C86, 12AU7 12B4, 6AL8 6BQ6GT, 6AX4GT 12AU7	Sel. Rect. 1B3GT	21ZP4A	45.75	14.5	All- Channel Tuner Optional	190	5, 9, 10
РИПСО	HF-200- 3W	6BZ7 12AZ7	6CB6 6CB6 6CB6	1N64 6U8* 6AU6 6AQ8	6BA6 6AU6 6T8 6V6GT	12AU7, 12B4 6AL5, 6BQ6GT 6AX4GT, 6U8° 12AU7, 12AU7	Sel. Rect. 1B3GT	17YP4 21ZP4A 21ZP4B		15	All- Channel Tuner Optional	200	5, 10
PHI	HF-200- 5W							21ZP4A	45.75	15	All- Channel Tuner Optional	215	5, 9, 10
	TV-197	6X8 6BZ7	6CB6 6CB6 6CB6	1N64 6AU6 6AQ5	6AU6 6T8 6V6GT	6CS6, 12AU7 6BQ6GT, 6ALS 6CD6G, 6V3A 12AU7	Sel. Rect. 1B3GT	24VP4A	45.75	18.5	All- Channel Tuner Optional	205	5, 10
	HF-207	6BZ7 12AZ7	6CB6 6CB6 6CB6	1N64 6U8* 6AU6 6AQ5	6BA6 6AU6 6T8 6L6GA	12AU7, 6U8* 6BQ6GT, 6AL5 6CD6G, 6V3A 12AU7, 12AU7	Sel. Rect. 1B3GT	27LP4	45.75	19	All- Channel Tuner Optional	205	5, 10
	HF-208							24VP4A	45.75	19	All- Channel Tuner Optional	205	5, 10

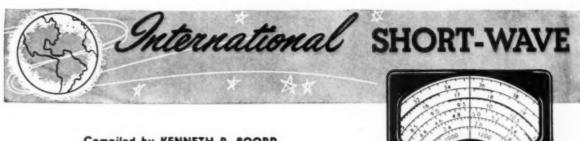^{1.} Video i.f. tubes only. 2. Includes detector and a.g.c. 3. Includes sync section and a.f.c. 4. CRT 2nd anode voltage. 5. Removable safety glass. 6. Local-fringe a.g.c. adjustment. 7. High-fidelity sound. 8. Aluminized picture tube. 9. TV-radio-phono combination. 10. Euilt-in antenna. 11. 82-channel tuner. 12. Adjustable dial light. *Part of tube is used in another section.



Compiled by KENNETH R. BOORD

HEN this month's column was prepared, a few stations had not yet gone on summer schedules: in such cases, you may find summer schedules one hour earlier than listed here-

Albania-Radio Tirana, 7.852A, noted with news 1400. (Pearce, England) Heard in English 1745-1800. (Eriksson, Sweden) More recently noted with English 1700-1730 closedown. (Cox, Dela.)

Algeria - Radio Algerie, 6.160, is heard best in France around 1300. (La Radio Mondiale, France)

Andorra-Radio Andorra, 5.990A, has French, Spanish programs 0630-0900, 1230-1900. (ISWC, London) Measured recently as 5.988 at 1725. (Ferguson. N. C.

Anglo-Egyptian Sudan-Radio Omdurman, 4.995, noted 1340 with Arabic music; 1350 with Arabic news. (Pearce, England)

Miss.. Angola - Anglado, reports CR6R0, 7.580A, heard 1300-1400, and Radio Clube de Benguela, 5.042, at 1700. Luanda, 11.862, noted daily from around 1300 to sign-off 1730, good level in Minn. (Rowell) CR6RG, Radio Diamang, 9.340, heard in Sweden around 1410. CWQRM. (Etersvep, Sweden) Noted in England 1330 with popular musicales and closing 1430 with "A Portuguesa." (Pearce)

Argentina - LRS, 11.880, Buenos Aires, noted 1600 announcing as Radio Splendid; LRU, 15.290, heard afternoons EST announcing as Radio El Mundo. (Cody, Ireland)

Australia - VLI6, 6.090, Sydney, N.S.W., noted 0600-0700. (Pearce, Ill.) VLM4, 4.920, Brisbane, Queensland, heard 0600 with news. (Murphy, N. Y.; Chatfield, N. Y., others) VLC9, 9.615, is good level 1000-1115. (Waltz, Washington; Forster, Ill.) Good over VLA15, 15.200, 2155-2315 to West Coast North America. (Kirby, Mo.)

Austria - Blue Danube Network, 5.080, heard in Europe 0630-0700. (URDXC) And on 9.617 at 0430. (Pearce, England) Vienna, 6.155, is heard in Britain closing 1828 after identification in German. (URDXC)

Balearic Islands - Radio Menorca now uses 7.415 around 1430. (ISWC, London) Heard near 7.405 at 1500 with music; generally closes after taking relay from Madrid 1600-1615. (Pearce,

Belgian Congo-OTC, 9.655, good to North America 1900-2200. (McCollum, Ohio: Foster, Ill., others)

Belgium - ORU. 9.767, Brussels, noted in clear 1945. (Rideout, Wisc.; Foster, Ill.)

Bolivia CP38, 9.442, La Paz, noted closing around 2128A. (Ferguson.

Bulgaria-Radio Sofia, 9.700, noted to North America 1800-1815, 1900-1930, 2000-2030. (Welch, Mass.) English heard 1500 on 7.256, 6.671. (Eriksson, Sweden)

Burma - Rangoon, 4.775A, is good 0915-1015. (N. Z. DX Times) Weak in Calif. (Morgan)

Brazil-PRLA, 9.770, Rio de Janeiro, is heard occasionally around 2030 with much classical music. (Niblack, Ind.) PRL7, 9.720, Rio de Janeiro, noted Sat. 2100 with announcements in English in musical session. (Anglado, Miss.) With news in Portuguese 2130. (de Neuf, N. Y.) Radio Clube de Pernambuco noted again on 11.865 from 1500 onwards. (Cody, Ireland) ZYR78, 11.925, Sao Paulo, noted 2200-2300 when identified as "Radio Bandeirantes." (Northrop, N. C.) ZYK3, 9.565, noted with "Brazil Calling" (English) 2005-2030. (Reidler, Pa., others)

British Guiana - ZFY lists 5,981, 3.255, at 0545-1145, 1445-2045 Sun.; weekdays 0515-1145, 1445-2045. (Pearce, England) Noted on 3.255 with news 2000, closing 2115. (Bellington, N. Y.)

British Honduras - Radio Belize, 3.300, 4.950, noted around 1900-2130 in English and (a little) Spanish. (Rowell,

British New Guinea - VLT6, 6.130, Port Moresby, heard 0450-0550 when is blotted out by CHNX, Halifax, N. S., Canada, coming on air. (Pearce, Ill.,

Canada-CFRX, 6.070, Toronto, Ont., is good level around 1600. (Welch, Mass.) VE9AI, 9.540, Edmonton, Alta., is again audible in Texas around 0900. (Stark) Canada noted over 6.08 at 0100-0145 with news, music. (Garren,

Cape Verde Islands - CR4AB, St. Vincent, has been heard in Britain on measured 7.092 at 1720. (URDXC) CR4AA, 7.398A, noted opening 1500; 1545 news in Portuguese. (Pearce, England) Good signal around 1700. (Sutton, O.)

Ceylon-Radio Ceylon, 9.52 noted to South India around 1100. (Zahner, Md.) Chile - CE1515, 15.150, Santiago, noted fair level 1830 in Spanish. (Hill, N. H.

China-Radio Peking, 15.060, noted 0400 with news, strong level. (Bates, Okinawa) Noted by Balbi, Calif., then on 10.20, 10.26, 9.08, 7.50, 6.20, 6.10; 11.67 does not carry news then; Shanghai noted by Balbi on 6.20, excellent signal around 0400; Balbi notes the 0930 news over 11.67 (not 11.69 as announced). Ferguson, N. C., recently heard Peking in native at 2040 on 15.060, 15.130A.

Colombia-HJCO-HJKA, 4.99A, Bogota, noted with program schedule in Spanish 0000-0005 and then closing with anthem, good level; HJKD, 6.000, heard 2000 with bilingual musical program in English-Spanish, good level; HJFX, 6.054, Cali, noted 2200-2300 with music, some QRM. (Koch, Ore.) HJAE, 4.940, Cartegena, heard closing 0000. (Murphy, N. Y.) Radio Maria, 4.824, Pasto, noted 2129-2205; when identifies, uses "Love's Old Sweet Song" as background music. (Roberts, Conn.) HJCT, 6.185A, Bogota, noted at good level evenings EST. (Strong, Md.)

Costa Rica - TIFC, 9.647, is good level to 2305 closedown. (Herd, Dela.) Due to power shortage, schedule is now 0600-1300, 1800-2300. (Cushen, N. Z.; Frazier, Texas)

(Continued on page 100)

This veteran SWL is Bill Roemer, Bowling Green, Ky. His well-equipped listening post includes a National HRO-50, a Hallicrafters S-19R, and DB22A (RME) Preselector, and a BC-221 frequency meter. During both World War II and the war in Korea, Bill did a splendid job of monitoring POW messages and then relaying them to the prisoner's families in the U.S.





Fig. 1. The tuning unit assembly and base of the tower. Access to bandswitch is through front door of the mailbox "cabinet."

Construction and operational details on a compact, highly efficient antenna system for the 80, 40, and 20 m. bands.

Levery amateur is faced with the problem of efficiently radiating the energy produced by his transmitter. The antenna described in this article operates well on 80, 40, and 20 meters, requires very little space, is reasonable in cost, and looks professional.

The antenna, a 44-foot vertical, is mounted approximately one foot off the ground supported by standoff insulators on a wooden mount. Ground wire radials are buried just beneath the sod and terminate at the base of the mount. The tuning units are placed in an RFD mailbox beside the antenna.

Some of the important features of the antenna include the following:

 Radiation of the energy at vertical angles which favor DX communications.

Excellent local coverage produced with vertical polarization.

Better communications with local mobile installations because they are all vertically polarized.

4. Buried coax line is used to feed the antenna on all bands. (RG-8U)

5. Harmonic radiation is reduced because of the low-pass filter action of the L-networks used to match the antenna and the transmission line.

6. The complete system can be erected on any small city lot.

7. The total cost is approximately

8. One final important feature—installation of the ground system is work, however the rest of the job is pure enjoyment.

An antenna height of 44 feet was chosen because this height will pro-

duce maximum radiation of energy, on 20 meters, at very low vertical angles. This was discussed in a previous article ("The Ground Plane Grows Up," May 1954, RADIO & TELEVISION NEWS). Briefly, the antenna is .63 wavelength on 20 meters and is similar to an extended double-zepp, except in this case it is vertical and worked against ground. This type of operation has been used by some broadcast stations to obtain added coverage. Note the 20meter vertical pattern shown in Fig.2A. There is a small high angle lobe caused by a phase reversal on a portion of the antenna. If the antenna was considerably longer it would become a poor radiator on 20 meters as the small high-angle lobe would develop into a large lobe and finally replace the lower lobe altogether. The antenna height is therefore limited by this fea-


Vertical radiation patterns are also included (Figs. 2B and 2C) for 40 and 80 meters. As can be seen from the patterns, 40 meter radiation is at a slightly lower vertical angle than 80 meters whereas 20-meter radiation is concentrated at very low angles. The radiated energy from the antenna on all three bands is concentrated in each case where it will be most beneficial for DX work.

The ground system used with this type of antenna is very important because considerable losses can develop at this point. The outside braid of the coax transmission line is connected to the ground radials at the base of the antenna support where the ground

wires are terminated. The ground wires, like spokes of a wheel, form radials from the base of the antenna. If the ground system is poor then losses are developed similar to those that would occur if a resistor were inserted in series with the transmission line. A ground stake is not satisfactory by itself, however it may be used in conjunction with the ground system described. The ground system should include as many radials as possible with lengths up to 1/4 wavelength or greater. The author's installation includes 16 radials which vary in length from about 25 to 45 feet. They are made of number 16 galvanized iron wire which is inexpensive and does a good job. Copper wire is slightly better but much more expensive. The radials are buried about 2 inches below the surface. The wire was stretched between two temporary stakes in the position desired and then the ground sliced beside the wire (using the wire as a guide). Two large screwdrivers were used to push the wire down in the slit in the sod. After the wires are in place the sod was then tamped back to normal. The ground installation task was made easier by heavy watering the night be-The coax feedline which runs under the house was also buried and brought out in the operating room in a coaxial wall receptacle mounted on the baseboard.

The tuning network, Fig. 3, for each band is simply a series coil and shunt condenser called an L-network. values used are dictated by the antenna impedance at the frequency of operation. The 80-meter tuning unit consists of a large shunt capacity (1200 μμfd.) and a large series coil (10 μhy.) The 40-meter unit consists of a series coil (2.1 µhy.) and a shunt condenser (215 µµfd.). The 20-meter coil has an inductance of .6 µhy, but no shunt capacity is used. The measured impedance of the antenna on 20-meters indicated that a shunt capacity of about 15 µµfd. would be needed on the antenna side of the network; however this is a very small value and in actual practice it was found unnecessary, possibly because the switch and wiring capacities to ground amounted to this value. The coils used were home constructed and self-supporting with the exception of the 80-meter coil which was found on a standard 2½ inch form. Coil lengths, diameters, and number of turns are listed in the parts list accompanying Fig. 3.

Several methods can be used to obtain the necessary capacity for the shunt condensers. A receiving-type variable can be used on 40 meterssuch as a 250 µµfd. unit. The author uses a 250 µµfd. variable rated at 1500 volts because it happened to be in the junk box. The 80-meter capacity presents a problem because of its large value. A good solution is to use a fixed mica condenser of 1000 µµfd. and a 210 µµfd. variable condenser in parallel to obtain the correct value. The current developed across the capacity is rather high because the reactance is low. This is not important with air dielectric condensers since they do not break down due to high current until the voltage rating is approached. Mica condensers, however, have definite maximum current limitations even though the voltage rating is not exceeded. This varies with the type of mica condenser, the frequency of operation, and its capacity. If you are using a full kilowatt purchase one of the large mica condensers made specifically for r.f. current, such as the Soler type XA, Aerovox 1994, or similar condensers, having a 5000 volt d.c. rating and a current capacity of about 9 amperes at this frequency. In the author's particular installation a similar condenser was used (1200 µµfd.), purchased at one of the local radio stores on their surplus table for \$.95. 1200 μμfd. is an odd value and probably is not available, however, the author has noticed numerous advertisements mentioning 1000 µµfd. condensers as surplus items at a similar price. Although there seems to be no specific current ratings available for the smaller transmitting mica condensers such as the C-D type 4 and 9 or Sangamo type A

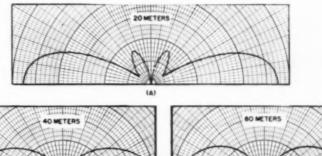


(6) (C)

Fig. 2. Vertical plane patterns of antenna at (A) 20, (B) 40, and (C) 80 meters.

and H (2500 d.c.w.v.), they are being used successfully in similar applications

Mr. Grammer in his article, "Pi-Network Tank Circuits for High Power" (QST, October 1952), describes the use of these smaller mica condensers in a pi-network in the output circuit of a high power amplifier. His experiments indicate that this type of condenser is capable of carrying about 3 amperes r.f. current, thus, for powers up to about 150 watts, a single unit rated at 1000 µµfd./2500 d.c.w.v. would be satisfactory. He mentions the TV 500 μμfd./10,000 d.c.w.v. type condenser works very well in this application; a pair of these in parallel could be used satisfactorily at higher powers. So much for the current limitations of mica condensers. Another method can be used to obtain the correct capacitive reactance (the one the author used). It consists of combining a fixed mica condenser with a small series coil. The coil reduces the capacitive reactance which is the same as increasing the capacity. Calculations had indicated the shunt capacity required on 80 meters would be slightly larger than is actually needed, thus a small coil was placed in series with the 1200 μμfd. (measured 1195 μμfd.) condenser so the effective capacity could be raised. Turns were shorted out in the

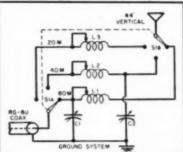

1200 μμfd. cond. (1000 μμfd. mica cond. in parallel with 250 μμfd. var. or any combination producing 1200 μμfd.—see text)

Cy-215 µµfd. cond. (low-voitage 250 µµfd. var. may be used)


L₁—80 m.—10 μhy., 18 t. #12 en. wound on 2V₂" dia. form, 3" winding length. (16 turns are used)

 L_2 —40 m.—2.1 µhy., 20 t. #12 en. airwound, 1" dia., $3\frac{1}{2}$ " winding length (19 turns are

 L_2 —20 m.—.6 µhy., 10 t. #12 em. airwound. 1" dia., 2" winding length (7 turns are used) S_1 —D.p., 3-pos. switch

Fig. 3. Antenna tuning unit. The 80 and 40 m. networks consist of a series coil and shunt condenser while the 20 m. network uses a coil. See text for details.

little series coil until the proper reactance was present. In the author's (Continued on page 88)

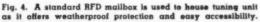


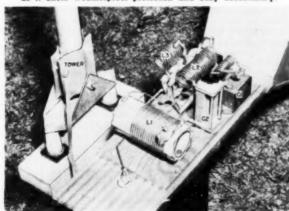


Fig. 5. Top cover of the mailbox may be raised to tune the unit or make adjustments. Normal access is through the door.

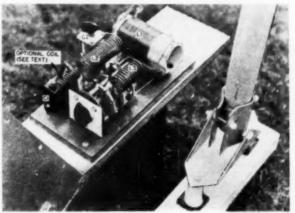



ARNEY, late as usual after his lunch hour, came charging into the service department only to be brought up short by the sight of Mac. his boss, wearing something that looked like a doctor's stethoscope. The gadget was plugged into a tape recorder; and the service shop owner, unaware he was being observed, was keeping time to the rhythm on the silently moving tape with a waving forefinger.

"Well, well! If it isn't Old Doctor Kildare himself!" Earney shouted gleefully at the nape of Mac's neck, delighted at catching his employer off guard. "What's your prognosis, Doc-

Rather sheepishly Mac removed the apparatus from his ears, shut off the recorder, and turned on his assistant with a fierce scowl. "My prognosis," he announced menacingly, "is that if a certain red-headed Irishman does not knock off his practice of sneaking up behind people and yelling at them, he is not long for this world."

"What you got?" Barney wanted to know

"It's a new idea in low impedance earphones. See this little housing on the back end of the phone plug?" Mac asked as he touched an object about the size of a small hickory nut sticking out of the "External Speaker" jack of the recorder. "Inside is a midget %" inch, six-ohm speaker. The output of this speaker goes through this flexible plastic tube to a 'Y' beneath the chin, and from there anodyzed aluminum tone arms carry the sound to both ears. The whole thing only weighs an ounce and a quarter. "What's the good of it?"

"Well, for one thing, it can be plugged directly into the external

speaker jack of any tape recorder for personal listening. That's handy when you want to listen to a tape privately or when you want to crank up the playback level for listening to a highfidelity recording without disturbing others. Also it looks like a good unit to use when people want earphones connected to a radio. This will allow us to make a quick, easy, and safe installation. By employing a miniature closed-circuit jack, the secondary of the output transformer can be hooked across the phones when the plug is inserted, and returned to the set speaker voice coil when the plug is removed. Since there is no metallic connection between the earphones proper and the plug, there will be no danger of the wearer being shocked, even when the phones are connected to an a.c.-d.c. set. "How's the quality?"

The manufacturer advertises 'response from 50 to 8000 cps or better. That does not say, of course, within what db limits this response is had. However, take a listen yourself to this recording of the 'Studies in Percussion' track by Hal Reeves that I took off Capitol's "Full Dimensional Sound" test record. Keep an ear cocked especially for the triangle, the tambourine, and the bass drum."

Barney adjusted the tips of the tone arms in his ears and listened carefully for two to three minutes. Then he cut off the recorder and announced importantly, "I may not have a golden ear, but those phones sound good to me. That tambourine seemed as though it were being shaken right in front of my face, and I could almost see the bass drum's stretched hide quiver as it gave that last 'whump.' "

"Not to change the subject," Mac remarked as he put the cover back on the recorder, "but never think I failed to notice you were late getting back from lunch again. What was it this time? Did you get held up with flying saucer traffic, or was it really something unusual?"

"Nope; the drugstore was just full of high school kids, and I couldn't get waited on. While sitting there, though, I really saw a demonstration of the power of advertising. Remember a while back when you couldn't turn on your radio or TV set without having a guy on it tell you all about lanolin and sheep's wool and his particular brand of hair dressing? Well, one of those high school hot shots came in and told the druggist he wanted something for his hair. The druggist asked what brand he wanted, and the kid just went 'Ba-a-a-a' like a sheep. Without saying another word the druggist reached up and pulled down the kind of hair dressing that bird on radio and TV was plugging. His message certainly must have got across!"

Mac chuckled at Barney's graphic description of the drug store scene as he said, "I'm glad you brought up the subject of advertising, for it's something I've been thinking about lately. If you're not in too great a hurry to get back to work, we might talk it over a little."

"I'll try to restrain myself," Barney murmured languidly as he collapsed on one end of the service bench.

'A fellow moved into our neighborhood recently," Mac explained, "and when he found I ran a service shop, he jumped on me all spraddled out. He says TV service advertising is strictly for the birds and that it makes no consistent sense. To prove his point, he pointed out several ads in a metropolitan newspaper. One shop harped on the expensive equipment and the advanced technical knowledge needed to do modern TV service work. On the next page another shop boasted that practically all service work could be performed right in the customer's home in a very short time.

"This guy then went ahead to say that twice he had had to call a service technician to repair his set. In each case the call was answered by a young kid who, as he put it, 'didn't look as though he were dry behind the ears yet.' This boy came in carrying a small tool box, about two dozen tubes, and a single meter-probably a v.t.v.m. In both cases he looked in the back of the set, noted a burned out tube, replaced it, and was on his way. Where was the 'expensive equipment?' this fellow wanted to know. As for 'advanced technical knowledge,' it required about as much of that as would be needed to find out which bulb was burned out in a floor lamp. According to the way my neighbor looks at it, that business about expensive and delicate instruments being needed to do TV work is a lot of hooey. So is the talk about technical knowledge. The fact that most TV repairs can be made right in the home

RADIO & TELEVISION NEWS



Save by ordering direct from manufacturer. (2) All high quality standard brand components. 3 increased knowledge through actual construction

Sound engineering insures
 excellent performance.

(5) Kit construction is fascinating and enjoyable.





New features unheard of in a kit oscilloscope have been added to the already popular Heathkit series. All top quality components are used including a brand new RCA 5UP1 CRT. Ten other first line tubes complete the lineup. Voltage regulation provides a rock steady pattern regardless of mornal line voltage variations. A built-in blanking amplifier eliminates the retractine entirely. Other important advantages are a phasing control, Z axis input, direct connections to the deflection plates, I volt peak-to-peak calibration voltage and a calibrated grid screen.

Wiring is simplified by the use of the harness technique which also results in a neat professional appearance. Extremely wide vertical bandwidth allows accurate reproduction of even a 500 KC square wave. Excellent focusing characteristics are made possible by the use of the new RCA 5UP1 CRT and a spot shape control. One of the most versatile of test matruments, the Heathkit 0-9 Oscilloscope will be invaluable in the radio and TV service shop, as a work project in schools and for all types of circuit investigation work in the laboratory. Its new features make Model 0-9 comparable in every way to many commercially built oscilloscopes selling for as much as \$400. Don't pass up this opportunity to add a really fine instrument to your service or experimental lab.

Heathkit VOLTAGE CALIBRATOR KIT

The use of a Voltage Calibrator will greatly increase oscilloscope usefulness. Provides a convenient method of making peak to peak voltage measurements by establishing a relationship between the unknown season and the Voltage Calibrator Voltage ranges. J1-100 volta peak to peak. The Voltage Calibrator features direct reading scales and a regulated power supply system.



MODEL VC-2 \$7750

Shipping Wt. 4 lbs.

Heathkit ELECTRONIC SWITCH KIT

The Heathkit Electronic Switch Kit The Heathkit Electronic Switch Kit will further extend scope usefulness by permitting simultaneous observation of two individually controlled traces. Continuously variable switching rates 10 cps to 2,000 cps in three ranges. Will also serve as a square wave generator over the range of switching frequencies.

We then the transport of the same of the sam



MODEL

Heathkit VACUUM TUBE VOLTMETER KIT

The beautiful new 1953 Heathkit Model V-6 VTVM, the world's most popular kit instrument, now offers many outstanding new features in addition to retaining all of the refinements developed and proven through the production of over 70,000 VTVM kits. The Heathkit VTVM now features extended voltage ranges with 50% greater coverage on the DC range. New 1½ volt low scale provides well over 2½ inches of scale length per volt permitting faster measurements with greater accuracy. AC and DC ranges are 0-1.5-5-15-50-150-500-1500 volts (1,000 volts maximum on AC). Ohmmeter ranges are X1, X10, X100, X1,000, X10K, X100K X1 meg. Measures .1 ohm to 1,000 megohms. Other features are db scale, center cacle zero adjust and polarity reversal switch. High 11 megohm input resistance virtually eliminates circuit loading.

The low anti-inflation price of this tremendously popular kit includes all tubes, necessary constructional material, test leads and the construction manual.



Heathkit AC VACUUM TUBE VOLTMETER KIT

MODEL AV-2 \$2950

Shipping Wt. 5 lbs. A new amplifier type AC VTVM that makes possible those sentitive measurements so essential in laboratory or audio work. Ten voltage ranges covering from 91 KMS full scale to 300 voits RMS full scale. Input impedance I megohm with frequency response 20-50,000 cycles. Ten DB ranges from -52 to +52 DB. Four diodes in meter bridge circuit for maximum linearity.



Heathkit HANDITESTER KIT

MODEL M-1 \$1450 Shipping Wt. 3 lbs.

The ever popular Handitester is now supplied with a Simpson 400 microsuppere meter movement. Provides AC and DC voltage ranges 0–10–30–300–1,000–5,000 volts. Ohmmeter ranges 0–3,000 and 0–300,000 ohms. DC current measurements 0–10 and 0–100 milliamperes. A completely self contained portable instrument.

HEATH COMPANY • Benton Harbor 15, Mich.

HEATHKITS for the ENGINEER

Heathkit VISUAL AURAL SIGNAL TRACER KIT



MODEL T-3 \$2350 Shipping

Designed especially for service applications in AM-SW-FM-TV repair work. HF and audio two channel input, More than adequate sensitivity—new noise locator circuit—calibrated wattmeter—substitution speaker—visual signal indication. Can be used with scope and VTVM, checks phono cartridges, phono mechanisms, microphones, tuners, etc. Let the Heathkit Visual Aural Signal Tracer help you.

Heathkit CONDENSER CHECKER KIT

An instrument designed solely for its particular job. Not a "aideline" or a multiple function instrument. Measures value and quality of unknown condensers and resistors. Capacity range .00001 mfd to 1,000 mfd. Resistance range 100 ohms to 5 megohms. Sensitive electron beam indicator—five polarizing test voltages—safety apring return leakage test awitch. An amazingly accurate in— An amazingly accurate in-strument at this low price.

Wt. 10 lbs.



MODEL C-3 \$1950 Shipping

Heathkit

RESISTANCE SUBSTITUTION BOX KIT

MODEL RS-1

Choice of 36 switch selected resistance values 15 ohms to 10 n TMA 1 watt 10% resistors. Buy several for those lab and service applications. megohms. All s ard RTMA 1

Ship. Wt. \$550

NEW Heathkit 20,000 OHMS PER VOLT

MULTIMETER

Here is the solution to all service problems requiring a portable meas-uring device of high accuracy, 20,000 ohms/volt sensitivity on DC and 5000 ohms/volt on AC. Full scale voltage ranges of 1.5, 5, 50, 150, 500, 1500 and 5000. DC current ranges of 150 microamperes; 15, 150 and 500 milliamperes; and 15 amperes. Resistances are measured from .2 ohms to 20 megohms in 3 ranges and decibels from -10 to +65 db.

Model MM-1 uses standard

commercially available batteries and is not affected by strong RF fields as encountered in and near transmitting equipment. 1% pre-cision resistors on a very easily wired ring type range switch and a highly accurate Simpson 50 microampere

meter fully qualifies the Heathkit Multi-meter for close tolerance laboratory and service work. The meter movement is placed in a recessed position for maximum non-glare readability. The kit includes the attractive black bake-

lite cabinet, 2 color meter scales, test leads, batteries and all other



MODEL MM-1 Ship. Wt. 6 lbs.

necessary components. Overall cabinet size is 5½ wide x 4" deep x 7½" high.

Heathkit SIGNAL GENERATOR KIT MODEL SG-8



\$1950

Ship. Wt. 8 lbs.

The standard service instru-ment for align-

ment for align-ment work, .1 volts output from 160 KC to 110 MC. Calibrated harmonics up to 220 MC. Internal (400 CPS) and external modulation. Pre-calibrat-ed coils for all 5 bands, Good sta-bility and accuracy. All test leads included.

Heathkit GRID DIP METER KIT

One hand operation. 5 pre-wound coils cover 2-250 MC. Controlled

250 MC. Controlled sensitivity. Usable as an oscil-lator or an absorption wavemeter. Extra low frequency coils avail-able.

MODEL GD-18 \$1950 Ship. Wt. 4 lbs.

Heathkit

TUBE CHECKER KIT



Checks overall tube quality, filament continuity, and in-dividual elements for shorts and opens. Features chart illumination, harness type wiring, and large 3-color meter scale.

Portable Model TC-2P at \$34.50, Wt. 14 lbs. No. 91-8 Cabinet only at \$7.50, Wt. 7 lbs. No. 355 TV Wt. 7 lbs. No. 355 TV 2 Picture Tube Adapter at \$4.50, Wt. 1 lb.

\$2950 Shipping Wt. 12 lbs.

Heathkit LABORATORY GENERATOR KIT



MODEL LG-1

Ship. Wt. \$3950

A professional laboratory instrument designed for instrument designed for extreme accuracy in frequency and output level. Colpitts oscillator operates in 5 ranges from 159 KC to 30 MC. Panel meter calibrated in output voltage and percent of modulation. Output in excess of 1 volts. Features complete shielding of oscillator, buffer and attenuator sections; regulated power supply and 50 hm output cable. Comparable instruments priced many times higher than the many times higher than the cost of this new kit.

Heathkit LABORATORY REGULATED POWER SUPPLY KIT



\$3350

Ship. Wt. 20 lbs.

A regulated variable 160-450 vol! DC output power supply for the lab or service shop. Accurate voltage and current measurements with large Simpson meter. AC supply 6.3 volts at 4 amperes—standby switch eliminates warmup time. Low hum content—5 tube circuit. AC and DC output voltages isolated from panel for maximum operational flexibility. for maxin flexibility.

Heathkit AUDIO





Ship. Wr. \$2950

HEATH COMPANY • Benton Harbor 15, Mich.

ERVICEMAN · AMATEUR · STUDENT

Heathkit IMPEDANCE BRIDGE KIT



MODEL 18-2

Modern design with built-in 1 KC gen-erator for AC meas-urements. A choice urements. A choice of the Wheatstone, Maxwell, Hay or capacitance capacitance com-parison bridges for

measuring resist-ance, capacitance, induc-tance, dissipation factor and storage factor. ½% resistors and precision mica condensers provide um accuracy. Completely

Ship. Wt. 15 lbs. AC operated.

Heathkit DECADE RESISTANCE KIT MODEL DR-1 \$1950

Individual switch select Individual switch selec-tion of twenty 1 % pre-cision resistors in 1 ohm steps from 1 to 99,999 ohms. Sturdy ceramic wafer switches featur-ing silver plated con-tacts and smooth, posi-tive detent action.



is the first successful low priced Q meter ever offered in kit form. Oscillator supplies RF in the range of 150 KC to 18 mc. Reads Q directly on calibrated meter scales. Measures Q of condensers, RF resistance and distributed capacity of coils. Calibrate capacities with range of 40 mmf to 450 mmf with \$4450 Ship. Wr.

Heathkit

COMMUNICATIONS RECEIVER KIT Full coverage from 550 KC to 35 MC on 4 bands



A typical Heathkit in-vasion of the laboratory instrument field. Here

is the first successful

ating frequen

(Less Cabinet)

Heathkit

KC to 35 MC on 4 bands, with good sensitivity and selectivity. Features ele-trical bandspread, BFO, headphone jack, slide rule dial with ham band identification, RF gain rule dial with ham band identification, RF gain control, noise limiter and ph one - st and by - C W switch. Top quality, high gain components used throughout. Pre-wound coils in a shielded turret assembly and a transfer

sneeded turret assembly and a transformer operated power supply assure trouble-free performance. Cabinet available sepa-rately. No. 91-10. Shipping wt. 5 lbs. Price \$4.50.

Heathkit

AUDIO OSCILLATOR KIT

MODEL AO-1 \$2450

Ship. Wr. 11 lbs.

or square or square
wave coverage from
20-20,000 cycles in 3
ranges. Variable 10 voit output level
at 600 ohms impedance. Thermistor
controlled linearity—precision multi-plier resistors—distortion less than
.6%. An outstanding instrument value
at this amazing low price. at this amazing low price.

Heathkit AMATEUR

TRANSMITTER KIT

Power input up to 35 watts on 80, 40, 20, 15, 11 and 10 meters. Can be crystal or VFO excited. Complete with modulator in-put socket and VFO power output socket and VPO power out-put provisions. Other desirable features are good shielding, AC line filter, key click filter, stand-by switch and a 52 ohm coaxial output. Model AT-1 is AC op-erated and is suitable as an exciter for a higher powered rig. Complete with full instructions for construc-tion and use



MODEL AT-1

\$2950 Ship. Wt. 16 lbs.

Heathkit DECADE CONDENSER KIT

vitch selected 1% switch selected 1% silver mica precision condensers providing capacity range of 100 mmf. to 0.111 mfd, in steps of 100 mmf.

MODEL DC-1 \$1650

Shipping Wt. 4 lbs.

Heathkit AUDIO GENERATOR KIT

range 18 cycle range 18 cycles

—1 megacycle
audio instrument at a remarkably low
price. Five continuously variable output ran-ges - 600 ohm output impedance— low distortion figure, less than .4% from 100 cps through audible



MODEL AG-8 \$2950

Ship. Wt. 11 lbs

Heathkit

BATTERY

ELIMINATOR KIT

Heathkit BAR GENERATOR KIT

Small, compact and easy to use, Model BG-1 supplies hori-zontal or vertical bars for TV linearity adjustments. Output cable clips directly to the TV receiver antenna terminals.

MODEL BG-1

WRITE FOR Free CATALOG

New 40 page 1954 Cat-alog lists all kits, speci-fications, achematics and latest price infor-mation.

Heathkit TELEVISION SWEEP



MODEL TS-3

Ship. Wt. 18 lbs.

Simplify your TV alignment jobs with the new Heathkit TS-3. Full coverage on fundamentals from 4 MC to 220 MC at an output of well over 100,000

microvolts . . Automatic blanking and wide range A triple marker system ranges from 19 MC to 180 MC using a Colpitts oscillator plus the 4.5 MC crystal controlled oscillator for check points (crystal furnished). Provisions are also made for using an external marker.

Featured is the new sweep system, using an *INCREDUCTOR controllable inductor. Sweep width is variable from 0 to 12 MC at the lower RF frequencies and increases to 0-50 MC at the highest , advantages are power supply regulation, constant RF output level, independent marker and RF output control circuits, low impedance output and properly terminated output cables. The construction mplete in all detail and with a reasonable amount of are, Model TS-3 will serve faithfully for many years to com-

*Trademark, C.G.S. Laboratories, Stamford, Connecticut

MODEL BE-4

6 or 12 volt operation with current and
voltage constantly
monitored. Double protection with a fused
transformer and autotered output and all heavy duty
components, Designed for auto
radio presigned of auto radio repair and as a storage battery charger.

HEATH COMPANY . Benton Harbor 15, Mich.

Heathket FM Heathkit NEW HEATHKIT WILLIAMSON TYPE TUNER KIT ECONOMY 6 WATT AMPLIFIER KIT AMPLIFIER KIT MODEL FM-2 The ideal amplifier for custom high fidelity audio installations. Tops in performance, value and flexibility of operation. Either Altec Lansing Peerfess or Acrosound output transformers available. Frequency response ±1 db 10 CPS to 100 KC, negligible hum and noise levels and plenty of reserve power for complete listening pleasure. First Williamson Type Amplifier supplied with matching preamplifier. \$2250 Shipping Wt. 9 lbs Dual inputs— separate bass and trobe tone controbe—output impedances of 4, 8, and 15 ohms. Performance far beyond that normally expected for the price. A-7C: Includes preamplifier for low level input devices. Price \$17.50 Sensitive transformer operated 8 tube circuit. Frequency cov-erage 88-108 mc. Pre-assem-bled and tuned "front end." Vernier tuning with slide rule type dial. PRICES OF VARIOUS COMBINATIONS: W-2 Amplifier Rit (Includes Main Amplifier with Peerless Gutput Transformer, Power Sup-ply and WA-P2 Preamplifier.) Shipping weight 38 lbs. Shipped express only NEW Heathbit Heathkit BROADCAST BAND HIGH FIDELITY 20 WATT RECEIVER KIT W-3 Amplifier Kit (Includes Main Amplifier with Acrosound Output Transformer, Power Supply and WA-P2 Preamplifier.) \$6050 Shipping weight 38 lbs, Shipped Sepress only AMPLIFIER KIT MODEL A-98 MODEL BR-2 \$1750 \$3550 W-3M Amplifier With Acrosound Cutput Transformer and Power Supply. 1 Shipping weight 30 Hs. Shipped express only. (Less Cabinet) Ship. Wt. Wr. 23 lbs. Complete receiver with chassis mounted 5.5° PM Speaker and new rod type antenna. Covers the full broadcast band (850 KC-1600 KC) with excellent sensitivity and selectivity. Operates as a receiver, tuner or a phono amplifeer. High gain ministure tubes and IF transformers. Easy tuning with direct planetary drive. Cabinet available separately, Part No. 91-9. Ship, wt. 5 sam the price 5 sam the pri new Heathkit Outstanding features of the Heathkit 20 Watt Amplifier include a frequency response of ±1 db from 20 CPS to 20 KC, less than 1% harmonic distortion at rated output, separate (boost and cut) bass and treble tone control%, 4 selected in put jacks, hum balancing control and output impedances of 4, 8, 16 and 500 ohms. Flexibility is emphasized in the input circuits with builtin preamplifier and proper equalization. HEATHKIT HIGH FIDELITY LOW PRICED Single UNIT PREAMPLIFIER KIT MODEL WA-P2 AMPLIFIER KIT \$1975 20000 MODEL W-4M Ship. Wt. 7 lbs. \$**39**75 Complete compensation for LP, NARTB, AES and early 78 recording characteristics. An ideal control unit for the custom Hi-Fi system. 5 individually controlled inputs, 4 turnover and roll-off switch positions, 3 twin triode tubes, cathode follower output, monitored recorder output, shock mounted tube chassis and proper shielding. All condensers are of the molded plastic type. Critical input circuits feature low noise deposited carbon resistors. Use it with any conventional high fidelity amplifier. Ship. Wt. 28 lbs. The famous Heathkit Williamson Type Amplifier is now available in a single chassis. Includes power supply and power amplifier. En joy the same high quality reproduction at less cost by eliminating the second chassis, connecting cables, etc. Size 15 ¼ "wide—7" high—9" deep. Model W-4 includes W-4M and preamplifier WA-P2. Shipping weight 35 lbs. Price \$59.50. HEATH COMPANY Benton Harbor 15, Mich. MAIL YOUR ORDER BLANK RDER TODAY TO THE HEATH COMPANY

SHIP VIA BENTON HARBOR 15, Parcel Post ☐ Express MICHIGAN ☐ Freight ☐ Best Way (PLEASE PRINT) MODEL NO. PRICE ITEM QUANTITY Enclosed find () check () money order for Please ship C.O.D. () postage enclosed for

ON PARCEL POST ORDERS insure postage for weight shown

pounds.

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery. ORDERS FROM CANADA and APO's must include full remittance.

MODEL A-78 \$1550

Ship. Wt. 10 lbs.

Dual inputs-

SERVICE HINTS ON CROSLEY TV SETS

MODELS 10-401, 10-404, 10-412, 10-414, 10-416, & 10-418

Unstable horizontal sync.

If the horizontal oscillator drifts, causing the receiver to fall out of horizontal sync after operating several hours, check C100, the .01-µfd. condenser connected to pin 6 of T_{im} , the horizontal oscillator transformer. This condenser, if it is of the molded type, may change capacity with temperature change sufficiently to cause the receiver to fall out of horizontal sync.

Replace the condenser with a .01µfd., 600-volt paper type, and realign the trimmer at the bottom of $T_{\rm res}$.

Carrier buzz.

To reduce carrier hum which may accompany high contrast on some sets, change condenser C_{122} (connected to pin 1 of V_{100} , 6AU6 sound driver), 100- $\mu\mu$ fd., 500 volts, to 47-μμfd., 500 volts.

Also change resistor R124 (in parallel with C_{122}) from 220,000 ohms to 47,000 ohms, 1/2 watt, and R138 (connected to pin 6 of V100) from 56,000 ohms to 27,-00 ohms, 10%, 1 watt.

Arcing between the 6BG6 and


damper-tube plate lead.

When experiencing breakdown due to arcing between the 6BG6 and damper-tube plate leads, install 31/2 inches of Fiberglas sleeving over the 6BG6 plate lead. This sleeving should be placed toward the terminal on the horizontal deflection transformer.

MODELS 10-401, 10-404, 10-412, & 10-418

Horizontal sweep sing.

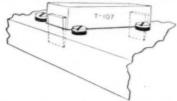This condition can be caused by vibration of the mounting bracket on the horizontal output transformer, T_{107} . This mounting bracket occasionally vibrates at a subharmonic of the 15,-750-cps horizontal sweep frequency. This can be corrected by inserting small wedges between each end of transformer and chassis. shown in the accompanying diagram.



It is not necessary to remove the chassis from the cabinet to make this


MODELS 10-404MU, 10-404M1U, 10-412, &

Insufficient vertical size.

To obtain sufficient vertical sweep, make the following changes:

1. Change resistor $R_{\rm m}$ from 5600 ohms to 4700 ohms, 10%, 1 watt.

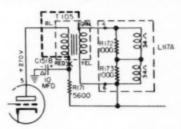2. Change the vertical output transformer, T.co., to an autotransformer by connecting the secondary winding in series with the primary, as shown by the dotted line in the accompanying diagram. (The diagram shows the cir-



cuit before changes.) To make this change, do the following:

a. Remove the red lead of the primary winding of T_{100} at the terminal board where it is soldered beneath the chassis. There is another lead to this lug which is red with a white tracer. Resolder the red lead to the adjacent lug to which two green leads are connected.

b. Remove the yellow lead of the Tion secondary winding and the yellow lead of the deflection yoke from the lug of the terminal board nearby where they are both soldered. Resolder these two leads to the lug where the red lead of T_{105} was formerly connected.

"SUPER V" MODELS (CHASSIS 426)

Poor vertical interlace, unstable picture, and intermittent streaks.

This combination is caused by an intermittent contact between the Aquadag coating on the picture tube and the grounding strap.

To correct this, take off the grounding strap and reform it so that it makes a firm contact at the Aquadag coating

when it is in place.

In cases where the Aquadag coating has become scraped off by the movement of the tube during shipment, reposition the strap so that the contact falls on a good area.

MODELS 11-442M1U, 11-444MU, 11-453MU, 11-460MU, 11-470BU, 11-472B1U, 11-474BU, & 11-483BU

Hum or buzz.

To reduce this condition, do the fol-

1. Make certain that the electrolytic condenser, C_{120} (one section of which goes from pin 6 of the 6AH6 video amplifier to ground), has a good ground connection by soldering the wire from the chassis to one of the ground lugs on the condenser.

2. Replace the shield in back of the contrast control if it has been removed.

New replacement control

helps you provide hi-fi reproduction at low-volume levels



There's nothing else like it for improving tone performance

Now, Centralab's new Senior Compentrol with level-set lets your customer control bass and treble range to suit himself — something he cannot do with an ordinary com-pensated volume control. A uni-versal unit, Senior Compentrol replaces any value without addi-tional amplification. You install it easily and quickly — make money

on the job.

Be set to cash in on today's increasing awareness of tonal qualities by your customers. Get several Senior Compentrols from your Centralab distributor - net price,

Centralab also has a Junior Compentrol. It is furnished in 1/2 and 1 meg., plain and switch types, for use in radio sets (5 or more tubes, AC or DC), audio amplifiers, or phono combinations.

Send coupon for 20-page booklet 42-182 telling the whole Compentrel story — or Centralab Catalog 28.

CENTRALAS. A Division of Globe-Union Inc. 910F E. Keefe Avenue, Milweukee 1, Wisconsin Send Catalog 28. Send Compentrol bulletin 42-182. Name Company Address



3 Self Supporting Rohn Towers To Fit Your Every Need

The No. 5 — The self-supporting tower for use up to 40', or guyed to 80'. An economical, yet sturdy, permanent tower!

The No. 10— The standard 12' design that is self-supporting to 50' and can be installed to 120' when gaved!

The No. 20— The heavy duty Rohn Tower, ideal for communication and where great height is required— self-supporting to 60', or guyed to 150'!

All Rohn Towers are in 10' sections - easily erected, transported and stored!

A COMPLETE LINE OF TOWER ACCESSORIES AND HARDWARE

A full line of Superior Design Tower accessories is available including guying brackets, house brackets, wall mounts for towers and masts, special tower bases such as peak and flar roof mounts, etc.

Contact your Rohn authorized representative or your distributor for FREE CATALOG or write . . .

MANUFACTURING CO. **DEPT. RTN 116 LIMESTONE BELLEVUE** PEORIA, ILL.



Sales acceptance has been phenomenal — thousands have been sold coast-to-coast — and the design has been one which has withstood every test known! Why "experiment" with an unproved tower design when you can sell Rohn!

So we ask you, "Why take chances with an untried tower? Be sure — sell Rohn — the only tower of its kind to withstand every test!

IN SALES

Rohn Fold-Over Tower only one c? its kind

usive with

110V, AC POWER SUPPLY FOR ANY 274-N RECEIVER

Just plug it into the rear of your 274-N RECEIVER . . any model. Complete kit and black metage case, with ALL parts and diagrams. Simple and easy to build in a jifty. Builters 24 voits plus B voitage. No wiring changes to be made. Designed especially for the 274-N receiver. Only \$8.95.

Filament trans. for 274N receivers. Pri. 116V, 60 cy. AC. Sec. 24V of .6A. An excellent buy at \$1.95 cs.

SPLINED TUNING KNOB FOR 274N RECEIVERS

An exclusive O-R item manufactured for us. Fits BC-453, BC-454 and other 274N receivers. This is a really hard-to-obtain item. Only. 89c ea.



OFFENBACH-REIMUS 1564 Market Street, San Francisco, Calif.

FACTORY REPAIRS ON ALL MAKES AND TYPES OF

TEST EQUIPMENT

Write Dept. 5 for BIG NEW FREE Catalogue GENERAL ELECTRONIC DIST. CO.

98 PARK PLACE, NEW YORK 7, N. Y. ...

World's Only Recorder of its Kind WALKIE-RECORDALL 8-LB SELF POWERED BATTERY RECORDER

AUTOMATIC UNDITICIES

RECORDING up to 4 hrs.
briefzese, cantaning hidden mike while
60 FF Abolus
Gletation, 2-way phone, Permanent, unaltervoict arrusus
American
MILES REPRODUCE CO., INC.

MILES REPRODUCE CO., INC.

NO MALE OR PLOSE

3. On sets equipped with a resistorcondenser unit, dress coupling condenser Cim (at pin 2 of Tion, sound i.f. transformer), as far as possible away from the resistor-condenser unit.

4. If necessary, remove resistor R_{141} , 22 ohms, at pin B of the ratio detector transformer.

5. Adjust the ratio detector transformer (T_{102}) secondary for minimum hum or buzz while the set is tuned to a station. Only a slight adjustment is required. If the screw is turned too far, the result may be weak or distorted audio.

6. Check over-all alignment.

Elimination of corona or arcing at the picture anode button.

If corona or arcing is experienced at the anode button, it is probably due to the accumulation of dirt or to the effect of a corroded rubber suction cover.

To eliminate this trouble, do the following:

1. Disconnect the anode lead from

2. Clean the area around the anode button with carbon tetrachloride or a scouring powder such as Bon Ami.

3. Add a protective coating such as Crosley appliance polish.

4. If the original anode connector is without a suction cover, thus permitting free accumulation of dirt, a new anode connector and lead assembly with a neoprene suction cover should be used to replace the original assem--30bly.

SHAFT COUPLINGS


By ARTHUR TRAUFFER

NEEDING some insulated couplings for 14" extension shafts, I dug into my radio scrap box and fished out some small knobs with set-screws in them. I filed the fronts of the knobs flat and cemented the knobs together (front-to-

front) using Duco cement. The photograph below shows the resulting neat and serviceable insulated coupling installed on the condenser shaft. When cementing the knobs toshaft. When cementing the knobs to-gether, be sure that the holes in the knobs line up perfectly so that there will be no eccentric motion of the extension shaft in relation to the condenser shaft.

If you prefer, you can bore through the knobs with a ¼" drill and then cement the knobs together bottom-tobottom. This may give you a better alignment of the knobs.

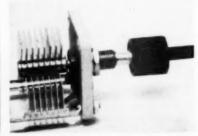Shaft coupling improvised from small knobs.



CRYSTALS =

Guaranteed to oscillate! Your choice of frequencies! Largest selection in the world!

NOTE: EVERY CRYSTAL TESTED FOR ACTIVITY REFORE SHIPMENT! All numbers listed are FUNDAMENTAL FREQUENCIES with fractions omitted.	NOVICE BAND Individually. Ea. AVAILABLE IN ETTHER IN: 344 All frequencies from 3556 KC V
FT-243 HOLDER Lots of 10 or more. Each	Examples: 3588, 3589, 3590, 3590, 310 All frequencies from 3701 KC Ti Examples: 3701, 3702, 3703 AVAILABLE IN FT-243 HOL All frequencies from 7176 KC Ti Examples: 7176, 7177, 7178
1015 2155 2480 2630 2775 2940 3090 3235 6075 6406 7150 7600 7870 8070 1110 2140 2485 2635 2780 2945 3095 3240 6100 6425 7113 7610 7800 8073 1110 2140 2485 2490 2460 7785 2950 3100 3290 6106 6449 7175 7620 7890 8073 1150 2155 2495 2645 2790 2955 3100 3290 6106 6449 7175 7620 7890 8073 1150 2155 2495 2645 2790 2955 3100 3300 6125 6450 7280 7839 7839 8075 1159 2155 2495 2645 2790 2955 3100 3300 6125 6450 7280 7839 7839 8075 1159 2157 275 2510 7655 2795 2800 3110 3310 6120 6445 7280 7839 7839 7831 8083 1152 2157 2157 2510 7655 2795 2800 7950 3110 3310 6120 6475 7275 7850 7910 8100 7900 8110 7950 7839 7839 7839 7839 7839 7839 7839 7839	MISCELLANEOUS 81.05 KC, 0x241 tube type (Used 1978) 1200 sc (9.584 & 8794) 1
FT-243 HOLDER Lots of 10 or more, Each,	1720 1930 2106 2115 2491 1738 1930 2106 2135 2491 1738 1930 2131 2226 2500 1746 1970 2155 2135 2510 1770 1990 2175 21340 2415 1790 2010 2199 2155 2527 1810 2030 2202 2156 2540 1830 2050 2215 2275 2559 1850 2015 2126 2230 2546 1870 2082 2235 2395 2587 CR-1A HOLDI 5020 5300 5590 6510 7010 5041 6 5520 5677, 6550 7020
FT-241-A HOLDER Lots of 10 or more. Each	5180 5550 5700 6550 7040 5208.3 5583.3 5722.2 6650 7080 DC-11A HOLDER 2589 2960 3
FT-241-A HOLDER Lots of 10 or more. Each	2740 2993 2 2750 3021 3 2781 3025 3 2781 3025 3 29030 2174 2350 2990 3250 4 2134 2326 2410 2800 3315 4
FT-171 Lots of 10 or more, Each	AR7-W 1500 to 1500 kg. 201 to 1500 kg. 200 kg.

Individually. Ea
MISCELLANEOUS & SHIP BAND FREQUENCIES
DC-34 & DC-35 CRYSTALS Your Choice. Ea. only 99c 2740 2415 2605 2851 3095 3395 3665 3870 4020 4175 4370 2755 2472 7625 7853 3117 3412 5 3680 3385 4030 4177 5 4380 2758 2435 7843 7849 3149 3432 5 3685 3890 4035 4192 5 4397 5 276 276 276 276 276 276 276 276 276 276
CR-1A HOLDERS Lots of 10 or more
DC-11A Lots of 10 or more. Each
F7-164 FC CR.4 ## F7-164 FC
BCA MODEL TYPE MC-7 AAD-A AR-4W of

U. S. CRYSTALS, INC.,

LOS ANGELES 17, CALIF.



The top quality of EMC precision instruments has been proven by years of coast-to-coast tests performed both in the field and on the



Exceptionally low prices on these quality instruments are made possible by combining every new engineering advance with EMC large volume production.

Convince yourself . . . check the features and prices of the two outanding examples noted below . . .

NEW MODEL 600 OSCILLOSCOPE

Compare these high quality features with scopes selling up to twice the price of the new model 600.

- the new model 600.

 Uses new 5 UP1 5" scope tube for sharp focusing and good intensity.

 Retrace blanking amplifier to eliminate confusion and give clearer pictures.

 Has built-in 60 cycle phasing control and sweep for TV servicing.
- Uses astigmatism control for better
- . Provision for 2 axis input or intensity
- Provision for Z axis input or intensity modulation.
 Synchronization available on position or negative phase of input voltage or from external source.
 Uses a 2 step compensated attenuator.
- Has a 2 stage push-pull vertical amplifier with sensitivity of .02 volts per inch. Multivibrator swap from 15 cycles to over 75 kilocycles.
- . Direct connections to scope plates

New Model 600 (completely wired and tested).

\$99.50

MODEL 106 VACUUM TUBE -VOLTMETER

mpare these high neters selling up wice the price

10

- ual triodes balanced bridge circuit ero center adjustment for TV and Fm
- ignment ses 1% precision resistors for voltage ultipliers
- scale deflection of 11/2 volts for both
- Full scale deflection of 149 volts for both AC-DC volts.

 1.meg isolating resistor in probe Measures resistance in 5 ranges from 2 ohm to 1000 megs.

 Space saving portable Bakefite case.

 419 " x 519 " x 22".

 *** Lowest on market r wired and kit form.
- Model 106, illustrated
- \$35.90 (Complete with all leads)
- Model 106, in kit form. 23.90 RF and high voltage accessory probes

ELECTRONIC MEASUREMENTS CORPORATION

280 Lalayette Street, New York 12, New York

Write department RN-6 for complete catalog.

MORE OLD TIME OPERATORS REPORT

By C. HOWARD BOWERS

T IS very interesting to note that the majority of the old time wireless operators we have contacted have prospered in their chosen field, and many have wound up as big wheels in their respec-tive communities. Take Sydney J. Fass, for instance; he now makes his home in Berkeley, Cal., but is identified as one of the larger radio and television dealers in San Francisco. Syd became interested in the fundamentals of wireless back in 1909 and, with some other lads, including Dick Johnstone, Bob Hatch, et al, they put in their spare time learning the code, as Syd himself describes it, "By whistling through their buck teeth!". Anyway, in building his first wireless rig he was aided and abetted by Haradan Pratt, who is now the Aide for Communications to President Eisenhower. From there, his efforts must have been effective because by 1911 Sydney, who was then sixteen, secured his Certificate of Skill from the U. S. Department of Commerce and Labor and soon after was a full fledged sea-going operator. He says he still has his original "ticket" which is endorsed by the skipper of the good ship "Falcon" which he claims was the first steel steam schooner ever built, also by skippers of the tankers "Oleum" and "Washtenaw"—two of the "foulest smelling crude oil carriers on the Coast!" After that came the old Pacific Mail Liners "San Juan" "San Jose" and "Acapulco" from San Francisco to Central America. An urge for more schooling brought

our ambitious subject ashore and in 1914 he graduated from the California School of Mechanical Arts after spending the summer of that year as operator aboard the Matson liner "Lurline Pacific ports to Honolulu, T.H. The seagoing urge still prevailed and young Fass continued on to the good ship "Geo. W. between West Coast ports and Elder" Central America.

In 1917, Uncle Sam called Syd for Navy duty and he saw plenty of action in

the European Theater.
World War II was no exception and
Syd was again in Navy uniform. However, he has now retired as a Commander after 33 years of Naval Reserve service

and a liberal collection of "fruit salad" "scrambled eggs".

During recent years he has followed the natural pattern—amateur radio— and now has one of the finest ham rigs we have seen in years. With a full kw. transmitter, and a Collins receiver, it's no wonder his name frequently appears in ham magazines as holder of DXCC and WAC awards—no wonder! His call is W6NZ and he has enough QSL cards to shingle a roof—a warehouse roof. That's not all. He has a nice wife and a home in the college town of Berkeley, California, across the bay from San Francisco. A success story, if we ever heard one! Continued good luck, Mr. Fass.

JE HAD to go clear across the continent Wto catch up with another West Coast Old Timer. It's the story of John M. Boyle, RFD #1, Alma, Georgia, as told to his friend, Jack Williams, of the same

John M. first succumbed to the wireless bug in 1911 in the days when iron men and wooden ships frequented San Francisco Harbor and when Pacific Street 'twasn't a boulevard. He reports having secured his Certificate of Skill from R. B. Woolverton, Wireless Inspector at San Francisco in 1912. His first seagoing job was wireless operator aboard the Schooner "Yosemite" sailing between Puget Sound and San Diego with stops at Portland, San Francisco, and San Pedro. Those were the good old days when L. Malarin was chief operator for Marconi and every trip into San Fran-cisco meant a trip to the Merchant's Ex-change Building to check with "L.M."

One small vessel followed another until 1914 when he signed on the "S.S. Uncas" operated by the Tank Storage and Carriage Company of London and sailing deep water between San Francisco and the Orient. It was easy those days to pick your own run and in 1914-1915 John pounded brass for Standard Oil Company on various tankers between San Francisco, Chile, Peru, and Van-couver. In 1916 he switched to the Ward Line and was so occupied until the Army tapped him on the shoulder in 1917 for a very important job as Corporal in the



Syd Fass (left) is a young-looking "Old Timer" but as photo below testifies he was an active "op" in the "Good Old Days".

Signal Corps. He followed this duty in 1919 with a tour for Marconi on transpacific ships to China and India. (We thought for a second he was going to slow down.) In 1920, John joined the U.S. Army Transport Service and was assigned to "USAT Mt. Vernon" on a voyage to Germany. However, just after passing through the Panama Canal the vessel lost a prop and the trip termintaed at Portsmouth Navy Yard, where he was assigned other duty. After his one hitch in the Army, John evened the score by joining the U. S. Coast Guard in 1914 as a Chief Radioman and served along the east coast until paid off in 1931.

Up to now, our fast moving companion had traveled on everything that boasted a wireless set—well, not quite everything, for in 1932 he accepted employment with the U. S. Airways as operator at various points including Cleveland, Pittsburgh, Eric and—yes he's coming to a stop—Alma, Georgia. There must have been other attractions at Alma besides being Chief Airways Operations Specialist for the now-called U.S. Civil Aeronautics Administration, but our wireless career-man concludes with, "Present communication is a far cry from the old days of 1912." To which we say, "Amen!" Our congratulations, Mr. Boyle on a job well done!

TVI Troubleshooting


(Continued from page 39)

quency of the beat. In the event that the lines are horizontal, as in Fig. 5, multiply the number of dark horizontal lines by 60 (since the vertical scanning frequency is 60 cps) for the beat frequency.

Unfortunately, all beat frequencies cannot be determined quite this simply because if the beat is high, one megacycle or more, the number of interfering lines becomes difficult to count. In those cases, use a scale and count the number of lines that occur in one inch. Multiply this number by the number of inches in the picture width, and then multiply this figure by 15,750 cps to obtain the frequency of the beat. In the case of modulated interference signals, make the measurement during the periods of no modulation. With a little experience, it is possible to come very close to the correct frequency even in the presence of the modulation.

A technician may find that in a particular case of interference, the beat frequency changes as he turns the receiver fine tuning control. This means that the interference is "tunable." What does this mean in terms of receiver functioning?

When the fine tuning control is adjusted, the frequency of the oscillator is changed and the i.f. frequencies that correspond to the r.f. video and sound carriers are changed. At the same time, during this fine tuning adjustment, there is absolutely no change in the frequencies of the r.f. video and sound carriers, and in the difference frequency between the two carriers (4.5 mc.). Also, the frequency of any outside interfering signal is not changed by any means within the receiver.

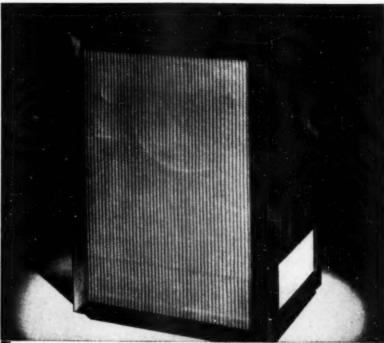

Two Great New Products!

*FISHER

Speaker Enclosure

■ THE FISHER Series 50-H Horn Speaker Enclosures can be used with 12" or 15" single, coaxial, dual or triaxial speaker systems! Your investment cannot be obsoleted, no matter how often you change speakers. These units feature instantly apparent, over-all balance, (rather than an overpowering, and therefore unnatural bass response). • Smooth response to below 30 cycles. • Does not require corner placement. • Air-loading of bass is over four times that of infinite baffle. • No listener fatigue, regardless of volume level. • Markedly improves any speaker system.

Model 50-HM (Mahogany) \$129.50 • Model 50-HB (Blonde) \$134.50

THE FISHER Factory Sealed Cartridge



• Here is America's first factory-sealed, moving coil phonograph cartridge. You are the first to handle the cartridge you buy. These units are specially made for us by Fairchild, acknowledged leader in the field. High compliance improves low frequency response, reduces record hiss. Diamond stylus exclusively.

Model 50-LP (33-45 rpm) \$37.50 Model 50-ST (78 rpm) \$37.50 Model MT-1 (transformer) \$8.75 Write For Full Details

FISHER RADIO CORPORATION
39 EAST 47th STREET * N. Y.



ENJOY 3 COLOR TELEVISION FILTER SCREEN NOW

Changes dult eye-straining black and white pictures into Seauritu cloir tones. Seconds to attach. No tools used. Melps eliminate glare. Order direct. Bend S1 for screen aise up to 18", \$1.30 size 28", \$2.30 size 28", \$3.50 size 28", \$3.50

Zingo Products, Johnstown 19, New York

Be a "key" man. Learn how to send and receive messages in code by telegraph men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Gustrelle, Candler System. Co. Dept. 2-d. Son 198. Denver 1. Colo. U.S.A.

These clues can help us to further identify the interference frequency and type. If the beat is due to an interfering signal heterodyning with the r.f. video carrier frequency, the beat will be untunable, i.e., the fine tuning control will have no effect upon the interference pattern on the CRT. For example, if an interfering signal occurred at 63.25 mc., which is 2 mc. away from the video carrier of channel 3, the oscillator and mixer when properly tuned, will produce a 45.75 mc. i.f. for the carrier and a 43.75 mc. i.f. signal for the interference (assuming a 41-mc. i.f. system). Detuning the oscillator will change the 45.75 mc. i.f. signal, but it will also change the 43.75 mc. i.f. interference signal the same amount, and the difference between the two signals will always be 2 mc.

If, however, the interfering signal entered through the i.f. "gate" at a frequency say of 43.75 mc. (police interference), tuning the oscillator to produce a 45.75 mc. i.f. for the video carrier would produce a beat of 2 mc. Detuning the oscillator in this case would change the 45.75 mc. i.f. for the video carrier, but it could not change the frequency of the 43.75 mc. interfering signal. Therefore, the beat frequency would change and the interfer-

ence would be "tunable."

The various "gates" previously discussed can be classified according to whether they are sources of "tunable" or "untunable" interference. The "tunable" ones are the i.f. and image gates; the "untunable" ones are the video, desired channel, and upper and lower adjacent channel gates. Since most of the internal sources of interference produce harmonics of the video i.f., the beat produced by them will be "tunable," since detuning the set changes the i.f. frequency and likewise, the frequency of the harmonics.

(To be continued)

PHONE JACK CASE By HUGH LINEBACK Oklahoma A & M College

FOR mounting a phone jack at the end of a cable; a neat housing can be easily made from the aluminum cans used for packaging cartridges of 35 mm film. A photo dealer, or a photographic friend, will have discarded containers.

used for packaging cartridges of 35 mm film. A photo dealer, or a photographic friend, will have discarded containers.

Holes for the jack and for the cable can be punched in the thin material with a center punch, and a rubber gromme! inserted in the lid opening to protect the wire.

Details of the handy phone jack case mounted at end of cable. It is easy to make.



RADIO & TELEVISION NEWS

CORONA RADIO KITS

EASY TO BUILD . EDUCATIONAL EXCELLENT RECEPTION

All hits supplied less were and solder. Please intiude 25% deposit with C.O.D. orders. Dept. N-6.

Broadcast Superhet

NO INTEREST!!

Buy on our radically new Time Payment

NO CARRYING



ures 6%" x 9%" x 4%"

Superior's new Model 670-A

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for elec-

REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries DECIBELS: -6 to +18 +14 to +38 +34 to +58

ADDED FEATURE:

The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

The Model 670-A comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operat-ing instructions.



Superior's new Model TV-11 BE 1

socket

Tests all tubes including 4, 5, 6, 7, Octal, Lockin, Peanut, Bantam, Hearing Ald, Thyratron, Miniatures, Sub-Miniatures, Novals, Sub-minars, Proximity fuse types, etc.

Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly Identity which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-II as any of the pins may be placed in the neutral position when necessary.

when necessary.

The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible

socket.

Free-moving built-in roll chart provides com-plete data for all tubes.

Newly designed Line Voltage Control compen-sates for variation of any Line Voltage between 105 Volts and 138 Volts.

NOISE 1857: Phono-jack on front panel for plug-ging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

to damage a tube by inserting it in the wrong

The model TV-ii operates on 105-130 Voit 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet ecospiete with portable cover. lator incorporated in this model will detect leakages even when the frequency is one

SUPERIOR'S NEW MODEL TV-40

. TUBE TES

leakages even per minute.

A complete picture tube tester for little more than the price "make-shift" adapter!! a

The Model TV-40 is absolutely com-plete! Self-contained, including built-in power supply. It best picture that the power supply is the picture that the such tubes; that is by the use of a separate instrument which is designed exclusively to test the ever increasing number of picture tubes!

EASY TO USE:

Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (ion trap need not be on tube). Throw switch up for quality test . . . read direct on Good-Bad scale. Throw switch down for all leakage tests.

Tests all magnetically deflected * tubes . . . in the set . . . out of the set . . . in the carton!!

SPECIFICATIONS:

- · Test all magnetically deflected picture tubes from 7 inch to
- 30 inch types. If you have the well established emission method. All readings on "Good-Bad" scale.

 Tests for inter-element shorts and leakages up to 5 megohms.

 Test for open elements.

Model TV-40 C.R.T. Tube Tester comes absolutely complete—nothing else to buy. Housed in round cor-nered, molded bakelite nered, mole case. Orly

MOSS	ELEC	TRONIC	DISTRI	BUTING	CO.,	INC.	
Dept.	B-102.	3849 Te	ath Ave	New Y	ark 34	NY	

Please send me the units checked. I am enclosing the down riease send me the units checked. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

																												200
Name.	*	*	×	*	×	×	*	*	*	*	*	*				*	*	*	*	*		*	×			*		C

																		٠
Address.	::	 	 	*	 			 	*	*	. ,		×	*		*		(

0	MODEL 670-A \$7.40 down paym monthly for 6	ent. Balance \$3.50
D	MODEL TV-11	Total Price \$47.50

C)	MODEL TV-11	T	otal	Pris	in 34	17.1
-	\$11.50 down payment	. 1	Bala	-	\$6.0	0
	monthly for 6 mon	121	ha			

0	MODEL TV-4	
	monthly for	ment. Balance \$4.00 3 months.
65	I anciese S	as down navment.

	-	I enclose 5	as down payme
CityState		Ship C.O.	D. for the down payment.

1



RADIO-TV Service Industry News

AS REPORTED BY THE TELEVISION TECHNICIANS LECTURE BUREAU

PERHAPS the most significant feature of the recent annual IRE Convention was the clearly evident passing of the vacuum tube from its place of dominance in the electronics industry. As one milled through the vast crowds that swarmed through the immense Kingsbridge Armory every day of the four-day show it was the widespread exhibition of transistorized devices that left the most striking and lasting impressions on many observers.

The rapidly growing magnitude of electronics as an industry was clearly evident in the tremendous volume of registrations at this year's show. And while major engineering attention was given to developments in color TV, transistors, and transistor circuitry, new electronic devices for applications in the medical, biological, and industrial fields indicated the broadening scope of the industry's activities.

In attending these engineering shows, your editors try to appraise these developments on the basis of their possible future effect on the activity of independent service. As "coming events cast their shadows before," the introduction of basically new equipment usually presages changes in the operational structure at all industry levels. This will be especially true of the service field as more complex circuitry demands more skillful technicians, and trained service business management finds ways and means to provide top-flight service and maintain a high level of customer confidence.

When black-and-white television was being readied for sale to the general public there were two schools of thought about its effect on the then radio servicing industry. One group held that monochrome TV would be much too complex for the average radio service technician to comprehend and that, as a result, manufacturers would be forced to set up their own servicing departments to handle the installation and maintenance of their receivers. The other group felt that TV would be absorbed by the radio service industry in time, and that servicing would be handled by thousands and thousands of individual technicians working from their homes and small, inexpensive business establishments.

Television did make some drastic changes in the structure of the independent servicing industry. It did not, however, fall into either pattern visualized by these two schools of thought. It established its own pattern and one that will be thoroughly capable of expanding with the needs of color TV and transistorized devices as they are sold commercially.

Pattern of the Service Industry

For the past six months the Bureau has been receiving registrations for its planned National Electronics Service Directory from service businesses all over the country. More than 15,000 of these registrations have been received and the information supplied on these thousands of registrations provides the clearest picture of the actual structure of what is known as the "independent service industry" that has ever been compiled.

At the present time a complete analysis of these registrations is underway. However, an analysis of a representative sample of these registrations has already been completed. Your editors feel that this sampling provides sufficiently accurate figures to illustrate the type of business structure that has been created to handle monochrome TV servicing.

It should be pointed out that the listings in the National Electronics Service Directory are restricted to full-time service businesses so that the figures cited here represent the activities only of recognized, established service businesses.

The average annual volume of business handled by the service businesses represented in the sampling analysis is \$33,463.41. For comparison of the present servicing industry with the prewar radio service industry consider the Department of Commerce figures on the average volume of business done by radio service shops in 1939—\$6103.00 per year. This would indicate that the average shop today is doing five times the volume of business that the average radio shop handled in 1939.

The average number of technicians employed in the surveyed service businesses is 4.19. The average number of technicians employed in radio service

YOU'LL FIND BARGAINS GALORE AT PLATT'S NEW "SUPERMARKET"

FL-S RADIO FILTER GENERAL ELECTRIC MAZDA LAMPS, #623, 24-28 Volts, 6 candle power-sensationally priced at only \$2.50 are hundred.



PRE-AMPLIFIER MODEL K-1

onographs. Operates 24-28 VDC, can be complete with PL 55 2 terminal \$3.95

BC-221 Frequency Meter

\$139.50 \$159.50 \$179.50

ply 3189.50 MODULATED TYPE with AC Power Supply \$199.50 MODULATED TYPE with AC Power Supply \$199.50 MODULATED TYPE with AC Power Supply \$199.50 MODULATED THE PRIO. MOTE THE STATE OF THE S SCR-274N

SCR-27 COMMA and ARC- EQUIPM	ND S	8	百
RECEIVERS 8C-453—190 to 550 KC 8C-454—3 to 6 MC 8C-455—6 to 9 MC 1.5 to 3	USED	USED \$24.95 14.95 12.95	NEN 549.9 24.9 18.9 29.9
TRANSMITTERS A-958—2.1 to 3 MC BC-457—4 to 5.3 MC BC-458—5.3 to 7 MC BC-458—5.7 to 9.1 MC T-15 ARC 5—500 to 900 KC	\$8.95	12.95 12.95	24.9 24.9 24.9

A-958—2.1 to 3 MC BC-457—4 to 5.3 MC		12.95	24.95
BC-458-5.3 to 7 MC BC-459-7 to 9.1 MC T-15 ARC 5-500 to 800 KC	\$8.95	12.95	24.95 24.95
ADDITIONAL EQUIPMENT	T		
BC-456 Modulator BC-450 Control Box (3 Receiver) BC-451 Control Box (Transmitter) BC-442 Relay Unit (ANT) Flexible Shafting with gear to fit	1.79	1.95 1.79	6.25 2.98 2.49 5.49
3 Receiver Rack Shock Mount for Receiver Rack	1.79	2.29 1.25	1.95 2.98
2 Transmitter Rack Single Transmitter Rack DM-33 Dynamotor for Command Set.		2.39	3.95 3.49 3.95

MULTI-TESTER FOUNDATION BIAS METER

omplete, Srand New. \$4.95

LP-21-A LOOP ed with BC-433 & R5-ARN-7 Army Com-ss Receivers. Excellent, used...... \$19.95




MN-26C INSTALLATION

This and perates to in-

sale 250. Receiver-Brand New	\$39.93
MN20E Rotable Loop	9.95
MN28 Remote Control Box	17.95
2 Flex Shaftings	5.00
1 Antenna Cable	2.50
2 Piuga	3.00
1 MN52 Azimuth Control Box	2.95
1 Left to Right Indicator	4.95
SPECIAL! Complete Installation	\$74.95
(You Save \$11.30)	

HEADSETS

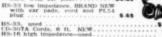HS-23 high impedance. BRAND NEW with ear pads. \$4.63 NEW with cor bous.
S-33 low impedance, BRAND NEW with ear pads, cord and PL54 plug.
5.65





HEADSET ADAPTER

Used with headsets HS-33 or HS-38—raising the impedance from low to high. Comes complete with PL 55 PLUG. ONLY 49:

SPECIAL!

45 Henry 60 ma 625 ohm. LIMITED QUANTITY OF THESE \$1.00

MICROPHONE SUPER-SALE MC-253, Cord CO-287, Plug PL-179 a JK-26 IJKE Carbon Lin Mike IJKE Carbon HRAND NI W HANDSET -BRAND NEW Vestern Electric Carbon Hand Mike with & PL-08 Plug. BRAND NEW

Now, here's your chance to pick up real super-bargains at PLATT'S newly enlarged glant retail store of 489 BROOME ST., N.Y. C. Unfortunately, this ad permits us to list only a few of our many, many sale items, so why not come down now and browns around.

TUBES

NEW	ZER	RECEIV	ER.	733-D.	NEW	8	39.95
			-				

TAKE YOUR PICK FROM THESE BARGAINS!



BC-357 RADIO BEACON RECEIVER

UHF Aircraft Receiver with fre-quency range from 62 to 80 mc for receiving 75 mc marker beacon sig-nals. Power requirements are 24 volts DC at .158 amps and 220 milliamperes. Used. SPECIALI SPECIALI \$7.95



T9/APQ-2 RADAR TRANSMITTER

80/115V 400-260-26 VDC. Designed primarily for air-craft operation.

NEW! \$19.95

BC-433		RA	DH	0	c	01	MP	A	55		RI	C	EI	VI	ER	t,		
200 tion,	le	8.5	tul	nes										ot	id:	1-	\$24	95
BC-434 BRA	_	CO	PET	ĦΟ	ĸ.		οх	. 1	OF	- 6	ЮO	VE						95



SENSATIONAL SALE! ARC-5/R-28 2 MTR RCVR \$19.95

ere is the 2-meter superhel u have been looking for? Ab-olutely one of the BEST seal-de today? Tunes from 100 to 16 Mes. in four crystal chan-to continuous tuning.) Tubs

Incup is as follows: 7174-RF, 7174-Miser, 2-128H7-1st and 2nd I.F. 16.9 Mc. 28L7-1et. AVC Spuelch, 128L7-1st audio-spuelch 1246-2nd sudio, 128H7-R.F. Osc.-4th Harmonic

ampliner. 12AH-2nd audio, 12SH7-R.F. Ozc.-4th Harmonic Gen. 717A-Trip. 12th Harmonic Gen. 717A_Dblr.-12th Harmonic.



TELEGRAPH KEYS



					•		,	
	137	i	×					\$1.50 1.50 .08
ì	138							1.56
١	141							.06
ı	145							3.95

ELECTRIC MEGAPHONE SYSTEM



For Rural Areas, Hotels, Commercial Steamers, Ball Parks, Etc.

NAVY type PAE-1 Electric Megaph is designed for voice reinforcement is manner as, but to a greater degree far acoustic megaphone. Consists of which contines a microphone and reg (le assembly). Portable Amplifier wh amplifies the output sternal of the STRATION GIVEN AT PLATT'S \$149.50

MINIMUM ORDER \$2.00

1 1.20 Immediate delivery — send 25 % deposit on C.O.D. orders. If send ing full remittance, silow for post- 7.95 age and save C.O.D. charges. All shipments F.O.B., N.Y.C. warehouse (N.Y.C. residents add sales tax.)

OC3/ VR105 . .80 6K8 OD3/ 6L6GA

VR15085	6L6M1.20	722A99
1B2269	6N7	801A19
1A769		82639
11.4	6SJ7 54	832A 6.95
2B22		0.024
2C26	68L759	
2C26A	6SN758	84129
2D21 1.18	6887 78	84317
2X2 39	6SU7 2.49	86419
3B22 1.19	6Y6	931A4.78
3D6	7C4 39	1626
5R4G5Y 1.18	12A655	163319
5U4	12AH7 . 1.20	20501.30
6AG5	12AT7	2050W 2.35
6AJ5 1.25	12C859	5654 1.85
6AK578	12H6	5670 3,25
6AK5W 1.48		
	12L829	5726 1.25
6AL549	128G7	5749 1.25
6AL5W78	128H759	5751 1.50
6AQ5	128J784	5814 1.70
6AS61.90	15R 39	6096 CT 1.78
6BA684	28D7 1.50	7193 19
6HE684	39/44 29	9002 69
6BQ61.15	114B29	9003 1.18
6C4 50	215A	E114849
6D4 2.50	221A29	RK34
6H650	316A29	VR9214
6J44.25	ANNA	VT12715

Cathode Ray



TUBE REJUVENATOR

TERRIFIC SAVINGE 996

BRAND NEW SCOTCH BRAND

SOUND RECORDING TAPE 111A SPECIAL! \$2.99



TUBES

TV ANTENNAS

RMS—8 Element Conical BRAND NEW \$2.95 DELSON - 10 Eler Conical - BRAND RMS-Flying Double "V"
--BRAND NEW . . . \$2.99

RMS-Indoor At (List \$6.95) S

300 OHM TWIN LEAD TV LEAD-IN WIRE

AWG22 strand copper, 55 mil. 2c per foot. \$1.78 per 100 ft. \$14.50 per 1000





AUTO ANTENNAS

CD 3 Section, 36 inch lend, TOP COWL MOUNT \$2.06

CAMBURN 3 Section, 36 inch, TOP COWL MOUNT...... 2.66

CR-1741 BUD DE LUXE CABINET RACKS

Overall Height 10 9/16°, Panel Space 8 1/4". Black Crackle Finish......\$9.95





SNYDER 2 SET TV COUPLERS

Permits simultaneous use of 2 receivers from one aerial installation.

SPECIAL PRICE.... \$1.98

SAVEL SAVEL SAVEL SCR-522 RECEIVERS

escillator assembly, frequency shifter tubes. Contains all Coils, Transers, Resistors, Condensers and other able parts. SPECIAL! 2 for \$10.00

PLATT ELECTRONICS CORP.

DEPT. A. 489 BROOME ST., NEW YORK 13. N. Y. PHONES: WO 4-0827 and WO 4-0828

Here's a TERRIFIC BUY for MOBILE HAMS!



FAMOUS BC-645

Transmitter-Receiver

Makes wonderful mobile rig
for 429-599 Me. Easy to
convert for phone or CW
2-way communication. CONVERNSTON DIAGRAM INCLUBED. This awell rig
rotations for practically a sona! You get it all, in
original factory carton, BRAND NEW, complete
with 17 tubes, less power supply.

Shpg. wt. 25 lbm.

Makes wonderful mobile rig
for 429-599 Me. Easy to
convert on phone or CW
2-way communication. CONVERNSTON DIAGRAM INCLUBED. This awell rig
originally cart over 319-00vertically a sona! You get it all, in
critically a sona! You get it all, in
original factory carton. BRAND NEW, complete
with 17 tubes, less power supply.

UHF ANTENNA ASSEMBLY,

CONVERSION BOOKLET. Instructions \$2.50

Excellent BRAND USED NEW **HEADSETS** H5-23 high impedance H5-33 low impedance H5-30 low imp (featherwt) H-16-U high imp (2 units) CD-307A cords, with PL58 ping and JK26 jack, 8' long 84.75 \$2.25 2.25 1.49 5.75 2.45 4.95 .99

ARC-S MARINE RECEIVER-TRANSMITTER Receiver 1.5 to 3 Mc. BRAND NEW, each Transmitter 2.1 to 3 Mc. BRAND NEW, each 26.50 Combination Transmitter and Receiver, complete with tubes 45.00



ALL COMPLETE WITH TUBES

PRICES SLASHED PRIVED SUBSECTION OF THE PRIVED SUBSECTION OF

ARC-S/T-23 Transmtr, with crystals, \$39.50 tubes, circuit diagram. Brand New

BRAND NEW MODULATED BC-221-AK FREQ. METER 8



BEACON RCVR BC-1206-C

Complete with 5 tubes. Tunes 195 KC to 420 KC, IF Frequency -135 KC. Receiver Sensitivity— 3 Microvolts for 10 Milliwatts Innedance—300

WILLARD 6-VOLT MIDGET STORAGE BATTERY

electrolyte \$1.95 WILLARD 2-VOLT STORAGE BATTERY. \$2.69 olyte, enough for two cells. bottle \$1.48

DYNAMOTORS Output 250V .08A. 579V .16A. 840V .25A. 172V .138A. 224V .07A. 1000V .380A. \$4.90 \$7.50 2.35 3.95 7.35 4.95 9.50 12.50

25% Deposit with order-Balance UM ORDER \$3.00. All Shipments

Radio Supply Co.
Dept. N-5
New York 7, N. Y., CO 7-4605

h: 16 W. Kinzie St., Chicago, III.

shops in 1939 was 1.3. Also, 22% of the businesses covered in the current survey are 1-man shops; 56% employ from 2 to 5 technicians; 18% employ from 6 to 10 technicians; and 4% employ more than 10 technicians. Back in 1939, more than 80% of the radio service businesses were 1-man shops and the percentage that employed more than 2 men was insignificant.

This clearly indicates the growth in size of individual service businesses and a pattern of operation that utilizes the services of four men on an average.

The operation of service businesses has been carefully studied by practically all of the major receiver manufacturers. Any manufacturer who produces equipment that requires continuing service must be constantly cognizant of the availability of competent service wherever his products are sold to maintain consumer confidence in his brand.

Parenthetically, it should be pointed out that, to the best of your editor's knowledge, none of the major set manufacturers have any plans whatsoever for creating their own companycontrolled national servicing departments to handle color TV installation and service. It has been proven that, in general, the most efficient, economical, and profitable method of handling consumer electronic service is through capably managed, competently staffed, independent service companies.

It is interesting to note that the analysis of service businesses showed 4% that employed more than ten technicians. It also shows that 4% handle air-conditioning installation and service. This would indicate that all large service organizations have turned to air-conditioning as a means of leveling off their service volume and maintaining their technical staffs the year 'round.

The survey indicates that most of the multiple-manned organizations have expanded their activities to include electronic devices other than home TV and radio sets. For instance, 70% handle wire and tape recorder service; 85% handle auto radio service, but only 13% are handling any work on 2-way communications systems. Four per-cent of these businesses have engineering facilities and have prepared themselves to handle closed-circuit television when that phase of TV starts to expand.

Effect of Color TV

It is possible to make a reasonably accurate projection of the future growth of an activity from an analysis of the need for the services it has to sell. In the case of color television receiver service it is quite obvious that considerably more service calls per set will be required than has been necessary on monochrome TV. The present national average of service calls per TV receiver is said to be somewhere around 2.9 calls per set in operation. The present estimate of the frequency of service that will be required on color TV sets is 12 calls per year. The in-



When it comes to high-voltage capacitors, you just can't beat CRL Precision Attachable Terminal Hi-Vo-Kaps for dependability. Here's why:

They are 100% factory-tested at twice rated working voltage — withstand continuous overload up to 40,000 v.d.c.

Terminals and taps have heavy 8-32 thread—cannot strip or break off, when terminals are tightened.

Terminals seat flat at bottom of tap. No gaps between terminals and capaci-tor body — no possibility of corona. Positive mechanical bond between stub terminals and internal electrodes pre-vents loosening, when terminals are attached.

Keep a stock of CRL Precision Attachable Terminal Hi-Vo-Kaps on hand. Separate packaging of terminals and capacitor body lets you buy only the terminals you need. See your Centralab distributor.

> Send coupon for bulletin 28-2 on CRL Precision Attachable Terminal Hi-Vo-Kaps.

Centralab

910F E. Keefe Send bul	Globe-Union In	CRL Precision
Name		
Company		-
Address	******	
City	Zone	State

vestment per technician in test instruments for field service is yet to be determined, but for many color TV ills a man will have to have more than a

There is no doubt that contract service will return with the sale of color TV receivers. However, manufacturers and distributors will be more cautious about the qualifications of the service companies they authorize to handle contract service than they were on monochrome TV. And they can be, for there are excellent service facilities available to them in capably managed independent TV service shops in every section of the country.

The present shops that are authorized by manufacturers to handle contract service on color TV receivers will expand their personnel and facilities to handle the volume of business they get. They will work with nonservicing dealers, of course, and even though they are factory-authorized service depots they will have to compete with other service companies for dealers' business.

TV service companies will avoid the mistakes that floored so many service businesses in the early years of TV. Over-expansion, unlimited dealer credit on contract monies, improper accounting and allocation of contract fees, and slip-shod handling of supplies and replacement parts—these are the things that finally spelled disaster to many service businesses in the late forties and early fifties.

Many radio-appliance dealers will add their own service departments to handle color TV installation and service. Thirty-six per-cent of the businesses included in the analysis of service businesses are radio-TV appliance dealers with major service departments. These companies have found their service departments to be consistently profitable operations. An expansion of service departments by set retailers will open up many good opportunities for present small shop operators who cannot finance color TV equipment, to take lucrative jobs as service managers for major retailers.

On the basis of 12 calls per year per set, independent service businesses that handle color TV should expand from an average of 4.19 men per shop to about 15 men per company. The present independent TV service industry can easily support this expansion because the management skill and "know how" is already there-developed by monochrome TV.

Selling Service

Regardless of how good a technician a man may be, if he doesn't get enough work week after week and month after month to pay all of his expenses, and provide a better-than-average income for his family, he will live constantly on the fringe of failure. The constant problem of any business is to maintain a consistent or growing volume of business. This is true of grocery stores, drug stores, department stores, and service shops.

There is no sure fire system of busi-



offers important easy-installation, low-maintenance business in your locality in:



GARDEN COURTS



















SHOPPING CENTERS

Check the new RCA Broadband Antenaplex Amplifier at your RCA Electronics Distributor's, or write Radie Corporation of America, Building 15-1, Dept. F-222, Camden, N. J.

SOUND PRODUCTS

RADIO CORPORATION of AMERICA CAMDIN'N

ENGINEERING PRODUCTS

In Canada RCA VICTOR Company Limited, Montreal





ARC-5/R-28 2-METER RECEIVER

Here is the 2-meter superhet you have been tor! Absolutely one of the BEST available Tunes from 160 to 156 Mes, in four crystal of (Easily converted to continuous tuning.) Tube is as follows: 717A-H.F., 717A-Mixer, 2-11st and 2nd i.F. 16.9 Me. \$24.50

ASB 5" OSCILLOSCOPE INDICATOR, New. \$9.95 ASB POWER SUPPLY, New. 4.80

SCR-183 TRANSMITTER RECEIVER. Complete with 12 V. dynamotor and tubes. 40, 80 meter. F.B. for mobile. New with service manual. \$24.50

TG-10 CODE KEYER

elf-Contained Automatic unit for code practice sig-nis from an inked type recording. Complete with tubes and electric eye; Audio freq. output of 800 PS. Nige: 11 x 34 x 18 ½—110-220 VAC 60 cy.— 8 HVM motor can be used for a turntable—Power nit can be used for a P.A. system—st. \$22,50



C.A.P. BC-625 VHF

Freq. range 100-156 MC. With modulation section and speech amplifier. Less tubes & crystals, with conversion dope. \$9.95 Used, good condition, (See Nov/53 CQ.)

ARB NAVY RECEIVER

105 to 9050 KC. Four Bands, Calibrated Dial, LF Ship-Bt 80 & 40 Meter-Complete with Tubes and Dynamotor. For 24 Volt operation; eachly converted to 110 V-12 or 6 Volt. Size: \$8\sum_1^4 \text{ 1}^2 \text{ 1}^2 \text{ 1}^2 \text{ 1}^2 \text{ 1}^2 \text{ 1} \text{ 1}^2 \text{ 1} \text{ 1}^2 \text{ 1}^2 \text{ 2} \text{ 1}^2 \text{ 2} \text{ 2}^2 \text{ 2} \

ID6/APN4



Made to operate in conjunction with Radio Receiver 19/APN-4. Unit uses 19 tubes, one 5° scope tube, crystal controlled standard oscillator, sweep circuits, marker pulses. Excellent cond. Less tubes but \$29.50

cond. Less tubes but \$29.50
WITH TUBES & CRIVETAL \$39.50
DVNAMOTOR SPECIAL: 9 V. Input, Output 450 V. 75 mils, With extended shaft and drive gear on one end. New

	ST HEADSET & MIKE BUYS
H-16U	MEADSET. 8.000 ohms
MG-18	HEADSET, New 2.48
HS-23	HEADSET. High imp. New 4.95
MS-30	HEADSET. Featherweight type. Low
temp	NEW \$2.49 USED 1.49
MS-33	HEADSET. Low Imp. New 8.80
MS-38	MEADSET. USED, excel, cond 1.49
NEV	3.50
85-38	MIKE. NEW 84.95 USED 2.78

To-MODULATION TRANSFORMER, For BC-610 Transmitter, Fri. 16,000 ohms CT: sec. 8,330 ohms @ 250 ma. Pully shielded steel case. New. \$34.50



Sound Powered Handset TS-10

no batteries o ternal power source. Ideal for TV installation work,

on projects, connecting outbuildings, includes 5 ft. cord. \$14.50 NEW. Ea. .. \$9.95 NEW Per Pr. \$18.50

LM METER. Frequency meter with modulation 125-20,000 Kc. With calibration

FREE HAM FLYER!

featuring Loads of Special Valu SEND FOR YOUR COPY TODAY!

RROW SALES IN

ness promotion for any business. Each city, town, hamlet, and community has its own small individualities, and local promotions will take these things into account when they are planned. Each type of business, too, has its individual characteristics, so a promotion that works well in one type of business will not necessarily work in another type.

Service businesses compete for dollars that set owners would much rather spend for other things. Television service should be the easiest type of service to sell because the product itself can be "romanced" even from the standpoint of servicing. It is the focal point of interest in the home and any consistent program detailing the beauty of better pictures or more enjoyable sound would have a more receptive audience than service promotional literature on any other device in use in the home. Yet only a handful of TV service companies have done more than advertise that they have the facilities to service TV sets when a set owner needs TV service. The most successful service companies use direct-mail promotions in preference to all other forms of advertising because they have accumulated tested mailing lists.

One of the most aggressive cooperative programs for service selling is one sponsored by the G. M. Popkey Company, a wholesale distributing organization in San Francisco. They set up an organization which is known as the GMP Qualified TV Service Dealers. Any servicing dealer or independent service operator in northern California can become a member of this organization by agreeing to strictly adhere to the code of ethics and signing a pledge to maintain high ethical standards in the conduct of his business.

The code of ethics provides:

1. Employ qualified trained personnel. No student shall be passed off as a journeyman technician.

2. Avoid trick advertising which offers to service or deliver materials under conditions which are questionable.

3. Issue a standard RETMA guarantee with all work.

4. Have sufficient and proper test equipment to insure good work.

5. Install only such parts and tubes as are really necessary to assure continued performance.

6. Use only new parts and tubes of equal or better quality than original equipment.

7. Issue an itemized bill.

8. Service sets at home whenever possible and practical.

9. Carry adequate insurance cover-

10. Be honest, courteous, and treat each client in an accepted professional manner.

Each member of the GMP Qualified TV Service Dealers signs the following pledge:

"I pledge that I will conduct my business activities as a dealer in such a manner as to cast no discredit on myself, my competitors, or the television service industry.

'I further pledge that I will promptly take all necessary steps to correct any legitimate complaints which may be brought against me during the course of my business.

"I further pledge my assistance to the G. M. Popkey Company in carrying out its plans for educating the public and to maintain the standards of ethical and technical practices in the industry.

In support of the GMP Qualified TV Service Dealers, the G. M. Popkey Company has sponsored a highly popular TV program, coordinated member advertising in local newspapers in support of this program, and just recently launched a TV service time payment plan that enables the members to sell service on a time payment basis with no down payment required and monthly payments as low as five dollars per month. The important feature of this plan to dealers is that the finance company handles the paper without recourse. Space does not permit a detailed outline of this plan but readers who are interested in having these complete details may obtain them by writing to TTLB Special Services, P. O. Box 1321, Indianapolis 6, Indiana. -30-

Jack Sterner, K&ATA; Dr. Jose Polak, XEIVA, vice-president of the Mexican Radio Experimenter's League; John Griggs, W&KW, ARRL director for Southern California; Guy Dennis. W&DI, U. S. convention manager; and Ed Luckey, W&MJ, public relations manager for the U.S. get together to discuss the international convention being held in Acapulco May 27th through 30th. The 22nd annual convention of the Mexican group is being opened to hams, technicians, engineers, service technicians, and electronic manufacturers throughout the world to help promote brotherhood and fraternity among such groups. In addition to exhibits, technical sessions, and contests the meet will feature a diversified program of fiestas, sightseeing trips, a banquet and ball, as well as fishing and cruising at the resort city of Acapulco.



Scope Calibrator


(Continued from page 42)

impressed on the plate exceeds the bias value. The plate of the second diode is biased negative with respect to ground by an equal amount so that there is no conduction across that section until the impressed negative voltage exceeds the bias voltage. When the voltage impressed across a diode section exceeds the bias voltage, diode conduction takes place, "shorting out" all voltage above the bias value, so that the peak value of the output voltage cannot exceed the bias voltage. In consequence of this connection, the sine-wave input is clipped, with the positive and negative peaks being equal and flat, and the peak-to-peak output voltage equal to the total bias voltage. This clipped sine-wave ("semisquare wave") output is then fed to a calibrated voltage divider through a calibration resistor, and from this circuit clipped sine waves of known peak-to-peak value can be coupled to the oscilloscope.

Rather extensive use of a simple unregulated oscilloscope calibrator of this design disclosed that, although it performed exactly as advertised, its utility was greatly restricted by vagaries of the local supply voltage. To improve the electrical operation, regulation of the bias voltage was necessary. At the same time, a few mechanical changes, largely a matter of personal taste, were found desirable. These included the addition of a strong handle on the case, to prevent droppage; replacement of the line cord by a plug; addition of new rubber feet; and addition of a pilot light, so that the calibrator would not be left on overnight. A change in binding posts, to match those used on other equipment was also made; and a fuse was added, so that the instrument would comply with the local electrical

This circuit as shown in Fig. 2 with all alterations incorporated is now operationally equivalent to the best 60-cycle calibrator now commercially available. The panel view of the modified calibrator is shown in Fig. 1. The handle, a Stanley #3 door pull, is ideally suited for electronic equipment because it is large enough to fit a man's hand, and the mounting holes exactly fit a standard 10-32 rack screw. During remodeling, all screw holes were tapped 6-32, and the self-tapping screws supplied with the instrument were replaced by 6-32 binding head machine screws.

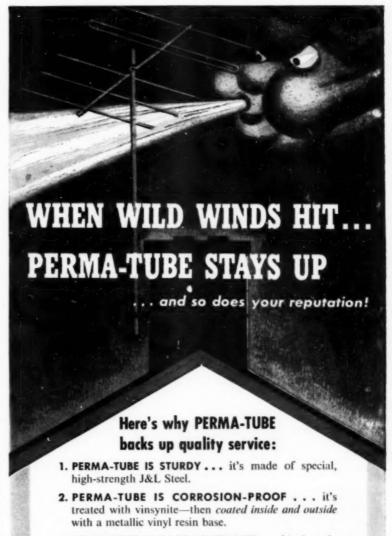Interior above-chassis view of the modified voltage calibrator is shown in Fig. 3. The socket for the regulator tube, an OB2, is mounted in the hole formerly occupied by the calibration resistor (after some reaming); and the calibration resistor was moved to a vacant area between the rear of the multiplier switch and the dual diode. So that the instrument would



PERMA-TUBE IS EASILY INSTALLED ... it's the only mast with both ends of the joint machine fitted.

Here's proof of Perma-Tube's superior strength.

Ordinary masts and Perma-Tube were subjected to regular deflection and permanent set tests with the following results:

and will be a second			
TV Mast Tested	Size and	B W Gauge	Bending Force To Produce 21/2-inches Set
Mast A	134" C	D x 20 Ga.	1870 inch pounds
Mast B	11/4" O	D x 18 Ga.	2740 inch pounds
Mast C	1.165" C	D x 17 Ga.	2780 inch pounds
Perma-Tube	114" C	D x 18 Ga.	2930 inch pounds
Mast D	114" 0	D x 15 Ga.	4370 inch pounds
Mast E	114" 0	D x 16 Ga.	4560 inch pounds
Perma-Tube	114" C	D x 16 Go.	5950 inch pounds

CHECK THE 500 HOUR MINIMUM SALT SPRAY TEST RATING OF YOUR TELE-VISION MASTS (Am. Soc. of Testing Materials—Spec. 5117-49T). Remember Perma-Tube passes this test... remains corrosion-proof.



Jones & Laughling

If you want professional sound quality



Sound engineers know that the selection of a fine amplifier, pickup and speaker system is only part of the story; that unless the turntable is of equal quality, music reproduction must suffer. That is why they insist on such high standards for turntable performance.

do as the professionals do...



Rek-O-Kut precision turntables are made to conform to the highest standards in the professional field, and they certainly represent the finest you can use in the home. A Rek-O-Kut turntable will make all the difference in the world. The finer your present system, the more apparent the improvement will be. Whether you select the deluxe T-12H or the standard LP-743, the entire performance of your sound system will become a new and thrilling experience.

REK-O-KUT precision turntable



Rek-O-Kut Precision Turntables are priced from \$59.50. Write for specifications and descriptive literature to Dept. J $\!-\!12$

The REK-O-KUT COMPANY

Manufacturers of Professional Disc Recorders and Specialized Sound Systems
38-61 Queens Bevievaré, Long Island City 1, New York
Export Division 458 Broadway, New York, U.S.A. Cables: Morhanex
19 Canada: Atlas Radio Corp., Ltd., 560 Ming Street, W., Toronto 28

GET INTO ELECTRONICS



You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. Il-8, or equivalent required. Begin Jan, March, June, Sept. Campus life. Write for catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Indiana

TV TRADE-IN SETS

Philco • Emerson • GE • Admiral
Motorola • Tele-King • Others
10"—\$17; 12" to 17"—\$20 up

Send check or money order now! List available—Add \$5 each for packing WASHTEK SERVICE CO. 1501 Boston Road, Bronx, N. Y. BA 3-9281

ARKAYKITS

RADIOS PHONOGRAPHS TV
TEST EQUIPMENT HI-FI
Write for FREE Brochuse

RADIO KITS, INC. . 120 Codar St., N. Y. 6

not creep out of calibration, a Millen shaft lock was added to this control. Optimum panel location for the pilot light is on the vertical center line, just above the upper edge of the Zshaped chassis. So that the pilot light bracket would seat firmly, a large washer, with the lower periphery flattened to clear the chassis and the upper to clear the cabinet, was placed between the panel and the pilot light mounting bracket. An Amphenol type 61-M plug was mounted in the center back of the chassis to replace the line cord. This also required enlarging the cord hole in the case.

Changes beneath the chassis were few, and consisted of adding a fuse clip (Fig. 4) in the a.c. circuit; mounting the dropping resistor for the regulator tube; attaching cable-clamp hold-downs over the two condensers; and recabling the wiring. The clamp ring of the a.c. plug was soldered to the chassis to prevent rotation or creeping of the plug. Under-chassis appearance of the instrument is shown

in Fig. 4.

These modifications necessitated readjustment of the calibration resistor. This was done in the following manner: The calibrator output was connected to the oscilloscope input, and both instruments were turned on and allowed to warm up and stabilize. A maximum reading of 100 volts peakto-peak was desired. As peak-to-peak volts are 2.828 times the r.m.s. value obtained from sine waves, a sine-wave voltage input of 35.36 volts r.m.s. is needed for calibration. With the multiplier switch of the calibrator turned to signal, this voltage (obtained from the filament supply of a tube-checker) was applied across the input of the calibrator, and a good a.c. voltmeter was shunted across it, to insure that the applied voltage, at the time of calibration, remained at 35.36. The oscilloscope gain was then adjusted until the sine-wave pattern was exactly two inches high (Any other convenient height may be used). The calibrator switch was then set to X 10. and the potentiometer to 10, and, being sure that the oscilloscope gain has not been changed and that the input voltage to the calibrator is still 35.36, the calibration resistor of the calibrator was adjusted until the semisquare wave pattern was exactly two inches high. After locking the calibrator shaft, and checking the adjustment, the calibrator was put in its case. It is now completely ready for operation.

This voltage calibrator performs satisfactorily in actual use, and appears to be operationally as good as some commercial models costing more than three times as much. Rather interestingly, although it would not be economical to make an oscilloscope calibrator "from scratch," it is definitely cheaper to modify a kit calibrator than it is to buy a commercial model, if your time is worth \$5.00 per hour or less!

-30-

RADIO & TELEVISION NEWS

Special Hi-Fi Offer



See what MUSIC at HOME gives you for 4¢ a week!

MUSIC at HOME will keep you posted on all phases of hi-fi music, and equipment for records, tape, and FM. A year's subscription provides —

MUSIC: Over 2,500 indexed listings of new releases in Your Record Shopping Guide; an expertly planned Home Record Concert for every week of the year, each with fascinating program notes; special articles on records, tape, and FM music, by nationally prominent authorities.

EQUIPMENT: The complete source of the latest information on hi-fi equipment, elaborately illustrated, explained in non-technical language, written by leading authorities.

INSTALLATIONS: Nearly a hundred different ways to make simple and elaborate hi-fi installations of correctly-matched components, that are as attractive in appearance as they are fine in performance.

OPERATION: Dozens of money-saving ideas about the correct use of hi-fi equipment, improving tone quality, keeping your system up-to-date, and doing your own service work when troubles develop.

MUSIC at HOME: These four departments, plus many special features, make this magazine your complete hi-fi guide. Order today! See for yourself.

Milon D. Dagon

is a new kind of "how-to-do-it" magazine, which covers the hi-fi field thoroughly, dramatically, and richly, as never before! Just as you must bear hi-fi music, you must see MUSIC At HOME to discover the pleasure it can give you, your family and guests.

To prove this... to let you judge the value of MUSIC At HOME for yourself, the publisher makes this special offer and money-back guarantee! Mail the coupon today, so you can be sure of getting the very first issue!

MILTON B. SLEEPER,	Publisher
207-D E. 37th St., N. 1	r. 16, N. Y.
Please enter my subscri My remittance is enclos	ption to MUSIC at HOME.
☐ \$1.00 SPECIAL 6	-MONTH RATE (3 issues)
\$3.00 for one year	(6 issues)
\$6.00 for 3 years Foreign postage,	
Name	
Address	
City	State



3-Bands, I-Vertical (Continued from page 67)

unit this took place when all turns but one were shorted out. The single turn lowers the reactance to the same value obtained with a 1200 µµfd. condenser. While discussing the 80-meter tuning network it might be well to mention that it is realized that the antenna can be brought to resonance and the feedpoint matched by using a slightly smaller inductance in the series position and substituting an inductance at the same point we are now using the shunt condenser. This eliminates the need for the large condenser, however, the network is no longer a low-pass filter and harmonics will receive little attenuation. By using the condenser, the system is properly matched and at the same time undesirable harmonics greatly attenuated.

An r.f. bridge was used to determine the values of resistance and reactance of the antenna on each band. This was necessary to provide information for designing the L-networks: however to duplicate the antenna system it is only necessary to have some form of standing wave indicator which can be placed in the transmission line so the tuning network may be adjusted to the exact value to produce a low standing wave on the line. It is only necessary to watch the standing wave indicator while making a small change in the shunt capacity of the L-network. After it is set at the lowest reading, the inductance is then adjusted slightly to improve the standing wave ratio even further, after which the condenser adjustment is made again. The two operations are repeated several times until the standing wave is reduced to a very low value. Since the network corrects for both reactance and resistance values of the tower it is possible to obtain an excellent standing wave ratio. It is better to adjust the system as described rather than trying to duplicate the original installation to the letter. Small variables such as proximity of the antenna to other objects or a slightly different base mount will make it necessary to make minor changes in the antenna tuning network settings.

You will notice that C1, the condenser used on 80 meters, is positioned on the coax side of the coil, while C_1 (40 meters) is on the antenna side of the coil. This is because the antenna base resistance is lower than the characteristic impedance of the transmission line when used on 80 meters. Just the reverse is true on 40 meters. In each case the antenna impedance is made to look like 52 ohms at the coax side of the network. The amount the impedance is raised or lowered by the network is determined by the relationship between the coil, condenser, and antenna impedance.

The tuning network assembly is enclosed in an ordinary RFD mailbox, see Figs. 1, 4, and 5. Several different

containers were tried but the mailbox has proved most satisfactory since it is rainproof, sturdy, and easily accessible. The rivets along the side of the box were removed so the top cover may be hinged back from the tuning units when they are adjusted. When changing bands it is only necessary to open the front door. The mail box is mounted beside the antenna base and a piece of copper braid about 10 inches long connects to the antenna. The braid was made from a piece of the outer conductor of RG-8U coax. Any double-pole, three-position switch with low-loss insulation will work well. The type used for high-voltage meter switching or tank circuits is excellent. Standard inductor clips are used to tap the coils. The tower consists of a 30-foot TV mast with two sections of thin-wall steel conduit added to the top to bring the total length to 44 feet.

The antenna has been in use for quite some time with satisfactory results. During the past "Sweepstakes" contest, while running 100 watts and using the antenna, 465 contacts were established in 69 of the 73 sections. The author is not attempting to say that this antenna will out-perform the well-elevated beam or a good rhombic but it works exceedingly well and fills a definition of the supersex ham.

nite need for the average ham.

DIODE CHECKER By PHIL WEISS

HERE is a simple and practical way to check a germanium diode detector in a TV set without unsoldering any leads. This is important since germanium diodes cannot stand much heat and the leads are usually pretty short.

Make up a gimmick consisting of a good germanium diode in series with a 3900 ohm load resistor. Attach an alligator clip to each end of the gimmick.

In order to test a germanium diode in a set, clip the gimmick across the diode and its load resistor, as shown in the diagram, being careful to observe the same polarity. Now turn on the set and observe the video across each of the two load resistors with an oscilloscope. If both diodes are good they will have approximately the same output. A bad diode will give little or no output across its load resistor.


If the TV set does not develop any i.f.

If the TV set does not develop any i.f. voltage at the input of the diode detector, a signal generator can be used. The generator should be set at some video i.f. frequency and modulated.

The gimmick can, of course, be used

over and over again.

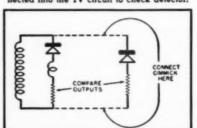How the gimmick described above is connected into the TV circuit to check detector.





"He Wants To Keep In Touch With WALTER ASHE"



HAMMARLUND HQ-140X Less speaker. Net \$264.50



ELMAC AF-67 TRANS-CITER Net \$177.00

ANNOUNCING the New JOHNSON VIKING RANGER TRANSMITTER

Self-contained power supply, VFO, modulator, TVI suppressed, 160 through 10 meters, 75 watts input on CW.

In kit form at low price to be announced.

Let nothing stand in the way of taking advantage of those fabulous Walter Ashe "Surprise" Trade-In Allowances on used test and communication equipment. Get your money-saving, trade-in deal working today. Wire, write, phone or use convenient coupon below.



HALLICRAFTERS SX-88 Less speaker. Net \$595.00





HALLICRAFTERS SX-71. Less speaker. Net \$249.95 Matching speaker. Net \$19.95

We want every ham to have the opportunity to own a new receiver for field day. We have a fresh stock of brand new, latest model SX-71 receivers on which we will out-trade all competition. Every set delivered in a factory-sealed carton and backed by Hallicrafters' 90 day guarantee. We will go all out to give you the highest tradein allowance in the country—plus immediate delivery. Try us and see for yourself!

All prices f. o. b. St. Louis . Phone CHestnut 1-1125

Walter Ashe RADIO CO. 1125 PINE ST. • ST. LOUIS 1, MO.

	R-54-6
WALTER ASHE RADIO COMPANY	
1125 Pine Street, St. Louis 1, Missouri	
Rush "Surprise" Trade-In Offer on my	
for	
(show make and model number of new equipment desired	d)
Rush capy of latest Catalog.	
Finne	
Address	
City Zone State	

Send for your copy today



Dept. RE 4109 Burbank Bivd., Burbank, Calif. P.O. Box 1167, Magnolia Park Sta. Cable: Harjo Phone: Victoria 9-2411

R.F. in Audio Systems (Continued from page 57)

Shielding and Grounding

1. Analyze and lay out the grounding system with care. Run a very heavy conductor from a central grounding point in the studio, either to a cold water pipe as close as possible to the street main-or to a transmitter-type radial ground system. Do not ground to a.c. conduit. One network uses #4 copper conductor in conduit for the ground lead and specifies a maximum d.c. resistance of .1 ohm over its length. Use a heavy conductor to bond all rack and console frames to the central grounding point which may be a heavy bolt in the bottom of one rack. Bond all amplifier chassis firmly to their racks.

2. Run a heavy ground bus up the inside of each rack and connect to it all cable shields and the low sides of any unbalanced circuits. The rack bus should be grounded to the rack frame. at only one point.

3. Shields and unbalanced circuits should be grounded only at one end to avoid ground loops which are one of the main causes of r.f. interference. When a shield or conductor is grounded at two points some distance apart, an r.f. voltage may appear across these points, since what appears as a dead short to d.c. may present an impedance to r.f.

4. Determine by trial whether or not to ground the center taps of balanced transformer windings and balanced pads. Such grounding may do more harm than good from an r.f. or longitudinal voltage standpoint.10

5. The r.f. pickup may occur in a preamplifier in which the input transformer secondary low side is grounded to the "B-minus" terminal of a distant power supply, instead of to the preamplifier chassis. See Fig. 2. An r.f. voltage may appear between the "B-minus" lead and the chassis and be coupled to the preamplifier proper through stray capacitances. The remedy is to ground the transformer secondary low side to the chassis, and remove the ground from the "B-minus" lead at the power supply, to avoid a ground loop.11

6. Use cables whose shields are tightly woven, especially in low-level circuits. This condition is often expressed as a high percentage of shielding. It should be a minimum of 80%, which means that the metal in the braid should constitute 80% of the braid area

7. In cases of severe r.f. interference, install a second shielding braid over the cable insulation. The added shield should be carefully soldered all around to the original braid. Whether this should be done at one or both ends should be determined by trial.

8. Use shielding covers on open-bottom amplifier and power supply chassis.

9. Shield the glass tubes in low-level stages, and make sure the shell of

In DETROIT it's AARON ELECTRONICS 6025 Mt. Elliott, Detroit 11, Michigan

20

TG-34-A CODE KEYER-115/2 \$24.95 o TG-34 \$19.95 CODE PRACTICE & TRAINING TAPES-FO e TG-34 and TG-10 keyers. Inked on 16 mm b) ft. reel. Complete set of 15 reels. We in wood currying case...

SIVIDUAL TAPES for the following ke 2, 26, 28, 211, 214. \$12.95 NEW in metal containers oa. SUPREME VOLT-OHM-OUTPUT METER-Model \$6.95 \$2.95 fier, knob, mfg. hwd. New. TECH. MANUAL for BC-221 Freq. Meters. \$1.25 NEW 115 VAC 60 cycle \$LOWER-1525 rpm.
Model 3571-approx. 100 cu. ft. dis. 342
2 outlet. Motor size 345 x 3 -has mounting bracket-with detachable heating element \$9.95 Less heating element.

ANTENNA—AN-75—7 ft, long in 0 se for use as portable or mobile ant. No PERMEABLITY TUNER—Has esc. coil for 5 tube superhet. Schemätic diagr \$1.25 \$2.00 \$5.00 NONETTE SPEAKER BOX Conta \$3.50 24 V Haydon timer motor. (See Feb. picture & compl. description: \$1.95 or TUMING UNITS from BC-375 xmtr-nier dials. 2—RF chokes. 2—4 pos 3 var. conds., cer. flex. coupt. \$2.95 25% WITH ORDER-BAL. INCL. POSTAGE C.O.D. MICHIGAN RESIDENTS ADD 3% SALES TAX



PERMA-FILM

- CLEANS! . . . dirt and oxidation immediately on contact.
- LUBRICATESI . . . one drop eliminates scratch, hum and noise.
- * PROTECTSI . . . assures continued top performance.



ELECTRONIC CHEMICAL CORP.

metal tubes (generally #1 socket pin) is grounded.

10. It may be necessary to shield not only the grid lead but also the plate lead and the plate load resistor in low level stages. The resistor shield should be of copper, brass, or other metal of high electrical conductivity.

11. Under extreme conditions of interference, build a shield of copper screening around preamplifiers, and a sheet copper shield around inductive elements like equalizers, and ground the shield. Larger sheet metal shields should have their edges turned over to form a flat surface on which to mount the cover. To maintain good contact for a removable cover, knitted wire mesh gaskets are available (Metal Textile Corporation, Roselle, N. J.). Such shields are obviously a "brute-force" expedient and should rarely be necessary in an audio installation.

REFERENCES

1. Remington Rand; "Television Interference," Third Edition.
2. E. I. DuPont de Nemours; "Radio Hazard in the Use and Transportation of Electric Blasting Caps," Technical Service Bulletin

13.

3. Young, P. A.: "Radio Interference in Areas of High Field Intensity," NARTB Engineering Handbook, Fourth Edition.

4. Gottlieb, Irving: "RF Sniffer," CQ, March 1951.

5. Merviman & Nixon: "Radio Interference Investigation, Suppression and Control," Proceedings of the IRE, January 1939.

6. Stephens, G. L.: "Radio Interference Suppression," Hiffe and Sons, London, Second Edition.

8. Stephens, G. L., "Radio Paterference Suppression," Hiffe and Sons, London, Sec-ond Edition.
7. Teegarden, John W.; "Household Radio Interference Elimination," RADIO & TELEVI-SION NEWS, September 1942.
8. Lee, E. M.; "Current Radio Interfer-ence Problems," Journal of the British In-stitution of Radio Engineers, November 1952.
9. Luona, Don: "The Persistent Buzz." Radio-Electronics, September 1953, page 90. 10. Augustadt & Kannenberg: "Longitu-dinal Noise in Andio Circuits," Audio En-gineering, January and February 1950. 11. Frayne & Wolfe: "Elements of Sound Recording," John Wiley & Sons, page 194. (To be continued) (To be continued)

MOUNTING CRYSTAL DIODES

By CHARLES ERWIN COHN

CRYSTAL diodes are handy components to wire into a circuit, but their installation is complicated by the fact that they can be injured permanently by excess heat during the soldering process. Furthermore, when wired and unwired many times in experimental work their leads tend to break off.

In the case of a resistor costing five cents one can take such a loss without too much grumbling, however a dollar diode is an entirely different matter and one always hopes to be able to salvage an otherwise good unit.

Soldering new leads to the diode is not too practical for the previously meationed problem of heat damage.

All of these considerations point to the desirability of a solderless mounting

for crystal diodes. Fortunately, there are two convenient methods available. Where it is possible to mount on a panel or chassis, the diode can be slipped into an 8AG fuse clip, which is just the right proportions to hold it firmly after the leads have been clipped off. Of course, this applies only to the Sylvania 1N34 and similar types with the ceramic body and two metal end caps.

If it is desired to mount the diode on leads, then the end caps can be pushed into octal-type grid clips. The National Type 8 is preferable because the diode end caps are slightly oversize.



CERAMIC CARTRIDGE

There is no wiser investment a phonograph owner can make than a TITONE ceramic cartridge.

Costing no more than ordinary "replacement" cartridges, TITONE gives a world of difference in results - an entirely new experience in true high-fidelity sound, no matter what the make of phonograph.

And only two models will replace most present-day installations!

No other cartridge gives all these features!

No preamplifier or equalizer needed . Unaffected by moisture or temperature · Wide frequency range · Outstanding response · High sensitivity • Low distortion • High compliance • No hum pickup • Superior tracking ability . Wide adaptability . Proper groove fit . Only needle rotates · Simple to replace

> Used by America's foremost manufacturers of high-fidelity phonographs, TITONE is an original discovery and development of the Sonotone laboratories. Literature available.

ELECTRONIC APPLICATIONS DIVISION

SONOTONE CORPORATION

Elmsford, New York

SPECIAL OF MONTH

Westinghouse 3" Panel Meter Model NX35 0-500 \$4.95 Microamperes DC...ea.

PLATE TRANSFORMER BARGAIN

MOBILE DYNAMOTORS

WESTON METERS

0-150 VAC Rectifier type	58.95	ı
0-50 V.D.C. (1000 ohms/v)	6.95	i
9-10 Volts DC (1000 ohms/v) "	6.95	ı
0-1 Ma (KV Scale)	6.95	,
0-50 Me OC	6.95	ŧ
Q-150 Ma DC	6.95	ı
O-1.5 Mills DC	6.95	
0-200 Microamps (Spec. Scale) Model 731	8.95	ı
0.1 Ma (0.100 Scale)	7.95	ø

PANEL METERS

BOY'T SURPLUS, G.E., WESTINGHOUSE, WESTERN ELECTRIC, SIMPSON, ETC.

3. MELEUS	3" METERS a
100-0-100 Microamp \$5.95	100-0-100 Micro-
0-80 ma BC 3.49	AMIRA
0-15 ma DC 3.49	0-800 Microamps 8.95
3" METERS	0-50 Mill 4.50 m
0-200 Microamps \$6.95	0-80 Mill 4.50
0-400 Microamps 5.95	0-150 Volts AC 6.95
0-500 Microamps 5.95	0-300 Volts AC 6.95
0-200 Milliamp 4.50	0-3 Amp RF 6.95
0-250 Milliamp 4.50	0-5 Amp MF 6.95
9-1000 Milliams 4.50	0-6 Amp RF 6.93

MANY OTHER METERS IN STOCK, PLEASE WRITE YOUR REQUIREMENTS.

Model		FREQUENCY METER	
Voits.	Regular Pr	ice \$100.06.	
Our I		\$2095 .	

OIL CONDENSERS

4	MFD-600VDC	8 .95		MFD-2000VDC	\$4.95	
10	MFD-600VDC	1.50	10	MFD-2000VDC	6.95	
3	MFD-1000VDC	.95	12	MFD-2000VDC	7.95	=
3	MFD-1000VDC	1.25	2	MFD-2500VDC	3.98	
5	MFD-1000VDC	1.95	4	MFD-2500VDC	5.95	
1.2	MFD-1000VDC	2.95	2	MFD-3000VDC	4.95	
15	MFD-1000VDC	3.50	- 5	MFD-4000VDC	1.50	
3	MFD-ISOOVDC	2.65	8	MFD-4000VDC	2.75	-
5	MFD-1500VDC	2.65	1.6	MFD-SOCOVDC	49.50	
-	MFD-1500VDC	2.95	. 1	MFD-7500VDC	1.79	
10	MFD-1500VDC	3.75	3	MFD-8000VDC	24.95	
18	MFD-1500VDC	4.50	1	MFD-20KV	49.95	
3	MFD-2000VDC	2.25	.00	025 MFD-25KV	8.50	
3	MFD-2000VDC	2.95	.00	1 MFO-SOKY	14.95	
4	MFD-2000VDC	3.95	24	MFD-240VAC	4.95	-
8	MFD-2000VDC	4.50	- 8	MFD-660VAC	2.95	

G. E. RELAY CONTROL

Contains a sigma midget 8,000 ohm, relay (trips at less than 2 Må), high impedance choke, bimotal strip, near pilot and many useful parts. The sensitive relay alone is worth much more than the total of the pilot and the sensitive relay alone is worth much more than the total of the pilot and the sensitive relay alone is sent to the pilot and the pilo

WIRE WOUND RESISTORS

		long that yo			We	ean s	upply	most	86	804,
		From	1	Ohm			Ohms.			.15
25	Watts.	From	1	Ohm	60	TOOK	Ohms Ohms	. Ea.		.30
		From		Ohma			Ohma.			.50

EIMAC VACUUM	I SOLA CONSTANT VOLT
CONDENSERS	TRANSFORMERS Input 98-135 Volts
12 MMF 32KVDC \$10.95	Output 115V Requisted
30 MMF 32KVDC, 12.95	500 VA

READ 'N' SAVE BARGAINS

His 700 Emphasies	81.25
Non-ind resistors, 250, 100 watt	.55
6 Henry 100 ma choken	.88
Heinemann cat brar, 5.5 amp, 110 V	.95
Var. ceramic trimmer 7 to 45 mmf	.25
Erie 500 mmf ceramicons	.50
8 Henry, 200 mill choke, full case	1.95
15V AC relay SPST 15 Amp contacts	1.75
220V AC relay SPST 15 Amp contacts	1.75
Sylvania 1N21 crystals	
.01 mmf, 1000 VDC Micas for	95
.0004 2500 VDC Mteas 8 for	9.5
.04 600 V Micas 8 for	- 0.5
the thirt a michael a service and the	.48
100,000 ehm, 100 Watt resist	.45
Fil. Transf. 115V, 60 cy Sec. 10V @ 1.75 Amp	1.25
Fil. Trans 115V. 60 cy Sec. 6.3V @ 7A	1.95

Min. Order \$3.00-25% with Order-F.O.B. New York,

PEAK ELECTRONICS CO.

66 West Broadway, New York 7, N. Y.

Phone WOrth 2-5439

WHAT'S New in Radio

The products described in this column are for your convenience in keeping upto-date on the new equipment being offered by manufacturers. For more complete information on any of these products, write direct to the company involved.

U.H.F. GRID DIP METER

Boonton Electronics Corp., Boonton, N. J. has announced a new u.h.f. grid dip meter, the Model 101B.

The instrument operates in the frequency range 300 to 1000 mc. in three steps. The frequency scale is approximately linear throughout the ranges which include 300-425 mc.; 425-650 mc.; and 650-1000 mc. employing three plug-in coils mounted externally on the u.h.f. probe, allowing ease of coupling to the circuits to be measured. The dial is individually calibrated to a frequency accuracy of ± 2%.

The instrument may be used to measure capacity, inductance, circuit "Q", and choke resonance as well as functioning as an auxiliary signal generator, an absorption wavemeter, and



as a means of determining many other factors in u.h.f. circuitry.

Full details on the Model 101B are available from the company without charge.

CD RECEIVER

A small radio receiver which can be worn like a hearing aid has been developed by two engineers at *General Electric Company's* Syracuse plant.

Designed primarily for civil defense applications where a compact, light-weight receiver operating from a minimum number of flashlight cells is required, the radio is tuned to a single broadcast frequency of 1240 kc.

The radio has a hearing-aid type earphone and weighs about five ounces. Further development work is being done before the radio is mass produced.

CONVERTER

Palisade Electronic Corp., 1025 Palisade Ave., Palisade, N. J. is now offering a new crystal-controlled converter, the UHF-C2.

The new unit tunes the frequency range 432-436 mc. and can be used with any receiver that covers from 11 to 15 mc. The chassis is of copperplated steel and uses five tubes. A 6AJ4 is used as a tunable tuned-line

r.f. amplifier, a 6AM4 is the mixer, a 6CB6 functions as the 11 to 15 mc. i.f. amplifier while two 6J6's are used as



the crystal oscillator and frequency multiplier. The input and output fittings are coax.

The approximate gain of the converter is 25 db and the noise figure is 7 db. Sensitivity is 2 microvolts. Buletin UHF-4 covering this unit is available on request.

SINGLE-SIDEBAND FILTER

Burnell & Company, 45 Warburton Ave., Yonkers, N. Y. is currently marketing a single-sideband filter for amateur receivers.

Designated as the Type S-15000, the new filter utilizes a toroid coil instead of the crystal filters formerly required. The unit is compact in size and easy to install. Fixed-tuned and hermetically sealed, it requires no adjustment, is rugged and trouble-free. It may be installed in any existing amateur receiver and is also suitable for incorporation in new equipment.

Descriptive literature, including a schematic and response curve, is available from Dept. D of the company.

RADIATION DETECTOR

El-Tronics, Inc. of 5th & Noble Streets, Philadelphia, Pa. has recently introduced a radiological survey instrument, the "Rad-Tek."

Approved for use by the Federal Civil Defense Administration, the new



unit was built to FCDA's rigid specifications and requirements. It is a ruggedized ionization-type of instru-

ment, and will measure radiation intensities from .02 to 50 roentgens per hour. It operates on ordinary flashlight and hearing aid batteries capable of giving over 100 hours of operation.

The unit is lightweight, watertight, and easy to operate.

AUDIO OSCILLATOR

The Nuclid Corporation, 45 W. Union St., Pasadena, California is in production on a new line of compact, fixed-frequency, low-distortion audio



oscillators, featuring zero impedance output of 10 volts at 2 watts and a variable voltage output at low impe-

The new DK-1 provides an inex-pensive source of essentially pure, highly stabilized sine-wave power for general lab use and production testing. Frequency coverage from 300 to 10,000 cps, by hundreds, is available in stock models while the range 301 to 9999 is available on special order at no extra

Housed in a ventilated metal case, the circuit is an LC bridge-type incorporating a high "Q" toroid, mica condenser and air trimmer, combined with a self-balancing feedback ampli-

HEATH PREAMP KIT

Heath Company of Benton Harbor, Michigan has added a preamplifier kit to its line of assemble-it-yourself

The Model WA-P2 has three highlevel and two low-level inputs with in-



dividual level controls for each input. There are two outputs-one to the main amplifier which is variable from 0 to at least 2.5 volts r.m.s. from any normal program source and one to a recorder input providing a minimum of .25 volt r.m.s. from any normal program source.

Frequency response is ± 1 db from 25 to 30,000 cps and ± 1.5 db from 15 to 35,000 cps. Low frequency compensation is provided by a four-position turnover control while the high-fre& vertical outputs 1 deflection yoke 1 filter choke 5 width and linearity controls 17 exact replacement flybecks 23 TV power transformers

SNEW TV REPLACEMENT COMPONENTS HAVE BEEN ADDED TO THE STANCOR LINE

STANCOR

YOUR MOST COMPLETE SOURCE OF TV REPLACEMENT TRANSFORMERS

28 flybacks (27 exact duplicates) 55 TV power transformers 8 deflection yokes

- 9 width and linearity controls 15 vertical outputs
- 8 blacking-ascillators
- 3 focus coils 5 füument tronsformers
- 22 filter chokes 19 audio outputs

NOW 172 TV REPLACEMENT COMPONENTS ARE IN THE STANCOR LINE



cer transformers are d in Sams Photofact



CHICAGO STANDARD

TRANSFORMER CORPORATION

3584 BLSTON AVE. . CHICAGO 18, ILL.

T. C. I. HELPED ME

Here is proven, practical, in-the-home training that pays off in bigger earnings! Want PROOF? T.C.I. Student Donald Bush, Beach City, Ohio, says: "Thanks to T.C.I. training I have almost doubled my pay in the past month," Every day, students and graduates from all parts of the country praise T.C.I.'s practical TV training as the key to greater earnings!





YOU CAN DO IT, TOO!

The T.C.I. secret to TV servicing auccess is down-toearth instruction in all servicing techniques used by
experts, plus actual work on a modern large screen
TV receiver furnished to you with the course at no
extra charge. No other training like it! You increase
your earnings with a few hours of spare-time training
a week. See for yourself. Whether you're a beginner
or experienced radio repairman,
send for full facts, catalog and
sample lesson FREE!

TELEVISION COMMUNICATIONS INST.
505 W. Washington Bird, Dept. 100
Chicage 6, III.

MAIL NOW FOR FREE BOOKLET

TELEVISION COMMUNICATIONS INST. 605 W. Washington Blvd., Dept. 160 Chicago 6, III. Hush FitEE Catalog and Sample Lesson. Salesman will not call. U Veterans: Address

ndsor T

Thousands of Service Organizations and Designs throughout America send us REPEAT orders month after month—they now KNOW you can DEPEND upon the WINDSOR premise of PEAK PERFORMANCE!

FORMANCE:
And here's why: Every tube we ship is first carefully tested in our laboratories, for maximum functioning characteristics, right in a radio or TV set—under actual operating conditions! That's why we setconditionally gustantee every Windsor Tube in accordance with the Standard Warranty: Full replacement of any defective tube within 50 days of purchase, excepting only burnouts and breakages. Each tube attractively packaged in individual Carton.

BUY-AND SELL-WINDSOR TUBES WITH CONFIDENCE!

Type	Each	Type	Each	Type Eac	h Type	Each
IA7GT IB3GT IH5GT	69	3Q5GT 384 3V4 5R4GV 5U4G	.62 1.00	6B8G	6 6K6GT 6 6K7	45
ILA4 ILA6 ILB4 ILCS	82 80 82	5V4G 5Y3G 5Y3GT 5Y4G 6A8GT	.37	6BD6 .5 6BE6 .5 6BF5 .6 6BG6G 1.4	6 688GT	.51 .75 .57
ILC6 ILDS ILE3 ILG5	80 .80 .80	6AB4 6AC5GT 6AG5 6AH4 6AH6	.82 .89 .68	6BH6	68F5GT 6 68H7GT	66 .52 .52
ILNS INSGT IR4 IRS	63 .85 .62	6AKS 6ALS 6AQS 6AQ6 6AQ7	.44 .51 .47	6BN6	68 N7GT 68 N7GT 68 Q7GT 61 ETB	.59 .46 .85
185 174 104 105	.62	6AR5 6AS5 6AT6 6AUSGT	.55	6C5GT .6 6CB6	8 6U8	. 1.09
1X2A 2X2 3LF4 3Q4	. 1.43	6AU6 6AV5 6AV6 6AX4	.85	6H6GT4	68 6Y6G	37

FREE! WINDSOR TUBE CADDY

The most practical Service-Aid ever designed for the radio and TV repairman. This ideal television carry-aid now offered free with every purchase of \$160,00 or accumulated purchase (talling \$160,00 within \$0 day, (You get caddy credit mema with cack purchase).

Windsor Tube Caddy may also be purchased outright for \$14.95.



- 163/s inches long x 81/s inches wide x 131/s inches

DON'T MISS THIS SENSATIONAL OFFER!

mindsor Electronic tube co 2612-N NOSTRAND AVENUE, BROOKLYN 10, N. Y.

TESTED and GUARANTEED for PEAK PERFORMANCE

Type Each 7A4/XXL .57 7A5 .70 7A6 .57 7A7 .58 7A8 .56	
7AD7 1.05 7AF7 .63 7AG7 .65 7AH7 .65 7AJ7 .70	Type Each 12BD651 12BE652 12BH769 12BY777
78454 78551 78652 287 .58 7C4 1.05	12J5GT48 12SA7GT57 12SH7GT67 12SK7GT55 12SL7GT67
7C556 7C650 7C758 7E585 7E665	128N7GT59 128Q7GT46 14A758 14AF768 14B650
7E7 .85 7F7 .69 7F8 .97 7G7 .85 7H7 .61	14C5
717	14F899 14J785 14N775
7R7	14R785 14S780 19BG6G 153 19T887 25BQ6GT 98
7Y4	25L6GT53 25W4GT53 25Z6GT46 35A555 35B553
12AU6	35C5 .53 35L6GT .52 35W4 .33 35Z5GT .33
12AX767 12AY7 2.15 12B466 12BA650 12BA768	500552 50C552 50L6GT52 117Z343 117Z6GT75

25% Deposit with Order. All mer-chandine F.O.B NYC. For orders loss than \$10, add \$1 handling cost. Deduct 2% if full remittance accompanies order. All morchan-dise subject to prior cale and price changes without notice.

Note to our Latin-American Friends: SE HABLA ESPANOL!

WRITE FOR ADDITIONAL TUBE TYPES AND PRICES. We also stock Special Purpose and Transmitting Tubes at similar savings! Dept. N-6

quency compensation is furnished by a four-position roll-off control. The unit has separate bass and treble tone controls with the bass control providing approximately 18 db boost and 12 db cut at 50 cps. Treble control provides approximately 15 db boost and 20 db cut at 15,000 cps.

DYNAMIC NOISE SUPPRESSOR

Hermon Hosmer Scott, Inc., 385 Putnam Ave., Cambridge 39, Mass. is currently marketing a new Dynaural noise suppressor, the Type 114-A. According to the company, the new




unit virtually eliminates turntable rumble and record scratch or hiss without losing music audible to the ear. It is designed as an accessory unit for use with the company's 99 transcription amplifier or with its 214 remote control amplifier.

Frequency response is flat from 19 to 20,000 cps. Two controls are provided, the Dynaural control for adjusting the degree of noise suppression and the Dynaural range control which offers a choice of 20, 12, or 6 kc. highfrequency cut-offs each with both rumble and scratch suppression, a position for dynamic rumble suppression only and a position for suppression off. The unit is normally plugged into a circuit between the preamp and subsequent amplifying stages.

BELL AMPLIFIER

Bell Sound Systems, Inc., 555 Marion Road, Columbus 7, Ohio is now offering a redesigned version of its Model 2199 amplifier.

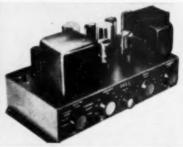The new Model 2199-B features a seven-position equalization and selector switch to compensate for five types



of recording curves and for radio and tape. A loudness control is also provided. Output impedances of 4, 8, and 16 ohms, plus an auxiliary high-impedance jack are also available.

A special input is provided for frequency-modulated and ceramic pick-



- TRACES TY SIGNALS
- LOCATES DEFECTIVE
- REQUIRES NO ADDITIONAL EQUIPMENT

Must for Every TV Technician

of or leaky

ELECTRONICS CO.

211-04 99th Ave.

Dept. 214 Queens Village, N. Y.

PREPARE FOR A GOOD JOB!

BROADCAST ENGINEER COMMERCIAL OPERATOR (CODE) RADIO SERVICING

Television Servicing

(Approved for Veterans) SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE 1425 EUTAW PLACE, BALT. 17, MD.



QUARTZ CRYSTALS

FT-243-.093" PIN DIA .-- 486" PIN SPC

FOR HAM AND GENERAL USE . GUARANTEED

4035 5500				7641	7873	1015	6150	6650	7400	8390
4080 5675				7650	7875	2125	6175	7000	7425	8400
4110 5700	5950	6675	7473	7673	7900	3500	6200	7025	7440	8425
4165 5706	5973	6700	7475	76.75	7906	3640	6440	7050	8025	8450
4190 5725	6240	6706	7500	7700	7925	3680	6450	7075	8050	8475
4280 5740	6250	6725	7506	7706	7940	3735	6473	7100	8073	8500
4300 5750	6273	6750	7525	7720	7950	3760	6475	7125	8075	8525
4397 5773	6275	6775	7540	7725	7973	3800	6500	7150	8100	8550
4490 5806	6300	6800	7550	7740	7975	3885	6506	7175	8125	85.75
4495 5840	6325	6806	7573	7750	8206	6000	6550	7200	8150	8583
4930 5850	6340	6825	7575	7773	8225	6025	6573	7300	8173	8600
5030 5852	6350	6850	7600	7775	8250	6050	6575	7306	8175	8625
5205 5873	6373	6875	7606	7800	8273	6075	6600	7325	8200	3650
5300 5875	6375	6900	7610	7825	8275	6100	6606	7340	8340	8700
5385 5880	6400	6925	7625	7840	8300					8733
6485 59nc	GADE	6950	7640	7850	8296	6140	SSAD	7375	B275.	

49c each -10 for \$4.00 99cea.10 for \$8.00

Pins, 486" SPC, marked in Chan-	LA
nel Nos. 0 to 79, 54th Harmonic	SCR
and 270 to 389, 72nd Harmonic.	522
Listed below by Fundamental	14" P
Frequencies, fractions omitted.	14.2
370 393 414 437 501 522 400 461	5910
372 394 415 438 502 523 440 462	6370
374 395 416 481 503 525 441 463	6450
375 396 418 483 504 526 442 464	6470
376 397 419 484 505 527 444 465	6497
377 398 420 485 506 529 445 466	6522
379 401 422 486 507 530 446 468	6547
380 402 423 487 508 531 447 469	6610
381 403 424 488 509 533 448 470	7350
383 404 425 490 511 534 450 472	7380
384 405 426 491 512 536 451 473	7390
385 406 427 492 513 537 452 474	7480

FT1718 BC-619 2 Banana Pluga 34" SPC Low Frequency-FT-241A for SSB, Lattice Filter etc., 093° CB-34/2" 8/PC
2030 2220 2320 2537 3650
2045 2258 2360 3202 3570
2065 2260 2390 3215 3580
2082 2280 2415 3237 2945
2105 2282 2435 3250 3955
2125 2290 2442 3322 3995
2145 2300 2532 3510
2155 2305 2545 3520

BC746 TUNING UNITS, CHAN-NELS 10 AND 12 -Foundation coils and condenser for 80 meter VFO or exciter—less stats 98c SEE ARTICLE BY W3FPQ IN MARCH '54 CQ.

48c each-18 lar 54.88 99c ouch - 10 for \$8.00

Spec.—200 KC or 500 KC in FT241A Holder.\$1.79 ca.



SZO TENTH ST. N. W.-WASH. D. C., DEPT. N

BAKER STREET

SCOTLAND YARD

WATERLOO BRIDGE

READ LONDON MYSTERY

MAGAZINE

Now on sale at leading newsstands

ups. Output power is 12 watts at 1/2 of 1% distortion with a peak of 20 watts to provide performance over a wide range of operating conditions.

Complete specifications on the Model 2199-B are available from the company.

PENTRON "TAPE-MATE"

Pentron Corporation, 221 E. Cullerton, Chicago 16, Illinois is currently marketing a new AM-FM tuner which incorporates a function selector with a tape position. Selection of this posi-



tion permits tape recordings to be fed through the tuner and modified by the tuner's tone control system.

The Model AFM permits program material to be recorded on tape at the same time it is being heard by listeners. A tape output is built-in and a flat response is fed to the recording device while the listener compensates the "listening program" to suit his own

Complete details and specifications on the Model AFM are available from the company.

NEW MICROPHONES

Altec Lansing Corporation, 161 Sixth Avenue, New York 13, N. Y. has just introduced three new microphones to the trade.

The new Model 21C is of the condenser type and is sufficiently small to be used on the coat lapel, be handheld, or stand-mounted. The Model 670 cardioid is similar in appearance to the manufacturer's Western Electric Type 639 but is a newer and smaller version.



ON THESE 5 BOOKS

SPECIAL OFFER on this

COMPLETE RADIO ENGINEERING LIBRARY

• 5 Volumes • 3872 Pages •

T HIS new, up-to-date edition of a famous, 5-volume library covers the whole field of radio engineering . . Includes latest facts, standards, data, and practice to help you solve hundreds of problems in any field based on radio. Books cover circuit phenomena, networks, tube theory, amplification, measurements, etc.—give specialized treatment of all fields of practical design and application.

and application.

SET INCLUDES: Eastman's Fundamentals of Vacuum Tubes, 3rd Ed.; Terman's Radio Engineering, 3rd Ed.; Everit's Communication Engineering, 2nd Ed.; Hund's High Frequency Measurements, 2nd Ed.; and Henney's Radio Engineering Handbook, 4th Ed.

SPECIAL LOW PRICE-EASY TERMS

SAVE \$10.00—Regular price of books is \$48.00; when bought as a set, you pay only \$38.00, and on easy terms.


	IO-DAT FREE IMIAL
!	McGraw-Hill Book Co., Dept. RTN-6, 330 W. 42nd St., N. Y. C. 36
	Send me for 10 days' FIREE trial, the RADIO EM- GINEERING LIBRARY. If not satisfied I will return books. Otherwise I will send \$8.00, plus delivery charges, then; and \$6 a month for 5 months, (We pay delivery if you send \$8.00 first payment WITH coupon; same return privilege.)
1	Print
1	Name
1	Btraet
1	City
1	Employed by This offer applies to U. S. only RTN-0

Please Mention

RADIO & TELEVISION NEWS

When Answering Advertisements

	DON'T RUIN your installation w	SIGNED FOR HIGHEST UHF GAIN with a lightning arrester of high insertion has Install
<u>in</u>	the JFD "3-IN-I" with the ultr of installations prove the "3-I	ad of a liabifity to your UHF or VHF installation— or low loss compensating coil circuit. Thousands N-P' gives the lowest insertion loss of any strain-relief lips and patented saw-tooth
	washers are exclusive JFD extras Write for Form 210.	
	1	I stainless steel mounting strap
LIGHTNING DRIESTER	Feld 1	
IFD MANUFACTURING CO.		3 For UIF-VIIF open wire
BROOKLYN I. NEW YORK	1 For all UHF or VHF tubular twin leads	2 For VIIF flat twin leads

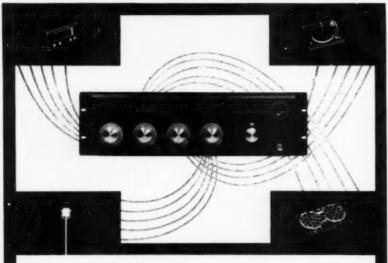

NOW FOR THE FIRST TIME

Mix Any Audio Sources With Plug-In Simplicity

You can do things you have never been able to do before using the Berlant Multichannel Mixer MCM-2. This versatile, four channel, high level mixer will mix any combination of audio inputs and feed any normal or studio line loads.

The built-in power supply makes this an extremely flexible unit, completely independent of any other equipment. Radio stations, recording studios, schools, musicians and users of public address systems will all find this rugged, high quality Multichannel Mixer invaluable.

Write for our bulletin 2JU01

Basic mixer \$137.50. Professional users, net price. BERLANT ASSOCIATES . 4913 W. JEFFERSON BLVD.

LOS ANGELES 16. CALIF.



Examine Free! Greatest Television Repair Book Ever Published

Here is the most complete and up-to-date book on television servicing available today—a book that gives you sure-fire how-to-do-it knowledge of TV repair, installation, maintenance, and troubleshooting.

Whether you're a professional serviceman or a hobbyist, you'll use this thoroughly practical handbook day in and day out to solve every kind of TV problem.

ITELEVISION SERVICING

New 1954 Edition, Completely Revised by Walter H. Buchsbaum

Nowhere else will you find as much detailed, step-by-step guidance on all the latest developments in TV sets—UHF tuners, converters, and late-model antennae large-screen tubes, automatically focused picture tubes, and transistors. The book brings you completely up to date on color, UHF, and special TV applications like industrial TV, theatre TV, and projection systems.



All Newl 2nd **Revised Edition** TRANSISTORS COLOR UHF and LATEST TV CIRCUITS

USE IT 10 DAYS FREE

ı

Coupon at right brings you TELEVI-SION SERVICING for FREE TRIAL for 10 days, without

PARTIAL LIST OF CONTENTS

deo IF alignment-sound channel alignment-aligning RF amplifier, mixer, and oscillator-how to develop a systematic, professional approach that wina customers for you and keeps them satisfied—where to locate the set— how to install antennae—final check-up,

ALIGNMENT AND INSTALLATION.

TROUBLESHOOTING—Six big chapters abow you how to diagnose and correct Inoperative Receiver—Loss of Synchronization — Defective Deflection — Poor Picture Quality—Proor Sound Quality—Proor Cathode Ray Performance. All you decide under which heading it falls, and look up the remedy in the appropriate chapter.

======MAIL THIS COUPON NOW======

PRENTICE-HALL INC., Dept. M-RTN-654 Englewood Cliffs, New Jersey

Send me TELEVISION SERVICING for 10 days' FREE TRIAL. Within 10 days I will return it and owe nothing—or keep it and send \$1.95 down (plus postage) and \$2 monthly for 2 months.

...... Zone.... State..... ■ SAVE! Send \$5.95 with this coupon, and we'll pay postage and packing. Same return privilege and guarantee.

The third microphone, the 21-BR-150, is a medical microphone which possess the ability to detect and register the beat of the human heart. It is intended for teaching and demonstration purposes in medical schools and for research and study applications.

-30-

Spot Radio News

(Continued from page 20)

made in this system for inclusion of simultaneous sound recording or of recording of color television.

RADAR EQUIPMENT, which will tell how successfully broadcasts from longrange transmitters, such as the "Voice of America," are reaching their destinations, was announced recently by the Air Force's Air Research and Development Command Headquarters in Baltimore.

The new setup, coded Cozi (communications zone indicator) was also said to indicate approximately how strong the signals are when they get to their destination, and might also reveal whether an enemy was deliberately jamming that particular frequency with static and interference.

To test a signal, the indicator equipment transmits a radar beam from the station's own antenna. The beam follows the same path taken by the radio waves. The difference, however, is that the Cozi beam comes back and tells where it has been, and often, whether it has run into any interference at its destination. The radar device is made in two units, each about the size of a steamer trunk; one is the transmitter and the other the receiver. In testing, it is necessary to interrupt the broadcast momentarily, while the radar beam is sent out. A reading is obtained instantly, and broadcasting is resumed without any appreciable break or loss of time.

The Air Force said that they intend to make extensive use of Cozi to increase the efficiency and reliability of its world-wide communications system. Interest has also been displayed by Radio Free Europe, and by several commercial radio stations in this country and Canada. It was also reported that several large industrial and shipping groups were studying the practicality of using the new radar system as a standard accessory for long-range, directional radio-broadcasting equipment.

INTERFERENCE has become one of the biggest jobs of the members of the FCC field engineering and monitoring bureau. With some 600,000 transmitters now authorized, it has become difficult enough to see that transmitters do not collide with another. But the field task has been magnified by the accidental or careless release of emissions by a host of new devices and gadgets which use r.f. energy for various non-communication purposes.

In their annual report, the Commis-

sion cited several odd cases of interference that came up during the year. Recently, many other unusual radiation cases have appeared. To illustrate, a resident of Chicago complained about the persistent annoyance to his and other TV receivers in the neighborhood. He was surprised to be told, after investigation, that the source was an electronic door-opening device on his own garage.

Complaints of interference which gave a Massachusetts city "pictureless TV" on one channel resulted in the cause being traced to test equipment in a local radio tube plant; one of the

complainants.

A new TV station which went on the air in San Diego, California, was blamed for spoiling reception from other stations. Inquiry showed that the fault was receiver overloading through the use of high-gain antennas employed by viewers to extend their reception to Los Angeles. Set owners were instructed to use a quarter-wave stub to remedy the trouble.

An investigation extending over many months was required to solve an intermittent TV interference problem in Marion, Mass. The cause was finally proved to be spark-type discharges in the antenna system of a military installation located in that

area.

A report from the Puerto Rico field office illustrated the down-to-earth human relations problems with which the Commission's engineers must deal in the course of their interference investigatory work. The case involved a complaint by a woman that a neighborhood ham station was interfering with the operation of a radio-phono. The amateur involved was elderly and in poor health, and his principal interest was his ham station which had been constructed and serviced for him by several fellow amateurs. Investigation of the ham gear revealed no trouble. And thus the FCC probers went to the home of the complainant. They found that interference was observed in an all-wave set only when it was in the phono position. It was further noted that the antenna consisted of a short length of insulated wire wrapped around a line cord of a very messy electric system. When the an-



A fascinating field! A great future! A good job or independence in a business of your own! TV is growing by leaps and bounds—1227 new communities, 1845 new stations given "go-ahead". Trained men are worth their weight in gold!

COYNE HAS TRAINED MORE SUCCESSFUL MEN

Thousands of successful men trained at COYNE
—the largest, oldest, best-equipped school of its
kind (established 1899). A Coyne-trained man
is a top-trained man. Coyne methods require no
advanced education or previous experience.

TRAINING TAILORED TO MEET YOUR NEEDS

Resident Shop Training—You can learn on real equipment in the Great Shops of Coyne. Learn quickly-easily at Coyne. Practical Technical methquichly-easily at Coyne. Practical Technical method gives practical experience on massive outlay of full-size equipment plus necessary technical traing. Finance Plan whereby you can enroll now and pay most of tuition later. Also Monthly Payment Plan especially designed for K-Vets. If you need part-time work to help out with living expenses while at COYNE, we'll help you get it. Coupon brings FREE BOOK and details.

OR

Coyne Tested Home Training—To those who cannot come to the Coyne shops here in Chicago, we offer modern, up-to-the-minute training designed to meet Coyne standards. Practical, down-to-earth, easy to follow, step-by-step instruction. So practical, you can quickly be earning money in

B. W. COOKE, President FOUNDED 1899

COYNE

A TECHNICAL TRADE INSTITUTE CHARTERED MOT FOR PROFIT SQS S. Pauline Street, Chicago 12, Dept. A4-T R5 ELECTRICIT - RABIS - TELEVISION - REFRISERATION - ELECTRONICS

Television and Radio while learning-personal sureceiving and indice the learning—personal supervision by Coyne Staff—men who know TELE-VISION AND RADIO, AND KNOW HOW TO TEACH IT—and the cost is low—you pay only for training—no costly extras. Send coupon below for Picture Folder and full details, including easy Payment Plan.

MAIL COUPON FOR FREE INFORMATION Mus.

Fill in and mail coupon, TODAY. Check the train-ing you're interested in. If you want information on both, check both. Com-plete details will come by return mail. No cost—No obligation—No salesman / will call.

B. W. COOKE, President COYNE ELECTRICAL SCHOOL 500 S. Paulina Street, Chicago 12 Dept. A4-TR5

Send details of your offer on training checked elow. This does not obligate me and no exterman rill call. I am interested in:

1 ☐ TELEVISION-RADIO HOME TRAINING TELEVISION-RADIO IN COVNE SHOPS

1 City State

Calvert Electronic	SP FOUNT OR OR	ORTH AVENUE YORK 3, N. Y.	INDIVIDUALLY BOXED STANDARD BRANDS GUARANTEED
185	7	2 1.75 1010—W. 6 5.95 1011—W.	E99 856A 1,19 E99 884 1,25 884 1,



They're small in size! They provide flexibility! They offer positive protection!

Dependability that gives you confidence. Flexibility that helps you do a better job! These are things you can count on getting in Centralab's new PA-1000 Series. See for yourself:

You got high-strength, high-resin, laminated phenolic insulation that exceeds Phenolic Standards Grade XXX.

You get one-piece shaft construction for accurate indexing. Adjustable stop permits selection of positions or continuous rotation (11 active positions, 1 off-position).

You get steatite spacers with nickelplated brass shafts, bushings, tierods, and nuts. All other metal parts are treated to pass 50-hour salt-spray test — a must for applications in a humid or salt atmosphere.

You can get complete switches or separate miniature phenolic sections, index assemblies, hardware, and accessories.

That's only part of the PA-1000 story. Get it all — send coupon for Centralab catalog sheet 28-1.

Then order Centralab Miniature Phenolic Rotary Switches from your Centralab distributor.

Centralab

CENTRALAB, A Division of Globe-Union Inc. 910F E. Keefe Ave., Milwaukee, Wisconsin
Send me Centralab catalog sheet 28-1.
Name
Company
Address
CityZoneState

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of construction permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

STATE	CITY	CALL	CHANNEL	FREQUENCY (msc.)	POWER*
Alabama North Dakota	Montgomery Grand Forks	WSFA KNOX-TV	12 10	204-210 192-198	316
South Carolina	Charleston	WUSN-TV	2	54-60	54.2
Texas Vermont	El Paso Montpelier	KELP-TV WMVT	13	210-216 60-66	49 18.3
Washington Wisconsin	Spokane Green Bay	KREM†	5	54-60 76-82	100

NEW CALL LETTER ASSIGNMENTS

Arkenses	Hot Springs	KTVR	9	186-192	
California	El Centro	KELB	16	482-488	
**	Stockton	KHOF	16 13	210-216	
Florida	Clearwater	WPGT	32	578-584	
Georgia	Macon	WNEX-TV	47	668-674	
Massachusetts	New Bedford	WTEV-TV	28	554-560	
Minnesota	Hibbing	KHTV	10	192-198	
New York	Bloomingdala	WBLD	5	76-82	
**	Syracuse	WHEN-TV	8	180-186	
Oklahoma	Tules	KSPG	17	488-494	
Pennsylvania	Sharon	WSHA	39	620-626	
South Carolina	Spartanburg	WSPA-TV	7	174-180	
Texas	Tyler	KLTV	7	174-180	
Wisconsin	LaCrosse	WTLB	38	614-620	

*ERP = (effective radiated power, kw.). = Call letters to be announced †=Temporary call letters.

tenna was unwrapped from the line cord and the line plug reversed, the interference ceased.

Some time later, however, another report was received from the same complainant. This time the agitated lady claimed that whenever she put her hand near the radio-phono pickup to change records, the amateur's voice would break through. This phenomena, she raged, was making her nervous and affecting her health. The investigating engineer discovered that the latest apparition was due to pickup in the phono-pickup leads. So he devised a wavetrap which eliminated the woman's haunt, and the amateur could continue to operate his station, which ac-

cording to him . . . "made life worth living."

FOR THE FIRST TIME since the Commission began processing of new applications for TV stations, the boys are out of the woods, at least for all practical purposes.

Hearings are now being scheduled as quickly as the respective applications in a particular city are in a position to be designated for hearing. Technically, said the Commission, applications will hereafter be considered chronologically, and the temporary processing procedure and city-priority listings will be discontinued.

Notwithstanding the cleaned-up slate,

NEW TV STATIONS ON THE AIR

(As of May 25, 1954)

The following new stations bring the lists published in previous issues up to date.

STATE, CITY	STATION	CHANNEL	RANGE (IN MC.)	WAVELENGTH (IN FT.)	POWER*
California Sacramento	KBIE-TV	46	662-668	1.49	207
Florida Orlando	WDBO-TV	6	82-88	11.8	100
Maine Portland	WGAN-TV	13	210-216	4.65	239
New York Kingston	WKNY-TV	66	782-788	1.26	21.4
Tennessee Chattanooga	WDEF-TV	12	204-210	4.79	105.2
Wisconsin Madison	WHA-TV	21	512-518	1.92	10.7
Canada Hamilton, Ont.	CHCH-TV	11	198-204	4.93	42.9
KETX, channel 19 channel 48, Oshko				ws, Virginia; and V	VOSH-TV,

The frequency of the video carrier = 1.25 + channel lower freq. limit. Total number of TV stations now on the air in U.S.: 384 (135 of which are u.h.f.). †Educational. *From Station CP application.

comparatively few station grants are being issued, because of hearing extensions, and delayed interest of many, awaiting the outcome of the Congressional investigation.

At this writing, channel assignments shown on page 98 have been made.

ONE OF THE MOST IMPORTANT anniversaries, of concern to every scientist in this country was celebrated in mid-Spring. The date . . . April 10 . . and the occasion, truly the birthday of American industrial progress. On that date, in 1790, George Washington signed the bill that established our patent system, which introduced a new era and sparked so many great inventions.

When Lee de Forest took the Edison effect, in a light bulb, and converted it into a tube, he probably little realized that he would live to see the day of our modern electronic industry, built up through a chain of ingenious inventions, protected by patents.

Certainly, April 10 is a memorable date that all should remember. . . L.W.

PACIFIC ARRL MEET

THE Santa Clara County Amateur Ra-dio Assn. is sponsoring the Pacific Div-ision ARRL convention in San Jose, California, July 3, 4, and 5.

The program for the first two days will be held in the Municipal Auditorium in San Jose with the last day devoted to outdoor activities. Harry Engwicht, W6HC, is chairman.



18 monthly payments of \$8.00

Cash price \$149.95 Now for the first time, a crystal

filter, an S-Meter, choice of electrical bandspread on amateur or SWL bands, an RF stage and 2 IF stages.

Write, wire, phone or visit either store today.

PRACTICAL, NEW, LARGE

Cash Monthly Cash

Down Payments Price

\$5.00 \$2.61 \$49.95

12.00 6.54 119.95

20.00 10.89 199.95

NC-183D 40.00 21.77 399.50

HRO-60 54.00 29.00 533.50

NC-88

NC-125



We Give... LONG LONG TRADES **LOW LOW TERMS** 10 DAY TRIAL FAST PERSONAL SERVICE

We WANT you to be SATISFIED

Ask any Ham about Henry We have All National Receivers in stock for immediate delivery, also National parts.





RADIO & TV Manuals

Nation Walliams

Your complete source for all needed RABIO and TV diagrams and service data. Most amazing values. Still sold at pre-Korean prices. Only \$2 to \$2 per volume. Every Radio manual contains large schematics, all needed alignment facts, parts lists, voltage values, trimmers, dial stringing, and service hints. Each TV volume is a practical treatise on servicing a full year's sets, with giant blueprints, was-forms, hints, alignment and voltage charts, production changes. See coupon at right for a complete list of those low-priced Sugreeme service manuals.

Supreme Publications

Sold by all Leading Parts Jobbers

Radio Diagram Manuci

1953 Radio Manual, \$2 1952 Radio 1951 Diagrams | EAC 1950 Manual (\$2.5 1949 Radio 1948 | PRICED AT ONLY | S 2

EACH

New TELEVISION COURSE

Amazing Bargain. Complete. Only \$3

COVERS EVERYTHING IN TV

Let these course lessons take you into TV servicing the easy way. The very first lesson of this sensational course tells how to do simple repairs. You can start earning money immediately. Second lesson tells you what of this sericational course tells how to do
simple replairs. You can start carning motes
immediately. Second lesson tells you what
is wrone, by just looking at the picture—
no instruments used. Lesson 4 has 32 large,
8½ x 11° gages and 28 large illustrations on
practical antenna installations and improvements, Another 12 lessons deal with troubleshooting, stagger-tuned I.F. alignment, intercarrier sets, UHF converters, use of TV
test equipment, picture analysis, new circuits.
TV facts that puzzled you will be quichly
cleared up. You will find you-relf doing TV
repairs in minute— instantly finding faults
or making needed adjustments. Most amazin bour own home. Look over this collection
of material, read a few lessons, apply some
of the hints. Then decide to keep the lessons
at the bargain cost of 31 full pictor, or return the material. Money back guaranteed.

PRACTICAL, NEW, LARGE Here is your complete training in television servicing. Amazing value at only \$3, complete. These new lessons cover every fact, adjustment and repair of all types and makes of TV receivers. Giant in size, mammoth in scope, just like other correspondence courses selling for over \$150.00. Our amazing offer permits you to obtain the course complete for only \$3 nothing else to pay. Easy-to-follow, well illustrated lessons on circuits, picture faults, adjustments, short cuts, about trouble-shooting, service hints, how to use test equipment, and many practical sections prepared by leading manufacturers. Just published. Send trial counon today and use the complete TV course at our risk, Satisfaction guaranteed, Your price for all lessons in large manual form, complete, postpaid, only \$3. Send trial-coupon now, NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 1760 Balsam Rd., Highland Park, I	k, IL	Park	yhland	d., Hig	iam R	Bal	1760	5,	DNS	TK	CA	ш	UE	P	ME	RΕ	P	U
---	-------	------	--------	---------	-------	-----	------	----	-----	----	----	---	----	---	----	----	---	---

	ATIONS, 1760 Balsam Rd., Highland Park, ILL
	Rush today TV manuals checked below and Radio manuals at left. Satisfaction guaranteed.
.50	Hadio manuals at left. Satisfaction guaranteed.
H	. Letest 1954 Television Servicing Manual, only , , \$3.
	1953 TV Manual, \$3. 1963 UHF Units, \$1.50
0	
	1950 Television Manual, \$3. 1949 TV, \$3.
Y	☐ 1948 TV, \$3. ☐ 1947 TV & FM, only \$2.
	☐ I am enclosing \$ Send postpaid.
	☐ Send C.O.D. I am enclosing \$ deposit.

Most - Often - Novded

1954

Television



International Short-Wave

(Continued from page 65)

Cuba—CMAS, 5.780, heard relaying program from Hollywood recently 1745. (Cody, Ireland) Santiago, 8.955, noted closing in Spanish-English 0030. (Barnard, Calif.)

Cyprus-Limassol noted on 6.790 at 2304 with news in Arabic, good level; weaker on 6.125, 6.170 in parallel. (Cox. Dela.) Heard on 9.650 at poor level 1025. (Barnard, Calif.)

Czechoslovakia-Radio Prague, 9.504, noted 1400 with English for Europe. (Sawyer, Ont.) On 7.255 to North America 1930. (Esser, Sexton, Pa.; Haycock, N. J.) Has repeat 2305 over 9.550. (Greco, N. Y.)

Denmark-OZF7, 15.165, heard opening 0400 with Town Hall chimes, anthem. (Pearce, England)

Dominican Republic-HI2T, 9.727A, noted in Spanish 1815-1830 with good music. (Rugel, Kans.) HIG, 9.590A, noted at good level in Spanish. (Barnard. Calif.)

Ecuador - HC2LT has moved to 6.885A from listed 6.795; generally good around 2200. (Hill, N. H.) HCJB, 11.915, noted 2100 with religious session in English, good level. (Sicks, Ore.) Heard on 9.743A at 0000 with German session. (Calos, Calif.)

Egypt-Radio Cairo, 9.475, noted in news session 1330-1340. (Leake, N. J.; Golden, Mass.) Heard on 15.315 ending English news 0840, then continuing with Eastern music. (Ferguson, N. C.) Arabic Service noted on 12.030, 7.060 around 0000-0200. (Cushen, N. Z.) At 1100 on 11.965 and near 7.035; another day at 1040 near 9.740; another day around 1400 near 7.060. (Pearce, Eng-

Ethiopia - Radio Addis Ababa, 15.054A, weekdays has news 1315. (Pearce, England) Noted with recordings Sun. around 1400-1430 close, widely heard in USA. (West, Va.; Sutton, O.; Huttemeyer, N. J., others)

Fiji Islands - ZJV3, 3.980, noted 0615 with music. (Sanderson, Australia) Has newscast 0400. (Morgan, Calif.; Saylor, Va.)

Finland - Helsinki, 15.190, heard opening 0430 with news in French, then news in English 0445. (Pearce, England) Should have news for America 0600 now.

France-Paris, 15.295A, noted opening 0820A with "La Marseillaise." (Silverman, N. Y.) Is using 7.220 for "French by Radio" 0245. (ISWC, London) Noted on 15.100 around 1030-1045. (Stark, Texas)

French Africa - Brazzaville, 9.440, good level in news 1745. (Grace, Conn.) Heard with English 1400 over 15.595. (Cox, Dela.)

French Guiana - Radio Cayenne, 6.232A, noted around 1730-1830 when closes with "La Marseillaise." (Swayer, Ont., others)

French W. Africa-Dakar, 11.894A, noted 1500 with news in French. (Pearce, England) The 9.562 outlet is



steel storage cabinets perfect for storing easily-lost small parts like condensors, small tubes, switches, nuts and bolts! Precision-made, finished in durable two-tone green enamel, complete with card holder. Available at your dealer's in two sizes—42c ea. in the small size (illus.), \$1.28 for the large.

EASY TO ASSEMBLE *Units interlock rigidly at top, bottom, sides to fit any space. SOME DEALERSHIPS OPEN

*Once again, enough steel is available to make Multi-Drawers available to new dealers! Write today.

THE CINCINNATI VENTILATING CO. INC.



- Measures actual picture signal strength, Indicates proper antenna orientation. Checks local oscillator radiation. Checks for interference. Aligns and Checks TV Booster efficiency, Ideal for antenna comparison tests

A MUST for any serviceman or installer! Location survey easily accomplished without the expense of complete TV receiver installation, reducing actual work to a one man operation. Eliminates guess work in determining type of antenna required at a given location.

Dial scale 30-20,000 and 30-500 microvolts. Incorporates a 12 channel VHF high gain Standard coil turret funer to which strips can be easily added for any UHF channel. Complete ready to use with operating instructions, circuit diagram, and all tubes included. Self contained power supply for 105-125 volts 60 cycles AC.

Rugged gray steel case with extra sturdy carrying handle. Size 8 x 10 x 12". Wt. 25 lbs.

	5C14.	Brand	New	and G	uaranteed.	\$47.4
	BUR	STE	N-	APP	LEBE	CO.
11	112-1	4 McG	e St.	, Kan	as City	i, Me.
10	Send	me	350	14. 5		enclosed.
Ne	me		**********		**************************************	
1 44	dress.			*********		nio-minimes
Cit	y				State	************

widely heard with English 1715-1730 on Mon., Wed., Fri., Sat.; Portuguese that time Tue., Thur. (Esser, Pa., others)

Germany—Cologne, 15.275, noted closing 0830 with announcements in German, English, French in beam to Far East; said 11.795 was parallel. (Silverman, N. Y.) This transmission heard opening 0530 on 11.795. (Pearce, England) Noted some days around 1315 on 11.795. (Niblack, Ind.) Radio Liberation, Munich, now uses 6.055, 6.175, 7.130. (ISWC, London) Home Service noted from NWDR, 6.075, Hamburg, at 1750 with classical music, announcements in German by man. (Bellington, N. Y.)

Greece—Athens, 9.607, has news in French 1230, in English 1245. Forces Station, Athens, near 7.420, noted 0730 with Greek Songs, and closing 1700 with Greek National Anthem. (Pearce,

England)

Guatemala—TGTN, 5.970, noted with Spanish music 2230-2300. (Middleton, O.) TGNC, 9.668, is good in English session 2200-2345. (Klein, Va.; Sexton, Pa.) And parallel over TGNC, 11.850. (de Neuf, N. Y.)

Guadeloupe—FGHAA, 6.066A, Basse-Terre, noted 1815 in French with QRM from XEXE, Mexico (Cox, Dela.) Poor level 1730 in heavy CWQRM. (Barnard,

Calif.)

Haiti—Radio Citadelle, 4VWA, 6.153AV, Cap Haitien, noted 1900 when identified in French. (Niblack, Ind.) 4VC, 9.485, is excellent around 1730. (Middleton, O.) 4VEH is using 9.658A mornings and 9.675 (Sun., Mon.) evenings EST. (West, Va.) 4VCP operates on 6.365, has French news 1850. (La Radio Mondiale, France)

Hawaii—VOA relay, 6.195, good in oriental languages 0630-0700. (Roberts,

Conn.

Holland—Hilversum noted on 6.025 at 1630-1710 at fair level in English. (Parsons, Pa.)

Honduras—HRN, 5.885, good nightly, best around 2000-2100. (Pearce, Ill.)

Hong-Kong—ZBW3, 9.525, heard 0600 with BBC news relay, then music. (Sanderson, Australia) Heard opening 0400 now—one hour earlier than formerly. (Balbi, Calif.)

Hungary—Budapest, 9.833, noted relaying Moscow from 1400. (Sawyer, Ont.) Heard on 6.248 with news 1500.

(Sutton, O.)

Iceland-TFJ, 15.175, Reykjavik, is heard Sun. (only) at good strength

1115-1130. (ISWL, England)

India—AIR, 5.990, noted with news and music; on 9.755 at 1930 with news; at 2030 with news on 11.870. (Sanderson, Australia) English news session ow are 1930-1940, 11.950, 9.755; 2310-2320, 15.130, 11.870; 0235-0245, 17.740, 15.380; 0835-0845, 11.960, 9.565; 1045-1055, 15.380, 11.920.

Indo-China (Vietnam)—Radio France-Asie, 15.420, noted 0430 with English program of music and news.

(Sanderson, Australia)

Iran—EQO, 3.786A, Teheran, is strong in New Zealand with French 1500, English news 1515-1530 close-

BUY DIRECT OUTSTANDING FOR HIGH FIDELITY!


AUDIO PRODUCTS CO.

NOW!...wih AFC

Callins Audia Products Ea is in on way

RECEIVERS

Each Collins Tuner Kit is complete with punched chassis, tubes, power transformer, power supply components, hardware, dial assembly, tuning eye, knobs, wire, etc., as well as the completed sub-assemblies: FM tuning units, AM tuning units, if amplifiers, etc., where applicable. All sub-assemblies wired, tested and aligned at the factory make Collins Pre-Fab Kits day to assemble even without technical knowledge. The end result is a fine, high quality, high fidelity instrument at often less than half the cost — because you helped make it and bought it direct from the factory.

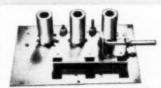

FMF-3 Tuning Unit \$1525

with AFC \$18.75
The best for FM. The most sensitive and most selective type of "front end" on the market. 6 to 10 microvolts sensitivity. Image ratio 500 to 1. 616 tuned RF stage, 6AG5 converter, 6C4 concillator. Permeability tuned, stable and drift-free. Chassis plate measures 6½"x4½". In combination with the IF-6 amplifier, the highest order of sensitivity on FM can be attained. Tubes included as well as schematic and instructions. Draws 30 ma. Shipping weight FMF-3: 2½ lbs. Dial available @ \$3.85.

IF-6 Amplifier 6 Tubes. Shipping Wgt. 3 lbs. \$1975


FOR USERS OF COLLINS TUNERS

Receive \$5.00 credit toward the new FMF-3A front end! Mail us your old front end with \$13.75 and we will send you the new, improved FMF-3A with A.F.C., or, remit the full amount of \$18.75 and when we receive your old unit in return a check will be mailed you for \$5.00.



AM-4 Tuning Unit

Tops in AM superhet performance! A 3-gang tuning condenser gives 3 tuned stages with high sensitivity and selectivity. Assembly is completely wired, ested and aligned ready for immediate use. Frequency coverage 540 KC to 1650 KC at a sensitivity of 5 microvolts. Tubes 68A6 RF amplifier; 68E6 converter; 68A6 IF amplifier and 6AT6 detector. Draws 30 ma @ 220 volts. Mounts on a chassis plate measuring 4'x7'8'6. Shipping weight 2½ lbs. Dial available at \$3.85.

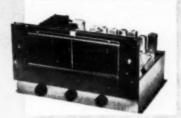


FM Tuner Kit

\$55

with AFC \$58.50

The FM-11 tuner is available in kit form with the IF Amplifier mounted in the chassis, wired only tested by us. You mount the completed RF Tuning Unit and power supply, then after some simple wiring, it's all set to operate. 11 tubes: 836 RF, cmp, 6AG5 converter, 6C4 oscillator, 6RA6 1st IF, (2) 6AU6 2nd and 3rd IF, (2) 6AU6 limiters, 6AL5 distriminator, 6AL7-GT double tuning eye, 5Y3-GT rectifier. Sensitivity 6 to 10 microvolfs, test then 1/2 of 1% distortion, 20 to 20,000 cycle response with 2DB variation. Chassis dimensions: 12½" wide, 8" deep, 7" high. Illustrated manual supplied. Shipping weight 14 lbs.

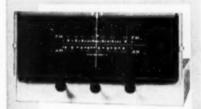

FM/AM Tuner Kit

\$7750

The original 15 tube deluxe FM/AM pre-fub kit redesigned on a smaller charsis. The tuner new measures 14" wide by 12" deep by 7½" high. This attractive new front and dial assembly opens up new applications where space is at a premium. Kit includes everything necessary to put it into operation—punched chastis, tubes, wired and digned components, power supply, hardware, etc. Kit comprises FMF-3 tuning unit, 15-6 amplifier, AM-4 AM tuning unit, magic

eye assembly and complete instructions. All tubes included. Shipping weight 19 lbs.

MAIL COUPON TODAY

To Collins Audio Producto Co Inc. RN-6 P O Box 364, Westfield, N. J. Tol. WEstfield 2-4390

☐ FM Tuner Kit ☐ FA	AM Tuner Kil	FMF-3 Tuning Un
[] with AFC	with AFC	with AFC
☐ IF-6 Amplifier	□ AM-4	Tuning Unit

STATE

			o seinor.	
DORESS		,		
TY				

Amount for Kit \$ See weights, add shipping cost \$...

WHEN YOU THINK OF TUNERS, THINK OF COLLINS AUDIO PRODUCTS



LIFETIME TAPE

is the ONLY

magnetic tape equal to this critical application"



That's what Dubbings Company, Inc., say of Soundcraft's LIFETIME Magnetic Recording tape. These nationally known specialists in the hi-fi field chose LIFETIME Tape for their new 15-minute test reels.

These amazing test reels accurately measure your tape recorder's wow and flutter, head azimuth alignment, frequency response, signal-to-noise ratio, signal level, tape speed. After exhaustive study of every available tape, Dubbings found that only LIFETIME was equal to the job.

And that's why you, too, should choose LIFETIME Tape for your critical applications. More and more radio, TV and recording studios insist on LIFETIME Tape for its strength; freedom from stretch and shrink despite temperature and humidity, permanence and high fidelity. Remember, LIFETIME Tape is guaranteed for a lifetime! Make your own test today!

REEVES SOUNDCRAFT CORP.

Dept. U6

10 East 52nd St., New York 22, N.Y.

"RACON" Radial Horn Famous Double Re-Entrant Type



(Med. \$8-35R) proof aluming tors, 360° H acoust, path), 179 BRAND NEW (List \$18.95

"KIMSUL" ACOUSTICAL CABINET LINING 1" thick, 16" wide. Per running yard...... 1.75 MC-211 RIGHT ANGLE DRIVE UNIT-en. 39c 6/1.96 50 WATT ADJUSTABLE RESISTOR, 125 ohms-WATT RHEOSTATS (IRC) . . . 15 ob WATT POTS . . . 100, 250 or 350 ohms—
es. 89c; 3/2.49 CRYSTAL MICROPHONE, Hi-fidelity, Ruider shock-mid, 134" x b4". Less b

XMAS IN JUNE !!

KITS!! KITS!! KITS!! A BARGAIN FOR EVERYONE!!!

RELAYS includes multi-contact & midget keying
types. SPECIAL! S assid 2.49
RF-ANTENNA-OSCILL. COILS std. b'cast & SW.
RADIO-TV BUILDERS LIBRARY for Students,
Hitel. Stille States. Park 1/1 Lty Military.
RADIO-TV SUILDERS LIBRARY for Students,
Hams, Servicers 25 assid. Radio & TV schematics.
Inel. Photofacts
Hier, Filliannacia
TUBE SOCKETS wafer, 4 to 8 pin. 12 asstd49
EXPERIMENTAL TUBES for Test, Research.
Schools, Fil. tested, Kit 40 asaid, revg. types 1.98
Schools, bit tested. But to seed, tive, tipes
RADIO HARDWARE TREASURE FULL LB. CAN of
Nuts. Screws, Washers, Lugs, etc 3 lbs. /2.49
MOULDED BANKLITE CONDENSERS 50mmf to
MOULDED BANKLITE CONDENSERS SOUTH
.2mfd, 200-600V.Micamold. Kit 50 anntd 1.98
100 asntd. 2.98
At Micco Manualty Description 19711
ALNICO MAGNETS Powerful Bar, Block, "U",



RADIO CORP.

ROUND, SQUARE, KEY and "D" OPENINGS QUICKLY MADE with Greenlee Radio Chassis Punches



Save hours of hard, tedious work . . . cut accurate holes in chassis for sockets, plugs, controls, meters, panel lights, etc. with GREENLEE Punches. In 1-1/2 minutes or less make a smooth hole in metal, bakelite or hard

rubber up to 1/16" thick. Easy to operate . . . simply turn with ordinary wrench. Wide range of sizes. Write for details. Greenlee Tool Co., 1886 Columbia Avenue, Rockford, Ill.

down. (Cushen) Johansson, Sweden. says noted with native and Western music 1300-1445 on 6.155, 9.680, 3.850. Eriksson, Sweden, says English 1515-1530 closedown is noted over 6.155. 9.680.

Iraq-Baghdad is now on 11.705. (Cushen, N. Z.) Noted by Collett, N. Z., opening 2330 with chirping of bird identification; has severe interference from Moscow from 0045; closes 0205. (Radio Australia)

Israel-Tel Aviv, 9.010A, noted in English 1615-1700 closedown. (Leake, N. J.) Heard with news 1515. (Welch, Mass.) Forces Station, listed 6.725, noted nearer 6.705 at 1445 with dance recordings, closing 1500 with "Lights Out" (bugle). (Pearce, England)

Italy-Rome, 9.570A, noted 1920-1935 with news, steady level. (Howard, Fla.) With French 1935-1945A. (Grace, Conn.) Lately, 9.780 has been noted in parallel. (Ferguson, N. C., others) Heard opening 0540 to Far East on 17.800, 15.400, 15.120. (Pearce, England) Noted on 7.290 at 2150 with news. (Bigley, Pa.)

Jamaica-Radio Jamaica, 3.360, noted closing 2308 with "God Save the Queen." (Bellington, N. Y.)

Japan-The first commercial shortwave station in Japan is expected to be on the air from "Nippon Tanpa Hoso" (Japanese Shortwave Broadcasting Co.) in July; will use JOZ, 3.925, 5 kw., and JOZ2, 6.095, 5 kw.; programs will include educational features sponsored by Japanese Ministry of Education; studios, transmitters are in Tokyo. (Wada, Japan, others) Tokyo noted on 9.695 at 0005-0100. (McDonald, Calif.) And then 0200 with news. (Kahan, Calif.)

Luxembourg - Radio Luxembourg, 6.090, noted around 1530 and later. (Sawyer, Ont.)

Madagascar-Radio Tananarive, 9.515, noted at weak strength 2300 in French. (Cox. Dela.)

Malaya-BFEBS, Singapore, noted opening 0415 on 15.435, 11.820, news 0415. Heard on 7.120, 9.690 at 1045 with BBC sports relay. (Cooper, Morgan, Calif.) Heard on 11.820 at 0800 with BBC news relay. (Sawyer, Ont.) The 11.955 outlet is again heard to 0930 closedown. (Stark, Texas, others)

Radio Malaya, 7.200, Singapore, noted 0630 with musical selections, then stock quotations. (Sanderson, Australia) Kuala Lumpur, 6.025, is good level 0630. (Christie, Calif.) Forces Station, Singapore, noted on 5.010A at 0745 with native music, man in Fijian; weak level. (Morgan, Calif.)

Monaco-Radio Monte Carlo, 7.349, noted daily around 1515-1730A signoff; fair level, mostly French, sometimes with English. (Levy, N. Y.) Noted on 6.03A at 1815-1845 in French. (Winthrop, N. C.)

Mozambique-The English request session from 2300 is noted over 3.480 parallel 11.742A, 4.916A. (Morgan, Balbi, Calif., others)

New Caledonia-Radio Noumea. 6.028A, noted opening 0200, good level but with interference from AFRS out-



BOOKS for Servicemen Amateurs

Experimenters

RADIO . T.V. . AUDIO . ELECTRONICS

New!

201. PRACTICAL TV ENGINEERING. By Scott Helt, New 2nd Ed. A definitive work with new chapters on color, u.h.f., and v.h.f. Mig. and sales engineers, broadcast engineers, students, and tech workers will all find this book an invaluable aid to a thorough understanding of this booming medium. 730 pages.

37.50

228. TELEVISION SERVICING. By Walter H. Buchabaum. This gives clear simple instructions on the installation and maintenance of every type of TV receiver . . . shows you how to locate and repair every conceivable trouble a TV set can have . . offers the latest information on the design and construction of TV receivers. It also devotes an entire, new chapter to color television, showing exactly how color TV receivers differ from blackand-white receivers.

229. TECHNIQUES OF TELEVISION PRODUCTION. By Rudy Bretz. This is a comprehensive handbook for the studio engineer and technician, covering all of the equipment and materials used in producing television programs. It deals with in producing television programs. It deals with the television cameraman, cameras, and camera handling; TV lenses; cutting; switching equip-ment; technical limitations and the production problems involved; graphic materials; projection equipment; mirrors and prisms; composite shots and the illusion of space; special effects with graphic materials; studio effects; electronic effects; television scenery, make-up, and lighting; audio problems in TV; and remote pickups. 464 pages. \$10.00

230. THE RADIO MANUAL, Fourth Edition. By George E. Sterling and Robert B. Monroe. No other single volume now available covers the entire field of radio so thoroughly-from elementary electrical and radio theory to the most advanced applications in AM, FM, and Television Broad-casting, Marine Radio, and Marine Navigational Aids, Emergency Services, State, Federal and International Laws. 820 pages.

232. RADIO TROUBLE SHOOTING GUIDEBOOK, 232. RADIO TROUBLE SHOOTING GUIDEBOON, vol. 1. By John F. Rider and J. R. Johnson. A troubleshooting guidebook that covers AM, FM, troubleshooting, undesired signals, weak signals, distortion, noise, dead receivers. 140 pages. 5½ x distortion, noise, dead receivers. 140 pages. 5½ x 32.40

205. HOW TO TROUBLESHOOT A TV RECEIVER. By J. Richard Johnson. A step by step guide for newcomers. \$1.80

206. UHF TELEVISION ANTENNAS AND CONVERTERS. By A. Lytel. Latest information on all types, covers latest UHF installation techniques. \$1.80



233. TV TROUBLESHOOTING AND REPAIR GUIDE-233. TV TROUBLESHOOTING AND REPAIR GUIDE-BOOK, vel. 2. By Robert G. Middleton. A gold mine of valuable TV service information. Trouble-shooting front ends; Servicing the Video. I-F strips; Faults in video amplifiers; Trouble analysis in sound I-F and detector systems: Practical pointers in audio amplifier servicing; Trouble it horizontal circuits. 160 pages. 8½ x 12. Paper covered.

Price \$3.30

234. THE RADIO AMATEUR'S HANDBOOK. Compiled by the American Radio Relay League staff. 800 pages, including catalog section. Price \$3.00

235. THE SATURDAY REVIEW HOME BOOK OF RECORDED MUSIC AND SOUND REPRODUCTION. By Edward Tarnall Canby, C. G. Burke, and Irring Kolodin. Here is complete, specific information on how to get the most out of improved equipment, how to choose among the wealth of neverordings offered, and how to get the ultimate in list-ning pleasure out of your collection. \$4.59

236. HEARING AIDS, THEIR USE, CARE, AND REPAIR. By M. Mandl. Provides information needed by users, prospective purchasers, dealers and servicemen. 90 illus. 158 pages. \$3.50

208. MODERN OSCILLOSCOPES AND THEIR USES. By Jacob H. Ruiter, Jr., 360 pages, 370 illus.

209. ESSENTIALS OF RADIO. By Sluraberg & \$6.75

211. INDUSTRIAL ELECTRONICS: An Introduction to Modern Industrial Electronic Practice. By Dr. R. Kretzman. \$5.50

224. RADIO DATA CHARTS. By R. T. Beatty. Charts required in the design of radio receivers cover such items as frequency, wavelength, inductance, capacity, frequency, self-inductance, r.f. coil windings, reactance of coils or condensers, trans former design, choke and transformer design. The only equipment necessary to utilize any of nomograms is a straightedge.

new!

4th Edition

225. TELEVISION SIMPLIFIED. By Milton S. Kiver. The most up-to-date, complete, and prac-

tical television handbook now available for repair men, radio workers and all who are interested in the practical opportuni-ties a working knowledge affords. Basic principles are ex-plained in language free of involved theory or mathematics from the analysis of circuits and operating fundamentals of

frequency modulation to the repairing of television sets and the explanation of an actual trouble shooting system

226. TELEVISION AND FM RECEIVER SERVICING. By Milton S. Kiver. New, third edition of this famous definitive text. Explanatory material is offered freely so that the student or novice technician may derive maximum benefit from this text. Eighteen chapters cover antennas, TV receiver installation, TV test equipment, r.f. stages, video i.f. and detector stages, video amplifiers, and a.g.c. systems, CR picture tubes, servicing intercarrier receivers, using TV test patterns, deflection systems, etc. Service technicians who have come to depend on Kiver as reference will welcome this \$4.20 new volume

A GREAT BARGAIN

227. TELEVISION REPAIR MAN'S TUBE LOCA-TION GUIDE. By William Prior, Jr. Almost every known make of set including over 4000 models are covered with tube location diagrams. Put it in your service kit, in your shop, in the home. Up to date



216. A GUIDE TO AUDIO RE-PRODUCTION. By David Fidel-man. An A to Z explanation of the reproduction of sound. Dis-cusses all phases of systems and requirements plus design, conrequirements plus design, construction, assembly, and testing of systems and components. Explains in detail the circuitry of preamplifiers and amplifiers; complete discussion of phono cartridges, tuners.



microphones, loudspeakers and enclosures. For the radio and TV service technician, engineer and ex-perimenter. Companion volume to Weiler's High Fidelity Simplified. 250 pages.

217. HIGH FIDELITY TECHNIQUES. By John H. Newitt. For the engineer, home builder of audio gear, service technician, studio personnel and professionals in the audio field. 12 chapts. in easy to read language.

218. RECORDING AND REPRODUCTION OF SOUND, 2nd Ed. By Oliver Read. A complete presentation of the entire subject of sound. Discusses modern theory and methods used in the recording and reproduction of sound, based upon years of experience and research. Includes charts and Appendix. 810 pages.

220. ELEMENTS OF SOUND RECORDING. By Frayne and Wolle. Covers everything in sound recording from the nature of sound to stereophonic recording. \$9.50

recording. 37.50
221. HiGH FIDELITY SIMPLIFIED, 4th Ed. By Harold D. Weiler. A non-technical explanation of hi-fi techniques and the necessary components which constitute a hi-fi system. Covers the latest tape recorders and the newest types of enclosures and speaker systems. 208 plates. \$2.50

HOME MUSIC SYSTEMS. By Edward T.
y. How to assemble parts at greatest sav-222. H Canby. ings

193.

223. HIGH FIDELITY HANDSOOK. By Greene, Radcliffe and Scharff. A virtual encyclopedia of step by step instructions, hundreds of diagrams that make it easy, inexpensive to select, install, assemble, and enjoy your own HI-FI system for records, tape. FM, AM, TV. Expert guidance in layman's language.

34.50

FOR THE YOUNG READER

231. ALL ABOUT RADIO AND TELEVISION. By Jack Gould, Radio and Television Editor. The New York Times. The how and why of radio and television are explained clearly and directly in simple language and with over 100 illustrations and diagrams. It shows how a picture is changed into electricity, how to build a foxhole radio, why we have networks, how to communicate with the moon by radar. 166 pages. 634 x 91/8.



Your Radio & TV News Book Service will attempt to procure any book in this field for you. Just send title, author and price.

MAIL		
MINIE	11113	POR

RADIO &	TELEVISION	NEWS BOO	K SERVICE,	Dept. Ré
201 East	57th Street,	New York	22, N. Y.	

I enclose \$	for which	n please ship por	stpaid books	circled or indicated
below. If not satis	fied I can retur	n them within 5	days for ref	und.

201 205 206 208 209 211 216 217 218 220 221 222 224 225 226 227 228 229 230 231 232 233 234 235 236

Any book not listed.....

Address

ALL ORDERS SHIPPED POSTPAID. Sorry, no COD's. Add 3% sales tax with orders for N. Y. C. delivery; add 25¢ per title for delivery outside U.S.A., except for APO's.



Plugged In for Easy Replacement

Polarized for Correct Positioning

Still Can Be Soldered In The Set

Available In All Sizes.
Write for Further Information.

When buying selenium rectifiers be sure to specify "PLUG-INS" ... they cost no more.

New 72-page Selenium Rectifier Handbook Available. Latest Engineering Information. Send For Your Copy. Price \$1.00.



RECTIFIER DIVISION

Dept. R-3, 415 N. College Ave., Bloomington, Ind In Canada - 50 St Clair Ave. N W., Toronto let on 6.040; closes 0535. (Sawyer, Ont.; Morgan, Christie, Calif.) Heard on 3.375 at 0530 with news in French, music. (Sanderson, Australia)

New Zealand—Revised summer schedules of Radio New Zealand include 1300-1545, 9.520; 1600-2345, 11.830; 0000-close, 9.520 to Australia. At 1300-1545, 9.540; 1600-2345, 11.780; 0000-to close, 9.540 to the Pacific Islands; close is 0545 weekdays, 0620 Sat., 0500 Sun. (Morgan, Calif.)

Nicaragua—Saylor, Va., says YNWW, Radio Sport, has moved from 7.850A to 8.000A, noted at 1800 and still going

strong at 2300.

Nigeria—Fairs, England, says Kaduna, 3.327, has increased power from 300 w. to 7.5 kw. and is audible in England around 1430. (URDXC)

North Korea—Radio Pyongyang, 6.250A, has Korean news and music around 0500. (Sanderson, Australia)

Norway—The summer schedules of Radio Norway include to North America, North Atlantic 2000-2100, 6.130, 7.210, 9.610, 1578 kc.; to North America West Coast, Pacific, East Africa 2300-0000, 6.130, 7.210, 9.610, 1578 kc.; on Sun. each transmission is extended by 20 minutes for "Norway This Week" (English). (Halvorsen, Norway)

Okinawa—VOA Relay Base is using 7.165A in parallel with 6.145. (Balbi,

Calif.)

Pakistan—Karachi's new 10 kw. outlet on 3.395 is strong with English news 1015. (Cushen, N. Z.) Heard on 9.645 at 2015-2100, good level. (N. Z. DX Times) Noted with news 1015 on 7.010; with slow-speed news 1310-1330 on 7.010, 6.235. (Pearce, England) Noted on 9.645 at 1930 with English program of news, music; at 1600 on 6.235. (Sanderson, Australia)

Panama—HORT, 6.060A, Radio Balboa, Panama City, noted at excellent

level 1930. (Niblack, Ind.)

Paraguay—ZPA4, Radio Stentor, 9.735, is scheduled 1730-2200, sometimes has bad QRM from HI2T, Dominican Republic; heard in Germany (ISWC, London) Radio Teleco, 11.85, lately has had fair signals as early as 1750; closes around 2105. (Gay, Calif.)

Peru—OAX4T, 9.562, Lima, noted closing 0000, good level. (Koch, Ore.) Is nice signal around 2015. (Hill, N. H.) Radio San Cristobal, 6.216, Lima, heard to 0000. Radio Excelsior, 6.153V, OBX4G, Lima, noted at fair level around 2400. (Rastorfer, N. Y.)

Philippines—VOA Relay Base, San Fernando, North Luzon, heard at good level 1030 on 9.655. (Churchill, Calif.) DZH8, 15.300, Manila, noted with news 2300. (Cooper, Calif.) Heard over 9.73 and 11.855 in English 1015-1030, both good level. (Koch, Ore.) Pitcairn Island—ZBP now operates

Pitcairn Island—ZBP now operates in English over 12.110, 500 watts, 0000-0100. (Scheiner, N. J.)

Poland—Warsaw, 11.740, noted with English 0730, good level. (Niblack, Ind.)

Portugal—Lisbon heard on new 12.140 outlet opening with time pips, "A Portuguesa" at 0945 and closing



Sudio Conter &

ALMAYS AN AUDIO PAIR

55 CORTLANDT ST., NEW YORK J. N. Y.

Editors and Engineers
RADIO & ELECTRONICS BOOKS

RADIO HANDBOOK. GIANT 13TH EDITION. A one-volume library of radio information with extensive, simplified theory. Detailed how-to-build-it date on dozens of items of practical radio equipment. Book No. E&E-RH13...\$6.00*

BETTER TV RECEPTION (in fringe and low-signal areas). NEW SECOND EDITION. The standard guide for installation technicians. A popular text for TV enthusiasts. Book No. E&E-TR2...........\$2.50*

WORLD'S RADIO TUBES (Brans' Vade Mecum) 9TM EDITION. Lists over 15,000 tubes from every tube making country. Printed in 16 languages. Back No. E&E-VM9...........\$5.00°

Send three cent stamp for circular with detailed contents of books listed.



1200; opening another day 0600. (Pearce, England) Noted on 9.74A at 1730 in Portuguese, strong level. (Chatfield, N. Y.)

Portuguese India-Radio Goa, 9.610, noted 1105 with popular musicals and songs in Portuguese; 1130 with request program in English. (Pearce, England)

Reunion-Radio St. Denis, 7.170, noted at poor level with heavy QRM

1015. (Barnard, Calif.)

Roumania - Bucharest, 6.143A and 9.570, is heard irregularly with English for North America now both 2200-2230, 2330-2400 closedown. (Morgan, Balbi, Cooper, Calif.) Audible 1430 with English on 6.210, 9.252A, 6.145, 9.570. (Pearce, England)

Sao Tome-CR5SC, 4.807, noted opening 1600 with 3 strokes of gong.

(Sutton, O.)

South Africa-SABC, 11.93, noted 1400 with news. (Pearce, England) Johannesburg, 4.895, noted with settingup exercises in Afrikaans 2345. (Cox, Dela., others) Heard on experimental 9.680 at 1135. (Calos, Calif.)

Spain-Radio Murcia, near 7.105, noted 1750 with Spanish recordings; closed 1800 with Nationalist March-Anthem; Santa Maria, 7.210, also audible with popular musicals 1745 and closed similarly 1800. (Pearce, England) After testing on 9.585 for a time, Madrid is back on 9.363 (permanently, says) with English still 1515, 1800, 2205A. (Parsons, Ray, Pa.; Strong, Md., many others)

Surinam-PZC, 15.405, Paramaribo, noted 1930 with dance music, announcements in Dutch. (Ferguson,

N. C.)

Switzerland-The 2030-2300 session to North America during summer is being radiated over 6.165, 7.210, 9.535.

Syria-Damascus, 7.235, noted in French 1530-1630, English then to 1730 closedown. (Pearce, England)

Taiwan (Formosa)-Taipeh's 15.235 and 11.725 outlets have had better signals lately with English 2300-2330, 0030-0100. (Gay, Morgan, Calif.) BED32, 9.778A, noted 0530 with Western music, then news in Chinese. (Sanderson, Australia) Heard in native on 7.134A around 0530-0730. (Chatfield, N. Y., others)

Tangier-"The Radio Voice of International Evangelism," Box 219, British Post Office, Tangier, listed frequency of 7.305, call of WIET, schedule of weekdays 1500-1600, Sun. 0800-0900. (Cody, Ireland) Heard closing 1600 with announcements in English, Spanish, and asking for reports. (Pearce, England) Reklame Radio, 7.305, is carrying out further tests irregularly around 1400-1500, 1700-1800; wants reports to Rosenorns Alle 58, Copenhagen, Denmark. (ISWC, London) This one noted 1440 with varied musicals. (Pearce, England) Has no regular schedule as yet. (Fledelius, Denmark) VOA relay of Radio Maroc, French Morocco, on 15.205 at 0730-0930 is widely heard throughout the world.

Thailand-HSK9, 11.670, Bangkok, noted with English and Thai identifi-

WE'RE IN OUR NEW BUILDING!



HALLICRAFTERS 5-40B \$119.95 HALLICRAFTERS SX-88 \$595.00



Per Month (12 months)

\$12.00 CASH DOWN

Communication receiver with built in speaker covering 540-Kc to 44 Mc in four bands. One RF stage, 2 IF stages.



Per Month (12 months) \$59.95 CASH DOWN \$32.42 18 MONTHS

Dual Conversion Receiver 535-33.3-Kc in 6 bands. 2 RF stages, variable 6 position band width selectivity, 250 cycles to 10 10 watt audio output. 17 tubes plus voltage regulator, ballast tube and rectifier.

	HALLICRAFTE	RS RECEIV	ERS AVAI	LABLE FOR	IMMEDIATE	SHIPMENT	
MODEL	12 MONTHLY PAYMENTS	DOWN PAYMENT	PRICE	MUMBER	18 MONTHLY PAYMENTS	PAYMENT	PRICE
5-38C	\$3.97	\$ 5.00	\$ 49.95 \$ 99.95	5-76	\$10.90	\$20.00	\$199.95
S-53A	\$7.95	\$10.00	\$ 99.95	SX-62	\$19.07	\$35.00	\$349.95
S-72 Port	\$8.74	\$11.00	\$109.95	SX-71 HT-20XMTR	\$13.62	\$25.00	\$249.95
5-77A	\$9.54	\$12.00	\$119.95	HT-20XMTR	\$24.50	\$44.95	\$449.50



CATALOG WRITE—WIRE | WORLD RADIO LABO 3415-27 W. Broadway Council Bioth, fowa PHONE 2-0277



offering the greatest selection of radio and television equipment, parts and supplies for the Novice, Experimenters, Hams and Professionals.

Get your BIG NEW 1954 WRL CATALOG.

Please send me

3' x 4' U.S. Rodio Map 25c

WRL XMTR Info New Catalog
Used Equipment List
NEW LOG BOOK 25c

Name Address

State



-reduced interference pick up-reasonable

Write Dept. RE-6 for literature on complete FENWIRE line including "TUF-GUY"... finest guywire made.


(Sold through jobbers only.)
*U.S. & British Pat. Pending

FENTON COMPANY . 15 Moore Street, N. Y. 4, N. Y. Tel. BOwling Green 9-3445



FINEST QUALITY STEEL SHANK AND SLEEVE BRIGHT PLATED FINISH STRONG PLASTIC HANDLE

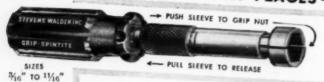WITH THE EASY "FINGER-CONTROL" GRIP AND RELEASE ACTION FOR THOSE HARD-TO-GET-AT PLACES -



BY THE MAKERS OF THE ORIGINAL

SPINTITE

WRENCHES

OVER 150 STYLES

Write for

catalogue

ONE HAND OPERATION-

- GRIPS nuts or bolts of any material
- · HOLDS firmly in any position
- TIGHTENS nut or bolt securely
- RELEASES at the pull of the fingers

STEVENS WALDEN

450 SHREWSBURY STREET - WORCESTER, MASSACHUSETTS MAKERS OF WORLD-FAMOUS HAND TOOLS FOR OVER 50 YEARS

HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO AND TELEVISION REPAIRMEN, SERVICEMEN AND STUDENTS



2 VOLS. 6 COMPLETE \$ | AO. A UDL LS T.V.-RADIO SERVICE LIBRARY—Highly Endorsed—1001 Facts—Over 1552 Pages—625 Hlustrations, Diagrams of Parts. Presents Important Subjects of Modern Radio, Television, Industrial Electronics, F.M., Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc.



-- MAIL ORDER----

AUDEL, Publishers, 49 W. 23 St., N.Y. 10, N.Y. Mail AUDELS T. V. RADIO SERVICE LIBRARY 2 Vols. \$6 on 7 days free trial, if 0. K. I will remit \$1 in 7 days and \$1 monthly until \$6 is paid, Otherwise I will return them.

Name	
Address	
Occupation	
Employed by	Rh

POWER TRANSFORMERS

Comb. Transformers 115V/50-60 cps. Input CT-479 7000V/018A (2 X Ind. V. Test) 2.5V 3.7.80 CT-138 520-6-520V/5008A 6.3V 3A 6.3V Comb. Transformers 115V/50-60 cps. Input CT7-501 650VCT 200MA. 6.3V/5A, 6.3V/5A 6.49 CT-444 230-0-230V/.085A, 5V/3A, 6V/2.5A 3.49

MOBILES! C.D. MEN! CAP!! PE-101 DYNAMOTOR-Converts

DYNAMOTORS

TYPE	VOLTS	AMPS	VOLTS	AMPS	PRICE
DM 416	14	6.2	330	.170	86.78
DM 33A	28	7	540	.250	3.95
8D AR 93	28	3.25	375	.150	7.50
23350	27	1.75	285	.075	3.95
S-19 Pack	12	9.4	275	.110	8.95
			300	.050	
PA-3A*	28	10	300	.260	6.95
			150	.010	
			14.6	8.	
PE TS CM	28	19	1000	.350	22.50
BD 69:	14	2.8	220	.08	12.95
D-4021	13.5	12.2	300	.200	
-		-	8.8V		12.50
SP 175	3.8	3.2	450	.06	4.49
DM 251	12	2.3	250	.05	6.98
2 Less Filt	100		· Repla	cement for	PE 94.
6 Mond fire					

INVERTERS

PE-218-H: input: 25/28 vdc, 92 amp. Output: i15v. 350/500 cy 1500 volt-amperes. NEW. \$37.50 PE-206: input: 28 vdc, 36 amps. Output: 80 v 800 cy. 500 volt-amps. Dim: 13"x5½"x10½". ey. \$22.50

COMMUNICATIONS EQUIPMENT CO.

cation prior to 0655 closedown with National Anthem. (Ferguson, N. C.) Heard closing Home Service around 0928. (Pearce, England; Sawyer, Ont., others) Noted 0415 to Thai Forces in Korea, closed 0520 and reopened 0525. (Balbi, Calif.)

Trinidad-VP4RD, 6.085, is good level 0545-0600 when often is blocked by YSC, El Salvador. (Pearce, Ill.) Just audible on 3.275 with news 2100.

Turkey-Ankara is noted in Europe well with English on 7.285, 9.465 at 1600-1645. ("SWL", Norway) TAT, 9.515, noted in English 1815-1900 to North America, good level. (Howard, Fla.; Welch, Mass.; Marsha, Pa.; Strong, Md.; Haycock, N. J., others) Technical University of Istanbul Radio,

7.030, noted 1425 with classical music. Vatican—HVJ noted with English 1000, 1315 over 9.550, 11.685. (Eriksson, Sweden)

Press Time Flashes

An interesting novel based on amateur (ham) radio is "Stand By for Danger" by E. G. Mygatt, published by Longmans, Green and Co. and which has been running serially in "Boys' Life," the national Boy Scout journal; included at the end of the book is some valuable factual information on ham radio, carefully checked by ARRL. This is a fine book for teen-agers written out of the author's "intense conviction that, so far, ham radio has only scratched the surface possibilities of direct communication between young people the world over."

"SWL" is the house organ of Kristiansand S. DX Club of Norway.

WWK37, Box 3746, San Juan, Puerto Rico, heard 1900 with test transmission; QSL letter states that Radio Corporation of Puerto Rico, which operates this one, uses it only for overseas radiotelephone service, is not a broadcasting station. (Smith, N. Y.) By now, Israel's new 50 kw. transmitter should be on the air. (Klein, Va., others) At press time, Niblack, Ind., reported picking up Radio Ceylon on new 11.770 opening 2030, announcing 7.190 as in

Summer schedule for the "Happy Station Programs" from Hilversum, Holland, Sun., are-0530-0700 to Europe, Asia, South Pacific, 17.775, 15.425, 15.220, 11.950, 6.025; 1100-1230 to Europe, Near and Middle East, 15.425, 15.220, 11.950, 11.730, 6.025; 1630-1800 to Spain, Portugal, South America, 11.730, 9.590, 6.025, and 2130-2300 to USA-Canada, 9.590, 6.025.

A new Brazilian is Radio Clube Paranense Ltd., C. Postal 448, Curitiba, Parana, Brazil, operating on 11.935 from around 1530; call is PRB2, is 1 kw., soon to be increased to 25 kw. Will have regular transmissions as soon as equipment installation has been completed. (ISWC, London) Sunspot count predictions, as heard from Berne, Switzerland, are-June 3, July 3, August 3, Sept. 3. (Ferguson, N. C.)

Cushen, N. Z., flashes that Radio Tahiti now is scheduled 2300-0000, 7.027 (Tahitian); 0000-0200, 6.135.

7.025, 7.125 (French); 1700-1715, 7.025, 7.125 (Tahitian), and 1715-1800, 7.025, 7.125 (French). Radio Espana Independiente, clandestine, has been heard in Britain on measured 7.616 at 1440. (URDXC)

Revised summer schedules for Radio Japan are 0000-0100, 9.695, 11.780; 0200-0300, 15.135, 11.780; 0400-0500, 15.135, 11.725; 0530-0730, 9.695, 7.180; 0745-0845, 9.695, 11.725; 0900-1000, 9.695, 11.725; 1000-1100, 9.695, 11.725; 1115-1215, 9.695, 11.725; 1230-1330, 9.695, 7.180; 1400-1500, 9.695, 7.180; 1800-1900, 15.135, 11.780. Domestic stations include 7.2755, 1500-0500; 7.285, 1600-0500; 4.910, 1600-1715; 9.655, 1725-0500; 15.225, 2200-2300, and 11.800, 0500-0800. (Wada, Japan)

At press time, Balbi, Morgan, Christie, Calif., furnished this latest data on Indo-Chinese stations—"Voice of Viet-nam" has news 0930 over 9.625, 6.17; the 7.29 outlet carries native-type program then; all three close 1000; 9.625 noted at excellent level opening 0400. Radio France-Asie noted on 6.115 with news in French 1015, closing 1030; heard on 9.750A with news 1100-1130 closedown; on 11.830 with news 0900, closing 1120A; the 7.230 outlet is heard in French and/or native from around 0500 and closing around 0900.

A station heard on 7.935A weak to fair around 0600 in Korean and with music is believed Pusan, South Korea, back on the air after having been destroyed by fire some months ago. (Balbi, Calif.)

Eddie Startz of PCJ, Hilversum, tells me it is hoped that Radio Nederland will have its first 100 kw. station in operation by the end of 1954, with three more to follow in 1955 and 1956.

A harmonic of CKCW, Moncton, New Brunswick, Canada, is widely heard at times around 7.300A.

Acknowledgment

Thanks for all the FB reports!!Keep them coming during the summer to Kenneth R. Boord, 948 Stewartstown Road, Morgantown, West Virginia, USA. Good listening, fellows!



Write us now for complete details!

Seletron and Germanium Division RADIO RECEPTOR COMPANY, Inc.

Sales Office: 251 West 19th Street, New York 11 Factories in Brooklyn, N.Y.

June, 1954



BUILD 15 RADI AT HOME \$1 With the New Improved 1954

Progressive Radio "EDU-KIT" NOW INCLUDES

SIGNAL TRACER

and

CODE OSCILLATOR

- . ATTRACTIVELY GIFT PACKED
- . FREE SOLDERING IRON
- . NO ADDITIONAL PARTS NEEDED
- . EXCELLENT BACKGROUND FOR TY
- . 10 DAY MONEY-BACK GUARANTEE
- . SCHOOL INQUIRIES INVITED
- · ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY

WHAT THE PROGRESSIVE RADIO

"EDU-KIT" OFFERS YOU

"The Progressive Radio "Ru-Kit" offers you a home study course at a rack bottom price. Our fit is designed to train Radio Technicians, with the basic facts of Radio Theory and Construction Fractice expressed simply and clearly. You will are a howeveen and Audie Amplifications involved Radio You will force how to identify Radio Symbots and Busgrams; how to build radios, using regular radio creat achemistre. The regular radio creat technicians involved hours of the regular radio creat technicians. You will learn how to operate Receivers, Transmitters, and Audie Amplificats. You will learn how to operate Receivers, Transmitters, and Audie Amplificats. You will learn how to operate Receivers, Transmitters, and Audie Amplificats. You will serve the receiver of the receiver of the receiver as the receiver and the receiver as basic education in Radio exactly the land you will be presented to the receiver as the receiver as basic education in Radio exactly the land you will be presented to the receiver as basic education in Radio exactly the land you will be presented to the receiver as the receiver as basic education in Radio exactly the land you will be presented to the receiver as the receiver rate Receivers, Transmitters, and Audie Amplifiers. You will learn revice and trouble-shoot radius. You will learn code. You will ning for F.G.C. license, lef, you will receive a basic education in Radio exactly like the

THE KIT FOR EVERYONE

Progressive Madio "Edu-Kit" was specifically propaged for any on has a desire to learn Madio. The Minha propaged for any on has a desire to learn Madio. The Minha propaged secondary that you the stightest background in science or radio. In the science of the sightest background in science or radio. Progressive Madio "Edu-Kit" is used by many Madio Schools and his country and abroad. It is used for training and rehabilitation Forces Personnel and Veterans throughout the world! instructions of the madio of the science of the sc

PROGRESSIVE TEACHING METHOD

Sold following a single way of the principle of "Learn by Bo refere you will build radius, serfere jobs, and conduct experiment trate the principles which you learn. These radius are designed ern manner, according to the hest principles of present-day education. You down the principles of present-day education. You begin by building a simple radiu. The next set that you lightly more advanced. Gradually, in a progressive manner, you will radic controlled the progressive manner, you will rest construction still more advanced multitube radius sets, and a nodern manner, according to the beek principles of present-day of reactice. You begin by building a simple redic. The next set that reacting the property of the set of the set of the set of the ourself constructing still more advanced multi-tube radio sets, a rook hise a preferacional Makes Technician. Altopether you will build provide the set of the

THE PROGRESSIVE RADIO "EDU-KIT" IS COMPLETE

Every pact had you need to included. These mets are individually make. Every pact that you need is included. These mets are individually make well as an Electrical and Made Tester. Complete, easy-to-follow instruc-s are provided: "Education of the Electric Complete, easy-to-follow instruc-s are provided: "Education of the Electric Complete, easy-to-follow instruc-s are provided: "Education of the Electric Complete, easy-to-follow instruc-s are provided in "Education" of the Electric Complete Complete Course, down to the amaliest detail.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing are included. You will be taught to re-ize the repair broubles. You will belief and flown to operate a profession in the property of the respective services and the respective way, you will provide the repairs. While you are looking in this proctical way, you will help do many a repair job few your neighbors and friends, and charge hick will far exceed the cost of the "Edu-Kit". Here is your opports learn radio quickly and easily, and have others pay for it. Our Consult excree will help you with any brothincal problems which you may have.

FREE EXTRAS

PREF EXIKAS

• ELECTRICAL & RADIO TESTER • ELECTRIC SOLDERING IRON • TV BOOK • RADIO TROUBLE-SHOOTING GUIDE • GONSULTATION SERVICE • QUIZZES • F.C.G. TRAINING Progressive "Edu Kits" Inc., 497 Union Ave., Dept. RN 30, Brooklyn II, N.Y.

MAIL TODAY—Order Shipped Same Day Received.

10 Day Money Back Guarantee. Include ALL FREE EXTRAS 5 and "Edu-Kit" Postpaid. I enclose full payment of \$19.95 (U.S.A. only). 210-250 V. Adaptor for "Edu-Kit" \$2.50.

Send "Edu-Kit" C.O.D. I will pay \$19.95 plus postage (U.S.A. only). I wish additional information describing "Edu-Kit". No obligation.

Send me FREE Radio-TV Servicing Literature. No obligation.

Name								 	
Address									

PROGRESSIVE "EDU-KITS" INC.

497 Union Ave. Dept. RN-30 Brooklyn 11, N. Y.

ARVEY HAS THE MOST COMPLETE STOCK OF MOBILE GEAR

GONSET Communicator II

A complete 2-meter station. Features builtin adjustable squelch and ear-phone jacks. Less crystal and mike

GONSET Super-Ceiver

Mobile receiver using any converter as tuning head. Complete with dual 6-12 volt pack

SONAR SRT-120

Improved mebile/fixed transmitter. Covers 80, 75, 40, 20, 15 and 10 meter bands. KIT with tubes

(less power supply)... \$159.50 FACTORY WIRED 198.50 EXTERNAL VFO HEAD 19.95

MAC Trans-Citer AF-67

Exciter, VFO driver, speech amplifier, and low power transmitter. Covers 160 through

Complete (less power supply) \$177.00

JOHNSON Viking

Mobile Transmitter Kit. Covers 75, 20, and 10 meter bands, plus spare \$99.50 VIKING Mobile VFO KIT (less tubes)..... 29.45

44.95

WEBSTER

Band Spanner Antenna-Tunes without coils by raising and lowering whip: \$29.50 75 thru 10 meters ...

MASTER Mobile Antenna

Tunes to 10 meters without coil... 75, 40, and 20 meter coils ___each 6.81

MORROW Converters

Tune 75, 40, 20, 15, and 10 meter bands. 58R-1-built-in noise limiter \$74.95 5BRLN-1-less noise limiter 5BRF-designed for FTR receiver... 67.95

MORROW FTR Receiver

Fixed tuned, Features new \$128.40 squelch circuit

SONAR Sonafone

Portable/marine radiophone. Complete 4channel, 2-way radio telephone. Complete with battery, tubes, antenna, \$198.50 and mike (less crystals)..... Add fed, tax 6.62 BATTERY CHARGER

Descriptive literature on request.

Generous Trade-In Allowances **On Your Present Equipment**

Anywhere in the world -

order by mail direct from Harvey. Enclose estimated shipping charge. Excess will be refunded.



The Crosley "Super-V"

(Continued from page 63)

tuned absorption-type trap. It is easily installed by sliding it down over the coil form of Lies to within approximately 3/32" of the secondary winding. (See Fig. 10.) It can be fixed in place by holding a hot soldering iron near enough to fuse the wax on the form. Once the coil is in place, it can be readily tuned by inserting the iron core in the top end of Lini and adjusting it to the setting where the interference disappears.

Bifilar-wound interstage i.f. transformers are used to obtain maximum gain and bandwidth, and a low time constant in the grid circuits.

Diode detection is used in the "Super-V." The diode is housed in the same envelope with the pentode used for the 3rd i.f. amplifier.

The video amplifier grid resistor, R_{119} , is returned to a point which is approximately 2-volts positive. This gives the video amplifier greater signal handling ability, and thus prevents the peaks of the negative-going sync tips from cutting off the tube at high-input levels. Without this positive-going bias, the sync tips are compressed (i.e., the ratio of the sync pulse to the total signal is reduced) in the plate circuit at high-signal inputs, causing unstable pictures or even a total loss of sync.

A double-tuned transformer, L_{100} , is used to couple the 4.5-mc. sound i.f. signal from the video amplifier plate circuit to the sound i.f. amplifier grid. This type of coupling provides maximum selectivity and, at the same time, the primary serves as an effective 4.5mc. trap to keep the 4.5-mc. sound i.f. off the picture-tube cathode.

An electrostatically-focused picture tube is used in the "Super-V." It has many features which warrant its use. Its adjustment is not too critical, it provides even focus over the entire picture, and the focus does not change appreciably with changes in line voltage. It also does not require a bulky focus coil or magnet.

A fixed voltage is applied to the focus element by connecting it to the +150-volt circuit. If, at some future date, a replacement tube is installed which requires a higher or lower focusing potential, it can be readily obtained by disconnecting the focus

Fig. 8. Bottom view of the continuoustype u.h.f. tuner. Note the shielding.

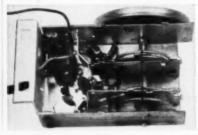




Fig. 9. Details of the balun for matching the 50-ohm input of the continuous u.h.f. tuner to the 300-ohm antenna line.

lead from the +150-volt circuit and connecting it either to the +260-volt or the +480-volt boost circuit, or to the chassis.

The brightness control varies the bias on the cathode of the picture tube. It is mounted on the vertical chassis just above the 25L6 audio output tube. (See Fig. 2.) In most locations, the brightness control does not have to be changed when tuning from one station to another. However, in cases where an external control is desired, a special extension shaft, Crosley part #158188, is available as an accessory item to adjust the brightness control without removing the back.

Sync and Sweep

The sync-clipper circuit uses the triode section of the 6AN8, and features a double time-constant circuit in the input stage. This provides maximum noise immunity for a wide range of noise impulses. The components have been grouped together in the printed-circuit Couplate, C129.

When a single time-constant circuit is used, high-noise impulses quickly charge the condenser (due to the low grid impedance of the tube when it is drawing grid current) to a peak value higher than the sync pulses. Thus, the bias on this tube immediately after a series of high-noise pulses is too high to allow the sync tips to cause the tube to conduct. The result is a loss of sync immediately following heavy noise pulses. To overcome this problem, a second time-constant circuit is used, consisting of the 330,000-ohm resistor shunted with the 270-µµfd. condenser. The 330,000-ohm resistor slows the charging time of the .01-µfd. condenser so its charge is determined only by the repetitive sync pulses and not by random noise. The 270-µµfd. condenser prevents attenuation of the horizontal sync pulses.

The 10,000-ohm resistor in series with the input to the Couplate isolates the stray capacity in the Couplate from the video amplifier circuit. The 25-µµfd, condenser from the sync clipper grid to ground is helpful in bypassing high-frequency video signals.

The output of the sync clipper is coupled in the usual manner to the triode section of a 6U8 sync amplifier. The output of the sync amplifier is coupled through the integrating network, C111, to the vertical oscillator circuit and through the 20-µµfd. condenser, Cita to the horizontal a.f.c. cir-

Because of its inherent stability, the time-proven "synchro-guide" or pulsewidth type of horizontal a.f.c. is used. This circuit is in most respects identical to that used in previous Crosley models. Should the horizontal hold control shift out of range, it can be brought back into range by adjusting the top core on the horizontal frequency coil, Time.

The horizontal sweep circuit is similar to the type used in previous models. There are, however, several important differences. Note that no horizontal drive or width controls have been provided. These have been eliminated in the interest of simplicity.

Horizontal drive on modern TV receivers is relatively non-critical, providing sufficient drive is used. The circuit constants in the "Super-V" have been chosen to provide ample drive, therefore no adjustment is required. In rare cases, a build-up of tolerances in circuit constants and tubes causes overdrive, which shows up on the picture tube as a vertical white line left of center on the tube. To correct this condition, a ½-watt, 22-ohm resistor can be inserted in the 25BQ6 cathode circuit in order to provide a small amount of degeneration. This resistor is used on later production receivers.


The same situation exists regarding width controls. Present-day practice calls for setting the width so that it is ample for low line-voltage conditions, and accepting the slight overscan that results at higher line voltages. In the "Super-V," the correct width at low line voltage is designed into the receiver. It may be noted, however, that a variation in width can be obtained by changing the value of the width condenser, C152. Be sure, however, to use a condenser rated at 3000 volts or more. Increasing the value of this condenser makes the picture wider; decreasing it makes it smaller. To prevent horizontal foldover, do not add more than 60 µµfd.

The vertical sweep circuit uses a 12BH7 in a direct-coupled circuit.

Sound Circuit

The 6BN6 gated-beam tube is a

Fig. 10. Method of installing the 27.9 mc. adjacent channel trap assembly over L.

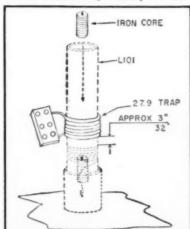

PRACTICE CODE TAPES

Code Training and Practice Inked Paper Tapes on MM 400 ft. Reels for telegraph and radio operation. Reels to a Set, in wood case—for use with TG-34A td TG-10 Keyers. \$12,95

SEPARATE TAPES for following lessons:

Tape #11-Traffic Tape #8-Code Groups
Tape #12-Traffic Tape #2-Receiving

Each on 16 MM Reel, in metal container: \$1.25 Ea.

TG-34A KEYER: 115 or 230 V. @ 50 to 60 cycle—KEYER TG-33A is an automatic unit for reproducing audible code practice signals previously recorded in ink on paper tape. By use of the self contained speaker, the unit will provide code practice signals to one or more persons or provide a keying oscillator for use with a hand key. The unit is compact, in pertable carrying case, complete with tabes, photo cell, and operating manual, Size: 18 3 16" x White They Latt:


BRAND NEW: \$24.95 . USED: \$14.95

TG-10 KEYER: Same function as TG-34A, only larger, using 2/687-2/646-2/6837-1/5046 Tubes and 1/923 Photo Cell. Housed in standard Metal Cabinet, can be removed for 19" rack mtg. Size: 11" H x 24" Wx 181½" D.

NEW: \$29.95 USED: \$19.95

ANTENNA EQUIPMENT

MAST BASES-INSULATED:

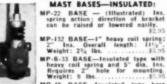

MP-48 BASE-Insulated type all spring, Requires 14" mos with heavy call spring hole. Weight; II lbs.

MAST SECTIONS FOR ABOVE BASES:

NEW-LOW-LOW PRICES ARC-5 COMMAND EQUIPMENT:

R-25	ARC-5	Rec. 1.5	to 3 MC.	No Tubes.	. Used :	814.95
R-26	ARC-5	Rec. 3 to	6 MC.	No Tubes.	. Used:	7.95
R-27	ARC-5	Rec. 6 10	9 MC.	No Tubes.	. Used:	6.95
R-28	ARC-5	Rec. 100	to 156 M4	. No Tubes	. Used:	12.95
T-20	ARC-5	Trans. 4	to 5.3 N	IC	New:	16,95
T-22	ARC-S	Trans. 7	to 9 MC		. Used:	14.93

274-N COMMAND EQUIPMENT:

BC-454 Rec. 3 to 6 MC	\$18.95
BC-455 Rec. 6 to 9 MC	9.95
BC-458 Trans. S.3 to 7 MC	9.95
BC-459 Trans. 7 to 9 MC	14.90
BC-456 Modulator	2.95
FT-225 Mtg. F BC-456 Used: 50c New:	.95
FT-220 3 Rec. Rack Used: \$1.50 New:	2,54
FT-221 3 Rec. Shock Used: .50c New:	
BC-450 3 Rec. Cont. Box Used: \$1.50 New:	2.00
BC-451 Trans. Cont. Box Used: \$1.00 New:	
PLUG-Maio for rear of Rec. or Trans	.50
DM-32 Dynamtr F Rec. 24V. Used: \$2.95New:	6.95
DM-33 Dynamic F. Modulator & Trans. Used:	2.9

TRANSFORMERS FOR COMMAND REC. & TRANS .:

600-0	6	00	5	A	C	3	A.	M/	15	12.5 Volt	V	2 ima	A.	11 108 11 108
600-0 V. @ l'rice 250-0 I A.;	.2	50	v	A	C	50	M	A	2	v.	1	Λ	4	6.3 V.
I A.;	11	5 V	olt		'rir	0313		H.	10	9 I'	rice			\$3.95

Address Dept. RN . Minimum Order \$5.00 Prices F.O.B., Lima, Ohio • 25% Deposit on C.O.D. Orders

Coaxial Cable & Connectors



CD-1071 CORD-With PL-259 Plugs each end. Re-movable Vinylite covering over Plugs, 50 ohm coax 2 F1, long. Prices: She Each-Or in Lots of 10 @ 500 Each.

PL-259-Plug ea. end & 32"-RG-54 U-58 ohm . . 500

TRANSFORMERS-110 V. 40 CYCLE PRI.: Volt CT-25A-10,000 V. Ins. OPEN FRAME-6" 5" x 4½"
3 V. I Amp. . . 1.25
4 V. ½ Amp. . . 1.80
—24—or 30 Volt 8 Amp. . . . 24 V. I Amp. 24 V. 6.5 Amp. CONSTANT VOLTAGE TRANSFORMER-115 V. 60

SOUND POWERED HEAD AND CHEST SET

Navy Type-No Batteries Required-ideal for TV Antenna installations and many other uses. 20 Ft. Cord. Used Tosted: \$5.95 EA.



TELEPHONE WIRE FOR THE ABOVE FIELD WIRE—2 Cond. Twisted, Weather- \$4.75 proof, Heavy Duty, W-110—525 Ft. Roll. \$4.75

DYNAMOTORS

HEAVY DUTY MOBILE DYNAMOTOR:

14 V. INPUT-Output: 1830 VDC 260 MA. Tapped 515 V. 215 MA. use (8) INPUT OUTPUT: STOCK VOLTS: VOLTS: MA. No. 14 VDC 230 90 DM-21

No. 1 DM-21 BD-87 DM-25 BD-77 DM-25 BD-77 DY-22 USA 0515 USA 0516 PE-103 PE-133 230 330 250 1000 90 150 50 350 125 50 110 160 \$8,95 8,95 29,95 4.95

12 230 90 PE-133 6.95 8.95 PE-101 DYNAMOTOR—6 or 12 Vell. (Reprints of original CQ conversion articles—6ct. & Dec., "52 issues—furnished.) This is the Dynamotor the Hams have been talking about! Easily adapted to supply 62 V. @ 156 MA. and 322 V. 125 MA. @ 12 Velts—6 07 090 V. 90 MA. and 160 V. 110 MA. \$4.95 @ 6 Velts — 6 Velts—7 Ve

BLOWERS-115 VAC 60 CYCLE



DUAL TYPE: 100 CFM. 4" in-take: 2" Dis. Each Side, Com-plete Size: 8" x 6". Order No. 1C880 COMPACT TYPE: 108 CFM. Mo-

Complete size: 414" W x 856" H x 816" D. O: No. 2C067
FLANGE TYPE: 140 CFM. 3½" intake: 2½" Dis.
Complete size: 7½" W x 2½" H x 6½" B. Order
No. IC007
FLANGE TWIN: 275 CFM. 4½" intake; 3½" x 3"
Dis. Complete size: 11½" W x 8½" H x 8-1/16" D.
Order No. 2C069 \$21.55

FREE CATALOG

LISTING HUNDREDS OF TRULY EXCEPTIONAL "BUYS" -- WRITE FOR YOUR FREE COPY NOW!

132 SOUTH MAIN ST. LIMA, OHIO

SAVE SSS THOUSANDS OF BARGAINS

Send Stamp for our GIANT CATALOG

UNITED RADIO CO. SEA MARKET ST HEWARK, N. J.

GET INTO TV SERVICING

WESTERN TELEVISION INSTITUTE

Check THESE N. J. R. T. TUBE PRICES

							Gu	arant	ee
Type	Price	Type	Price	Type	Price				
1A7GT	.45	SAKS	.75	6L6	.62		ALL I	NJRT TUI	BES
1B3GT	.67	GALS	.37	6R7	.49			BRAND N	
1H5GT	.38	6AQ5	.37	654	.38			D FULL	
1L4	.50	6AQ6	.36	658GT	.51			ANTEED	
INSGT	.62	SATS	.37	6SA7GT	.41				
185	.48	GAU4GT	.70	6SD7GT	.39		O	NE YEAR	
155	.40	GAUG	.40	65K7GT	.39				
174	.46	6AV6	.37	6SL7GT	.49	_			
104	.48	6AX4GT	.55	65N7GT	.50				
105	.40	GBAG	.40	6597GT	.37				
1 X 2	.65	68A7	.57	678	.57	Туре	Price	Type	Price
3A4	.43	6BC5	.49	GUB	.59	12BA7	.57	35A5	.49
3LF4	.49	68D6	.45	SVSGT	.38	12BE6	.41	3585	.38
304	.48	GBEG .	.37	6W4GT	.42	1.2847	.65	35C5	.38
305GT	.48	6BG6G	1.20	6W6GT	.45	12BY7	.65	35L6GT	.45
354	.48	6846	.45	6X4	.35	12827	.65	35W4	.37
3V4	.50	6816	.41	GXSGT	.35	125A7	.58	3523	.43
SAZ4	.50	6BK7	.89	7E6	.35	125K7	.58	35Z5GT	.45
5U4G	.55	6BL7GT	.65	788	.63	125L7GT	.49	42	.40
SYBOT	.39	SBOSGT	.70	12AL5	.40	125N7GT	.50	43	.53
523	.45	6BQ7A	.92	12AT6	.35	12507	.55	45	.53
5Y40	.39	6827	.95	12AT7	.65	12587met		5085	.41
6A3	.57	6C4	.39	12AU6	.38	12V6GT	.50	SOCS	.41
SAS	.49	6CB6	.45	12AU7	.55	198666	1.15	SOLGET	.59
6A84	.42	SCDSG	1.15	12AV6	.50	IDIA	.75	70L7GT	1.07
GAF4	.92	6F6	.45	12AV7	.60	25BOSCT	.75	76	.42
BAFS	.75	6/5	.40	12AX4GT	.55	251.6GT	.40	11723	.39
SAGS	.47	616	.50	12AX7	.55	25W4GT	.45	117L7GT	1.19
6815	.73	CHECT	37	12846	40	2574	37	2276741	1.25

T.V. PIX TUBE \$1.39
HI PO TV RECTIFIER TUBE
Replaces \$U4G, lasts longer.
Makes picture
brighter, larger \$1.39

FREE FIVE 1L4 TUBES INDIVIDUALLY CARTONED LIST \$11.25 WITH EVERY ORDER OF \$25.00 OR MORE.

Many 7 volt types not listed. All tubes individually boxed. For orders under \$10 add \$1 handling charge. Tubes offered subject to prior sale. Prices subject to change. All orders shipped F.O.B. 2% discount if full remittance accompanies order. 25% deposit on c.o.d. thipments.

SEND FOR FREE TUBE LISTING



NEW JERSEY TELEVISION SUPPLY CO.

Sole Distributor of NJRT Tubes 906B WESTFIELD AVE., ELIZABETH, N. J. EL. 3-6166

New EICO PROBES



SCOPE PROBES

SCOPE DEMODULATOR PROBE KIT \$3.75 WIRED \$5.75

LOW CAPACITY PROBE KIT \$3.75 WIRED \$5.75

DIRECT PROBE
KIT \$2.75 WIRED \$3.95



VTVM PROBES

VTVM RF PROBES KIT \$3.75 WIRED \$4.95

PEAK-TO-PEAK PROBES KIT \$4.95 WIRED \$6.95



See these amazing probe values at your jobber today. Write now for FREE catalog RP 6. Read EICO'S other ads in this issue—turn to Advertisers Index!



ELECTRONIC INSTRUMENT CO., Inc. 84 WITHERS STREET, RECOKLYN, NEW YORK

New 2-Speed Magnemite



for Greater Recording Versatility in the Field:

For Nature Sounds, Music, Street Sounds, Interviews, Conference Recording, Courtroom Reporting, Missionary Work, Testimony Recording.

The only two-speed battery-operated springmotor recorder that meets primary and secondary NARTB standards for flutter, frequency response and dynamic range. Records and plays back frequencies up to 15,000 cycles. Features real portability, constant tape speed and independence of AC source. Models available for tape speeds of 15/7½ jps and 7½/3¾ jps. Quick change without sacrificing equalization.

These tiny recorders weigh only 16 lbs. with self-contained batteries that last 100 hours and include built-in monitoring and headphone playback facilities. Smaller than a portable typewriter (8 x 10 x 11 inches), the two-speed Magnemites* do away with cumbersome generators, storage batteries, rechargers and may be operated anywhere.

Write for complete technical literature and direct factory prices to Dept. RT

AMPLIFIER CORP. of AMERICA 397 Broadway, N. Y. 13, N. Y. multipurpose tube that functions in this chassis as an FM limiter, detector, and 1st audio amplifier. This particular circuit was selected because the 6BN6 detector requires much less i.f. drive to obtain effective limiting than a conventional ratio detector, resulting in a better signal-to-noise ratio at low inputs. It has a high audio output, sufficient to drive the 25L6 directly, thus taking the place of an audio amplifier. The adjustable control ("buzz control") in the cathode circuit of the 6BN6 makes it possible to obtain a very effective intercarrierbuzz null. Although the circuit is critical as to adjustment, it can be easily aligned on a local TV station, thus eliminating the need for an FM generator. The adjustments can be made without removing the cabinet.

To align the circuit, refer to Table 1. Due to the interaction between the quadrature coil adjustment and the buzz control setting, and since a few degrees turn in either direction can throw the alignment off, it may be necessary to repeat the adjustments several times. Typical symptoms of a misadjusted sound circuit are excessive sync buzz, weak sound, and distortion in the sound—all of which can be corrected by properly aligning the sound circuits.

Before proceeding with the alignment of this receiver as per the instructions given in Table 1, connect the negative lead of a 3-volt bias battery to the white lead coming from the tuner, and the positive lead of the battery to the chassis. In Table 1, where reference is made to the rear of the chassis, it means the side of the chassis with the tubes.

HAMFEST-PICNIC

THE North Fork Amateur Radio Club of Southwest Oklahoma is holding its annual hamfest and picnic at Quartz Mountain State Park on June 12 and 13.

Prizes and a generous measure of fun await attendees. Reservations may be made with Elmer Triplitt, secretary, Savre, Oklahoma.

Jerry B. Minter president of the Audio Engineering Society, and Harry N. Reizes, managing director of Audio Fairs, sign a sponsorship renewal agreement as C. R. Sawyer of Bell Labs and Walter Stanton of Pickering, governors of AES, look on. The AES will sponsor the Audio Fair for the years 1954 and 1955. This year's event will be held October 14, 15, 18, and 17 at the Hotel New Yorker in New York City.



MODEL 27-Z TESTER

\$10.95



RADIO CONTROL

CAN CONTAINING 4 CLARE TYPE K \$2.95

HILT ADDITIONS AND ADDITIONS OF THE MANUAL M

FILTER-CAPACITOR STEALS!

- Dual 6 MFD, 600 VDC, oil-filled, hermetically scaled, gives you 2 ladder sections, or paral-lel for 12 MFD. Only \$1.28, two for \$2.49. 1 mfd, 600 VDC, oil, hermetically
- 3)

\$45.00 HI-FI HEADSET AT \$7.95

24-HOUR TIME SWITCH-

90% DISCOUNT! neon signs, neurosite in the first production of the f

24 Vib. 3. \$2.90 mechanism mechanism . \$2.90 mechanism . \$1.5 V. 60 excles to 24 V. 60 for alone solonoid & many other uses . \$1.50 for alone solonoid & many other uses . \$4.50 for alone for alone solonoid . \$1.50 mechanism . \$4.50 mechanism . \$4

12 V. RECEIVER DYNAMOTOR

\$4.95

GENERATOR-ALTERNATOR SPECIAL 120V AC PLUS 28.8V DC units in one package, each complete in it removable contributal sing clutch and the realternator. Clutch maintains armature spec n-alternator. Clutch maintains armature speed of print for drive speeds varying between 2400 and print. Outputs 120v, 800 cy, 1 ph., 1080 VA 28.5 v, 25 A DC. Brive it from ensitie or elec-motor. With diagram and instructions. \$9.95 cellent condition.

I.TAGE REGULATOR (Carbon piles for als

200 AMP 24 V. GENERATOR

narine-aircraft-tarm and Heavy Duty 24:30 y charging-welding-etc. Heavy Duty 24:30 4400-8000 RPM, G.E. type 2CM-8182 (Air P1). Excellent condition. A \$47.30 \$9.95



12 V. DYNAMOTOR D. W. Thomas Engin ing. Inc.: NEW! Guaranteed. Re

You conect for either to a 350 or 600 v. @ 200 ms. inst. \$9.95

B'CAST, LIGHTHOUSE, AERO

plete installation. loop, azimuth control. ga, loop transmission ematics. Easily sonver

ver & Loop Brand New, with tubes. \$69.50

rd.; 0-1 ma \$3.95, 500-0-500ua \$3.9

G. L. ELECTRONICS, INC.

905 S. Vermont Ave., Los Angeles S. Calif. mum Order \$5.00 Total, 25% Deposit Required rices F.O.B. Los Angeles, Calif. Buyers Add Sales Tay GET ON OUR MAILING LIST

SCHEMATICS-CONVERSIONS FOR SURPLUS GEAR

NEW LIST! MANY ADDITIONS! Send stamped, self addressed envelope for List C. Add 25c for chart explaining AN


BOX 1220 GOODHEART BEVERLY HILLS, CAL

Within the Industry

(Continued from page 26)

at its new 422,000 square foot television set assembly plant in Batavia, N.Y. . . . EL MEC LABORATORIES has moved its entire plant and office to 730 Boulevard, Kenilworth, N.J. The new location provides approximately twice the space for engineering, development, and manufacturing as was available at the old location . . . BUX-TON INDUSTRIES, manufacturer of a line of TV antennas, has moved into a new plant at 88 North Fair Oakes Avenue in Pasadena where almost triple the old plant area will be available . . . TELE-MATIC INDUSTRIES, INC. has opened a warehouse at 6115 Denton Drive in Dallas to service the southwest territory . . . GENERAL ELECTRIC **COMPANY** has consolidated its Indiana receiving tube manufacturing operations at its Tell City plant and will close its feeder operation at Huntingburg. The processing formerly done at Huntingburg has been transferred to the new Tell City plant addition . . AEROVOX CORPORATION has opened two new plants in California. One plant will house the company's CINE-MA ENGINEERING CO. division at 1100 Chestnut St. in Burbank and the other will house both ACME ELECTRONICS. INC. and the Pacific Coast division of the parent firm at 2724 S. Peck Road, Monrovia . . . FEDERAL ELECTRIC PRODUCTS COMPANY has completed new executive and sales headquarters at its Newark, N.J. plant. The new addition provides approximately 12,000 square feet of space . . . PRECISION APPARATUS CO., INC. will move its manufacturing, engineering, and administrative facilities to a new plant in Glendale, Long Island by midsummer. The new two-story air-conditioned building occupies a plot of ground running from 84th St. to 88th St. south of Cooper Ave. in Glendale . . . STRU-THERS-DUNN, INC. has moved to Lambs Road, Pitman, N.J. The firm was formerly located in Philadelphia ZENITH has opened a new high-fidelity salon at 333 N. Michigan Avenue in Chicago.

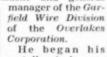. . . ERIC B. T. KINDQUIST has been appointed vice-president and general



He began his metallurgical career in the research laboratory of International Nickel Co., later becoming a re-

search engineer for RCA at Harrison, N.J. He received his degree in chemical engineering from Pratt Institute and has taken graduate work at N.Y.U. and Ohio State.

The Garfield firm manufactures a line of wire for the electrical and electronic industries.

Saves service time! Reduces your investment in parts!



individual components And its stability assures long life . . . happier set-owners

When you run up against one of the millions of old radio and TV sets that were built before PEC's were used, do you waste costly time trying to locate a shorted or intermitant overcons. tent component?

You don't have to--you can r place an entire section of an old-style circuit with a single PEC. And you can do it at a part-cost of as little as 36¢ to 81¢ net!

For example, if the trouble is in the vertical integrator of a TV set, you can replace the whole section with a vertical-integrator PEC plate. If the trouble is in the audio detector of a radio set, you can replace the entire section with an audio detector PEC plate.

Why risk service "call-backs", by replacing only one old-style company.

replacing only one old-style compo-nent? All the other parts are the same age-replace 'em all with one PEC

New, revised Centralab Printed Electronic Circuit Guide No. 3 tells the whole story—and shows circuit schematics that help you install PEC's. Send coupon for free copy.

Centralab

CENTRALAB, A Division of Globe-U 910F E. Keefe Avenue, Milwaukee	
Send me a free copy of the 1s of the Centralab Printed Circuit Guide No. 3.	954 edition Electronic
Name	***********
Company	*******
Address	***************************************
CityZoneS	





most powerful fringe area market today . . . the one and servicemen are buying s. Clear, sharp, exceptional to 200 miles. Here is the eption up to 200

THE ONLY CHASSIS WITH 10 WATT PUSH-PULL HI-FI AUDIO SYSTEM AT

Complete with Two Speakers—12" Hi-Fi Wooter and Tweeter With UHF 83 Channel Converter-\$211.90 Detailed Service Manual & Schematic-Write for FREE Descriptive Folder

COMBINATION SAVING! • 630 FA-2A Chassis
• 21" Picture Tube
• Mah, Consolette Cabinet
With mask, glass, tube mig brackets FOR THE 3 UNITS

TV PICTURE TUBE SALE

Standard Brands. Factory New. Guar, 1 year.

Techmaster 513995 Techmaster 2430-9 Chassis. 24" 4 27" Rect.

TV GOLD PLASTIC MASKS

BARGAIN CABINET BUY

630 FA-2A Chassis. Complete with \$49.95

Send for complete cabinet brochure

Send Postcard to Be Put on Mailing List We Won't Be Beat on Hi-Fi Equip. REGAL

FM-AM RECEIVER



Also complete line of Tuners, Amplifiers, Speakers, Phono Pick-Ups and Cartridges and Changers

Fisher
Garsad
Gardel
Garanes
Grommes
Jensen
Fickering
Wharfedale

AIREX RADIO CORP. SHOWROOM: 171 Washington St., N. Y. 7 Cortlandt 7-5218

NEW TV PRODUCTS on the Market

Brach Manufacturing Corp. of 200 Central Ave., Newark 4, N. J. has released its Model 556 "Delta-Vee" beam for v.h.f.-u.h.f. black-and-white and color reception.

Channel Master Corporation, Ellenville, N. Y. is offering its "Econo-Vee" Model 411 antenna to the trade. This fully preassembled antenna is designed to operate effectively in secondary and fringe u.h.f. areas as well as primary v.h.f. areas.

Fink Electronics, Inc., 518 E. 95th St., Chicago, Ill. has introduced an indoor antenna which the company claims is effective even with color TV. Known as "Diron," the new antenna covers all v.h.f. television channels plus the FM frequencies. It comes completely assembled and tested.

Insuline Corporation of America, Manchester, N. H. is offering a "Combo-Fan" which may be used to convert existing v.h.f. antennas to u.h.f. recep-The device is a fan-shaped, weatherproof, all-aluminum antenna giving high gain on channels 14 through 83 without affecting normal operation on the v.h.f. channels,

JFD Manufacturing Company, Inc., 6101 Sixteenth Ave., Brooklyn 4, N. Y. has restyled its "Pace-Setter" series of conical antennas for channels 2 to 13. This new series features seamless aluminum cross arms, dowel-reinforcement at both ends for extra strength, wood-dowel reinforcement of the aluminum elements, and a double reinforced U-bolt mast clamp assembly.

Television Hardware Mfg. Co., 919 Taylor Ave., Rockford, Ill. is offering two new window-mounted TV antennas for applications where roof mounting is impractical or forbidden. The "bow tie" style is designed for u.h.f. reception while the "double V" model can be used for u.h.f. and v.h.f. in primary and secondary signal areas. The "Window-Tennas" are now at distributors.

Tricraft Products Company, 1535 N. Ashland Ave., Chicago 22, Ill. is now marketing a new indoor u.h.f. antenna, the Model 222 "Radome." This moderately priced unit covers channels 14 through 83 and measures 12" x 12" x 3%".

COLOR TY TUBES

CBS-Hytron, Danvers, Mass. is currently in production on two new tubes which have been developed specifically for color TV circuits.

The 3A3 is a high-voltage, half-wave vacuum rectifier designed to be used in the high-voltage system of a color set. It may also be employed in any rectifier application where high peakinverse plate voltage and high-peak

plate current are required. Bulletin E-225 gives complete data on this tube.

The second tube is the 6BD4, a highvoltage regulator for anode and convergence supplies in color receivers. Bulletin E-226 gives complete specifications on this tube.

LARGE COLOR TUBE

A new color television picture tube that produces a 20" (diagonal) color picture, comparable in contour and size to the standard 21" black-andwhite tube, is now under development at the Electronic Tube Division of Westinghouse Electric Corporation.

A significant advancement in the new tube is its larger screen size coupled with the use of a phosphor screen which has 20 complete color groups per inch compared to 17 previously used. This gives improved resolution and good color definition at normal viewing distances. The total viewing area is approximately 200 square inches.

"CHROMALYZER"

Telechrome, Inc., 632 Merrick Road, Amityville, Long Island, N. Y. has developed an elaborate test unit for checking and aligning home color receivers, the Model 636-B "Chromaly-

The new instrument provides all the standard color signals needed for service work. By push-button control, the unit produces eleven bars of blue, red, magenta, green, cyan, yellow, G-Y (greater than 90 degrees), R-Y, B-Y, Q, I, in addition to black, white, sync, and color burst.

Light and portable and held to high accuracy by crystal control, the unit



operates with a self-contained, fullyregulated power supply and produces signals at video or r.f. with both picture and sound carrier on any channel from 2 to 6.

COLOR SIGNAL GENERATOR

Radio Corporation of America, Camden, N. J. has developed an inexpensive color signal generator for use in TO THE

E.E.

PHYSICS GRADUATE

WITH EXPERIENCE IN

RADAR

OR

ELECTRONICS

HUGHES RESEARCH AND DEVELOPMENT LABORA-TORIES ARE ENGAGED IN A CONTINUING PROGRAM FOR DESIGN AND MANU-FACTURE OF ADVANCED RADAR AND FIRE CONTROL SYSTEMS IN MILITARY ALL-WEATHER FIGHTERS AND INTERCEPTORS.

THE GREATEST advancements in electronics are being made in this sphere because of military emphasis. Men now under 35 years of age will find this activity can fit them for future application of highly advanced electronic equipment.

YOU WILL serve as technical advisor in the field to companies and government agencies using Hughes equipment.

TO BROADEN your field of experience in radar and electronics you will receive additional training at full pay in the Laboratories to become thoroughly familiar with Hughes radar and fire control equipment.

AFTER TRAINING you will be the Hughes representative at a company where our equipment is installed; or you will advise in the operation of Hughes equipment at a military base. (Overseas assignments, single men only.)

HUGHES

RESEARCH AND DEVELOPMENT LABORATORIES

SCIENTIFIC AND ENGINEERING STAFF

Culver City, Los Angeles County, Calif.

Assurance is required that relocation of the applicant will not cause disruption of an urgent military project. television stations to expedite installation or performance checks of color TV receivers in homes while black-andwhite programs are on the air.


The new device, when used by the station, will enable service technicians to check color set reception during normal servicing hours without waiting for color signals to be aired.

The color test signal is a narrow vertical yellow-green bar which is visible at the extreme edge of color receivers but is practically unnoticeable on black-and-white sets.

The device will be made available through the company's Engineering Products Division.

COMBINATION TUNER
General Instrument Corporation is now offering a combination all-channel v.h.f.-u.h.f. tuner, the Model 80.

The new unit is composed of a new

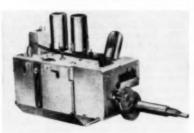

13-position turret-type v.h.f. tuner (Model 78) and a new, compact, continuously-tuned u.h.f. unit (Model 79). The combination unit is so designed that the v.h.f. section can be purchased and installed separately in sets. If the manufacturer's market should change. he or his distributor can add the u.h.f. section in the field.

The combination tuner measures less than 7" long and 31/2" wide and was designed especially to meet the demand for smaller cabinets and larger picture tubes.

NEW ROOF MOUNTS

Commercial Products, 201 Division Street, Toledo 2, Ohio has announced five new models of roof mounts for simplified installation of TV antennas.

Designed to be used with "walking up" masts, the new units are in addi-tion to the four already offered by the company.

A catalogue containing complete details on all nine of the mounts is available on request.

ANTENNA ROTATOR

Crown Controls Company, Inc., New Bremen, Ohio has added a new unit to its line of antenna rotators.

A new design permits the entire mast assembly support to be preassembled, thus simplifying installation. The size of the mast support base has been increased to provide a wider, stronger support for antenna masts. It will accommodate masts from ¾" to 2" and up to 175 pounds in weight.

The unit also features an exclusive "weather - guard" design, automatic braking which prevents coasting and windmilling, a lifetime-lubricated con-



V. E. C. TUBES Minimum Order \$7.00

RAND NEW BOXED BRANDED

100% GUARANTEED

Use This Ad As Your Order Form TYPES AT 29¢

QUANTITY	TYPE	QUANTITY	TYPE
******	813	*******	35W4
	823 6×4		11723
	6XS		
	TOTAL	******	TOTAL
	TYPES	AT 39e	
QUANTITY	TYPE	QUANTITY	TYPE
*******	155	*******	6W4GT
11071777	109		12ALS
	SAR4		12AUG
	SALS	41111111	12846 12846
	SAUS	4444444	12856
	SAVE		125Q7 25L6QT
	604	*******	25W4GT
	676		2576
	686	1777177	3505
	65Q7		
	TOTAL.	Account	TOTAL
		AT 49¢	
QUANTITY	TYPE	QUANTITY	TYPE
	147	*******	6805
	11.4	******	6886
	186	*******	60'6
	174		65A7
	304		6507
	354	******	646
	374	******	125A7
	574		5085
	6AGS		SOCS
	TOTAL		TOTAL
	TYPES	AT 590	
QUANTITY	TYPE	QUANTITY	TYPE
	103GT	1111111	651.7
2111111	16.6		66M7 12AU7 12AM7
	308	10000000	22754
			13887
	68A7		128A7
	68A7 68DS 6J6	*******	128A7 128H7 125L7
	68A7 68DS 6J6 638		128A7 128M7 125L7 125M7
	68A7 68DS 6J6	*******	128A7 128H7 125L7
	SMAT SMDS SJB TOTAL TYPE:	AT 690	128A7 128M7 125L7 125M7 TOTAL
QUANTITY	GNA7 GNDS GJG GSA TOTAL TYPE!	S AT 69¢	12RAT 12RMT 12SLT 12SMT TOTAL
QUANTITY	GMA7 GMDS GJG GSB TOTAL. TYPE: GAKS GAKS	AT 69¢	12RAT 12RMT 136LT 126NT TOTAL TYPE 6T6 8UB
QUANTITY	GMA7 GMBS GJ6 GSB TOTAL. TYPE: TYPE: GAKS GAIS GBK7 GBL7	AT 69¢	TYPE
QUANTITY	GMA7 GMD5 GJ6 GSB TOTAL TYPE: GAKS GAKS GBK7 GBL7 GL6	S AT 69¢	TYPE 6UB 12AV7 12AV7 12AV7 12AV7 10TA
QUANTITY	GMA7 GMBS GJ6 GSB TOTAL. TYPE: TYPE: GAKS GAIS GBK7 GBL7	AT 69¢	TYPE
QUANTITY	GMA7 GMD5 GJ6 GSB TOTAL TYPE: GAKS GAKS GAKS GAKS GAKS GAKS GAKS GAKS	S AT 69¢	TYPE 6UB 12AV7 12AV7 12AV7 12AV7 10TA
QUANTITY	GMAT GMOS GJE GSE TOTAL TYPE: TYPE: GAMS GAMS GAMS GAMS GAMS GAMS TOTAL TYPE: TYPE:	S AT 69¢ QUANTITY	12RAP 12RAP 12SAP 12SAP TOTAL TYPE 6TG 6UG 12ATP 12AYP 19TG TOTAL
QUANTITY	GRAT GRAD GRAD GRAD GRAD TOTAL TYPE: TYPE GAKS GALS GRAD GRAD GRAD TYPE: TYPE SRES	S AT 69¢ QUANTITY S AT 79¢ QUANTITY	12RAP 12RAP 12SL7 12SL7 12SN7 TOTAL TYPE 61G 12AT7 12AT7 12AT7 12AT7 12AT7 12AT7 12AT7
QUANTITY	GMAT GMOS GJE GSE TOTAL TYPE: TYPE: GAMS GAMS GAMS GAMS GAMS GAMS TOTAL TYPE: TYPE:	S AT 69¢ QUANTITY	12RAP 12RAP 12SAP 12SAP TOTAL TYPE 6TG 6UG 12ATP 12AYP 19TG TOTAL
QUANTITY	GRAT GRAD GRAD GRAD GRAD GRAD GRAD GRAD GRAD	S AT 69¢ QUANTITY S AT 79¢ QUANTITY	12RAP 12RAP 12SL7 12SL7 12SL7 12SL7 12AT7 12AT7 12AT7 12AT7 10TAL TYPE 6827 25826
QUANTITY	GRAT GRAD GRAD GRAD GRAD GRAD GRAD GRAD GRAD	S AT 49¢ QUANTITY S AT 79¢ QUANTITY	12MAT 12MAT 12MAT 12SLT 12SLT 12SLT 12SLT 12SLT 12SLT 12SLT 12AVT
QUANTITY	GRAT GRAD GRAD TOTAL TYPE GAMS GAMS GAMS GAMS TOTAL TYPE TYPE TYPE TYPE TYPE TYPE	S AT 69¢ QUANTITY S AT 79¢ QUANTITY S AT 99¢ QUANTITY	128AF 128AF 128AF 128AF 128AF TOTAL TYPE 6UB 12AFF 12AVF 12A
QUANTITY	GRAT GRAD GRAD GRAD TYPE GAKG GAIS GAIS GAIS GAIS TOTAL TYPE: TYPE: TYPE: TYPE: TYPE: TYPE: GRAD GRAD TYPE: TYPE: GRAD GRAD GRAD TYPE: TYPE: TYPE: GRAD GRAD GRAD GRAD GRAD GRAD GRAD GRAD	S AT 69¢ QUANTITY S AT 79¢ QUANTITY S AT 99¢ QUANTITY	128A7 128M7 128L7 128L7 128L7 128L7 128A7 128A7 107AL TYPE 6817 25806 TOTAL TYPE 11806 117L70T
QUANTITY	GRAT GRAD GRAD TOTAL TYPE GAMS GAMS GAMS GAMS TOTAL TYPE TYPE TYPE TYPE TYPE TYPE	S AT 69¢ QUANTITY S AT 79¢ QUANTITY S AT 99¢ QUANTITY	128AF 128AF 128AF 128AF 128AF TOTAL TYPE 6UB 12AFF 12AVF 12A

FREE with every order of \$20.00 or more—famous "Oxwall" magnetic screw driver kit. Includes all sizes-Philips head, long handles to get in those tight spots, etc. 7 screwdrivers in all. May be purchased outright. 3 for \$5.50 \$1.99 each

VIDEO	FLECT	RIC	CO.		O. Bo	
	complete magnetic					
\$		Amoi	unt enc	lose	d	

Address

City Zone .. State. PLEASE PRINT CAREFULLY

TRAINING SERIES" now appearing in

the Monthly REPORTER for the Electronic Service Industry



brings you a complete education in COLOR TV based on practical experience with actual receivers, and firsthand data developed exclusively by the editorial staff of PF INDEX . . . appearing month after month. You won't want to miss a single issue ... so get

AT YOUR PARTS DISTRIBUTOR get it each month only 25¢

denser motor, and 365 degree rotation in 60 seconds.

Complete literature is available on this new rotator.

NEW MALLORY CONVERTER

P. R. Mallory & Co., Inc. of Indianapolis, Ind. has announced the availability of a concealed u.h.f. converter, the Model 188.

According to the company, the new unit is the first all-channel converter designed to fit completely inside a TV set. Installation requires no chassis or cabinet alterations. All that can be seen of the finished installation is the clear plastic selector dial and switch.

The converter offers a choice of mounting positions, left, right, or inside top of the cabinet.

CONTINUITY TESTER
Kapner Hardware, Inc., 2248 Second Ave., New York 29, N. Y. is now offering a self-contained, all-electric continuity tester, the Model 170-A.

The instrument indicates resistance from a fraction of an ohm to 5 megohms. A safeguard resistor limits the output to 1 ma. The testing procedure is simple and quick. One lead is clipped to one side of the circuit or resistance under test while the test prod is then touched to the other side. An indicator light tells whether the resistance is low, high, or open.

It can also be used for checking filaments of all radio and television tubes. The low output of the unit makes it impossible to damage even battery or hearing-aid tubes.

TUBES FOR COLOR TV

The Tube Department of General Electric Company has announced the development of four new receiving type tubes which have been designed for color TV sets.

The new units include a 2V2 highvoltage rectifier; a 5AU4 high-output, full-wave rectifier; a 6AR8 sheet-beam synchronous detector; and a 6BU5 high-voltage pentode for shunt regulation.

Complete information on these new tubes is available from the Tube Department at Schenectady 5, New York.


TELEVISION ADAPTER

Textronix, Inc., P.O. Box 831, Portland 7, Oregon has announced the availability of a new television adapter, the Type 124.

The new unit adapts any triggered



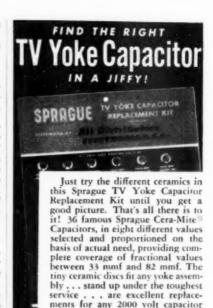wide-band oscilloscope to the observation of the composite video signal. The delayed-trigger output of the new unit



SPRAGUE PRODUCTS COMPANY

which may appear in original equipment. Complete instructions are on

the face of the tough, paper-board

card, conveniently punched for hang-

ing over the service bench. Get

yours now! Ask your distributor for Sprague Kit CK-1. Only \$12.60 List!



is continuously variable from zero to 25 milliseconds after receipt of a vertical sync pulse. By adjusting the delay, an oscilloscope can be triggered at the start of any desired line in a field. A panel push-button provides instant shift to the opposite field. Triggering occurs at half the television vertical rate. Duration of the output pulse is less than 1 microsecond and amplitude is 2 volts posi-

To make use of the time-marker output of the Type 124, the scope should have a positive gate output and a CRT cathode terminal.

COMPONENT TESTER

Transvision, Inc. of New Rochelle, N. Y. has recently introduced a new



TV component tester which will check the following parts: flyback transformers and yokes, selenium rectifiers, and picture tubes as well as reactivating the picture tubes.

The new component tester will make positive checks on color tubes and extend the life of weak color tubes with low emission, Additional information on the unit will be supplied by the manufacturer on request.

NEW "TENNA-TIE"

Channel Master Corporation of Ellenville, N. Y. is now offering an improved version of its "Tenna-Tie," an inter-action filter which joins highand low-band v.h.f. antennas for use with a single transmission line.

The new unit now incorporates separate high- and low-pass filters, replacing the parallel resonant circuit previously used. With the new circuit, the installer may connect leads of any length between the antennas and the unit without affecting the efficiency of the filter. Lead lengths are no longer critical.

The new version is catalogued as Model No. 9033-A.

COLOR TEST GEAR

The Tube Division, Radio Corporation of America, Harrison, N. J. is in production on three types of test equipment essential to the installation and maintenance of home color television receivers.

The new equipment includes the

BC669

Crystal Controlled Radio Receiver and 50 Watt Transmitter—freq. range 1700 to 4400 KC—com-plete with tubes, used, excellent \$59.50

CRYSTAL SETS (for above)

PP-51/APQ9 Rectifier Power Supply ains 4 each 5R4 tubes; 2 each 1 mfd. 2 each 4 mfd. @ 1000 VDC oil-little other parts. Brand new in origin

NEW TG-34A PORTABLE KEYER

115 or 230 v; 50 to 60 cycle, complete tubes, photocell and carrying case.....\$2 Used, exc.\$14.95

BC-929-A

Contains power supply 110 V. 400 cycles, has 7 tubes such as 3CPI, brand new, complete with \$14.95 tubes. Each Oll CONDENSERS

8 mfd.									0	8c
66 600	VDC								0	00
			10	for-	50	OO.				
Oil Fill	led-	1 mfd.	85	360	By				.95	ra.
		200	at	400	0v				.75	ea.
EE65	Test									
trouble	7183	In a street	Les 1	N.THO	Higgs	500	maralas	to in	CHART	in the same
Care.	Now			Spe	TRAFE?	6.00	see Dans.	(c. 111		OF

NATIONALLY ADVERTISED TUBES

58P1 \$239 304TL ..\$3.95 38P1 40 58.00 304TL ..\$3.95 20895 720BY ..19.95

1625, 1626, 33, 34, 954, CK1005, 627G, 9602, 9006, 1619, 955, 9004, 12A3, 1F4, 1F5, 211, 6F5, 1629, 19, 50, 12L8,

10 for \$3.00

R-1/AR-1-220 MC converted with minor becomes a high gain converter with two RF amplification—(complete with dia-\$3.95

DYNAMOTORS

	Input	Output	Price
D-1	5.6V	425 @ 375MA	514.95
D-2	14V	375 @ 150MA	7.95
DM-32A	28V@1.1	250 @ 60MA.used	2.95
		new	7.50
D-101	27V@1.75	285VC075 amp.	1.95
		3 for	5.00
DM-33 .			2.95

Hundreds of items in stock, WRITE FOR NEW BULLETIN AND PRICES. Shipments F.O.B. warehouse. 20% Deposit on orders, Minimum order \$5.0. Illinois residents, add regular sales tax remittance. Prices subject to change without

R W ELECTRONICS

Dept. N, 2430 S. Michigan Ave. Chicago 16, III. PHONE: Calumet 5-1281-2-3

FOR YOUR CONVENIENCE ELECTRONICS TRADING POST 1632 Venice Blvd. Les Angeles, Calif.
Phone: Richmond 7-4104

Command Equipment (274N-ARCS, ATA) 190-556 KC 57.955 1,5-3 mc 5.95 3-6 mc 5.95 6-9 mc 5.95 6-9 mc 5.95 3-Hee, Rack 5.95 3-Control Head 1,00 12.95 J-47 Telegraph Key......98c

ARC-5/R-28 2 MTR RCVR

meter superhet, absolutely one of the EST available today! Tunes from 100 to 6 mes, in four crystal chantels. (Easily neerted to continuous tuning.) Complete

BC1267 TRANSMITTER AND RECEIVER

RECEIVER

154 to 186 Mcs., IKW pulse oscillator, superhet circuit, 2 RF stages, and 5 stagger tuned 15's, includes 21 tubes; 2C26(2), 3E27/8278(1), 4AG5(7), 6C4(1), 4E5(1), 4D4(1), 4AX5(3), 4J5(2), 4S1(1), 4V6(1), 9006(1); can be easily converted to 2 meter converter and outboard amplifier, ship. wh. 75 lbs., complete with conversion instructions (NOTE: 3E27/8278 is worth \$10.00 alone) 3' meter excellent condition (less tubes) good condition

with 21 tubes. \$24.95

with 21 tubes...

BROADCAST BAND and AERO

Ideal for Use in Boots, etc.

ALL UNITS BRAND NEW EXCEPT CONTROL BOX 569.50

Mikes, Headsets & Microphones T-26 Telephone chest unit with F-1 Electric Transmitter

CD-367 Ext. cord for HS-23-33 Like new \$.79....new 1.29 Throat Mike—T-30...new .98

| Throat Mike—T.00 | new | 98 | | 16 | Mike | Nav Type | new | 98 | | 16 | Mike | Nav Type | 17 | Mike | 18 | Mike | Mike | 18 | Mike | 18

4 for \$12.00 Low Freq, Crystals—FT 241 A for SSB, intitic filter, 1/2* spc. 54th harm channels listed by fund. Fractions omitted.
See previous Radia-TV News Issues for frequencies

49c each 10 for \$3.00

NAVY ARB RECEIVER

NAVY ARB RECEIVER

Ke thru 9 Me. Includes broadcast band. Can be served easily to a good ham received. 28 V. DC input, each of the standard that is a delixe type super-like receiver. The standard clearly considered the standard electric that the standard electric the standard electric to 110 V. AC receiver. Complete with tubers (977, 128A7, 3–128F7 and 12 A. C. Irail is built on nt of chassis. Electric driven or manual band change the Weight 28 lbs.

6 6 % x 7 " x 15". Complete with tubes \$39.95 Complete with tubes \$39.95

RADIO and TELEVISION ELECTRONICS



in all Technical Phases New Classes (Day and Evening) Start 1st of Dec., Mar., June, Sept. Free Placement Service for Graduates For Free Catalog write Dept. RN-54

RCA INSTITUTES, INC.
A Service of Radio Corporation of America
350 WEST 4TH ST., NEW YORK 14, N. Y.



Get More Service Calls with EICO DECALS For Store Windows & Cars.

Write EICO Brooklyn 11, N.Y. Dept. RD-6



NEW ironmes CUSTOM HI-FI COMPONENTS

216BA Basic Amplifier—New 2 in 1 Tri-Linear Triode amplifier. Wider frequency range. Higher power. Lower distortion. Improved version of two popular proved version of two popularion to operates as an advanced Williamson circuit. 2—in Tri-Linear position, it hecomes a super-powered tapped screen circuit. 599.50


New equalizer pre-amplifier— New equalizer pre-amplifier con-trol is period atyled cabinet. Full frequency range. Lowest distortion, Negative feedback around each stage. Exact equal-ization for any record by indi-vidual turnover and roll-off con-trols. Step-type base, treble controls, ideal remote control for finest amplifiers, \$99.50. Cabinet extra.

206PA De Luxe Pre-Amplifier— New complete equalizer pre-amplifier 4-knob control. Rec-ord compensator switch with 3-channel input selector for cor-rect playback curves. Feedback magnetic nick-un equalization mplifier 4-knub control. Rec-rd compensator switch with the control of the control of the control of the control of the cet playback curves. Feedback in records. Designed for ampli-nagmetle pick-up equalization, although the control of the cont

1008A De Luxe Ampillior—A basic unit for the average hi-fi home system. Full range repro-duction with low distortion and reserve power with tonal quality to rival costlier ampiliers.

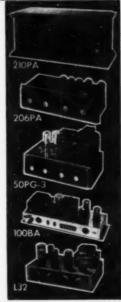Write teday for FREE detailed Information!





PRECISION ELECTRONICS, INC. 9101-RC KING AVENUE FRANKLIN PARK, ILL.

> COMMUNICATIONS RECEIVERS



COMPLETE KIT-This kit is complete COMPLETE KIT—This kit is complete with every part necessary to assemble into a finished receiver, including tubes and cabinet. Chassis is punched and marked. Mount the parts, wire it, align it and you have a fine receiver of commercial appearance, that can't be beat for 3 or 4 times the price. Parts layout, schematic diagram and alignment instructions are supplied. Special sonity F.O.B. Chicago and subject of the price of the parts of the price pressonly F.O.B. Complete Kit Special Special

JENSEN TYPE "J" CABINETS

Famous Peri-Dynamic Principle incorporated this Jensen Model J-61 Speaker Cabinet. Finish in simulated brown leather with grained effe with chrome trimmed grille. Besigned for speaker but adaptable for up to 10°. Wall or P. Mounting. 1634, High x 1234 Wide x 614 Deep. Original individual Jensen Boxed.

Regular \$9.30 Value for only ea. \$2.95 Lots of ten @ only ea. \$2.50

BOULEVARD ELECTRONICS, INC.

Mail Order Address: 1229 W. Washington Blvd., Chicago, III. Store Address: 4054 W. Belmont Ave., Chicago, III.

RCA WR-61A, a service-type color-bar generator; the RCA WR-36A, a portable dot-bar generator; and the RCA WO-78A, a 5" dual-bandwidth oscilloscope.

The line was developed with the needs of service technicians, design engineers, and color receiver manufacturers in mind. The dot-bar and colorbar generators are wholly new types of test instruments while the oscilloscope has been redesigned for color applications.

FLYBACK-YOKE TESTER

Electronic Instrument Co., Inc., 84 Withers Street, Brooklyn 11, N.Y. is currently offering a flyback transform-

er and yoke tester in both kit and wired instrument form.

The Eico Model 944 operates on the griddip principle and detects even a single shorted turn. It has separate calibration for air core and iron core flybacks to insure accurate testing of all

types of video flyback transformers.

The unit may also be used to check and test the continuity of any inductance whose impedance is not too low. The 41/2" meter with its three separate three-colored scales makes for easy reading. The tester measures 81/2"x5"x 5". In kit form it is known as the Model 944-K.

TY COMPONENTS
General Instrument Corporation's
F. W. Sickles Division, Chicopee, Mass. is now in production on a new line of television components.

included among the new products are a horizontal deflection yoke, a horizontal convergence coil for color sets. a low-voltage high-sensitivity deflection system for 17 and 21 inch blackand-white 70 degree sets, as well as flybacks, purity coils, and delay lines for color TV and a number of components which may be used interchangeably or with slight modification in both color and monochrome sets.

CONTACT CLEANER

Workman TV, Inc. of Teaneck, N. J. has developed an electronic contact and tuner cleaner and lubricant which is being marketed under the tradename "Wissh".

The new formula is designed to perform the dual function of cleaning parts, points, and tuners as well as acting as a lubricant for the equipment.

The product is now available at local jobbers.

U.H.F. TUNER

Granco Products Inc., 36-17 20th Avenue, Long Island City, N. Y. has developed a new "Hideaway" tuner for u.h.f. conversion applications.

For concealed installation with a minimum of effort, the compact metalcased tuner mounts at the rear of the TV set. Just the slide-rule tuning dial



RADIO AND TELEVISION SUPPLIES

protrudes slightly above the top while the tuning knob and selector switch are accessible at the right rear. The unit can also be placed on top or alongside the TV set if concealment is not required.

Three models of the "Hideaway" are currently available.

SELF-SUPPORTING CONTROL

Chicago Telephone Supply Corporation, Elkhart, Indiana has announced the availability of a new variable composition resistor which features a unique self-supporting snap-in bracket designed for mounting directly to a printed circuit panel.

The Type YGC-B45 simplifies assembly by snapping into place on the printed circuit panel. The control is held tightly by the mounting bracket during the soldering process and is permanently anchored to the circuit panel by solder. The bracket eliminates the need for a separate supporting panel and the usual mounting hardware.

Manufacturers are invited to write for complete details on this control.

PRINTED CIRCUIT AID

Gorn Electric Company, 871 Main St., Stamford, Conn. is now offering a new receptacle connector with 6, 8, 10, 12, 15, 18, or 22 contacts to receive printed circuit cards.

The body of the connector is compression molded melamine for high dielectric and mechanical strength. Contacts are of spring-tempered beryllium copper, gold plated over silver for ease of soldering and prevention of corro-

Design of the contacts provides positive mating of the connector with printed circuit cards of from .061" to .071" thickness. Proper tension to insure constant conductivity is maintained at all times. -30-

"Ultra-Linear" 6V6's

(Continued from page 45)

10 to 15 watt power range. For many people this power range is ample for all home requirements.

Careful listening tests have borne out the justification for the "Ultra-Linear" conversion. Particularly in the low frequency range there is substantial improvement. The solidness and clarity of the heavy bass passages is a revelation when one contrasts old and new amplifiers. The silkiness and smoothness of the treble range also stand out in a side-by-side comparison. In short, the improvement in measured characteristics is confirmed and substantiated by a corresponding improvement in listenability.

REFERENCES

1. Hafter, David & Keroes, Herbert I.;
"An Ultra-Linear Amplifier", Audio Engineering, November 1951
2. "Improving the Williamson
Amplifier", Radio & Television News, February 1953

OSCILLOSCOPES

ARE "GOLD MINES"!


how to use them fully on all types of service jobs!



Learn to handle the oscilloscope fully on all types of AM, FM and TV service work—and watch your efficiency MODERN OSS ILLOSCOPES AND THERE USES, a feat-innumed 236-page book by Jacob II. Butter, Jr., of the Allen B. DuMont Laboratories contains exactly the help you need—written in a way you can clearly understand. It shows you how to use your 'scope for fax accurate work on all types of jobs from trouble-hosting criterial commonents, how to analyze patterns fast and accurately. 370 helpful literature of the controls and how to analyze patterns fast and accurately. 370 helpful literature of the controls and how to said country of the controls and how to use oscilloscopes. How to interpret oscilloscopes and to mean so much to you in terms of helm alternative to helpful the controls and how to scilloscopes where the controls and how to scilloscopes and how to the controls and how to scilloscopes where the controls and how to scilloscopes and how to the controls and how to scilloscopes are the controls and how to scilloscopes are the controls and how to scilloscopes are the controls and how to scilloscopes and how to scilloscopes are the controls and ho

10-DAY FREE MAIL ORDER EXAMINATION

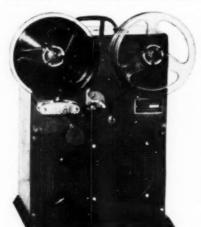Dept. RN-64, Rinehart & Co., Inc., 232 Madison Ave., New York 16, N. Y.



COMMUNICATIONS TYPE TAPE RECORDER

Ready To Operate COMPLETE

with plastic base tape, patch cord, and all features to record, playback, erase, rewind, dual track at two speeds, $7^{\rm L}_2$ and 3% inches per second.

SPECIFICATIONS: Solid aluminum drive mechanism. Heavy flywheel. 110 volt, 60 cycle AC phono motor. Shure Bros. Model 815 head responds to more than necessary to cover frequency sponds to more than necessary to cover frequency range of standard broadcasting. Takes seven inch reels. Wow and flutter sufficiently low to be im-perceptible to the ear in the service for which this machine is intended. Case 11"x15"x5". Natural wood finish. Total weight less than 15 pounds. Natural

NO MIKE REQUIRED

Properly damped built-in feature permits use of speaker for microphone with greater sensitivity than usual home recorder type crystal microphone. No breath blasts or nisses. May be used for close talking or will pick up normal room conversation. This feature eliminates mike and cord troubles. Positively does not sound like a cheap intercondition of the average radio. Any standard Ytal mike may be connected, however, if the user prefers. Patch cord permits recording directly from the output of any phone, radio, TV, or amplifier speaker.

MANUFACTURER DIRECT TO YOU—GREATEST TAPE RECORDER BUY EVER OFFERED

AMPLIFIER: Uses simple, novel three tube hi-gain circuit employing 12SL7, 50L6, 50Y6 to drive a good quality 6" speaker. This self-compensating circuit automatically provides erase cur-rent and DC bias for recording, and on playback will drive the speaker to full room volume without excessive distor-tion. Single control for record-play-back. This very simple circuit using high quality components is as easy to service as an AC-DC radio. No trick oscillators or special knowhow required

THIS ADVERTISEMENT WILL NOT BE REPEATED

Dealer-distributor arrangements will not permit us to make this wholesale, direct-to-user offer again. See this machine at your dealer's after July 1.

The requirements for low cost manufacture of this unit do not allow us to carry stock. ALL ORDERS SUBJECT TO SOME DELAY. We will forward prompt acknowledgement and shipping date upon receipt of your order. \$59.00 postpaid. C.O.D.'s one-third cash. ABSOLUTE MONEY BACK GUARANTEE with one-year parts warranty. Send orders to-

ULTRA-AUDIO BROADCASTING SYSTEM

1815 ADAMS AVENUE SAN DIEGO 16, CALIFORNIA

ELTRON TUBE:

GUARANTEED! . . . LOWEST PRICES EVER!

All tubes indiv
PRICE TYPE
45 5Y46
53 523
62 6A8
51 6K7
51 6AG5
41 6AG7
51 6AG5
51 6AG4
43 6AL7
51 6AG5
51 6AG PRICE TYPE

48 615GT

48 616GT

48 616GT

48 616GT

48 616GT

51 68A7GT

78 68A7GT

78 68A7GT

78 68L7GT

60 693

95 694GT

41 694GT

51 684GT

41 694GT

51 684GT

51 684GT PRICE TYPE
49 12AL5
61 12AT6
31 12AT6
31 12AT6
41 12AU7
65 12AV6
45 12AV6
65 12AV6
65 12AV7
66 12AX7
69 12AX7
69 12AX7
69 12AX7
69 12BX7
76 12BA7
76 12BA7
80 12BE7
77 12BA6
78 12BY7
43 12BY7
44 12BY7
45 12BY7
47 12BY7
48 12BY7
49 12BY7
4 All tubes individually boxed . . . unconditionally guaranteed for one year. idually boxed ...
PRICE TYPE PR .49 68C5 ...
44 68E6 ...
45 68E6 ...
46 68E6 ...
47 68E6 ...
48 68E6 ...
49 68E6 ...
49 68E6 ...
49 68E6 ...
40 68E6 ...
40 68E6 ...
40 68E6 ...
41 68E6 ...
42 68E7 ...
48 68C7 . for one year.
PRICE TYPE
43 125076T
43 125076T
23 1986667
44 1258466T
44 1258466T
45 12566T
46 13585
47 13556T
46 13584
46 13584
46 13584
46 13584
46 13584
46 13584
46 13584
46 13584
46 13585
40 12566T
40 12566T
40 12566T TYPE TYPE 0Z4 1A7GT 1B3GT 1H5GT 1L6 1L6 1L6 1L7 1R5 1R5 104 105 1X2 2A3 2A7 3Q4 3Q5GT 384 3V4 5V4G 5V4G 5Y3GT

\$5.00 list value Sonus Sox of Radio & TV components includ-ing resisters, condensers—con-trols, and many other items with each order of \$25.00 or more.

We now have a complete tine of special gurpose and frans-

mitting tubes in stock. Write for quotations on your requirements-Dept. T.

We guarantee your orders to be shipped the same day they are received! Minimum order \$10.00. 25% deposit on C.O.D. orders-

save parcel post charges. Orders accompanied with full remittance will be shipped prepaid anywhere in continental U.S.A. All orders subject to prior sale. Send for FREE Complete Tube Listing

FREE One alled this will be shipped FREE this any order accumpanying this ad.

	5 P E	CI	AL!	
wh	ile	20.	10	for
they	iast	39 -	ich \$3	.50
Type	Type	Type	Type	Type
106	154	1629	22	39 44
1076	1 H46	33	35/51	46
1070	ams	33	30	1550

TELTRON ELECTRIC COMPANY

428 Harrison Ave., Dept. RN-6, Harrison, N. J.

Phone: WAverly 6-1333

SAVE MONEY ON INSTRUMENTS!



How to do better, faster testing with fewer

How to use old instru-ments in new ways . . .

How to select the instruments you REALLY need unnecessary ones . .

How to evaluate instrumest readings and put them to practical use.

BASIC ELECTRONIC TEST INSTRUMENTS

by Rufus P. Turner

234 pages, 171 illus., Price \$4.00

Written especially for servicemen, amateurs and experimenters, this new book is a complete training course in instruments. Over 60 instruments—from the most modern TV pattern generators to grid-dip oscillators and special-purpose bridges—are fully explained. Work saving short cuts are outlined. You learn how to put your old instruments to new uses and thus avoid busing costly new ones. Tells all about current & soltage meters; ohmmeters and V 0. M's; V-T voltmeters; power meters; costilloscopes; r-f test oscillators; signal tracers; title testers; TV linearity pattern generators and dozens more. oscilloscopes; r-f test oscillators; signal tracers; tub-testers; TV linearity pattern generators and dozens more

READ IT 10 DAYS at Our Risk
Dept. RN-64, Rinchart & Co., Inc., 232 Madison Ave., New York 16, N. Y.
Send Turner's BASIC ELECTRONIC TEST INSTRU- MENTS for 10-day examination. If I decide to keep look, I will then remit 84.00 plus postage in full payment. Otherwise. I will return book postpaid and owe you nothing.
Name
Address



Built To Do Any Important Job Better!

Mobile Antennas

The finest low-cost mobile you can buy! Center-loaded coil can be used for 75 or 20-meter operation or variations secured by jumpering. Also available for special Civil Defense uses such as 2000-3000 kcs., 2374 kcs., and the 3105, 4325 and 4585 kcs. marine bands.

Get special Bulletin from your jobber or write direct.



5423 HIGHLAND AVE., NIAGARA FALLS, N. Y.

Mac's Service Shop (Continued from page 68)

by a man who has not been shaving too long, using only a v.t.v.m., proves to him he is right."

"He has built up quite a case," Barney observed.

"On the surface, yes; but it has a lot of holes in it. As I told him, you do not need to have a long gray beard to be a TV expert because television itself, as we know it, is hardly ten years old. Youth, with its eagerness to learn about new things, is a natural for this brand-new field. Probably the age of the youngster who fixed the set would be about the same as that of the men who are designing, testing, and flying our modern jets; and the Air Force seems satisfied with the job they are

"I also pointed out that when he called for service he was doubtless asked about the make, model, and symptoms of his receiver. Using this information, the technician called upon his technical knowledge and his rich fund of experience and probably made a very shrewd guess as to the likely cause of the trouble before he hung up the telephone. Then he consulted his service library, in which he would have invested a minimum of \$400, to determine exactly what tubes he would need to take along for that particular job. Finally, from his array of service instruments, in which he would have invested from \$1000 upwards, he selected the one best suited to determine whether or not the set could be repaired in the home if his original guess as to the cause of trouble proved wrong."

"The knowledge and equipment that a set owner sees displayed when a technician makes a home call is only a very small per-cent of that at his disposal," Barney threw in. "It's kind of like an iceberg that has nine-tenths of its bulk hidden below the surface supporting the one-tenth that is in plain view."

"Exactly," Mac agreed. "At the same time I must admit my neighbor has a point in there being inconsistency in service shop advertising. When one shop talks about the expensive equipment and extensive technical knowledge needed to perform service work and another stresses how quickly and easily it can be done right in the customer's home, this is confusing to say the least.

The inconsistency lies in the fact that two different types of service operation are being described. Abrupt set failures are usually produced by faults that can be quickly detected and corrected by a skilled technician right in the home. On the other hand, all television sets are subject to a gradual deterioration in performance as the months go by. Tubes lose a bit of their emission; condensers develop slight leakage: resistors change value; dirt accumulates on the tube face and on

RADIO & TELEVISION NEWS

STAN-BURN 5-P-A-R-K-S

CATHODE RAY TUBE SPECIALS

One	Year	Guarantee	3
G. E.		STAN-BURN	- 5
	14.95	108P4\$1	0.20
10FP4A	21.10	12LP4 1	1.90*
12KP4A	24.45		3.95
	18.75		1.90 *
12QP4A/B1014			1.90
Dumont	21.00		4.50
	28.75		5.60
	24.50		7.50
15DP4/B1014			7.50
Dumont	23.75		7.50*
16AP4A	30.95		7.50
	25.25	16CP4 or A 1	7.50
16GP4 or B	31.25	16FP4 1	7.50
	24.20		7.50%
C16KP4A			7.50
(Aluminum) .	28.35		3.00
	25.25		9.00
16WP4A	28.50		3.50
16WP4A	26.50		1.00
	31.25		
	24.25 30.30		8.50
	23.90		1.60
17CP4	23.90		2.60
	29.00		3.00
	41.50		24.00
20CP4	30.00		23.90
20LP4	37.50	19AP4A	24.90
	42.00	20CP4 2	23.95
21EP4	31.80		15.50
	36.35		16.50
24AP4	78.50		19.00 *
QUAN		CRT USERS	0.00
MAUD		CHT USERS	

24AP4 78.50 24AP4 49.00 QUANTITY CRT USERS
We will give you DuD allowances if you ship them
to us Prepaid. 10 CRT's minimum shipment. WRITE

ANTENNAE SPECIALS

RED DOUBLE "V" Antenna\$2.19 \$1.88
DOWELED INSERTS 2.98 2.79
Folded Hi Straight Low Quick Rig
WINDOW CONICALS 4.95 3.75
MASTS S FOOT SWEDGED 79
MM313 10 FOOT PLAIN 1.39 1.29 M
TV WIRE 42 MIL 300 OHM \$ 0.05 M Ft.
CHASSIS 630 TECH-MASTER
Model 1930 with Cascode Tumor \$149.50
OPEN FACE CABINET 42.00%
TAPE RECORDERS IN STOCK
PENTRON - Model 973C - 2-speed Tape Re- corder Write for Price
MADIO CRAFTSMAN
Model C400—HI-Fi Amplifier Net 42.90 Model C10—AM-FM Tuner Net 131.50
Medel CS00-Williamson Amplifier Net 99.50
We also carry MASCO-BOGEN FILOT, etc., Amplifiers,
Pre-Amps, FM Tuners and WEBSTER Tape Recorders.
8x9 PM Speaker \$ 3.98 630 Vert. Blocking
7" PM Speaker . 3.98 OSC. XForm89 70° Yoke 1.98 Cascode Tuners 14.95 2
630 Vert output Dumont 21.25 mc. 14.95
wpright 1.98 Famous Inputuner, 10.00
630 Vert., output TV Permanent Magnet 2 potted

AUTHORIZED DISTRIBUTORS for general Blectric, Kenrad, Tung-Bol, National Union, Be Wald, Regal, Automatic and General Spoters.

Be Wale, Regal, Automatic and General Be Wale, Regal, Automatic Custom-Built Radios for Plymouth, Ford, Chronolst and many others, always in shock. We carry a Complete line of Hi-FiGELITY and sound equipment. Send us your requests, we also carry a complete line of sopular makes of a complete complet

STAN-BURN RADIO und :

MOVING?

Please Advise
Our Circulation Dept.,
64 E. Lake St.,
Chicago 1, Ill.
Please Allow 30 Days

for Change of Address

the selector contacts; circuits drift out of alignment. The total effect of these defects is arrived at so gradually that quite often the owner fails to notice how much his reception has suffered. The only way in which the receiver can be restored to the kind of operation it had when it was new is for the receiver to be checked over completely, using expensive and delicate instruments that cannot be lugged around in a service truck. In other words, a receiver cannot practically be kept in first-class working condition unless it makes periodic visits to a service shop.'

Mac paused for a moment and then went on. "What I am going to try to do in our advertising is to persuade our customers that this is so. To get the point across, I'm going to resort to analogy. For example, to reach the women customers, I plan to say something like, 'If you are a good housewife, you sweep and dust every day; yet you still give your home a general housecleaning at least once a year. Your TV set needs a complete going over once a year, too.' For the men I propose something like this: 'If a fan belt breaks, you stop in a filling station for a new one and are on your way; but every so often you leave your car at a garage for a complete check. Your TV set deserves a careful annual inspection also.' Then I'll go ahead to urge our customers to let us have their sets while they are on vacation. This, of course, will help fill in our slack summer season; but more important, it will give us plenty of time to go over each set completely, locating and correcting every defect, and to bench-test it thoroughly-something we can't do when the customer is yelling for it back every hour on the

"Are you going to say this will prevent the customer's having set failures during the rest of the year?"

"No, because no one can honestly promise that. A tube heater can open up or a condenser pop at any time. Certainly the likelihood of failure will be lessened by these annual checks, but the principal advantage to the customer will lie in the fact that his set will be operating in tip-top shape. If a particular part fails, it can be replaced with confidence that this will be all that is needed to restore the set to perfect operation. We cannot guarantee uninterrupted reception with these annual checks, but we certainly will be able to promise good reception; and you know as well as I how many sets we see that produce some kind of a picture and some sort of sound but are a long, long way from providing the kind of reception they were designed to give."

Barney heaved a big sigh and slid off the bench. "And I was just looking forward to a nice long slow-business summer," he murmured.

"My deepest sympathy," grinned Mac. "You certainly are the most abused service shop assistant that ever soldered a lead!"



Totally unaffected by heat, humidity, or vibration

Talk about ceramic capacitors being made to order for mobile applications—Centralab DD16's fill the bill on every count.

First of all, they're just right for size. They were originally designed for use in electric shavers, so you know they're small. And that's one reason why they're so widely used as buffers in auto radios.

There are other reasons, also. Though DD16's are small in size, they're big in efficiency. They're 100% inspected and tested at twice rated working voltages. And they maintain high capacity and performance up to + 85° C. operation.

Yet, with all this, Centralab DD16's cost less than ordinary paper or mica capacitors of equal rating (35¢ list).

DD16's are conveniently packaged five per envelope, 25 units per carton. Keep a supply on hand for all your mobile needs. See your Centralab distributor.

Send coupon for bulletin 42-202.

Centralab

PIOF	LAB, A Division of Globe-Union Inc. Keefe Avenue, Milwaukee 1, Wis.
Cer	end me bulletin 42-202 on stralab Ceramic Disc Buffers
Name.	
Addre	15
City	() State

A RIDER BOOKS for JUNE

ADVANCED TELEVISION SERVICING TECHNIQUES

written by the RETMA (Radio Electronic Television Manufacturers Association) Pilot Training School Teaching Staff.

A completely NEW approach to books for TV service technicians. Written by experts who are teaching every day.—The contents have been tried and proven to be the finest ever written. Completely practical. A step-by-step approach to how to service every section of a TV receiver with every kind of test equipment—by resistance measurement, by voltage measurement, by means of the scope. It explains the uses of test equipment of all kinds in connection with TV receiver servicing, such as sweep generators—signal generators—vacuum tube voltmeters.

This is not a theory book! It is a book which every technician can use on the bench—and every student in a TV school can use, because it tells what-to-do and how to-do.if.

Never a book like this. Words alone cannot describe it. You have to see it to believe it! Approx. 175 (8½x11") pages.

Attention teachers:—the main book above and a laboratory manual for it as well as The Teacher's Guide also are available. Write for details.

write for complete 32 page

NEW RIDER CATALOG

SPECIALIZED AUTO RADIO MANUALS

Cover 5 years production (1950 thru 1954) of factory installed car radios, Identical data from other sources is just not available! Each volume contains: Parts list, Schematics, Tube layout, Voltages, Trimmer Location, Chassis Views, Chassis pictures, Dial stringing and complete installation and removal information.

VOL 2-A

Buick . . . Cadillac . . . Oldsmobile 200 (8½x11") pages, illus. \$3.00 VOL 3-A

Chevrolet, Pontiac, GMC Trucks, Chevrolet Trucks 128 (8½x11") pages, illus. \$1.80

COLOR TV DICTIONARY by J. R. Johnson

First complete explanation of new color TV terms with their definitions that everyone—service technicians, students, engineers, amateurs—interested in color television must be familiar with. This is more than a dictionary! Over 50 illustrations.

Approx. 72 (51/2x81/2") pages. R-C AND R-L TIME CONSTANT

edited by Alexander Schure, Ph.D., Ed.D.

FIRST IN A SERIES of review books written expressly for the student who is studying electronics or the technician who has studied electronics and wishes to understand Time Constant (R-C and R-L) more clearly. I supplements the contents of courses in text books which are on a technical institute level. Covers practical applications of Time Constant and how it effects circuit operation.

About 48 (51/2x91/2") pages.

Buy these books now from your jobber, bookstore—if not available from these sources, write to:



A VIDEO-MAGNETIC TAPE RECORDER

Details on an improved system for recording TV pictures on standard recording tape. The unit is now in production.

A RE-DESIGNED and improved video tape recorder has been announced by Bing Crosby Enterprises, Inc. of Los Angeles. The new "VTR" systems are now ready to be put into production in limited quantities for military applications.

Operation of "VTR" is based on a method which is introduced primarily to conserve tape velocity. In this way at least 15 minutes running time is possible from reels of reasonable size. Ten tracks are employed simultaneously for recording video information. An eleventh track records the necessary vertical and horizontal synchronizing signals while the twelfth carries the sound channel. On playback, signals from the ten video tracks combine to produce a high-definition picture.

An alternating signal is recorded on each track. Both positive and negative halves of this signal represent bits of picture information. This alternating rate is 169 kc. Consequently each head records 339,000 bits per second and since there are ten heads the system is capable of recording 3,390,000 bits per second, or video signal information up to 1.69 mc.

It is not necessary to employ bias in this form of recording since the minimum signal amplitude remains sufficiently high to result in linear amplitude response.

On playback each of the ten video heads is excited by a strong carrier frequency rate of 169 kc. amplitude modulated in accordance with the original video information. By means of a full-

> John T. Mullin, chief engineer of Bing Crosby Enterprises, explains new "VTR" system to TV and movie star Dan Duryea.

Close-up of the tape drive mechanism



wave rectifier, each signal is converted at the output of its preamp from 169 kc. a.c. to d.c. with a strong 339 kc. component. This rate is used to control the sampling pulse generation and timing since it exists even at minimum signal levels.

The vertical and horizontal sync signals are recorded in track number eleven since they must be played back free from the results of sampling. If this were not done, the playback sampling rates would cause the horizontal sync to lock in incorrectly at certain places in the picture.

The sound is recorded on one track by means of a high-quality FM system. A carrier of 100 kc. is modulated through wide deviation from 50 to 150 kc. On playback this results in a better than 65 db signal-to-noise ratio measured below ½ % harmonic distortion.

The machine occupies a floor area of 40" x 26". It operates the tape at 100 inches-per-second. It can accommodate reels of tape providing more than 16 minutes of continuous recording, thus sufficient overlap time is allowed for starting a second machine where half-hour programs are re-broadcast.

In operation, tape unwinds from the left spindle, past the capstan drive and head assembly to be taken up on the right hub. Rolls of tape are essentially self-supporting. No reels are required for ½" tape. For re-winding at high speed, a "tight winder" is employed. No equipment other than drive motors is concealed in the cabinet.



RADIO & TELEVISION NEWS

Certified Record Revue

(Continued from page 58)

Ponderous crashing chords from trombone and tubas. Trumpets, in a very high and strident register. Almost all of the brass work in this composition is in the form of short, staccato bursts and will tax the transient response of your system. The percussion I still don't believe! Thundering bass drum and tympani so sharp and clean, you can literally "feel" the tautness of the drumskins! In the section called the "Evocation of the Ancestors" there is a series of tympani rolls followed by another staccato figure, which is quite fantastic. I guarantee this will make you sit bolt upright, and start you to wondering whether your speaker cone can withstand this assault! The strings are in this work too, and are clean and edgeless. However you don't seem to notice them as much in this composition, partly because there is so much else going on, and partly because they are used in pizzicato fashion so often and blend in with the other rhythmic elements. In the finale, the "Sacrificial Dance," the orchestra virtually explodes in as madly orgiastic sound as you're ever likely to hear again. So furious and complex is this last section that Stravinsky made some revisions in it in 1943 to make it easier to perform. Mr. Dorati has essayed the original version and the Minneapolis has responded with magnificent precision. Acoustically, the recording has just the right amount of reverb. Too much in a work like this could be disastrous, making the sound run together and completely destroying its distinctive texture. In spite of all these huge sonorities and what may seem to some like special effects, especially in the percussion, I can assure you that this disc was recorded with the usual "Olympian" technique, meaning the single Telefunken mike and the transfer from tape to disc via the Miller cutter. Well, that's it. I know this review has been longer than most, but it was necessary to justify my enthusiasms. The recording conformed perfectly to the AES curve and the surfaces on my copy were quiet.

STRAVINSKY PULCINELLA

Cleveland Orchestra conducted by Igor Stravinsky. Mary Simmons, soprano; Glenn Schnittke, tenor; Phillip Mac-Gregor, bass. Columbia MI.4830. Gregor, bass. Columbi. NARTB curve. Price \$5.95.

While we are on the subject of Stravinsky, let's stay with him awhile and give "ear to this latest version of his one act ballet with song," "Pulcinella." The notation "after Pergolesi" is usually added to the title, because of the derivative source of much of the score. However, it would be a gross error to convey the idea that this work is anything less than a major and distinctive effort by Stravinsky. It is true that there are certain passages which are Let MILTON S. KIVER Help You Prepare For U.H.F.-TV, Color

Easy to TRAIN AT HOME This Practical Way!

Men with the right training in Television Servicing are in big demand . . . pull down big pay. T.C.I. TRAINS YOU RIGHT with easy-to-follow technical training designed by servicemen, for servicemen! You learn practical, professional type Television Servicing without leaving your present job. Included are money-making extras such as set conversion, master antenna installation, U.H.F.-TV NTSC Color System and field servicing short cuts. You can start earning Television money after the first few lessons. You learn to test, trouble shoot and repair all types of TV sets the proven, practical way!

HERE'S HOW YOU GET EXPERIENCE!

You train on your own large screen modern television receiver, furnished as part of your course. This set is yours to keep! As, an optional feature you can get two weeks of actual field experience out on service jobs and on the repair bench for Chicago's largest independent servicing organization. You learn Television Servicing by actually domy Television Servicing to sexually domy Television Servicing to you for the practical know-how you need to qualify for BIG MONEY in this fast-growing field! Age is no burrier, Many TCI students are over 40!

VETERANSI

ACT NOW! Mail coupon for FREE Catalog and SAMPLE LESSON. Write TODAY!

TELEVISION COMMUNICATIONS INSTITUTE

605 W. Washington Blvd., Dept. BB, Chicago 6, III.



YOU GET and keep modern large screen Television receiver.

YOU DO actual testing, servicing, trouble shooting and repairing

BEGINNERS! LEARN ABOUT BEGINNERS! LEARN ABOUT
NEW BASIC TV COURSE!
You don't need radio experience taryou You don't need radio extended the practical home-study train state cleavaint. Start eart of the training from the coupon for details.

MAIL NOW FOR FREE BOOKLET

MILTON S. KIVER, President TELEVISION COMMUNICATIONS INSTITUTE 605 W. Washington Blvd., Dept. B8 Chicago 6, III.

Rush hall facts on practical TV training. I am not obligated. Salesman will not call. Name Veterans: check bere Address City Zone ... State

BEGINNERS check here for information on Basic Television Course.

A SIGNAL GENERATOR OFQUAL WERSATILITY TTENTION

WIDE RANGE"

ONLY \$6750

706A

Equivalent in performance to signal generators priced as high as \$125.00

COMPARE THE VALUE—compare the price! You will find that the RCP 706A Signal Generator feature for feature is the finest performer in its class.

VERSATILITY: Continuous coverage from 150 KC to 220 Mc. in 8 ranges. Six FUNDAMENTAL ranges cover up through 55 Megacycles. ACCURACY: within 1% of calibration adjustment.

STABILITY: and constancy of calibration is assured by special electron-coupled circuit design, permeability adjusted coils and air trimmer capacitators.

MODULATION: 400 cycle sine wave audio oscillator with modulation continuously variable from 0% to 80%. Above 80% has no practical application. At this point tremendous distortion occurs in all sitnal generators. Unmodulated signal is available if desired

ATTENUATION: Ladder type step attenuator consisting of a multiplier and fine attenuator control AUDIO OSCILLATOR: 400 cycles at 50 ohms output impedance is available for external use-terminals

Eight scales are clearly calibrated—continuous read-ing from 150 kilocycles to 220 megacycles. Planetary drive gives vernier tuning with no backlash. Tube complement—6BA6, 68J7, 6X4.

A high quality instrument in performance, construction and appearance. Size 18"25" 27" Wt. 14 lbs. Complete with leads, ready for operation on 105-150 voits. Occupies.



Write for latest catalog to Boot, RE-S

RADIO CITY PRODUCTS CO., INC.



152 W. 25th Street New York 1, N.Y.



The new ERIE "D-54" Catalog includes descriptions of the new line of Temperature Compensating Tubular Ceramicons and Disc Ceramicons . . . plus the long-time ERIE Standard numbers and all items introduced since publication of our last catalog. Many items are illustrated.

Ask for it at your distributors, or write Dept. B for your copy.

ELECTRONICS DISTRIBUTOR DIVISION Factories ERIE, PA. + LONDON, ENGLAND - TRENTON, ONTARIO

ERIE RESISTOR CORPORATION Main Offices ERIE, PA

MAKE MONEY.

practical way

Pay as You Wire

I WILL HELP YOU to start learning TV the practical way — by assembling a TRANSVISION TV RIT in EAN STAGES. For only \$39 you get PACKAGE #1 (standard first pkg, for all of our kits). This package gives you the BASIC CHASSIS and over 450 TV COMPONENTS with complete Instructions, Drawings, Photos, Service Booklei, and a year's subscription to my "TV and Electronics Notes". When ready, you order the next stage (pkg. #2), etc. Low prices make your complete.



0

Shows 6 Great TV Kits:

EXCLUSIVE: Only Transvision TV Kits are adaptable to UNF. Ideal for FRINGE AREAS. No Provious Technical Knowledge required. Write now!

TRANSVISION, INC., Dept. NG. NEW ROCHELLE, N. Y. MAIL THIS COUPON TODAY --

Educational Director
TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. N6

Send FREE copy of your new TV Kit Cutolog.

Address

TUBES

PRICES SLASHED FAR BELOW WHOLESALE!

Standard brands only! One of largest stocks in U.S. We sell-buy-trade. WRITE FOR FREE CATALOG JUST OFF PRESSES.

.70 | 65F5 .90

184	1.20	65F7 1.00	0A2 .95	
147	.85	6507 .75	082 .99	
108	.80	65H7 .78	1021 3.50	ė.
1Ce	1.00	6517 .60	2AP1 6.95	
107	1.00	65K7 .60	2051 3.99	ŧ.
1021	1.00	SSL7GT .7S	2021 1.19	
165	1.00	65N7GT .85	2826 3.25	
167	1.00	65Q7 .55	2X2 .69	1
1LA4	.90	69R7 .70	3FP7 1.99	
1LC6	.90	6557 .90	3GP1 1.99	ŀ
ILNS	.90	65T7 .65	3HP7 2.99 SAP1 3.25	
INSGT	.65	6T8 .75	58P1 3.25	
184	.90	6V8 1.00 6V6GT .70	58P4 3.25	п
185	.78		5FP7 1.95	п
1X2A	.90	6W4GT .60 6X4 .60	12AY7 .50	
3A4	.80	eved .as	1148 .49	
306	.49	764 .99	304TL 6.95	
3Q4	.60	707 .90	701A 4.50	
SOSOT	.80	707 .90	807 1.50	
354 574	1.40	7N7 .90	811A 3.49	
5U40	.70	12A6 .85	813 7.95	
5V4	1.00	12AT7 .98	829 6.50	
SX4	.65	12AU7 .95	8308 1.95	
SYBGT	.45	12C8 .80	866A 1.30	
SY4G	.55	12H6 .62	872A 1.95	
6A7	1.00	1215 .60	931A 4.50	
606	.98	1247 .80	938 5.80	
606	.85	12K8 .89	955 .49	
6F6	1.10	125C7 .89	956 .49	
6F7	1.25	125F7 .99		
6FBG	1.10	125M7 .70	957 .40	
6666	.85	125L7GT .92	958A .89	
646	.65	125N7GT .80	809 2.90	
618	.68	125Q7 .65 12587 .49	878 2.00	
BBIB	1.00	125R7 .49 1486 .79	922 1.30	
6K7	.75	2316GT .69	923 1.30	
6L6 6L7	1.50	31 .39	959 1.50	
6L7	.98	33 .39	2050 3.30	
654	.60	34 .39	2051 .95	
65A7	.80	4925 .60	8654 1.50	
mant.		4444 160		

VEEDER RT. COUNTER



ELECTRONICS Dept. R-E 7552 Melrose Ave Los Angeles 46,

\$1.25

little changed from Pergolesi, but the rest bears the unmistakable imprint of Stravinsky. He has freely transposed, embellished, introduced the rhythmic figures so typical of his other works, and changed harmonies. The result is something that sounds "18th Centuryish," but obviously is not.

If you are at all familiar with Stravinsky, no more than a few bars will serve to identify this as his music. The parts for voice do not bear any direct relation to the plot of the story and are in fact, more or less incidental. Brief as they are, they are nonetheless pleasant little airs and are sung admirably by the soloists involved. Stravinsky has handled the orchestra so well, that although there are no tympani or percussion instruments in the score, the strength of the rythmic means, especially in the strings, is such that you would swear this is percussion. A thoroughly delightful work, this is by far the best version on discs. The other versions are more fragmentary and are not particularly distinguished for their sound. Here, the knowing hand of Stravinsky is much in evidence. Under his direction this is a much more lively and spirited work than a hearing of the other discs would seem to indicate. The sound is splendid. Columbia has managed to combine the need for sharp. "close-to" recording, essential to the delineation of this work, with a good spacious acoustic perspective. Woodwinds are especially clean and crisp. If you have never been overly impressed with this work, try this version. It could well change your mind. Approximately 2 db of bass boost added to the NARTB curve made the recording sound better to me.

MASSENET WERTHER

Ferrucio Tagliavini, tenor; Pia Tassi-nari, soprano; and others with Orchestra of Radio Italiana (Turin) and chorus conducted by Francesco Molinari Pra-delli. Cetra C1245. AES curve. Price \$17.85. Three discs.

This is a brand new recording of "Werther," superior in nearly all respects to the other effort on Urania. The opera itself is not heard very often these days, which seems strange to me as it has much to recommend itself over many "staples" in the current repertoire. Taken from Goethe's "The Sorrows of Young Werther," it is admittedly a gloomy work. Nevertheless, it is so cleverly written, that the characters in the secondary roles add a great deal of life and zest to the plot. At least they act as a balance to the virtually psychopathic Werther. Mounted in a snappy new setting by the "Met," and cast as well as has been done in this recording, I'm sure the opera would find new favor. It is in the casting where this recording shines, as the illustrious Tagliavini gives an exciting and moving portrayal of Werther. Pia Tassinari is in splendid voice as the beloved "Charlotte." Marcello Cortis is an effective "Albert" and Vittorio Neviani, a sympathetic "Sophie." The other roles are equally well sung; espe-

- Grind your own crystals to desired frequency for ham bands.
- * No elaborate frequency measuring equipment needed. Your receiver is sufficient.
- * All crystals tested for activity!

CONTENTS OF BASIC KIT

- A) 9 good, commercially-made crystals for re-grinding. Mounted in original holders with fundamental frequencies indicated on holders.
- B) I master crystal for calibration purposes.
- C) Crystal grinding components.
- D) Easy-to-follow instructions.
- E) Material to re-mark holders to your new frequency.

Kit No. 1 1 80 Meters

Includes Basic KIt and crystals mounted in DC-34 & DC-35 type holders. Pin spacing: 34". Crystal holder dim.: 136" x 136" x 136" x vin the banana plug \$7.95 sockets. Price per COMPLETE KIT...

Kit No.2 M40 Meters

Includes Basic Kit and crystals mounted in FT-243 holders. Pin diam.: .093". Pin spacing: .486". Holder dim.: 13/16" x 11/4" x 7/16". Will fit into any standard octal tube

Kit No. 3 1 2 Meters

Kit No. 4 to 2 Meters

CRYSTAL BUYERSI WE HAVE LARGEST STOCK OF CRYSTALS IN THE WORLDI SEE OUR APRIL '54 ADS IN RADIO & TV NEWS AND C.Q. FOR COMPLETE LIST.

NOTE: Check, cash or M.O. IN FULL MUST ACCOMPANY ORDERS, NO C.O.D. Items sub-ject to prior sale and change of price without notice.

805 S. UNION AVE., LOS ANGELES 17, CALIF Fhanet: DUnkirk 1-3020 - DUnkirk 1-3029



MOVIES ON APPROVAL

DANCE FILMS for home movie shows. Write today and we'll send you a 50-ft. POSTPAID ON APPROVAL. (Return film and 25c within 5 days without obligation, if it's not worth more than the \$1.50 we ask). BONICA NEWSREEL CLUB, 6516-RT Avenue, Hollywood 28, California.

cially noteworthy is Giuliano Ferrein as the "Bailiff." The ensemble work was good, but it is in this department that the Urania disc at least was its equal. Pradelli lends his considerable talent to the proceedings and his orchestra is always complementary and in balance with the vocalists. Sound is generally well above average, as far as operatic recordings go. Strings were smooth, woodwinds a little ragged, brass was bright and clean, but unfortunately at times became somewhat strident. Percussion good, except for occasional muddiness. Over-all, a thoroughly enjoyable recording, highly recommended to those of you who are looking for an opera a little off the beaten track. AES curve was adequate with a slight assist in the bass and a slight cut in the treble helping the balance.

PIANO CONCERTO #3 PROKOFIEV

PIANO CONCERTO #3 Julius Katchen, pianist with L'Orchestre de la Suisse Romande conducted by Ern-London LL945.

est Ansermet. Lor curve. Price \$5.95.

This record would be distinguished if for no other reason than the coupling of these two great concerti. This has always seemed to me to be an eminently logical pairing, instead of the opposite-ends-of-the-poles repertoire both works have been saddled with. Happily, there is much more musical substance here than in previous recordings of these concerti. The Bartok concerto has always impressed me as being one of the composer's most listenable works. Oh, it has all of the usual dissonances associated with Bartok, but its construction is so clever, that this element seems less apparent. In addition, since this is the last of Bartok's works and a product of his more advanced years, it is possible to detect more than a little "mellowing" in his musical philosophy. Of the two other recordings of this work, only the Sandor-Ormandy version on Columbia offers this new disc any competition. Julius Katchen is a better pianist than Sandor, and Ansermet's supporting reading more perceptive than Ormandy's. There is much to be said for Katchen's precision and ultra-careful phrasing, but it is this very quality that keeps this from being an outstanding reading. Sandor misses a few notes here and there, and in general is not the craftsman that is Katchen. But for all this, his reading is full of dash and fire and Katchen suffers by comparison. Soundwise this is a different matter. The Columbia piano had a tone that was on the hard side, and the orchestral accompaniment was restricted in range. This is not too surprising, since the Sandor recording appeared early in the LP catalogue, and I'm pretty sure it was a transfer from 78 rpm. Good sound for its day, but not equal to this present recording. The piano here is liquidly beautiful, very clean toned, little evidence of wow or flutter. The piano is used quite percussively in this score, and this quality is recorded with virtually no harshness

COMMUNITY MASTER TV **Antenna Systems**



The Finest Systems at Lowest Cost of Installation and Maintenance

Proven in thousands of difficult installations

A few of the many ADVANTAGES

- 1. Highest power output allows longest cable runs.
- 2. Central system with only I point of service.
- 3. Operates up to 500 TV sets from I amplifier.
- 4. Lowest cost per out outlet.
- Maximum signal to each set with minimum interference.

Engineering advice. Send us your problem for quick solution,

. Also: COIN TV SETS

featuring custom-quality, powerful fringearea chassis up to 27".

> Get full details about these 2 great products now. Write:

TRANSVISION, INC. NEW ROCHELLE, N. Y.

******************* WORLD'S LARGEST MANUFACTURER OF CUSTOM BUILT TELEVISION

SILVER ROCKET 630 CHASSIS Featuring Syncromatic Tuning

NO DRIFT UHF-VHF-DX

ONLY THE MATTISON 630 ELIMINATES DRIFTING APART OF PICTURE AND SOUND ON UHF, VHF and DX RECEPTION. SELECT YOUR CHANNEL... SOUND IS AUTOMATIC. (Syncromotic tuning is an exclusive Mattison 630 Circuit)

Tube Complement: 29 tubes 3 rectifiers 1 CRT

SILVER ROCKET **630 Chassis with** built in UHF Tuner



• All Channel JUHF Tuner

UHF Cascode I.F. amplifier adds additional I.F. stage. Very important because UHF transmitters operate with moderate power and RECEIVER must be ensitive to give top notch UHF performance.

SILVER ROCKET 630 CHASSIS · with TUNEABLE ·

BUILT-IN BOOSTER



Tuneable Booster

Broad band single knob centrol pre-amplifier
built in te eliminate long leads which may
cause regeneration and attenuation of signal. ONLY THE MATTISON 630 CHASSIS HAS AN ALL CHANNEL TUNEABLE BUILT-IN BOOSTER THAT INCREASES SIGNAL STRENGTH UP TO 10 TIMES.

ALL CABINETS MADE IN MATTISON'S OWN CABINET FACTORY. AVAILABLE IN EVERY FINISH AND STYLE. WRITE FOR COMPLETE CATALOG

DEALERS! SERVICE MEN! Here is your opportunity to become the "Important" TV Dealer in your area for THE FINEST CUSTOM-BUILT LINE OF TV RECEIVERS. FREE! Write for Mattison's merchandising portfolio explaining the "UNASSEMBLED PLAN" and "\$1,000,000 FLOOR PLAN."



Mattison Television & Radio Corp. 10 West 181st St., Dept. RN, N. Y. 53, N. Y. ****************** or "ringing." Ansermet maintains a fine rapport with the pianist throughout the work and his orchestra is well recorded with sharp, incisive strings, clean woodwinds, and solid, authoritative percus-

In the Prokofiev 3rd, we have a similar situation with the Bartok recording, though on a lesser scale. By that I mean that Katchen again comes off as the best pianist, as compared to the artists on the three other discs of this work. And once again, in spite of his technical superiority, his reading is less exciting than is, for instance, the late William Kapell's. I'll admit that Kapell's essay of the score might be called theatrical; but this music can stand up to that sort of treatment and I find I prefer it to the leaner, less hurried, more deliberate reading of Katchen. The situation is the same with the sound. The London disc is far superior in all respects to either the Angel, Victor, or Columbia efforts. In fact for many of you this superiority of sound may be the deciding factor, for if the Katchen readings are not outstanding, they are nonetheless honest and competent. All a matter of taste in this. A few db of bass boost helped the ffrr curve in my set-up. Quiet surfaces.

LISZT MEPHISTO WALTZ CHOPIN

BARCAROLLE IN F SHARP MINOR Leonard Pennario, pianist. Capitol H8246. AES curve. Price \$2.98. The popular "Mephisto Waltz" is

given a supercharged reading on this disc by Leonard Pennario, a young pianist who is really making quite a name for himself. He takes the florid, flamboyant passages of this work at a terrific pace, and from his sheer momentum makes this overblown piece newly enjoyable. In the "Barcarolle," Pennario calms down and the result is a finely wrought performance, a model of balance and good taste. The sound of the piano is good on this disc, but for my taste a little too "close" with "dry" acoustics. The AES curve was adequate without further adjustment. Very quiet surface.

BARBER ADAGIO FOR STRINGS ROUNDS COPLAND QUIET CITY CRESTON

TWO CHORIC DANCES Concert Arts Orchestra conducted by Vladimir Golschmann. Capitol P8245. AES curve. Price \$5.70. Another in the exemplary series of

the Concert Arts Orchestra so successfully introduced last month by Capitol. Some of Capitol's very finest recording is to be found in this series, as this latest disc will testify. Two of the numbers have been recorded before on Mercury discs. These are the "Adagio for Strings" and "Quiet City." There is very little to choose between the performances on the two labels. The "Adagio" is conducted at almost the identical tempo by Hanson and Golsch-

RECORDING TAPE (PLASTIC BASE) 40% OFF (NEW)

ratus vs. phistic tape with plastic reel included. Each reel individually boxed. Choice of nationally famous top quality brands such as: 28001 3.201 Revves (SPN-12: 3.20; Audio (1251) 3.25; Sectén (111.4) 3.25; Paracoustic (711.4) 3.25; Irish, Professional grade (211 RPA) 3.30.

FREE! A 7.95 tape carrying case included with purchase of 12 new tapes!

* * * * * * * * * * * * USED RECORDING TAPE (PLASTIC BASE) 1200 Feet Wound on Plastic Reels

\$1.99 (1-23) reels \$1.75 (48-95) reels \$1.79 (24-47) reels \$1.71 (96-143) reels \$1.68 (gross or more)

**Standard hub plastic reel sup-plied with above. For tape wound on professional 214 hub, add 5¢ extra per reel. **Empty 7" tox (2 cover) for above reels 5e each (not sold at this price separately).



of new tape, recording blanks, at low prices. PLEASE INCLUDE

COMMISSIONED ELECTRONICS CO. 2503 Champlain St. N.W., Washington 9, D. C.



Electronic Engineers

MORE JOBS than graduates

Demand for our engineering graduates exceeds supply.

Effective placement. Study in this world-famed college established 1884. Quarters start June. Sept., Jan., March. Approved for Korean Vets.

Bach. Sci. degree in 27 months

Complete Radio Eng. courses . . . TV, UHF and FM. Also Mech., Civil, Elec., Chem., Acro. and Adm. Eng.; Bus. Adm., Acct. Small classes. Well-equipped labs. Modest costs. Prep. courses. Write Jean McCarthy, Director of Admissions for Catalog and Campus View Book.



TV INDOOR ANTENNA \$125

The best antenne buy of the year
A high gain, low loss metal tape antenna in
kit form, you assemble it. This indoor station
getter is equal to or better than an outdoor job.
Your choice of channels 2 thru is (State channels
desired). Complete kit mailed Postpaid only
\$1.75.

RIVERWAY INDUSTRIES—A
1135 - 8th Ave. LONGVIEW, WASHINGTON

Please Mention RADIO & TELEVISION NEWS

When Answering Advertisements

mann and the trumpet soloists in "Quiet City" have no particular advantage of one over the other. The Mercury disc has a slight edge in the matter of sound. "Rounds" and the "Two Choric Dances" are new to LP. "Rounds" is scored for string orchestra, and is typical of the work of David Diamond. Well constructed, with an economy of means, it belongs to the "listenable" school of modern music. Excellent string work throughout this work. The outstanding work on this disc is the "Two Choric Dances" of Paul Creston. This work is liberally sprinkled with atonal devices, which however are used to good purpose in the dance rhythm-jazzy type scoring. This piece really gets wound up and generates a lot of excitement in the closing passages. The recording is excellent with good clean strings, nice bright brass and notable percussion. I think the first disc in this Concert Arts Orchestra series was the better of the two so far recorded, but this is still decidedly worth your while. Golschmann maintains an excellent balance and tempo in all of these works, and the orchestra (as I observed last month) is very good indeed. The disc conformed perfectly to the AES curve. Usual quiet Capitol surfaces.

BACH, J. S. CHRISTMAS ORATORIO

Gunthild Weber, soprano; Lore Fischer, soprano; Heinz Marten, tenor; Horst Gunther, bass; with orchestra and choir of Detmold Academy of Music and Collegium Pro Arte, conducted by Kurt Thomas. London "Editions de L'Oiseau-Lyre" 01.50001/3. NARTB curve. Price \$17.85. Three discs.

This is a notable recording in many ways. Primarily significant is the fact that this is one of the initial releases by London of the long-awaited "Editions de L'Oiseau-Lyre." This French company, which is now tied up to London for release of its material in this country, has a long history as an organization catering to the musical connoisseur. A listing of its first releases by London is indeed imposing, and I am looking forward most eagerly to hearing these and subsequent releases. The "Christmas Oratorio" has been recorded twice previous to this version. This effort is by far the best, although the Vox discs have many good points. In matter of performance, this is closest, I think, to the original intent of Bach. Grischkat's tempo was too draggy in the Remington version, and Grossmann's tempo a little too fast in the Vox reading. Thomas takes the middle road between these extremes and comes up with a finely paced, beautifully detailed reading. He maintains a good balance between the vocal elements and the orchestra, and uses good taste in the matter of the climactic sections. The Vox edition had a generally better level of soloists than this version, but these are competent enough with an especial bow to Lore Fischer for her splendid work. Sound is much superior to either the Vox or the Remington editions. Brass is heavy, weighty, and imposingly authoritative.





HERMON HOSMER SCOTT, INC.

385 PUTNAM AVENUE, CAMBRIDGE 39, MASSACHUSETTS

FOR THOSE WHO SEEK THE ULTIMATE IN HIGH FIDELITY CABINETS



Klipsch REBEL IV by Cabinart

- A Klipsch Corner Horn Enclosure designed especially for manufac-ture by Cabinart.
- Two-way system performance. So flexible in design so as to provide you wide latitude in determining your listening requirements. Removable panel allows for a variety of speaker com-binations. For example, in the 12" Klipsch you can install a single 12", two 12" speakers or a tweetertwo 12" speakers or a tweeter-woofer combination.
- Attractively styled to blend with any interior decor, the Klipsch Rebei IV by Cabinart cames in Limed Oak, ney Walnut, French Mahagany and Black Lacquer.

"Popularly Priced"

*\$69.00 Net for 12" model

*\$87.00 Net for 15" model


by Cabinart

G& H WOOD PRODUCTS CO.

75 NORTH 11th STREET, BROOKLYN 11, N.Y.

Pioneers in radio furniture for high fidelity equipment

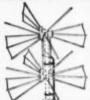SUPER RECEPTION IN FRINGE AREAS AT BARGAIN PRICES!



360° Super Directronic Electronically Rotates in All Directions VHF-UHF CHANNELS

Exclusive Engineering and de-sign cuts costs to

Powerful, 24 element 2 bay Directronic antenna is electronically beamed to any transmitter in fringe area by 6-position selec-tor switch. No motors or

TREMENDOUS BARGAIN IN CONICALS

TRI-X CABLE.



2-Bay 16-Element CONICAL ARRAY

WITH HI-BAND ADAPTERS STURDY 35" ELEMENTS

\$499 EACH IN Single Lots

3 Two-Bay Arrays per carton without Tie Rosts 13.50 carton 4 Bay Ultra-Fringe Stacking Assembly for Above Model 4B 1.95 set

New Spring-Summer Catalog Available

lational Electronics

HOUSE OF TV VALUES 106 Delco Building Cleveland 3, Ohio

CONVERT YOUR 6V6 AMPLIFIER TO ULTRA-LINEAR OPERATION



ULTRA-LINEAR WILLIAMSON **ACRO TO-310**

Get more out of your amplifier with the ACRO TO-310. Just a few resistors and condensers are involved in converting to ultra-linear operation — layout remains the same

SPECIFICATIONS ● Response-1 db. 2 cps. to 200 kc.

- 30 watts of clean power within 1 db. 20 cps. to 30 kc.
- Less than 1% IM at 20 watts.
- Square wave transmission to 50 kc.

ACRO TO-300 ... net \$24.75 ACRO TO-310 ... net \$18.75

(TO-310 used to change over 6V6 amplifier to ultra-linear operation)

ACRO TO-330 ... net \$39.75

(Push-pull parallel ultra-linear operation using 4 KT 66's, 5881's or 807's to deliver a power output of 60 watts.)

Shipping wts. (10-300-7 lbs.)

(10-310-6 lbs.) (10-330 -- 17 lbs.) ORDER BY MAIL!

Send check or M.O. Include postage.

SERVICE CO. OF PENNA., INC. 7th & Arch Streets, Phila. 6, Pa. Strings are very smooth, and there is some wonderful woodwind and organ reproduction. The chorus numbers 220 members and seems better disciplined than the choirs used in the other two readings. This is a massive work, and a poor performance can make it seem endless. This version avoids this difficulty and can easily be digested in one listening. I would not vouchsafe to say that this recording is the last word on the "Christmas Oratorio," but it is a fine addition to everyone's library until something better comes along; since this work is very large and expensive to record, you might have quite a wait. 2 db of bass boost on the NARTB curve made the recording sound better to me. Surfaces were quiet.

RORODIN

POLOVETSIAN DANCES IN THE STEPPES OF CENTRAL

IPPOLITOV-IV ANOV CAUCASIAN SKETCHES

New York Philharmonic Orchestra conducted by Dimitri Mitropoulos. Columbia ML4815. NARTB curve. Price \$5.95.

A potpourri of works in the standard repertoire, which have been recorded numerous times before. As far as performance is concerned, Mitropoulos shines here with vigorous, forceful readings. Except for the "Caucasian Sketches," in which Desormiere on London is a notch or two better, these are the best readings of these warhorses available. The superiority in sound is even more evident and hi-fi fans will love the "Polovetsian Dances." Plenty of the bing and the bang here! Beautifully clean cymbals and big, big, tympani. Exceptional string tone, and playing by the N. Y. Philharmonic is superb. If you don't already own these works or you're looking for better sound, this is highly recommended. Disc followed the NARTB curve perfectly. Surfaces in my copy a little "ticky."

A CEREMONY OF CAROLS

The Copenhagen Boys with Enid Simon, harpist; Mogens Woldike, choirmaster, conducted by Benjamin Britten. Lon-don LD9102. ffrr curve. Price \$2.98. This recording is typical of what

London is turning out in their new lowpriced (\$2.98) LD series. I absolutely agree with London that there is a great mass of musical material that is too short for a 12" LP and too long for 45 rpm discs. The 10" LP has been an obvious medium, except for the bug-a-boo of price. Now that this has been overcome, I think you will find a growing catalogue of these "in between" works is a certain development. London is also operating on the premise that the discs must be first class in sound as well as repertoire, if they are to succeed. Suiting words to actions, their first releases in this series are quite splendid. This lovely work of Britten has been recorded by the Robert Shaw Chorale on Victor, where it occupied one whole side of a 12" LP. The Shaw version was very good with his wonderfully precise singers, but I find the boys' choir used herein, much



12 basic shaft types available from 3/8" to 10" in length, including auto types, insulating nylon, many others

Adashaft Radiohms

Centralab's patented Adashaft design lets you (1) speed service; (2) give your customer both control and shaft for no more than the cost of

an ordinary control.

The basic Adashaft control has a stub shaft you can use "as is" as a short, screwdriver-slotted unit. Or you can easily attach any of 12 basic shafts. Thus, you can have any resistance you want, including dualtapped types - with any shaft. An instant, positive lock gives you a solid, well-aligned unit every time.

After adding the shaft you need, you can convert the unit to a switch type, with Centralab "Fastatch" type KB line switches.

Your Centralab distributor has Adashaft Controls in the popular model "B", 15/16" construction. Order from him.

Send coupon for bulletin 42-199 with complete Adashaft information.



Adashaft Kit No. AB-100 An assortment of 39 most popular most popular controls, switches, shafts, shaft extensions, and couplers. In hinged-lid plastic box. \$13.38 net.

Send me Centralab bulletin 42-199.
Name
Company
Address
CityZoneState

CENTRALAB, A Division of Globe-Union Inc.

more in the spirit of the music. The boys are beautifully trained and benefit, of course, from the composer's guidance in the performance. The recording is startling in its clarity, with the harp in perfect balance with the young voices. If you don't know this music, try this for a real off-beat vocal treat. One of the loveliest things on records. The ffrr curve was right" as is, no fiddling necessary.

MATHIS DER MALER CONCERT FOR STRINGS AND BRASS

Philadelphia Orchestra conducted by Eugene Ormandy. Columbia ML4816. NARTB curve. Price \$5.95.

A new recording of one of my favorite works, and one that was badly needed. "Mathis der Maler" is certainly one of the masterpieces of twentieth century music and I think the best thing to come from the pen of the versatile Paul Hindemith. Intensely dramatic, the score is a tremendous achievement in the art of powerful, evocative orchestration. You will find the atonalities that Hindemith is noted for in this music. You will also find some of the most beautiful, almost 'other-worldly" music ever written.

Ormandy's performance is magnificent. While the old Hindemith performance on Capitol is good, it suffers from the relatively poor sound, and the fact that it is broken up on two sides of a 10" LP. Curiously, the Hindemith and Ormandy versions are almost carbon copies in matter of tempo, something that does not happen too often. Ormandy is evidently fully "at home" with this music and he makes the best of it. The strings of the Philadelphia are a miracle of tone and precision. brass is properly weighty, and percussion is more than adequate to the demands of the score. I thought that the reading by Guido Cantelli was very good on the Victor label, but Ormandy's exposition is head and shoulders above it.

The "Concert Music for Strings and Brass" is more in keeping with what most people expect of Paul Hindemith. Dry, almost astringent scoring characterizes this piece, which also is a much more dissonant affair than the "Mathis der Maler." Again the string work of the Philadelphia is cutstanding and there is also some magnificent playing from the French horns and trombones. I noticed something I thought was odd when I listened to both of these works, one after the other. This was that while the "Mathis der Maler" is an excellent recording, it did not seem to have the brilliance and range of the "Concert Music for Strings and Brass. An examination of the record jacket disclosed that both works were recorded at the Academy of Music in Philadelphia, but nearly a year separates the "Concert Music" from the earlier "Mathis der Maler." I concluded the difference in sound was due to the constructional changes which were undertaken at the Academy during 1953, and which were tacitly announced with



OPERATIONS" by HAROLD E. ENNES



on Telecasting

Director, Technician, and to all Students of CONTENTS:

A Partial List of Authoritative Chapters:

Basic Telecasting Equipment; The TV Cam era; The TV Control Room; Fundamentals of TV Studio Lighting and Equipment; Network Program Relay Systems; TV Operational and Maintenance Practices; Technical Production of TV Shows; Field Equipment and Micro-Wave Relays; Analysis of Video and Audio Transmitting Plants; Technical Definitions
- PLUS HUNDREDS OF OTHER SUBJECTS

Here, in one complete, easy-to-understand volume is the whole fascinating story of Tele-casting operations. Whether you are a Chief Engineer, Production Director or Technical casting operations. Whether you are a Chief Engineer, Production Director or Technical Director; if you are now working in or planning to work in TV, or if you are simply interested in Telecasting, this book is meant for you. Here is practical, useful information that makes you familiar with the equipment and techniques used in Telecasting, tells you everything—answers all your questions about TV production and transmission. If you work or are interested in Telecasting, you'll want this vast wealth of reliable information—you'll want this book in your library. Order your copy today! our copy today!

600 Pages, 450 Hustrations

	Hard Covers \$795 ORDER
	Order from your electronic parts distributor or bookstore, or write direct to Howard W. Sams & Co., Inc. 2203 E. 46th St., Indianapolis 5, Ind.
	My (check) (money order) for \$
į	Name
į	Address
i	CityState

Communication

Engineers

with experience in the fields of

Systems Engineering Information Theory Circuit

Development
Electromechanical
Development

Equipment Engineering

THE OPENINGS

Advancements in the fields of wave propagation, translation of information, communication theory, circuit techniques and equipment miniaturization have created a number of new openings for qualified engineers in the Hughes Advanced Electronics Laboratory,

AREAS OF WORK

Assurance is propay anten relocation of opplicant will not cause disruption of an urgent mulitary project.

The communication group is concerned with the design and development of unique radio communication systems and with exploiting new radio communication techniques. Specialists in propagation phenomena, antenna systems, network theory, magnetic recording, wide-band amplification, and intricate electromechanical devices are active in this program.

Hughes

RESEARCH AND DEVELOPMENT LABORATORIES Scientific and Engineering Staff CULVER CITY, LOS ANGELES

COUNTY,

CALIFORNIA

the Columbia recording of Tschaikovsky's "Pathetique." This is a good opportunity to study the way these changes have affected acoustic perspective, over-all brilliance, etc. At any rate, this is a top-notch record and is worth your attention. NARTB curve was better with a little bass boost. Quiet surfaces.

Color TV

(Continued from page 49)

control for the luminance signal. A contrast control for the chrominance portion of the signal is mechanically ganged to the luminance contrast control, thereby insuring that both signals will be varied in equal amounts. This is required to maintain the proper voltage relationship between the two signals.

A 4.5 mc. trap in the cathode leg of the 1st video amplifier attenuates any 4.5 mc. voltage that may develop in the video detector through the beating of the video and sound carriers.

For the color TV video amplifier circuit shown in Fig. 9, the detector stage is formed by using one-half of a 6BK7 duo-triode. The grid and plate are tied together so the triode function as a diode. The second triode section of the 6BK7 is operated as a cathode follower, thereby permitting a number of circuits to obtain their signals from the detector without imposing any capacitive loading on this stage.

The plate circuit of the cathode follower provides signal voltages for the sync separator, a.g.c., and burst amplifiers. The cathode of the same tube contains a 500-ohm potentiometer which provides the signal for both a luminance amplifier and a bandpass amplifier and controls the contrast for both channels simultaneously.

The brightness or luminance signal

is amplified by a single triode stage and then passed through a 1.0 microsecond delay line that is terminated in the matrix network. There are no special traps in this circuit, but response falls off rapidly beyond 3.2 mc., attenuating any color subcarrier and 4.5mc. voltages that might be present.

(To be continued)

ARIZONA HAM PLATES

ARIZONA'S amateurs have won a dramatic victory with the recent passage of their call-letter license plate bill. Two previous attempts had received only lukewarm support in the Legislature. The current bill won support because of a unified program followed by the hams. Features of "Operation Call-Plate"

Features of "Operation Call-Plate" included a state-wide simulated demonstration from the capitol grounds, operation from the floor of the House, and an hour-long test of the emergency nets on a state-wide basis.

Similar programs by hams in other states might go a long way toward getting official approval of call-letter plates in the states where such requests have been rejected or not considered. —30—

TAPE IDENTIFICATION

By I. GORDON HOLT

TAPE recordists who must use reclover and over often find that the back of the reel box becomes a mass of scrawlings, crossings-out, and unsuccessful crasures. A simple way to mark the boxes legibly and temporarily is to use a bright red grease pencil of the "chinamarking" variety.


marking" variety.

One of these pencils, which can be purchased at any stationer's store, will have clear markings that can be easily and completely erased from reel boxes with an ordinary art gum eraser.

with an ordinary art gum eraser.

The grease pencil is also capable of writing identification material directly on metal or plastic tape reels. It can be removed from plastic reels by rubbing with a dry, clean piece of cloth, while a cloth moistened with carbon tetrachloride will clean the metal reels. —30—

View of World Radio Laboratories' radio "supermart" salesroom. The firm has recently moved into a new, air-conditioned, fireproof building at 3415-27 Broadway in Cedar Rapids, Iowa. In addition to the "supermart" pictured, the new facility includes a hi-fi sound room, an amateur radio display room with transmitting facilities for visiting hams, a printing plant, export department, modern lunchroom, moil order department, a large warehousing area, a factory, and general office space. A full acre of parking area is provided for the firm's "drive-in" customers.

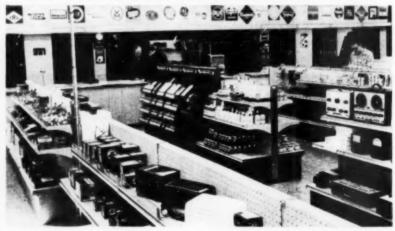

"TELEVISION SIMPLIFIED" by Milton S. Kiver. Published by D. Van No-strand Company, Inc., New York. 527 pages. Price \$6.75. Fourth Edition.

That a new and enlarged edition of the author's basic television text is now available should be good news to all Kiver fans

As with the previous editions, the author has treated his subject matter clearly, concisely, and completely. The only prerequisite for an understanding of this text is a working knowledge of standard broadcast receivers.

This new edition contains many new illustrations and schematics as well as two completely new chapters on u.h.f. and color television. The added material includes more data on TV tuners. an explanation of keyed a.g.c. systems and their application, d.c. video amplifiers, and cascode amplifiers and their operation. In addition to an enlarged intercarrier receiver section, two television receivers are completely analyzed and the new 45 mc. i.f. systems as well as the older 25 mc. i.f. circuits are discussed.

Those who use this book as a nomestudy text will find the self-check questions at the end of each chapter particularly valuable. Whether the reader uses this book as a basic text or as a reference volume, he will find it a uniformly valuable addition to his library.

"HIGHLIGHTS OF COLOR TELE-VISION" by John R. Locke, Jr. Published by John F. Rider Publisher, Inc., New York. 43 pages. Price 99 cents. Paper bound.

This compact little book, written by an engineer from General Electric Company's radio and television department, is an introduction to the subject of color based on the standards recommended by the NTSC, and subsequently adopted by the FCC.


The discussion deals with only those features or circuits which are unique to color receivers. Circuits and techniques found in standard monochrome receivers are not covered. The discussion covers colorimetry, the NTSC color signal, the transmitter, the color receiver, the tri-color picture tube, and color receiver circuitry.

Those interested in the new medium will find this book enlightening and instructive, providing information that applies to all receivers designed to conform to the NTSC standard.

. . .

"ELEMENTS OF MATHEMATICS FOR RADIO, TELEVISION AND ELEC-TRONICS" by Bernhard Fischer & by Bernhard Fischer & Herbert Jacobs. Published by The Macmillan Company, 60 Fifth Avenue, New York. 522 pages. Price \$7.20.

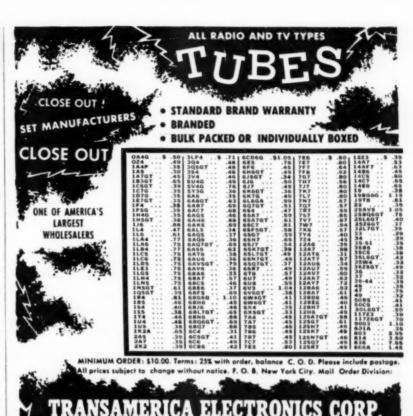With the passing of the "screwdriver" mechanic and the introduction of new and more complex circuitry,





MASCODE MODEL ABY AUTO, ALL CHANNEL VHF 2 TUBE TV BOOSTER Features a new low-noise cascade circuit, Fully automatic—no tuning. Best for all TV receivers, old or new. Boosts all channels 2 to 13—automatically Brings up station atrenth an average of 18 times on all coan-nels 2 through 13. Low noise factor (approx-nels 2 through 13. Low noise factor (approx-Hilling

WESTERN ELECTRIC HEARING AID

Write for free catalog.


NEW YORK, N.Y. 100 Sixth Ave. BROWX M V 542 E Fordham Rd NEWARX M.J. 24 Central Ave. PLAINFIELD M.J. 139 West 2nd St.

BOSTON MASS | 110 Federal St

Acrosound Ultra-Linear



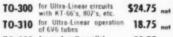for the ultimate in High Fidelity amplification



TO-330 for push pull parallet Ultra-Linear circuits 39.75 net TO-350 for Ultra-Linear 100 watt amplifiers with 6146 tubes 49.50 not

It takes more than a tapped output transformer to make an Ultra-Linear amplifier. It takes the exclusive patented Acrosound Ultra-Linear transformer designed for this application and crafted to the most rigorous specifications. Whether you build your own, convert an existing amplifier, assemble a kit, or buy a manufactured amplifier you can have genuine Acrosound Ultra-Linear circuitry, the finest available. Full transformer data and high fidelity circuits are available on request.

ACRO PRODUCTS CO., 369 Shurs Lane, Phila. 28, Pa.



available at leading

MULTIMETER

- COLOR METER SCALE
- * 2 COLOR SWITCH PLATE COMPLETE BUILDERS AND USERS MANUAL

Instrument has 15 Ranges of Volts, Ohms, Mills and Output A.C. and D.C.

When Ordering Specify if Meter to Be Used

POSTPAID IN U.S.A. No C.O.D. or Stamps

makit Products ROBERT HILLIARD CO.

Inglewood, California



INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD CHICAGO 40 ILLINOIS

THREE TOP BRANDS ONLY! AT TREMENDOUS SAVINGS OVER REGULAR WHOLESALE

OTHER TUBES AVAILABLE AT SAME LOW, LOW PRICES

Latest Code Dates • Boxed • Fully RTMA Guaranteed | Brand New Pix Tubes Full One Year Guarantee

JUNE SPECIAL! 17BP4...15.95 with old tube

0	Mith M Tube	9	ld Tute	
10BP410.45	9.95	16GP420.45	16.95	
12LP412.95	11.95	16RP418.95	15.95	
12LP4A14.50	11.95	178P419.95	15.95	
12QP412.95	11.95	17CP420.95	17.95	
14CP414.95	13.95	19AP423.45	19.95	
15AP415.95	14.95	19AP4A23.95	19.95	
16AP418.45	16.95	20CP425.45	19.95	
16CP4A19.45	15.95	20HP426.95	20.95	
16DP4A.,17.45	15.95	21EP426.95	20.95	
16EP4A20.45	16.95	21AP426.95	21.95	
16FP417.45	15.95	21FP427.95	21.95	

Special Pix Tube Brightener. Each.....\$1.59\$149.00 Double V Ant. ...\$2.39 each Lots of 6..... \$1.98 1,000 Ft. 300 Twin Lead......\$10.95

Send for FREE CATALOG of Additional Tubes and Parts

STUART ELECTRONIC DISTRIBUTORS

Minimum Order \$10.00 Dept.-R-6

149-09 Union Turnpike Flushing 67, N. Y. OLympia 8-3553, 4352

TERMS: 25% Check or Money Order, Balance C.O.D., F.O.B. New York. Satisfaction Guaranteed or money back in 10 days.

"cut and try" methods of servicing are gradually being replaced by formalized procedures based on mathematical formulas.

The book is divided into two separate sections, the first dealing with the principles of arithmetic and their application to problems in radio and television. The second section covers algebraic material which deals with negative numbers, literal equations, ratio and proportion, exponents, elements of logarithms, and a discussion of sine and square waves.

An interesting and surprising addi-tion to the text is a section on "busi-ness mathematics" for radiomen. This chapter includes procedures for computing profit and loss, compound interest, amortization, and installment selling rates. Five appendices provide basic material on wire sizes, logarithms, decibels, etc.

The authors provide a number of exercises throughout the text and when these are solved and checked against the answers provided, the user can evaluate his grasp of the subject matter.

In specializing on mathematics for the industry, the authors have granted a real boon which has long been withheld from the radio-TV worker.

"TELEVISION SERVICING" by Walter H. Buchsbaum. Published by Prentice-Hall, Inc., New York. 359 pages. Price \$5.95. Second Edition.

The problem of keeping up with the fast-moving television industry would be a hopeless one were it not for the fact that magazine and book publishers have assumed the responsibility for keeping the industry informed.

This second edition of Mr. Buchsbaum's basic servicing text has been revised and brought up-to-date with the progress that has been made since the original volume appeared in 1950.

Like the first edition, the book is divided into three parts and covers the theory of TV circuits in relation to the technician's work, the second section covers the actual installation of antennas and receivers, while the third part covers troubleshooting procedures.

The material presented is basic, simply written, and completely understandable. The layman or television student can derive almost as much benefit from the discussion as can the more seasoned technician

The author's presentation is familiar to readers of this magazine and those using this text will find that same practical and enlightening treatment as characterizes his regular contributions to RADIO & TELEVISION NEWS,

"INTRODUCTION TO COLOR TV" by M. Kaufman & H. Thomas. Published by John F. Rider Publisher, Inc., New York. 137 pages. Price \$2.10. Paper bound.

This little handbook has been designed for the service technician, student, and engineer who wants to keep abreast of current color developments. The receiver circuitry covered is based

TAKE IT FROM EDWIN SCHAFFER:

"KRYLON TV Acrylic Spray cuts down contract calls, and spreads the word about my servicing reliability!"



Edwin G. Schaffer, President, Edwin G. Schaffer Co., 7920 Frankford Avenue, Phila., sprays hi-dielectric strength KRYLON on the high voltage sections of TV receivers to prevent corona . . . and he also sprays KRYLON on antennas to weather-proof them. KRYLON TV Acrylic Spray is crystal clear . . . gives lasting protection. It's the push-button spray coating that's STAL CLEAN become the TV industry's most use-

KRYLON, INC.

ful right-hand man!

2038 Washington Ave., Phila 46, Pa.

Krylon also available in Bright Aluminum, Flat Black, Glossy Black, Touch-up White, and Bright Gold.

AT TV JOBBERS EVERYWHERE

TREMENDOUS SAVINGS ON PRECISION RESISTORS

10%, carbofilm, Histability, Low temperency, Jan. specs., new, packed in indi-

es.
1att. Type CPSE_06 each
1 1206, 1500, 2200, 2700, 3300, 4706, 5
1 12000, 15000, 18000, 20000, 21
0, 47000, 56000, 62000, 68000, 82
06, 130000, 150000, 180000, 22
06, 270000, 330000, 470000, 510
00, 1 mg, 1

1 Watt. Type CPI. .08 each Ohms, 100, 2500, 3300, 5100, 75000, 1000 2.2 meg.

Watt, Type CPI 10 each

FOB Rochester, N. Y. Open acct. to rated firms.

R. C. CAGAN SALES

P.O. BOX 1152

ROCHESTER 3, N. Y.
Warehouse, 1045 Mt. Read Bivd.

on the NTSC system and represents the earliest production ideas.

Since industry thinking on singlegun and tri-gun tubes for the new receivers has not been crystallized, the authors have "played it safe" presented both systems—the tri-gun tube in greater detail as it is being used more extensively at present.

Of special interest to technicians is the inclusion of two complete color receiver schematics for study purposes.

While few color receivers are in the hands of the public at the present time, the day the first colorset arrives at the express office is too late for the technician to think about "boning up" on the circuitry. Progressive and alert technicians will recognize the trend and prepare for a successful and lucrative chromatic future.

"TELEVISION SERVICING COURSE" compiled by M. N. Beitman. Published by Supreme Publications, Chicago, 192 pages. Price \$3.00. Paper bound.

This book is designed as a homestudy text for those with a working radio knowledge but no prior television training.

Rather than involve the student in a complex discussion of transmission of TV signals, etc., this text plunges right into the subject matter by considering simple adjustments that can be made by the veriest tyro. From this beginning the material becomes progressively more advanced and covers circuit faults visible on the tube, locating bad tubes by checking the picture tube, antenna principles and practices, CR tubes, how to troubleshoot a receiver, converters and tuners for u.h.f., TV test equipment and alignment, step-bystep procedures for aligning four popular TV receivers, and advanced troubleshooting by means of television picture analysis.

Those seeking a fast-moving introduction to television servicing will find this book a practical answer to their problems.

"SPECIALIZED HOME AND PORTABLE RADIO MANUAL" compiled by the Rider Staff. Published by John F Rider Publisher, Inc., New York. 96 pages. Price \$1.65. Paper bound. Volume 8

This volume is devoted exclusively to RCA receivers and covers sets produced in the period June 1951 through December 1953.

Each receiver model covered is pictured and described. Alignment procedures are outlined and the complete schematic and parts list provided. The manual is designed to be used on the service bench—the type is large and clear and the circuit diagrams are jumbo size for high-speed servicing of the receivers.

These specialized manuals meet a definite need for authoritative and lowcost service data.

The earlier volumes are still available. Information on them will be supplied by publisher.

REAL SAVINGS!

AT PART-MART

TV VOLTAGE REGULATOR

A Best Buyl Designed to insure max, performance of any TV set when low hollow followed interferences between the failures. Increases sensitivity. Eliminates intermittent sync and occitit. 300 Watt rating ample for voltages from 90 to 135. Perfect for TV set or other appliances rated under 300 Watts Edity madematic with pliances rated under 300 Watts. Fully automatic with low, high or normal selector switch. Wt. 3 lbs. No. F5126.



ADJUSTABLE ION TRAP



Newest Beam Bender with adjustable feature which allows magnetic field to be varied between 32-55 gauss. Will replace old style ion traps having specific magnetic fields. One universa ion trap to take care of all youneeds! Wt. 8 ozs. No. FS111.

3 FOR 1

38c EA.

SPECIAL! INDUCTUNER

Below wholesalet Fopular 3-gang funer for replacement or in own designs for TV and FM receivers and boosters. Continuous tuning from 52-120 mc and 175-210 mc with 4 turns of 3" shoft. Size, 41136" x 216". Wt. 3 lbs. No. LF108. 2.49 EACH.



TRIPLE-PLAY CARTRIDGE

G. E. RPX-050. Only a limited quantity left at this price! Popular variable reluctance cartridge. Plays all records. Complete with dual sapphire-tipped needle: .001" tip 4.39 IA. 78 rpm. Wt. 6 oz. No. LF 120. for 33 1/2 and 45 rpm: .003 tip for

CHECK-MATIC PEN

ANYONE WITH A CHECKING ACCOUNT needs this famous 2-in-1 Check-Matic Pen! You get a durable Ball-Point Pen (worth the price alone) that writes over 75,000 words PLUS the amazing 75,000 words PLUS the amazing Check - Matic Check Protector! Prevents fargery by embossing and printing indelible lines over amount. NOBODY can write aver if without detection, Protects thousands of checks. Black with Goldsands of checks. Black with Gold-tolor caps. Fully Guaranteed. WE PAY POSTAGE, Stock No. GF123.



3 SPEED "INTERMIX" RECORD CHANGER



our make latest dessen, fully automatic changer at record lose. This generies performer plays all P. 10° and 12° records is esquence. "Free Ficating." featherweight tone arm has Webstele over cartridge and dual needles for 33½, 45 and 78 rgm mod for excellent fonal reproduction. Automatic shut diff after record. Other tim drive furnishe action and constant spee. or excellent tonal reproduction. Automatic shuf-off after Direct rim drive furnishe action and constant speed wow: free operation Easily installed. Will not jam. Dim. x 511_m, clearance required above and 21_m below. Complete with Phono and AC Cords. Fresh steck. and the production of the pro

MALLORY TV-101 UHF CONVERTER

Brand New! Continuous tuning type with Built-in Antenna. Maroon cab. Compl. with all Tubes. Wt. 5 lbs. No. SF127.

with oil lubes. Wt. 5 lbs. No. 5F127.
Write for Additional Listings
INCLUDE POSTAGE—Excess Promptly Returned
TERMS: FO.B., N.Y.C.—MIN. ORDER \$3.00—
25% Deposit on C.O.D. Orders. SAVE C.O.D.
CHARGES—REMIT IN FULL PLUS POSTAGE. Excess Promptly Returned. SUBJECT PRIOR SALE.

PART#/MART ROCKVILLE CENTER L. I., N. Y.

GO MOBILE FOR JUNE! GO COLUMBIA FOR VALUES!

METER RECEIVER: 6 tubes with 9 1.F. \$5.95 stages, Good cond.
Less tutes
ARCA VP TRANSCRIVER: For novice, 3ARCA VP TRANSCRIVER: For novice, 3ARCA VC TO CAP, ALL TUBES included.
\$27.50

- arine, as well as aircraft and ham bands with minds of the collection of the collect

AMATEUR CRYSTAL KITS!

grinding components. It Easy to below many performance of the second of

COMMAND EQUIPMENT
8C-483 .1055 KC Receiver
8C-946 .52-1500 KC Hrondeant 24.50
ARA 1.5-3 Receiver for marine use
name as SCR-274N)
8C-454 3-6 MC 10.95
BC-454 New
BC-455 G-0.1 MC
8C-455 Brand new
8C-486 Modulator (SCR-274N) 3.95
2.1-3 ARA Marine Transmitter, New 19.95
BC-696 H-4 MC Transmitter 39.00
8C-487 4-5.3 MC Transmitter 8.95
BC-458 5.3-7 MC Transmitter 6.98
8C-456 7-9.1 MC Transmitter 12.05
R-26 VHF ARC-5 receiver freq. 100-156
MC 22.50
7-23 VHF ARC-5 transmitter freq. 100-
156 MC, with all tubes 24.50
86-443 Antenna Helay w/condensar 3.89

6 VOLT CONTROL RELAY

NEW SIG. CORPS RELEASE

LATERT FIELD TELEPHONES: made of lite-weight aluminum, Waterproof, Long range, Has the state of the state of the state of the handlest with F-1 button. Easily converted to ter-rine phone patch. Complete with batts. BRADN NEW, FFR PAR.

SCR-SIS UNF ELECTRONIC ABSOLUTE ALTIMETER

ses, cables with plugs, mounts, etc. es. BRAND NEW. \$19.95

2 for \$5.00 3 for \$5.00 SRAND NEW SPLIT STATOR CONDENSERS. 2 meter. Each 496 WESTERN ELECTRIC HANDSETS. With F-1 Button,

| His new Special this month only! ... En. \$2.95 | TEST EQUIPMENT—Write for special prices| | TS-102A AP | TR-928 | TS-35A/AP | TS-928/KM-2)PCM | RP0-17 | H-948/KM-2)PCM | RC-600 | TS-7 ASQ | TS-7 ASQ | TS-7 ASQ | TS-7 ASQ | TS-14 AP | RC-1066A | O73/URT | TS-14 AP | RC-1066A | TS-7 ASQ | TS-7 ASQ | TS-14 AP | RC-1066A | TS-7 ASQ | TS-14 AP | TS-14 AP | RC-1066A | TS-14 AP | TS-14 AP | TS-14 AP | RC-1066A | TS-14 AP | TS-14 AP | RC-1066A | TS-14 AP | RC-1066A | TS-14 AP | TS-14 AP | RC-1066A | TS-14 AP | TS-14 AP | RC-1066A | TS-14 AP | RC-106A | TS-14 AP | RC-1066A | TS-14 AP YOUR NAME WANTED! Get on our mailing list to re-MINIMUM ORDER \$3.00. All orders F.O.B. Los Angeles. 28% deposit required. All items subject to prior sale.

COLUMBIA ELECTRONIC SALES

This Will Save You Money Because You Are Constantly Needing and Buying **Resistors and Condensers** One Pound Assortment!!!

Resistors (Averaging 140 ea to a pound) \$1.50 per lb.

Mica Condensers (Averaging 116 ea to a\$1.50 per lb.

These items are **Unused** and are guaranteed. What do you pay for them elsewhere? A postcard will put your name on our mailing list. Write for our free list showing VT and commercial equivalent tube numbers.

P-A-R-T-S, INC.

2005-15 Empire Ave., BURBANK, CALIF. THORNWALL 2-5349 VICTORIA 9-2834

MANUFACTURERS' LITERATURE

The various listings presented in this section are for your convenience. The bulletins, unless otherwise indicated, are available to all our readers. For prompt attention write directly to the manufacturer for this literature.

SHALLCROSS BULLETIN

Shallcross Manufacturing Company, Collingdale, Pa. has issued an engineering bulletin which gives complete specifications and laboratory performance data on its "P" type encapsulated precision wirewound resistors.

This unusually detailed bulletin, L-30, lists eleven different "P" type resistors in both radial lug and axial lead styles. Charts showing the effects of temperature cycling, load life, moisture resistance, and short-time overload tests are also included.

Copies of this bulletin are available only on letterhead request.

THORDARSON CATALOGUE

Thordarson-Meissner, Seventh and Bellmont, Mt. Carmel, Illinois has announced the availability of a new catalogue covering the *Thordarson* line of transformers and reactors and featuring a new, complete TV replacement section, a new output transformer chart, and complete cross-reference

Catalogue 400-L may be obtained without charge from the company.

ACOUSTICS STANDARD

The American Standards Associa-tion, 70 E. 45th Street, New York 17, N. Y. has just completed and published a new standard for letter symbols for acoustics.

The standard presents symbols and terminology used in studies of acoustical, shock, and vibrational problems. Harry F. Olson of RCA was chairman of the committee that set up the new

Known as "The American Standard Letter Symbols for Acoustics, Y10.11-1953." the new publication may be obtained from the Association for \$1.00

TRANSISTOR CURVE TRACER

Magnetic Amplifiers, Inc., 632 Tinton Ave., New York 55, N. Y. has published a bulletin describing its automatic universal transistor curve tracer.

The new booklet, which is available without charge, explains the operation of the unit and details both electrical and physical specifications.

BATTERY PROMOTION

National Carbon Company is now distributing a new motion display, promoting the year around uses of portable radios, as the featured piece in its complete point-of-sale kit on Eveready batteries.

In addition to the motion display, the kit includes small cards, a jumbo banner, pennants, streamers, and a copy of the 1954 radio battery replacement guide.

The kit is available through the company's distributors who will provide details on how it may be obtained free of charge.

TEST EQUIPMENT

Complete specifications and data on its test equipment line have been included in the new catalogue just released by Clough-Brengle Co., 6014 Broadway, Chicago 40, Illinois.

Catalogue No. 54-A lists sweep generators, b.f.o.'s, automatic generators, transmission measuring sets, r.f. signal generators, capacity-resistance-inductance bridges, and extended range audio oscillators.

Dept. RE of the company will supply a copy of this publication without

RIDER CATALOGUE

John F. Rider Publisher, Inc., 480

Canal Street, New York 13, N. Y. has announced the availability of its 1954 book catalogue.

The publication contains 32 pages and is a complete, up-to-date listing of the latest books. "Tek-File." and manuals published by the company. Copies of the catalogue are free and are available from the company's distributors and bookstores or direct from the publisher, Box RC-54.

SOLENOID CATALOGUE

West Coast Electrical Mfg. Corp.'s AC Division 215, 233 W. 116th Place, Los Angeles, California now has available a new AC solenoid catalogue.

The new publication presents in easy-to-read form, solenoid design information, engineering drawings, solenoid performance charts, work and temperature curves.

This catalogue is available only on company letterhead request.

MALLORY GUIDE

A cross-reference guide, covering radio and television components by means of manufacturers' part numbers, has just been published by the Distributor Division of P. R. Malloru & Co., Inc., P.O. Box 1558, Indianapo-

Separated into four sections, the guide provides a cross reference for dry electrolytics, TV and radio controls (including carbon and wirewound single-section, universal-section, and





for FREE Catalog 553

FULL-GRIP, VELVET-ACTION



LOOK at these STEVE-EL "Steals"

Very limited quantity!
First come, first served!
SONORA 3-SPEED RADIO-PHONO





Batteries for above \$2.84 Write Dept. RN-6 for latest STEV-EL

FREE!)

for latest STEV-EL SUPER-VALUE catalog. Hundreds of values.

STEVE-EL Electronics Corp.

preassembled dual controls and "L" and "T" pads), radio and TV selenium rectifier stacks, and communications and auto radio vibrators.

Copies of the new guide are available from the firm's distributors or from the company direct.

ONAN PLANTS

D. W. Onan & Sons Inc., Minneapolis 14, Minn. pictures and describes six interesting installations of its electric generating plants in its new pocketsize, 12-page booklet.

The new publication is Volume 10, No. 2 of the company's publication "Power Points Digest" and will be sent without charge to those specifying the volume and issue number in their requests.

ANTENNA DATA

Tennalab, Quincy, Illinois has issued a two-color, four-page bulletin covering its line of TV antennas.

Pictured and described are units for all-channel applications, single-channel yagis, multi-channel yagis, and accessories to be used with the various antennas.

A copy of the new publication is available upon request.

SCOPE HANDBOOK

The Hickok Electrical Instrument Co., 10524 Dupont Ave., Cleveland 8, Ohio is offering a 24-page handbook on cathode-ray oscilloscopes to service engineers, technicians, experimenters, and students.

This free publication contains an explanation and illustration of the basic characteristics of the oscilloscope, explains how it works, and provides tips on its more general uses. The handbook also lists features and performance specifications on models ranging from a 3" portable unit to large technician bench models as well as the highly accurate industrial-electronic laboratory types.

CONDENSER DATA

The Astron Corporation, 255 Grant Avenue, East Newark, N. J. is offering a copy of its new condenser manual, AC-4, which contains detailed engineering data and specification information on its complete line.

Condensers are grouped into three broad categories; electrolytic, paper, and metallized paper. Within each category, the condenser types are grouped according to operating temperature range and construction styles and ratings that are available as standard.

The catalogue is available on company or professional letterhead request only.

MAST TUBING

Bellevue Tube Mill, Inc., Box 4465, Philadelphia 40, Pa. has just issued a revised catalogue of its products which is being distributed to interested persons without charge.

The catalogue illustrates and de-

You Can Become an

ELECTRICAL ENGINEER

with a Bachelor of Science Degree
IN 36 MONTHS



Major in Electronics or Power at Milwaukee School of Engineering

Everyone knows the tremendous opportunities ahead in electrical engineering. The expanding field of color television alone is one example. In addition to the demand for engineers, thousands of engineering technicians are needed. The Milwaukee School of Engineering can prepare you to become an engineer in 36 months or an engineering technician in 12 to 18 months. It'll pay you to look into it today. No obligation.

Technician and Service Courses — 12 to 18 months

In 12 months you can be a radio technician. An additional 6-month course qualifies you as a radio-television technician with an Associate in Applied Science degree. Or you can earn an industrial electronic technician certificate in 12 months.

These technician courses form the first third of the program leading to a B. S. Degree in Electrical Engineering. Twenty-one subjects studied include electronics, electronic engineering, and electronic design.

Also offered are: radio-television service course (12 mos.); electrical service course (6 mos.); general preparatory and refresher course (3 mos.).



Faculty of specialists — 50,000 former students — Annual enrollment from 48 states and 23 foreign countries — Non-profit institution — 51st year of service — Course approved for veterans — Residence courses only.

MILWAUKEE SCHOOL OF ENGINEERING

D	IILWAUKEE SCHOOL OF ENGINEERING ept. RN-654, 1025 N. Milwaukee Street lilwaukee 1, Wisconsin
ti	end me [Free illustrated booklet on oppor- inities in Electrical Engineering m Free illus- ated booklet on careers in Radio TV.
1	am interested in
N	ame
A	ddress
- 0	Ity Zone State
11	f veteran, indicate date of discharge

The NEW MOSLEY [] A | [N

HERE'S HOW THE "ORIENTOR" SAVES TIME AND MONEY ...

- Permits ONE MAN To Do The Job Formerly Requiring Two!
- ✓ Makes Possible Use Of Low Cost, Portable VOM To Read Relative Video Signal Strength!
- ✓ Eliminates Need For Extra Wires From Set To Roof?
- Use To Determine Best Lateral, Vertical and Directional Orientation Of Antenna!
- ✓ Aids In Determining If Transmission Line Is Functioning Properly!

Try it on your next installation job. You'll quickly see why the MOSLEY "ORIENTOR" has been termed "The TV Installers' Handlest Tool Since The Step-ladder...!



THE NEW MOSLEY "ORIENTOR", includes dual isolation network units, ready-to-use leads for connecting unit to set without removing chassis and complete instructions. Catalog 903, Dealer Net, just \$7.50 Descriptive Folder, Form 903, Sent Upon Re

Write for your FREE copy of new MOSLEY TV Accessories Catalog Sheet, Tells HOW DEALERS CAN MAKE MORE INSTALLATION PROFITS! Ask for FORM D-1.

Electronics, Inc. CHARLES ROCK ROAD 8622 ST. ST. LOUIS 14, MISSOURI

Radio engineering is a big field. There's room for yeu in it—if you're good. Get first-class training at Indiana Tech. Intensive, specialized course, including atrong basis in mathematics and electrical engineering, advanced radio theory and design, television, electronics. Modern inhoratories. Low rate. Also 8.8. DEGREE IN 27 MONTHS in Accommunical Chemical, Citl, Electronic Chemical, Citl, Citl, Citl, Chemical, Citl, Citl, Chemical, Citl, Citl, Citl, Chemical, Citl, Citl, Citl, Chemical, Citl, Citl, Chemical, Citl, Citl, Citl, Chemical, Citl, Citl, Chemical, Citl, Citl, Chemical, Citl, Citl, Chemical, Citl, Citl, Citl, Chemical, Citl, Cit

INDIANA TECHNICAL COLLEGE

364 E. Washington Blvd., Fort Wayne 2, Indiana Please send me free information on B.S. Engineering Degree in 27 months as checked.

Radio-Television

Aeronautical
Electrical

Name

CRYSTALS!

COMPLETE SET-80 CRYSTALS COMPLETE SET—120 CRYSTALS g from 370-540 Ke., 72nd Harmonie. INCLUD-KC. CRYSTAL KC. CRYSTAL KC. CRYSTAL KC. CRYSTAL KATOR: 12 V. 35 A. Used cond... TRANSFORMER. Drl. 110 @ 2 am

EXTRA! See Dur Ad in April '54 Radio News

400 MICA CAPACITORIS. Asserbed. Mounted
10 to a strip. All 400
AND ARCA CAPACITORIS. Asserbed. Mounted
10 to a strip. All 400
ARW-2 REMOTE CONTROL RECEIVER. New \$2.95
All merchandise sold as is. Write for quantity
discounts I fems subject to prior sale. Send
for FREE Catalogue!

J. J. GLASS ELECTRONICS CO.
1613 S. MAIN ST. LOS ANGELES IS. CALIF.



Sensation of the 1953 New York Audio Fair

Elimination of rubber idlers by a belt drive assures a smooth drive system. Turntable assembly is suspended on coil springs equipped with felt shock absorbers to absorb vibration. This minimizes feed-back from the loudspeaker, rumble from street traffic, oil burners, etc. Nylon bearing eliminates metal to metal contact-provides quiet operation



with negligible lubrication. The bottom thrust ball rides in a special hardened and polished seat. A 25 lb. turntable assures stabilized speed. Choice of mahogany or blond finish.

COMPONENTS CORP. DENVILLE, NEW JERSEY

scribes the company's line of electrowelded TV antenna masts and butt and lock seam tubing. The antenna masts are 1¼" o.d. "3-Cote" units while the other sections illustrated are 1¼" o.d. "2-Cote" 20-gauge sections.

Requests for catalogues should be addressed to Dick Morris, the sales manager. -30-

MORE SERVICE GROUPS

N the March issue of RADIO & TELE-VISION NEWS, on page 84, there appeared a list of radio and television service associations in the United States and Canada. Since that list was published the following additional associations have been brought to our atten-

Associated Qualified TV Technicians, 406 W. Capitol St., Jackson, Miss.— Ivan Scott, Pres.; M. M. Sage, Sec'y.

Radio & Television Electronic Technicians, 52 E. 19th St., New York 3, N. Y.—Charles J. Vassallo, Pres.; Carlos

Boxill, See'y.
Northeast Television Service Dealers
Ass'n., 6321 Frankford Ave., Philadelphia 35, Pa.—R. H. Cherrill, Pres.; Roy Colen, Sec'y.

Southern Pennsylvania Radio & Television Technicians Ass'n., 734 E. Market St., York, Pa.—Joseph Hauser, Pres., Willard Stroyer, Sec'y.

PHOTO CREDITS

Page	Credit
36 (center) Official Defense	
38, 39	t Laboratories
43, 45Acro Prod	lucts Company
46. Bogue Electric Man	ufacturing Co.
47Westinghouse	Electric Corp.
54, 55. Radio Corporati	ion of America
59, 60, 62, 63, 108 Crosley Division, Av	vco Mfg. Corp.
110	Audio Fairs
120Bing Crosby Er	nterprises, Inc.
128World Radio	Laboratories

ADDENDUM & ERRATUM

In connection with Fig. 5 of "A Transistorized Light-Beam Communications System" (May 1954) there is a slight possibility of damaging the transistor if a pot is used for resistor R and the pot is turned to zero. To avoid damage the authors suggest that a 47,000 ohm fixed resistor should be placed in series with a 1 megohm pot for R thus eliminating any chance of transistor burnout. The maximum resistance which gives undistorted output should be used to conserve power and reduce transistor collector power dissipation.

In the article "The Audio Cathode Fol-wer" which appeared in the April 1954 issue, the captions for the photographs on page 51 were inadvertently interchanged. In addition, although not too clearly indicated, it was not the intention of the author to provide construction details on the tone

entrols and preamp.

The photographs were included merely the equipment he used with his

driver unit.

Rate 50c per word. Minimum 10 words

RADIO ENGINEERING

COMPLETE radio, electronics theory & practice: television; broadcasting; servicing; aviation, marine, police radio. 12 or 18 months. Catalog. Valparaiso Technical Institute, Dept. N. Valparaiso, Ind.

FOR SALE

ISOLATION transformer 35w 117v sec. 117 or 135 plus 6.3v 45a tap. 3 lbs. \$2.45 plus postage. Send for Flyer. Surplus bought. Empire Electronics Co., 409a Avc. L, Brooklyn 30, N. Y.

DIAGRAMS—Radio \$1.00; record changers, re-corders \$1.25. Television with service data \$2.00. Where model unknown, give part numbers. Kra-mer's Radio Service, Dept. 853, 36 Columbus Ave., New York 23, N. Y.

TAPE Recorders, Tapes, Accessories, Unusual Values, Dressner, 624-R East 20th St., N.Y.C. 9

FREE: Get our monthly electronic lists. Dick Rose, Everett, Wash.

RESISTORS, condensers, micas, electrolytics, tabulars, latest pigtail types, new, every piece usable, some short leads. 5 lbs.—\$5.00, 10 lbs.—\$8.50. Prepaid. Cagan, Box 1152, Rochester, N. Y.

TUBES and equipment bought, sold, and changed. For action and a fair deal, write I Gensler, W2LNI, 136F Liberty, N. Y. 6, N.

BRAND New Components. Give away prices gigantic lists. Roland Bond, 6255 Desco, 1 25, Texas. sco, Dallas

CODE practice oscillators New, guaranteed, \$4.00 postpaid. Stout, 2241 E. Broadway, Muskegon, Michigan.

CUSTOM Built Hifi: Speaker, Bass Reflex, 15-inch Co-axial. Amplifler Triode, High Gain, U. T. C. Components. Jensen Customode Cabinets. Blonde Mahogany (Rare at any price) Turntable Recko-cut 3 speeds, dual Livingston Arms G. E. Broad-cast, Including packing and crating price \$1050.00. C. Chadwick, The Manor, Alden Park, Phila. 44, Panna.

CIRCUIT Diagrams will save your precious time. Radio \$1.00. Television \$2.00. Give make and model. Carleton Radio, 39 Daniel, East Hartford

TELEVISION Receivers, \$30 up. W4 South Randolph, Arlington 4, Virginia W4API., 1420

TV-FM antennas. All types including UHF. Mounts, Accessories. Lowest prices. Wholesale Supply Co., Dept. II, Lunenburg, Mass.

AN/Apr-1, other "APR-," "ARR-," "TS-,"
"LE-," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment.
Describe, price in first letter. Engineering Associates, 434 Patterson Rd., Dayton 9, Ohio.

Sweep & Marker Gen., xtal controlled, new 3.60 value, \$495.00. W. Vogel, 1108 Lexing-\$900.00 value. \$495.00 ton, Wheaton, Illinois.

USED Radio Vibrators Rejuvenated \$1.25 each, 30 day guarantee. Radio Products Service, S. J. Boysel, 204 N. Florence Street, Springfield, Ohio.

USED Television sets \$25.00. Jones, 1115 Rambler Ave., Pottstown, Pa.

ALUMINUM tubing, angle and channel, plain and perforated sheet. Willard Radcliff, Fostoria, Ohlo.

\$96.00 TRADE-IN allowance for any Tape Recorder on purchase of new, latest model Concertone Pro-fessional Tape Recorder. Other terrific bargains! Telcoa Audio Exchange, Azurelee Dome, Globe 6— 2611 Malibu, Calif.

WANTED

HIGHEST prices paid for RC610 transmitter, JB70 junction box, BC339 or BC729 Ant. tuning units, BC614 speech amp. & all BC610 coils & TU'S, TS181/AP spectrum analyzer, G. R. VTVM Model 1800A, Dumont 334A Scope, Boonton Q Meters Model 260A and 190A with accessories. Transmitting tubes 3C22, 3C45, 3D21A, 3E29, 4C37, 4D21, 4-125A, 5C22, 450TL, 723AB, 819, 813, 829B, 832, all W. E. tubes. We buy all types. Receiving, transmitting, industrial, "TAB," 111 Liberty St., N. Y. 6, N. Y.

WILL buy all ART-13/type T-47A \$200.00: ART-13/type T-47, \$150.00; BC-348 unmodified \$65.00, BC-348 modified \$50.00: APN-9 \$200.00: ARC-3 complete \$600.00: R77 Receivers \$300.00: ARC-1 \$300.00: BC-312 \$60.00: BC-342 \$60.00. Ship via Express Co.D., subject to inspection to: II. Finne-gan, 49 Washington Avenue, Little Ferry, N. J. TELETYPEWRITERS, tape send-receive or re-ceive only, Model 14, any quantity or condition. Box 540, Radio & Television News.

MINIFON Recorder must be reasonable. A. Siegel, 1516 Shakespeare Ave., N.Y.C. 52.

BUSINESS OPPORTUNITIES

SALESMEN—Part or full time—Sell at Manu-facturers low prices Television wire to local Appliance-Radio-Service repair stores. 109 commission—original and repeat orders with Appliance-Radio-Service repair stores. 10% Appliance-Radio-Service repair stores. 10% commission—original and repeat orders. Write for free samples. No charge. King Mfg. Co., 43 Huron Rd., Mohegan Heights, Yonkers, New York.

CORRESPONDENCE COURSES

USED correspondence Courses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Ala.

MISCELLANEOUS

FREE money saving bargain list 10 MFD/ 600WV Oil Capacitor 98c; RCA 3APIA \$5.95; add postage. Mark Electronic, 1888 Randell Ave. postage. Mark Bronx 72, N. Y.

SPEAKERS repaired, wholesale, guaranteed. Jobbers wanted. Amprite Speaker Service, 70 Vesey St., New York 7, N. Y.

BUILD your own electronic e organ or miniature W6DEG, 1552 Church electronic brain. Jim Kirk, St., San Francisco 14, Calif.

SPEAKERS repaired, guaranteed, 24 hours service, 50% off dealers. Send to Dept. A. Sweeney's Reconing Service, 922 W. 5th, Winona, Minnesota

CATALOGUES, Brochures, Layouts. Creative In-dustrial Art. Gilbert Associates, 275 Fifth Ave., N.Y.C., Mu 4-0680.

TEST Equipment Repaired and calibrated by fac-tory staff. All makes. Solar, Simpson, Triplett, Heath, etc. Immediate service. Douglas Instru-ment Laboratory, 176 Norfolk Avenue, Boston 19,



.33

SZ3

TOP QUALITY **FULLY GUARANTEED TUBES** BELOW MFRS' PRICES

Our new policy brings you greater to thought possible! As a GOODWILL offering, we are given ing, such month, a number of the control of the c

6N7 6Q7 6R7 654 657G 65A7 .47 .82 .69 .49

6L7G

.39

We specialize in TUBES—of every kind and description—serving the industry

1A7	400	OACI.	.07			245	. 10 1	for weeks	De serving	the industry
	.49	SAF4	.89	6SD7GT.	.38	7 V 7	. 19 2	Aware in	More than 30	teasablile 00
IARS	.39	6AF6	.75	65F5	.45	7W7	.85	Alberta in	itock for IMMI	DIATE DE
1AX2	.61	GAGS	.46	65F7	.59	7×7	.70	CLASS MA	ncluding hard-to	and and di
183	.59	6AG7	.95	65G7GT	.40	774	.44	continued a	tumbers. All tu	Red and dis-
IDEGT .		GAIS	.89	65H7	.60	724	.49	tively tester	d in our fully	nes exhaus.
	-77	6AKS .	.49	65H7GT.	.50	727	.65	ratories, an	d in our fully eq d re-tested at to	ulpped labe-
IGGGT .	.25			65J7 .	.39	10V	.69	ment, Fill	ONE NEAR	ime of ship-
INSGT .	.48	6ALS .	.29			1246	.59	All tubes to	CHE-AFWH C	UARANTEE
1166	.59	6AQ5	.37	65K7	.40	12887	.89	dated.	idividually boxe	d and code.
1L4	.45	GARS	.39	GSL7GT.	.49	12ATG	.39	untura.		
ILA4	.79	6ASS	.50	65N7GT.	.49					
ILAG	.79	GATG	.37	6507	.41	12AT7	.55			
1LB4	.79	GAUG	.40	65R7	.45	12AU6 .	.39	Type Price	Type Price	Type Price
ILCS	.69	GAVS	.79	65T7	.49			122339	49 44	2040 . 6.95
1LC6	.79	GAVG .	.37	6T8	.59	12AU7	.49	148469	5085	204489
ILDS	.77	GAX4GT.	.55	6U79	.48	SZAVA .	.49	14A5 59	50CS 44	2021 . 1.09
1 LE3	.78	687	.95	6U8	.59	12AV7 .	.69	14AF7	50L6GT .55	212626.95
ILGS	.77	688	.85	EVEGT .	.39	12AX4GT	.59	1488 65	50X664	3C24 . 1.75
11.044	.78							140769	SOYEGT. S9	211 2.31
ILNS	.59	6B8G .	.29	6W4GT	.39	12AX7 .	.59	148783	56 49	304TL 7.50
INS	.61	SRAG	.40	6W6	.46			1457 67	57 58	316A . 2.50
IPSGT .	.56	68A7	.56	6×4	.36	128A6 -	.49		58 58	446A . 3.40
19567	.57	68C8	.49	SXSGT .	.35	12806			70L7GT. 1.00	705A . 1.50
184	.89	68D6	.44	6X8	.74	12856	.49	5 44V. 00 4 10 10 10 10 10 10 10 10 10 10 10 10 10	71A54	7158 . 6.50
		6886	.37	6276	.78			1474	7643	717A
1R5	.42	6866	1.18	7A3	.59	12847 .	-65		78 55	721A 2.50
184	.58	58H6	.45	7A6	.69	128Y7 .	.65	19866		726A . 9.50
155	.42		.42	7A7	.69	128Z7 .	.63		81 1.11	BOIA39
1506	.48	68K7	.95	7807		12C8	.34	197879	82 69	BO3 . 2 90
174	.48				.95	12FSGT.	.38	2244	8379	#15 3.90
194	.48	6806	.79	7AG7	.55	1246	.45	25AVSGT .84	8454	82665
105	.48	6BQ7A		7AH7	-56	1235GT .	.39	258Q6GT	8559	836 3.95
			.88	784	.44	12J7QT .	.58		89/Y29	837 1.40
IXZA .	.55	68Z7 .	.79	788	.59	1287	-55	.68	1172338	841 1.30
2A3	.95	6C4	.37	786	.59	1248	-58	25L6GT39	117746T .75	842 60
2A4G	.99	6C5	.39	TC4	.58	12LBGT	1.30	2525 64		860 6.85
2AS	.59	6066	.57			12Q7GT.	.59	25Z60T44		864 85
2A6	.49	6C86	.85	7C5 .	.49	1258GY.	.61	2644	205195	874 1.30
2A7	.64	6C86	.45	202	.65	125A7GT	.64	2738	9001 1.49	95434
287	.62	6CD6	1.10			125C7 .	.69	32L7GT98	9002 98	955 54
2×2	.39		.69	785	.59	12555	.49	2000	9003 . 1.48	
2×24	1.15	508G	.98	767	.65	1255767	.69	35W4	9004 97	CK1005. 60
384	.44		.46	747	.59	12507	.75	357445	900668	IBIE . 1.95
3A5	.93		.39	717	.75	12547	.75	3523 43	CATHODE MAY	1619
3A8	.60	656	.45	767	.79	12517	.59	3525GT 48	3EP1 8.50	1624 . 1.70
387	.39				.59				58P1 3.55	
306	.39		.93			125K7G7	.62			162820
3LF4	.79		.69	787	.62	125L7GT	.49		58P4 5.99	162649
		6G6G	.65	707	.61	125N7GT	.58	4523	SCP1 5.99	162944
394	.48	6H6	.49	787	.65	1250767	.56	4649	78P7 . 7.45	1630 1.10
SQSGT .	-55	6/5	.40	787	.85	12587 .	.49	4789	12DP7 .19.50	1611 1 40
354	.48	6.16	.49			****		*******	16HP4A 24.95	163265
3V4	.51	617	.49	3				4	16DP4 .24.95	163380
ST4	1.28	618G	.95	FREE	OF	FFR! 50	ven A	asorted 12, 7, 2	INDUSTRIAL	1634 I.10
5U4G	.53	6K7	.39				1 00	nd 2-volt type	1822 . 1.80	719355
		SHEG	.65			lue appros.			1824 8.89	8012 2.50
5W4	.50	61.5G	.79		tu ea	nik niget i	in. 23	19.00 or more! 9	18 2 . 1.90	BO13A. 3.80
5X4	.50	6L7	.85	6000000		*****		Consessor	IP 1.95	8020 2.90
Our Cale	i. wa									

Our Cain is YOUR GAIN too! Enormous valume of our Tube business enables us to absorb everhead costs and pass on to you substantial savings in the form of Sensationally Low Prices, on the Items shown below:

STANDARD BOOSTER



werful 12-iannel TV

\$6.96

TRACTOR RADIO

With whip anterina. For 6 Volt Operation. List \$99.75. \$29.77 Your Net Cost, Each.

HEADSET SPECIAL

Exceptionally fine army-navy spec. headphones, individually boxed.



FREE! SEND FOR OUR LATEST LISTING. Min

ELECTRON TUBE WHOLESALERS, INC. 140 DUANE STREET . NEW YORK 13, N. Y. . Phone: BArclay 7-7616

FIVE TOP NAME BRANDS



Savings!

FIRST - FULLY GUARANTEED
LINE - INDIVIDUALLY BOXED
TO SECONDS - NO REHASHED "BARGAINS"
TO REACTIVATED TUBES. YOU CAN PLACE YOUR
ONFIDENCE IN OUR DEPRIOABLE, NEW TUBES.

TOP

Tube Orders Over \$25.00, with full remittance, PREPAID to you in U.S.A.

DE LUXE TUBE CADDY
This newly designed Tube Caddy is light weight
and compact. 1894.984.94.139.7 Russredty constructed, reintoreed throughout. Holds approx. 130
STEELEAN Empters and Eools. 512.08

TWO-COLORED TUBE CARTONS, with new Nafety Partitions. Pre-conts Tube Breakase. This Super-disease Red and Black the Breakase. This Super-disease Red and Black the Minimum: 106 any one size. Quantity prices on request. SACH Minimum: 106 any one size. (SAUS, SELS, SEL). 5.012 EACH MINIMUM: (SAUS, SALE, SEL). 5.012

Terms: 25% with order, balance C.O.B.
Minimum Order \$5.00
All merchandise guaranteed. F.O.B., N.Y.C.
PMOME: REctor 2-2562

BARRY ELECTRONICS CORP.
136-F LIBERTY ST. N. Y. 6, N. Y.

OF advertisers

JUNE 1954

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

the possibility of an occasional change or	omission in the preparation of this index.
ADVERTISER PAGE	ADVERTISER PAGE
Aaron Electronics 90	Mallery & Co., Inc., P. R4th Cover
Acre Products Co130	Mattison Television & Radio Corp124
Airex Radio Corp112	McGraw-Hill Book Co 95
All Channel Antenna Corp 22	Miles Reproducer Co., Inc
Allied Radio Corp	Mosley Electronics, Inc
American Television & Radio Co 88	Moss Electronic Distributing Co., Inc 79
Amplifier Corp. of America110	most annual annual and the contract
Arkay Radio Kits, Inc 86	National Company31, 78
Arrow Electronics104	National Electronics of Cleveland126
Arrow Sales, Inc. 84 Ashe Radio Co., Walter 89	National Radio Institute
Atlas Sound Corp	New Jersey Television Supply Co
Audel Publishers106	new series reference cupping our minimum
D-101	Offenbach-Reimus 74
Baltimore Technical Institute	
Bell Telephone Laboratories	P-A-R-T-S, Inc
Berlant Associates 96	Part Mart
Bonica Newsreel Club123	Perma Power Company
Boulevard Electronics, Inc	Philco Corporation
Brook Electronics, Inc 89	Pickering & Company, Incorporated 14
Burstein-Applebee Co	Platt Electronics Corp 81
CBS-Hytron 13	Precision Electronics116
Cagan Sales, R. C	Premax Products
Calvert Electronics Incorporated 97	Premier Radio-TV Supply
Candler System Co	Progressive "Edu-Kits," Inc
Capitol Radio Engineering Institute 19	Pyramid Electric Company
Centralab	Tyramia Erective Company
Channel Master Corp	R.C.A. Institutes, Inc
Chicago Standard Transformer Corporation 93	R W Electronics115
Cincinnati Ventilating Co., The100	Radiart Corporation, The
Cleveland Institute of Radio Electronics 15	Radio City Products, Inc
Collins Audio Products Co., Inc101	Radio Corporation of America 83
Columbia Electronics Sales	Radio Craftsmen, Inc., The
Communication Equipment Co	Radio Receptor Company, Inc107
Components Corp134	Radio & Television News Book Service103
Concord Radio114	Rad-Tel Tube Co
Corona Radio & T.V. Co 78	Raytheon Manufacturing Company2nd Cover Reeves Soundcraft Corp
Coyne Electrical School 97	Rek-O-Kut Company, The
Davis Electronics125	Rider Publishers, Inc., John F
DeForest's Training, Inc 5	Rinehart & Co., Inc
	Riverway Industries124
Editors & Engineers, Ltd	Rohn Manufacturing Co 74
Electronic Chemical Corp	2
(EICO)	Sams & Co., Inc., Howard W114, 127 Sarkes-Tarzian, Inc104
Electronic Measurements Corporation 76	Scott, Inc., Herman Hosmer125
Electron Tube Wholesalers, Inc135	Steeper Publisher, Milton B 87
Electro-Voice 8	Sonotone Corporation 91
Erle Resistor Corporation122	Sprague Products Company
Fair Radio Sales109	Sprayberry Academy of Radio 23
Fenten Company105	Stan Burn Radio & Electronics Co
Fisher Radio Corporation10, 77	Stevens Walden, Inc
G & G Radio Supply Co 82	Stuart Electronic Distributors
G & H Wood Products Co	Sun Parts Distributors, Ltd 95
G. L. Electronics, Inc	Supreme Publications
General Electric Co 21	Sylvania Electric Products, Inc 7
General Electronic Dist. Co 74	"TAB"138
Goodheart, R. E	Television Communications Institute93, 121
Greeniee Tool Co102	Teltron Electronics Co
Harjo Sales Co	Transamerica Electronics Corp129
Harvey Radio Company, Inc	Transvision, Inc122, 123
Heath Company	Triad Transformer Corp 24
Henry Radio Stores	Tri-State College124
Henshaw Radio Supply	Tung-Sol Electric, Inc 16
Hughes Research and Development	Ultra-Audio Broadcasting System
Laboratories	United Radio Co109
Indiana Technical College134	Universal Service Co
Instructograph Company	University Loudspeakers, Inc 26
International Rectifier Corporation 20	U.S. Crystals75, 123
International Resistance Company 3rd Cover	Valparaiso Technical Institute 86
	Video Electric Co
JFD Manufacturing Co	
JSH Sales Co122	Walsco Electronics Corporation 33
Jones & Laughlin Steel Corporation #5	Washtek Service Co 86
	Western Radio & Television Institute109 Wholesale Radio Parts Co., Inc
Kedman Co124	Windsor Electronics Tube Co
Krylon, Inc131	World Radio Laboratories105
Lafayette Radio129	
Leotone Radio Corp102	Zingo Products 78

INDIVIDUALLY BOXED

OVER 300

ompare! Save!..on RAD-TEL

Type OA2

OA4

OB₂

OC3

OD3

OZ4M

1A7GT

1AX2

1F7

166

1H4

114

116

11 A4

1LA6

ILC5

ILC6

1LD5

ILE3

1LG

1LH4

ILN5

INSGT

1P5GT 1O5GT

185

155

1T4

1114

105

1X2A

2A3 2A4G

2W3

2X2

3A4

3E5 3LF4

3Q4 3Q5GT

354

3 V 4

5U4G

SW4CT

5Y3GT

5Z3

6AB4

SAF4

6AG5

6AH4

6AH6

6AK5

6AK6

6AL5

6AQ5

6AQ6

6AR5

6ASS

6AT6

6AU4CT

6A15

6AG7M

6A7

1H5GT

1B3CT

Type 6AV6

6B4

6BA6

6BA7

6BC5

6BD5

6BD6

6BG6G

6BL7GT

6BO6CT

6BH6

6B16

6RN6

6C5

6CB6

6CD6

6F5GT

6H6GT

6JSGT

6K6CT

6K7

6L6

607

6L7M 6N7M

657M 658GT

6SA7GT

6SD7GT

6SF5GT 6SG7GT

6SH7GT

6SI7GT

6SK7GT

6SL7CT

6SN7GT

6SO7GT

6SR7GT

6SS7GT

6118

6X4

6X8

6Y6C

7A4

7A5

7A6

6V6CT

6W4CT

6W6CT

6X5GT

6AX4CT

.68

.81

.55

.47

.62 6BE6

.73 6BF5

43 6RE6

29

.69 6BQ7

.79 6C4

59

69

.69

.67 6E5

49 6G6

49 616

49 617

.43

24

38

46 654

48

.49

51

.55

.37

.45

69

.86

.90

48 6T4

.99 6T8

.57 6116

73

65

.55

.59

.38

.39

.37

.37

.50

.37

Type 7AF7

7B4 .65

785

787

705

7C6

7E6

7E7

7F7

7L7

7X6 7X7

7Y4

7Z4

12A6

12A8GT

12A09

12AT6

12AT7

12AU6

12AU7

12AV6

12AV7

12AX4

12AX7

12AY7

12BA6

12BA7

12BE6

12BF6

12BH7

12BY7

12BZ7

12H6

12K8

1207

1258GT

12SF5 12SG7

25J7M

12SK7M

12SL7GT

12SN7CT

12507GT

12V6GT

12X4

14A4

14A7

14B6

14AF7

125A7GT .65

125K7GT .63

12C8M

12SC7M

12BD6

.37

39 786

.49

.45

.39 7E5

1.25

.46

.43 7H7

.83 7K7

.79 7N7

90 **707** 7R7

.90

.39 7V7

1.11

.48

30

.59 12AL5

.41

.43

.52

.**43** .47

.37

.44

.64

.68

63

.45

.69

.38

.43

46

41

49

.41 1215

48

.52

37

42

99

.80

50

61

.50

.44

.44

.37

.37

.75

.48

47

59 14A5

.69

.68 .68 1486 .79 1488 Price

44

49

69

.59 14R7

79 14Y7

.59

.69

69

66

89

89

54

69

.37

37

.66

38 35Y4

.54

.39

.63

.56

50

38 45

.60

.51

63 50B5

.65

56 50Y7

63

42

59

.63 83V

.47

52 85

.56

.46

.38

.69

.63

.63 Hi-Po

63 1

Type

14E6

14E7

4F

14H7

1417

14N7

457

14X7

19BG6

19C8

19T8

24A

25AV5CT .83

25BO6CT

25W4GT

25L6GT

25Z5

25Z6

32L7

35B5

35C5

35W4

35Z3

36

41

42

43

45Z3

4575

50A5

50C5

50Y6

56 49

57

58

75

76

80

84/6Z3

117L7

117P7

117Z3

11726

807

866A

1274

70L7

50L6GT

35Z5GT

35L6CT

26

Philco TV BOOSTER

095

Granco "Star" UHF CONVERTER



22.45 29.97

STANDARD BOOSTER



Amplifier ained AC cabinet.

Lots of 3 6.95 6.45 UNIVERSAL FLYBACK

SELENIUM RECTIFIERS Mfd. by FEDERAL



PRICE 590 .79c .84c 1.25 250-1010A 1.75 250-1028A 1.75 .1.39 350-1238A 1.59

350-1023A 1.50

1.85

CATHODE RAY TUBE REJUVENATOR



09

1.39

New Parts At Old Fashioned SAVINGS! All

VOLUME CONTROL KIT



Kit of 10 in cludes wire-wound, dual and carbon The price of one (1) for the quantity of ten (10). Short and long shaft.

Lots of 3 Kits 1.59 Ea. 1.79 PER KIT

SOLDERING

9.71

35¢ **

-Giant 21" Picture



TABLE MODEL TV

and 70 UHF static Order No. 46U.

BATTERY RADIO



TERMS: A 25% der



INDOOR ANTENNA

nna...3.95

RESISTORS (Asst. of 200) Uninsulated, 1/2 Watt, 1 Watt, 2 Watt, and some 10 Watt, and 110.00. \$1.39

2-STATION INTERCOM



.68 6AU5CT .82 7A7 .46 7A8 6AV5GT 83 7AD7

115 Coit St., "Integrity Is Our Chief Asset Irvington 11, N. J.



PLEASE: Send full remittance . . . allow for postage and save C.O.S. rfund all unused money!

Send For FREE Ellustrated PARTS CATALOGUE

Essex 5-2947 SOOn of Bernand

Price

88

65

30

84

79

.89

30

95

69

79

.51

66

49

45

30

89

40

.39

.41

47

.54

.59

47

.39

42

42

.55

44

40

.55

.52

.51

.61

49

.50

49

49

58

60

97

.49

44

.57

47

.68

.46

59

.99

99

.37

69

90

1.39

#567 1.39

.30



Tube Sockets CINCH-JOHNSON-AMPH

JOHNSON EQUAL

STEATITE	\$1.00
0 1 2 2 0 4 7 (R 2 0 H) 55c; 3 for	1.00
- 193-911 (879A)	4.80
# 122-237 (813) SOc; 3 for	1.00
# 122-234 (5D21-715)1.25; 4 for	3.98
# 124-213 (304TL)1.30; 2 for	2.49
z 122-227 (1625) 30c; 4 for	1.00
E 122-225 (807)38c; 4 for	1.30
g 40-8811L (Maginal) 59c; 2 for	1.00
5 prong (Acorn) 38c; 4 for	
4 prong (5C22-8008), 1.20; 4 for	
a prong tot 22-amost	
Octal (low-loss micz ring mtg. 10 for	1.00
Octal (mica) ring mtg	
Octal (ateatite) ring mtg 12 for	
Octal (bakelite) ring mtg 15 for	
Octal (bakelite) saddle mtg 18 for	
Octal (mica) saddle mig 12 for	1.00
Octal (steatite) saddle mtg 12 for	2.00
Loktat (steatite) ring mtg 10 for	2.00
Loktal (micz) saddle mtg 12 for	1.00
7 pin min (mica) base shid 12 for	2.00
7 his min (mica) bottom mtg 10 for	1.00
7 pin min (blkt) rubber	
shock mig	2.00
7 pin min waffer	1.00
9 pin min (mica) bottom mtg. ,12 for	2.00
9 pin min (blkt) bottom mig , 7 for	1.00

Write for qty price and other types 100 WATT SEC PHOTOFLASH KIT Includes ML Flash Lamp Flash 100 Watt Second, 100 Watt Sec Resistence

Cable. Power Trans. ConCable. Power Trans. C

PHOTOFLASH LAMPS

Replaces Max. Each 150
PA104/U5W 150
Replaces Max. Each 250
Replaces Max. Eac

EQUIPMENT BUYS
1-222A SIG GEN 8-15MC 45-76MC (150-230M: HARMONICS) 578.00
6C221 Freq Meters 125-20,000KC \$128.00
LM Freq Meters 125-20,000KC \$48.00
T89.APT3 XMTTR 300-1300MC Less 300-1600MC T88 APTS XMTTR 300-1600MC Less Tubes CPS APS18 Less Tubes \$38.00 CPS APS18 Less Tubes \$35.00 PE103 6 & 12 Dyna Supp 4 BC654 \$30.00

TWINEX & COAX CABLE
300 0MM Twines 65Mil Henry
Duty, Burable, 13 139
1040 Ft \$1:00; 5000 Ft \$50
1040 Ft \$1:00; 5000 Mil Mrs
Ity, But 100' \$3.29; 1000' \$22
MGNU \$2 0Mm 100 ft \$1:00
MGNU \$2 0Mm 100
MGNU \$2 0Mm 10 TWINEX & COAX CABLE



Alboo COMYNETS

Alboo Magnets, India O Magnets, India O Magnets, India I mel work, 2 wire nets, India I mel work, 2 wire nets, India I mel work, 2 wire nets, I mel of the I m

**Cone Woofer23W.20-1RC/3DB.\$32.44

AUDIO COMPONENTS
Extraction of the components of the component

TUBE CADDY AVY DUTY TUBE CASE
16" plywood, Lock-corred construction. Durable
stic handle, nickel plants

eiving tube order. TOGGLE SWITCHES
SPOT 10A/120V center off
AVN1020-11.
SPOT 10A/120V center off
AVN1020-11.
SPOT 10A/120V center off
SPOT 10A/120V ANSI0020-10
SPOT 10A/120V



A BUY THAT'S WATCH THIS SECTION

WATCH THIS SECTION
EVERY MONTH

RMEOSTATS-OMRITE-IRC.-W. LEONARD
15 ohm 25W w/knob, 81.10; 10 for \$7.00
20 ohm 50W Model J. 1.98; 10 for 14.00
0 ohm 50W Model J. 1.98; 10 for 14.00
125 ohm 25W Model H 1.10; 10 for 7.00
125 ohm 25W Model H 1.10; 10 for 7.00
250 ohm 25W Model H 1.10; 10 for 7.00
250 ohm 25W Model H 1.10; 10 for 6.00
250 ohm 25W Model H 1.10; 10 for 7.50
800 ohm 25W Model H 1.10; 10 for 7.50
800 ohm 25W Model H 1.28; 10 for 15.00
200 ohm 25W Model H 1.28; 10 for 15.00
200 ohm 25W Model H 1.28; 10 for 9.00
2000 ohm 25W Model H 1.28; 10 for 9.00
2000 ohm 25W Model H 1.28; 10 for 9.00
2000 ohm 25W Model H 1.28; 10 for 9.00
2000 ohm 25W Model H 1.28; 10 for 9.00



HI-MEG HI-VOLT IRC RESISTORS

TV CONICAL ANTENNA All Channel, inclds 8 elements, Cross Bar &

incids 8 elements. Cross Bar & Clamp Window CONICAL ANY All Channel, Styrdy Const, Mounts outside window. \$3.95 \$ FOOT Interlocking Mast Sections. Hyy Duty, rustproof. 2 for \$1.49, 10 for \$7

INDUSTRIALS WRITE ON YOUR LETTERHEAD FOR POWER RECTIFIER CATALOG

SELENIUM RECTIFIERS

RECTIFIES

We specialize in Rectifiers and Power auplifiers and Power au

RECTIFIER CHOKES

Ohm 87.95 Ohm 14.95 Ohm 29.95

new scientum type. \$11.98; 3 for \$33
HIGH CURRENT PWR SUPPLIES 000

Variac, Volt any Meters, Revitch, TermisMeters, Revitch, TermisDuty Steel Cabinet,
Duty Steel Cabinet,
Obs., 220V to order Write's
Obs., 220V to order Write's
Obs., 220V to order Write's
Cabinet, Tawlia Cabinet,
Tawlia C. 248VDC at 24 Amp. . 8 47.75
Tawlia C. 248VDC at 24 Amp. . 129.50
Tawlia C. 248VDC



table DC Power full wave recti , 6000 MFD con Filter, fused. (tely built, rest Input 115V 6 put 0 to 6VIM 1 2DCF. \$1

NEW RELAY LIST Tremendous Price Reductions R1971 Stevens Arnold Resonant Relay g189. Plug-in Freq. 240cy. 85.98; 3 for \$15

Tremendous Price Reductions
18573 Stevens Arnold Resonant
Relay g 189, Plur-in Freq, 240cy.
25.90, 35.98; 3 for \$3.5
22WEH Western Elect. Mercury Relay
D-171584 Dlucin. SPD Transfer contacts
36VDC/4500, Onn./9MADC. 5.7.75; 3, \$24
2500. Glun/3MAD plur-in SIG 227.757; 1, 524
2500. Glun/3MAD plur-in SIG 227.757; 1, 524
2500. Glun/3MAD plur-in SIG 227.757; 1, 524
2500. Glun/3MAD plur-in SIG 227.758; 1, 524
2500. Glun/3



FILTER CHOKES
Check These Reduced Prices
(fly/80/Ma H'sld/3KVinn . \$2.25
HS/40/ma Prices
HS/40



6.3 Volt 3% Amp Continuous. 115VAC input. Size 25:16"H.2"L.11\""" mig entr 2\"\"," inv channel ntg RM. SM. Mfrs. Job-bers, Dirs. Order now this \$1.98 value.

"TAB" SPECIAL \$1.00 12 for \$10.00; 100 for \$75.00

OIL CONDENSERS

OIL CONDENSERS

NEW WAREHOUSE LISTING

0023MED 25kV \$4.00.2 for \$7.00

1023MED 25kV \$4.00.2 for \$7.00

1034ED 25kV \$4.00.2 for \$2.00

MED 1500V \$5.00 for \$2.00

MED 1500V \$5.00 for \$2.00

MED 1500V \$3.24 for \$1.00

MED 1500V \$3.00 for \$2.00

MED 300V \$5.00 for \$2.00

MED 300V \$5.00

MED 300V \$5.00 for \$2.00

MED 300V \$5.00 fo

OIL CONDENSER
SPECIAL
10 MFD \$1.75 ea.
600 VDC lots of 3

lots of 3 not including x 334W x Quantities.




11 THAT'S AUY BUY . DEPT. 6-RN 111 LIBERTY STREET NEW YORK 6, N. Y., U. S. A. Money Back Guarantem (Cost of Mdse. Only) \$5 Min. Order F.O.B., N.Y.C. Add Shpg. Charges or 25% Dep. Tubes Gtd. via N.-Exp. Prices subject nge Without Notice. Rector 2-6245

"TAB"

ASSURED ELECTRICAL ACCURACY

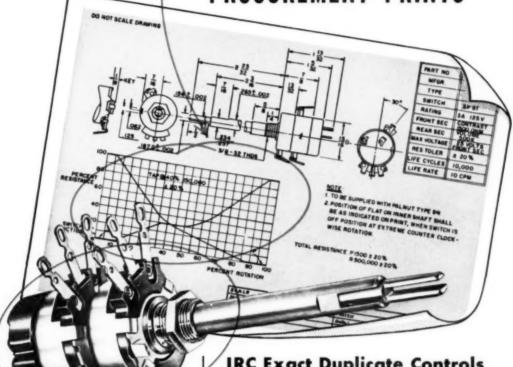BASED ON MANUFACTURERS' PROCUREMENT PRINTS



ONLY IRC GUARANTEES

ACCURATE ELECTRICAL OPERATION AND SATISFACTORY MECHANICAL FIT

OR DOUBLE-YOUR-MONEY-BACK

Electrical specifications of this typical manufacturer's procurement print are exactly duplicated by IRC's QJ-412 control (shown). CONCENTRIKIT assembly includes P1-206 and R1-223 shafts with B17-109 and B13-133X Base Elements and 76-1 Switch.



Wherever the Circuit Says -----

IRC Exact Duplicate Controls

Are Double-Money-Back Guaranteed

Based on set manufacturers' procurement prints, only IRC Exact Duplicate Controls are double-money-back guaranteed for accurate electrical operation. This firm guarantee applies to both IRC factory-assembled Exact Duplicates and universal CONCENTRIKIT equivalents.


Set manufacturers' electrical specifications are closely followed.

Resistance values are carefully selected to match. Tapers are watched carefully; IRC doesn't arbitrarily substitute tapers to obtain wide coverage.

For exact duplicate controls of guaranteed accuracy, specify IRC. Most Service Technicians do.

INTERNATIONAL RESISTANCE CO.

415 N. BROAD ST., PHILADELPHIA 8, PA.

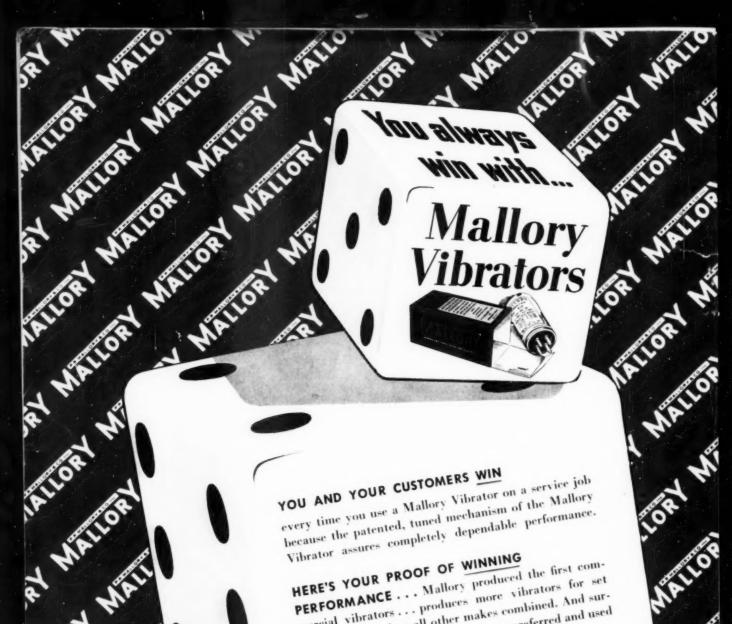

ALLON MALL Another Mallory Winner!

The new Mallory Vibrator Guide is a complete cross-reference and service guide. It has always been the accepted reference book for vibrator selection. Get one from your Mallory distributor. MALION MAIL ay Mallory

AY MAI

ALION

every time you use a Mallory Vibrator on a service job because the patented, tuned mechanism of the Mallory Vibrator assures completely dependable performance.

HERE'S YOUR PROOF OF WINNING PERFORMANCE . . . Mallory produced the first commercial vibrators . . . produces more vibrators for set manufacturers than all other makes combined. And surveys show that Mallory Vibrators are preferred and used by 5 out of 6 servicemen.

always ask for Mallory Vibrators by name. Use them for STICK WITH THE WINNER ... all your car radio service jobs.

AY M

PR MALLORY & CO INC